
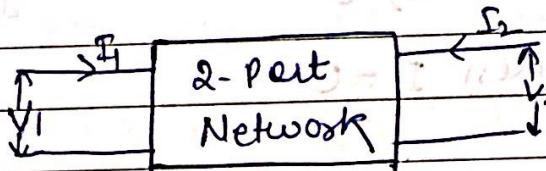


2-Port Networks

11

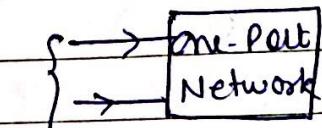Port: A terminal pair is known as 'port' if current entering at one terminal is equal and opposite to the current leaving the other terminal.



→ In 2-port network there are four variables
Two voltages (V_1, V_2)
Two currents (I_1, I_2)

out of these four variables, two variables may be considered as 'independent' and two variables as 'dependent'.

→ one of the ports is called the input port, while the other is termed as the off port.

① Z-Parameters | open circuit Parameters | Impedance Parameters:-

$$(V_1, V_2) = f(I_1, I_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$[V] = [Z][I]$$

DOMS

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{---(1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{---(2)}$$

→ Determination of 2-Parameters:-

Case 1: when $I_2 = 0$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \& \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

Case 2: when $I_1 = 0$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad \& \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$


$Z_{11} \rightarrow$ Input Driving Point Impedance with the output part open circuited.

$Z_{21} \rightarrow$ forward Transfer Impedance with the output part open circuited.

$Z_{12} \rightarrow$ Reverse Transfer Impedance with the input part open circuited.


$Z_{22} \rightarrow$ output Driving Point Impedance with the input part open circuited.

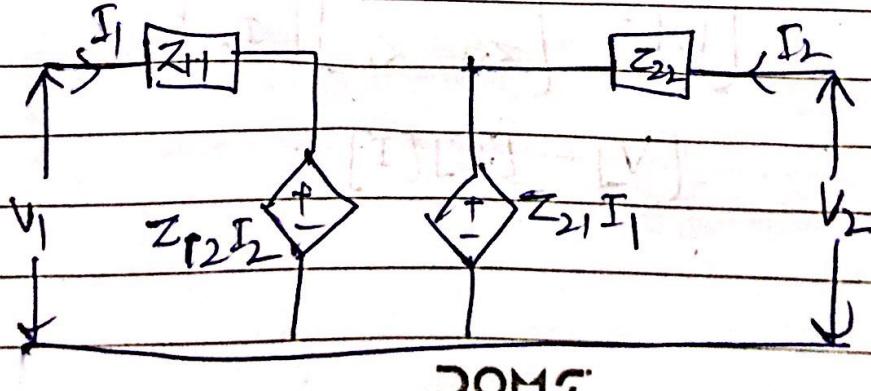④ → Equivalent Circuit of 2-Port w/o in terms of 2-Parameters.



Q.1 for a given network, find Z-parameters.
and also draw the equivalent circuit
of in terms of Y-Parameters.

Sol^n

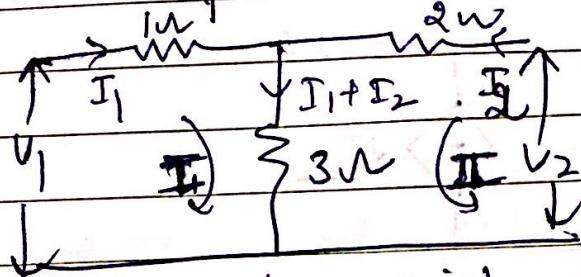

Applying KVL in first and second loop:-

$$V_1 = 1 \cdot I_1 + 3(I_1 + I_2)$$

$$\boxed{V_1 = 4I_1 + 3I_2} \quad \textcircled{1}$$

$$V_2 = 2I_2 + 3(I_1 + I_2)$$


$$\boxed{V_2 = 3I_1 + 5I_2} \quad \textcircled{2}$$

On comparing eqn ① & ② with the eqns of Z-Parameters, we find

$$Z_{11} = 4\Omega, \quad Z_{12} = 3\Omega$$



$$Z_{21} = 3\Omega, \quad Z_{22} = 5\Omega$$

equivalent circuit

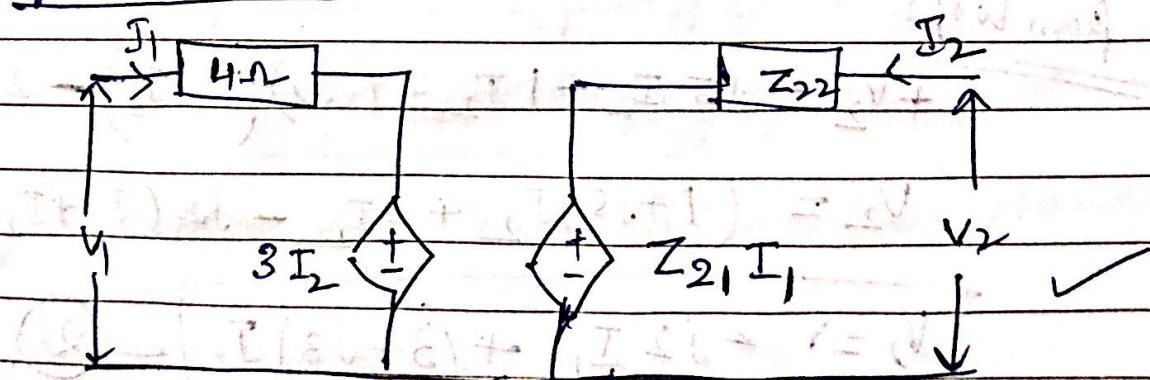

DOMS

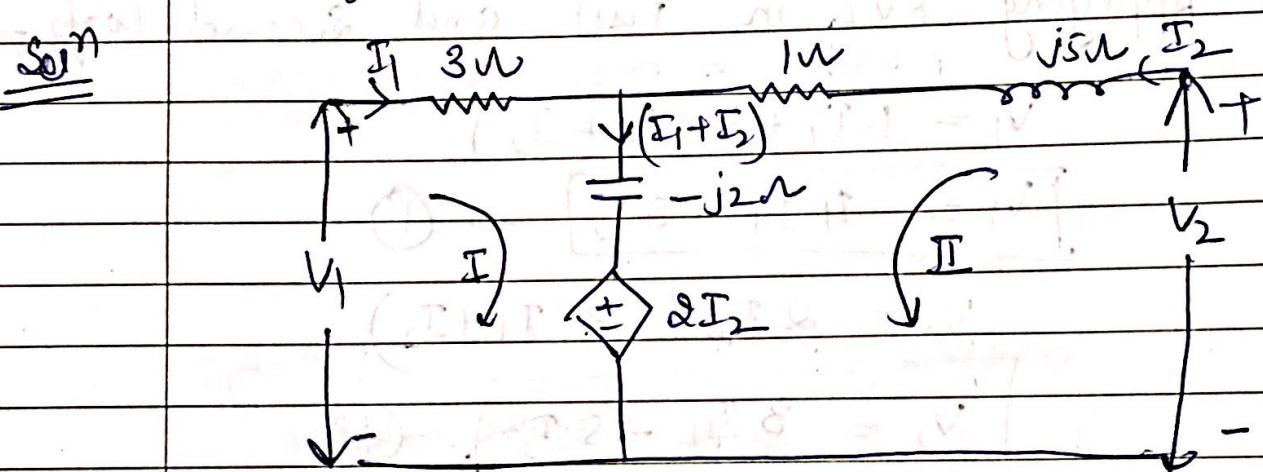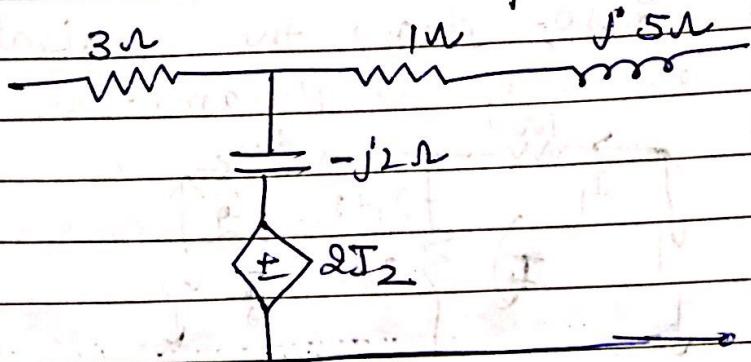Q.2 Calculate Z-Parameters of the given network.



from loop 1

$$+V_1 = 3I_1 - (j2)(I_1 + I_2) - 2I_2 = 0$$

$$V_1 - 3I_1 + j2I_1 + j2I_2 - 2I_2 = 0$$

$$\boxed{V_1 = (3-j2)I_1 + (2+j2)I_2} \quad \text{--- (1)}$$

from loop 2

$$+V_2 - j5I_2 - 1I_2 - (-j2)(I_1 + I_2) - 2I_2 = 0$$

$$V_2 = (1+j5)I_2 + 2I_2 - j2(I_1 + I_2)$$


$$\boxed{V_2 = -j2I_1 + (3+j3)I_2} \quad \text{--- (2)}$$

DOMS


On comparing eqn ① & ② with standard eqns of Z-parameters, we have:-

$$\boxed{Z_{11} = (3-j2)\Omega, \quad Z_{12} = (2-j2)\Omega \\ Z_{21} = (-j2)\Omega, \quad Z_{22} = (3+j3)\Omega.}$$

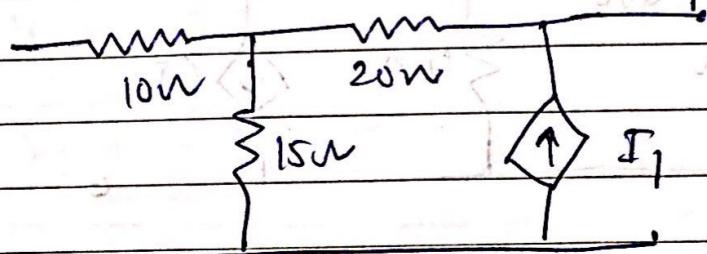Q.3 Determine the Z-Parameters of given Network.



Solⁿ

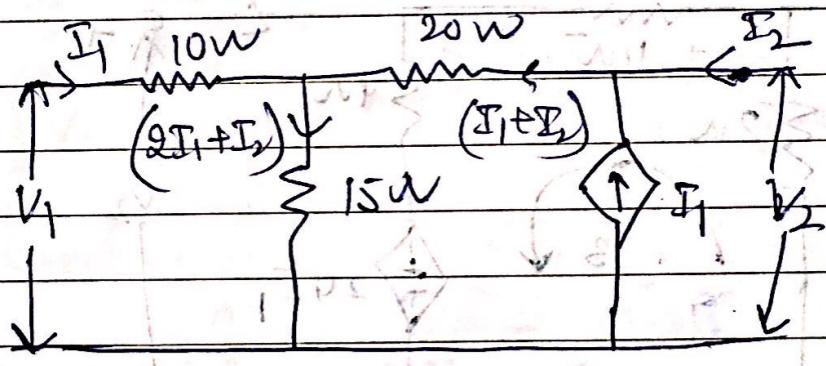

$$V_1 = 10I_1 + 15(2I_1 + I_2)$$

$$\boxed{V_1 = 40I_1 + 15I_2} \quad \textcircled{1}$$



$$V_2 = 20(I_1 + I_2) + 15(2I_1 + I_2)$$

$$\boxed{V_2 = 50I_1 + 35I_2} \quad \textcircled{2}$$

On Comparing these eqns with standard eqns of Z-Parameters,

$$\begin{array}{ll} Z_{11} = 4\Omega & Z_{12} = 15\Omega \\ Z_{21} = 5\Omega & Z_{22} = 35\Omega \end{array}$$

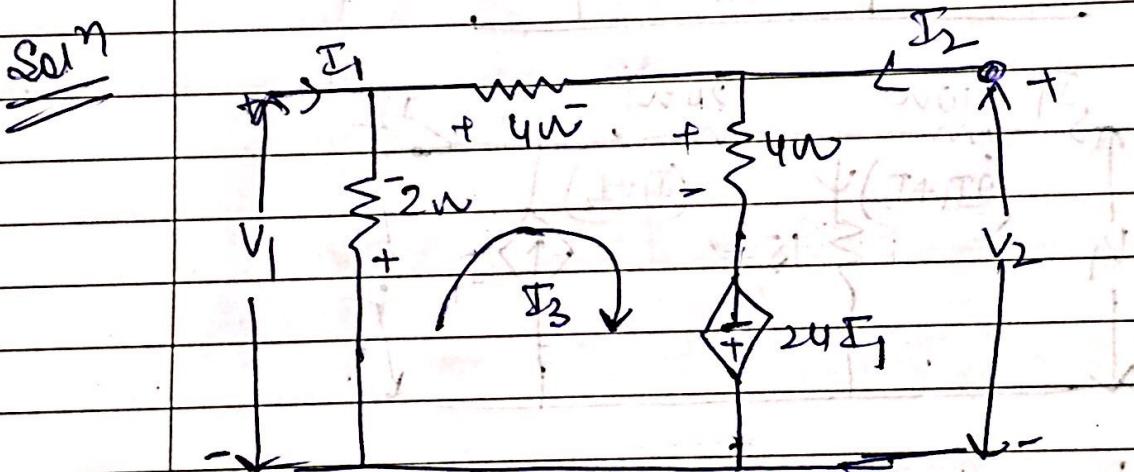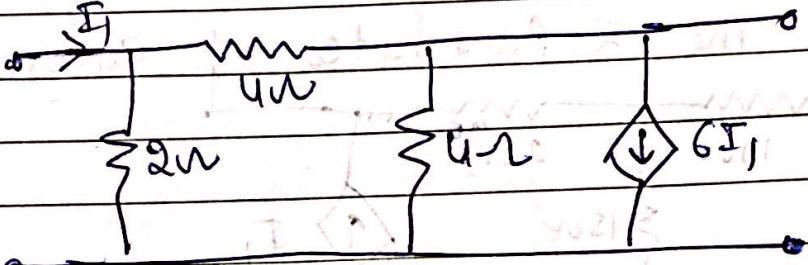Q. 4 Calculate the Z -parameters of the given network.



$$V_1 = -2(I_1 - I_3) \quad \textcircled{1}$$

$$-2(I_3 - I_1) - 4I_3 - 4(I_2 + I_3) + 24I_1 = 0$$

$$-2I_3 + 2I_1 - 4I_3 - 4I_2 - 4I_3 + 24I_1 = 0$$

$$26I_1 - 4I_2 - 10I_3 = 0 \quad \textcircled{2}$$

$$I_3 = 2.6I_1 - 0.4I_2 \quad \textcircled{3}$$

DOMS

$$+V_2 - 4(I_2 + I_3) + 24I_1 = 0$$

$$V_2 = 4(I_2 + I_3) - 24I_1$$

$$\boxed{V_2 = -24I_1 + 4I_2 + 4I_3} \quad (4)$$

Putting value of I_3 from eqⁿ (3) into eqⁿ (B) \Rightarrow (4)

$$V_1 = 2I_1 - 2[2.6I_1 - 0.4I_2]$$

$$\boxed{V_1 = -3.2I_1 + 0.8I_2} \quad (5)$$

$$V_2 = -24I_1 + 4I_2 + 4[2.6I_1 - 0.4I_2]$$


$$\boxed{V_2 = -13.6I_1 + 2.4I_2} \quad (6)$$

on comparing eqⁿ (5) & (6) with eqⁿ (1) & (2) - P:


$$Z_{11} = -3.2 \Omega, \quad Z_{12} = 0.8 \Omega$$

$$Z_{21} = -13.6 \Omega, \quad Z_{22} = 2.4 \Omega$$

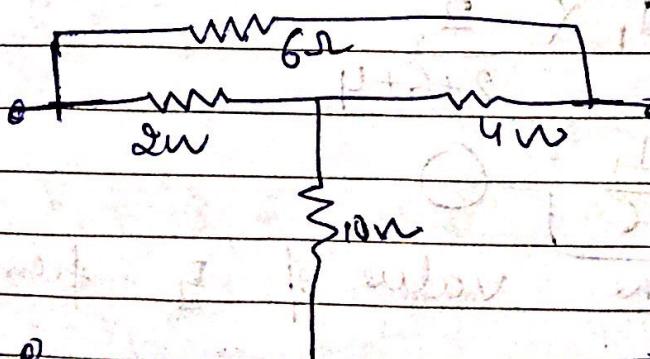
Q.5 obtain the open-circuit parameters of the given network:-



DOMS

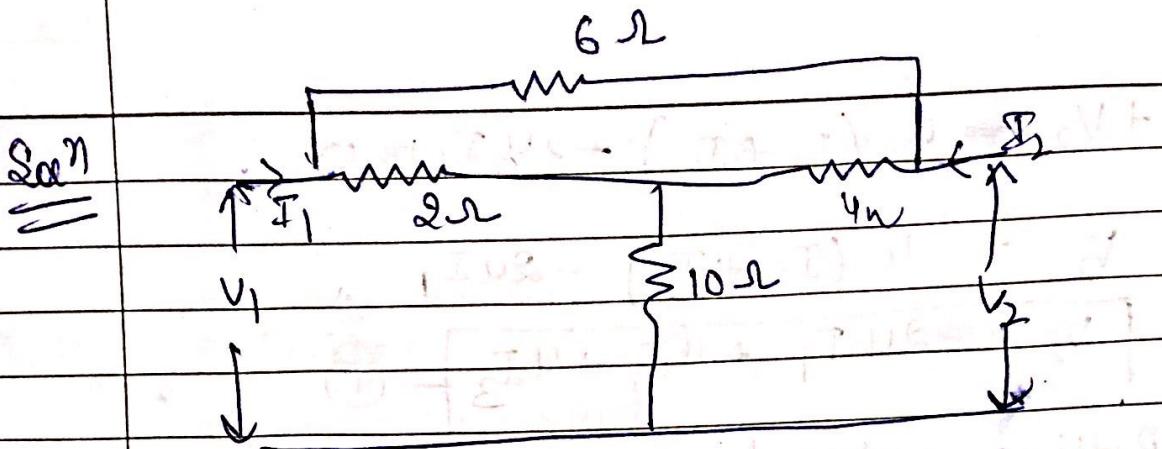

Case 1: when $I_2 = 0$

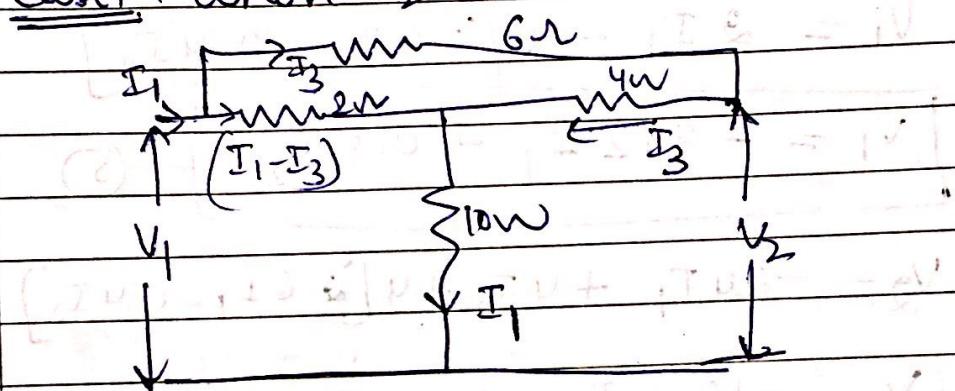

$$V_1 = 2(I_1 - I_3) + 10I_1$$

$$V_1 = 12I_1 - 2I_3 \quad \text{--- (1)}$$

$$V_2 = 4I_3 + 10I_1 \quad \text{--- (2)}$$

Using Current Division Law:-

$$I_3 = I_1 \times \frac{2}{2+6+4}$$

$$I_3 = \frac{I_1}{6} \quad \text{--- (3)}$$

Putting the value of I_3 from eqⁿ (3)

into eqⁿ (1) & (2):-

DOMS

$$V_1 = 12 I_1 - 2 \left(\frac{I_1}{6} \right)$$

$$V_2 = 4 \left(\frac{I_1}{6} \right) + 10 I_1$$

$$V_1 = \left(\frac{70}{6} \right) I_1$$


$$V_2 = \frac{9}{3} I_1 + 10 I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{35}{3} \Omega$$

$$V_2 = \frac{32}{3} I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{32}{3} \Omega$$

Case 2 : when $I_1 = 0$

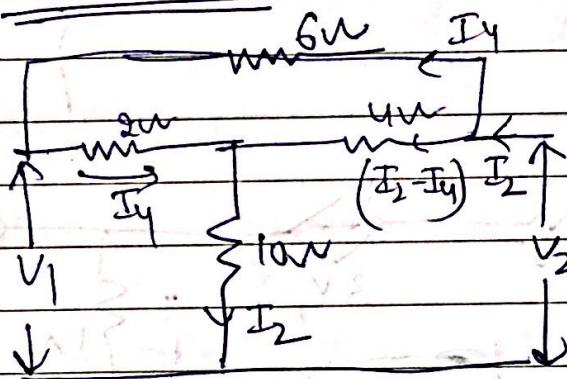

$$V_2 = 4(I_2 - I_4) + 10 I_2$$

$$V_2 = 14 I_2 - 4 I_4 \quad (4)$$

$$V_1 = 2 I_4 + 10 I_2 \quad (5)$$

Using Current Division Law:—

$$I_4 = I_2 \times \frac{4}{6+4+2} = \frac{2}{3} I_2$$

$$V_1 = 2 \left(\frac{I_2}{3} \right) + 10 I_2 = \frac{32}{3} I_2$$


$$Z_{12} = \frac{V_1}{I_2} = \frac{32}{3} \Omega$$

DOMS


$$V_2 = 14I_2 - 4\left(\frac{I_2}{3}\right) = \frac{38}{3}I_2$$

$$Z_{22} = \frac{V_2}{I_2} = \frac{38}{3} \Omega$$

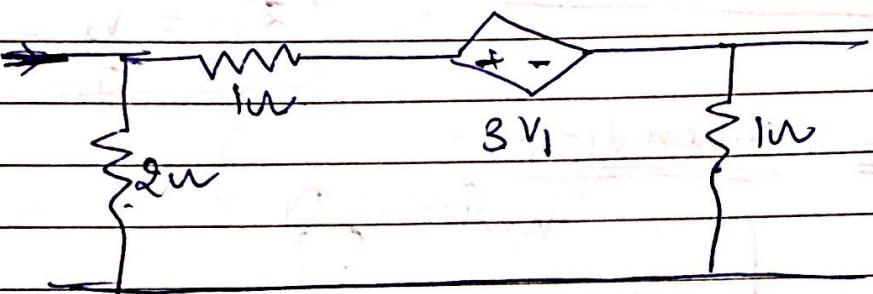Q.6 find the Z-Parameters of given network:-



Soln

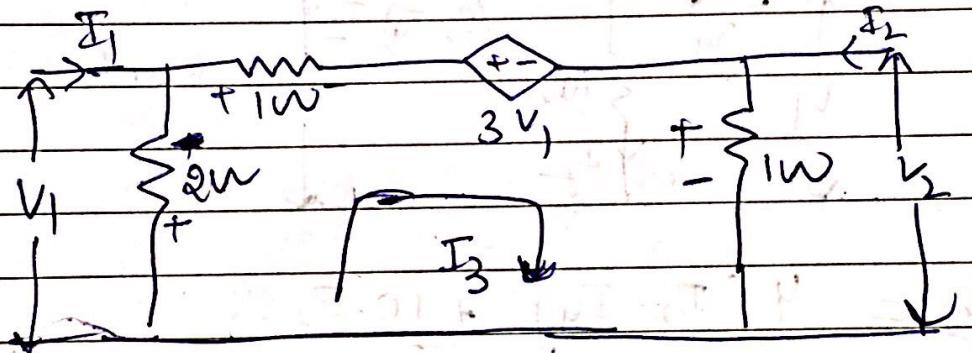

$$V_1 = 2(I_1 - I_3) \quad (1)$$

$$V_2 = 1(I_2 + I_3) \quad (2)$$

$$-2(I_3 - I_1) - 1I_3 - 3V_1 - 1(I_2 + I_3) = 0$$

$$-2I_3 + 2I_1 - I_3 - 3V_1 - I_2 - I_3 = 0$$

$$2I_1 - 4I_3 - 3V_1 - I_2 = 0$$

$$4I_3 = 2I_1 - I_2 - 3V_1$$

$$\text{So } I_3 = \left(\frac{I_1}{2} - \frac{I_2}{4} - \frac{3}{4} V_1 \right) \quad (3)$$

Putting value of I_3 from eqn (3) into (1) & (2):

$$V_1 = 2I_1 - 2 \left(\frac{I_1}{2} - \frac{I_2}{4} - \frac{3}{4} V_1 \right)$$

$$V_1 = -2I_1 - I_2 \quad (4)$$

$$V_2 = I_2 + \left(\frac{I_1}{2} - \frac{I_2}{4} - \frac{3}{4} V_1 \right)$$

$$V_2 = \frac{I_1}{2} + \frac{3}{4} I_2 - \frac{3}{4} V_1 \quad (5)$$

Putting value of V_1 from eqn (4) into (5):-

$$V_2 = \frac{I_1}{2} + \frac{3}{4} I_2 + \frac{3}{4} (-2I_1 - I_2)$$

$$= \frac{I_1}{2} + \frac{3}{4} I_2 + \frac{3}{2} I_1 + \frac{3}{4} I_2$$

$$V_2 = 2I_1 + \frac{3}{2} I_2 \quad (6)$$


on comparing (5) & (6) with eqn of 2-Parameter

$$Z_{11} = -2\Omega, \quad Z_{12} = -1\Omega$$


$$Z_{21} = 2\Omega, \quad Z_{22} = \frac{3}{2}\Omega$$

Ans.

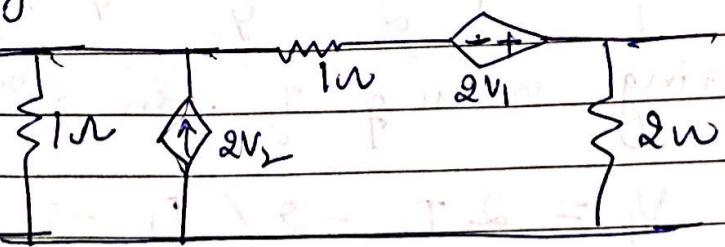Q.7 for a given network calculate Z-parameters.



Soln

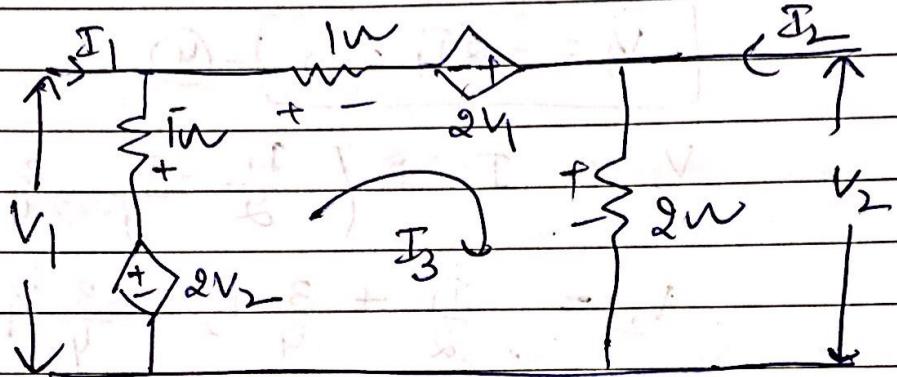

Applying KVL:-

$$V_1 = I_1 \cdot (1R) + 2V_2$$

$$V_1 = I_1 - I_3 + 2V_2$$

$$I_3 = I_1 + 2V_2 - V_1 \quad \text{--- (1)}$$

$$V_2 = 2(I_2 + I_3) \quad \text{--- (2)}$$

$$+ 2V_2 - I_1 (2R) - I_3 + 2V_1 - 2(I_2 + I_3) = 0$$

$$2V_1 + 2V_2 = -I_1 + 2I_2 + 4I_3 \quad \text{--- (3)}$$

Putting the value of I_3 from eqn (1) into eqn (2) & (3).

DOMS

$$2V_1 + 2V_2 = -I_1 + 2I_2 + 4 \quad (I_1 + 2V_2 - V_1)$$

$$\text{or} \quad [6V_1 - 6V_2 = 3I_1 + 2I_2] - \textcircled{4}$$

$$\text{And } V_2 = 2I_2 + 2(I_1 + 2V_2 - V_1)$$

$$[2V_1 - 3V_2 = 2I_1 + 2I_2] - \textcircled{5}$$

$$-3V_2 = 2I_1 + 2I_2 - 2V_1$$

$$-6V_2 = 4I_1 + 4I_2 - 4V_1 \quad \textcircled{6}$$

Putting value of $-6V_2$ from eqⁿ $\textcircled{6}$ into $\textcircled{4}$:-

$$6V_1 + (4I_1 + 4I_2 - 4V_1) = 3I_1 + 2I_2$$

$$2V_1 = -I_1 - 2I_2$$

$$V_1 = -\frac{1}{2}I_1 - I_2 \quad \textcircled{7}$$

Putting value of V_1 from eqⁿ $\textcircled{7}$ into eqⁿ $\textcircled{4}$:-

$$6\left(-\frac{1}{2}I_1 - I_2\right) - 6V_2 = 3I_1 + 2I_2$$

$$-3I_1 - 6I_2 - 6V_2 = 3I_1 + 2I_2$$

$$-3I_1 - 6I_2 - 3I_1 - 2I_2 = 6V_2$$

$$-6I_1 - 8I_2 = 6V_2$$


$$\text{DOMS} \quad V_2 = -I_1 - \frac{4}{3}I_2 \quad \textcircled{8}$$

So Comparing $\epsilon^{\text{in}} \textcircled{7}$ & $\textcircled{8}$ with $\epsilon^{\text{in}} \textcircled{1}$
 Z - Parameters:-

$$Z_{11} = -\frac{1}{2} \Omega, \quad Z_{12} = -1 \Omega$$

$$Z_{21} = -1 \Omega \rightarrow Z_{22} = -\frac{4}{3} \Omega$$

Q.8 find Z-Parameters of given network:-

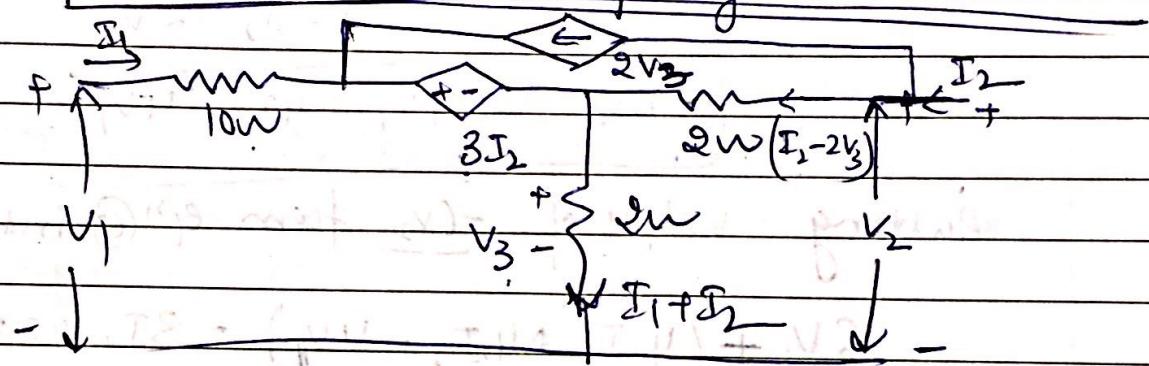

Soln

$$V_1 = 10I_1 + 3I_2 + 2(I_1 + I_2)$$

$$V_1 = 12I_1 + 5I_2 \quad \text{--- (1)}$$

$$V_2 = 2(I_2 - 2V_3) + 2(I_1 + I_2)$$

$$V_2 = 2I_1 + 4I_2 - 4V_3 \quad \text{--- (2)}$$

$$V_3 = 2(I_1 + I_2) \quad \text{--- (3)}$$

Putting value of V_3 from $\epsilon^{\text{in}} \textcircled{3}$ into $\epsilon^{\text{in}} \textcircled{2}$:

$$\epsilon^{\text{in}} \textcircled{2}:-$$

DOMS

$$V_2 = 2I_1 + 4I_2 - 4[2(I_1 + I_2)]$$



$$V_2 = 2I_1 + 4I_2 - 8I_1 - 8I_2$$

$$\boxed{V_2 = -6I_1 - 4I_2} \quad \text{--- (4)}$$

So, comparing eqn (1) & (4) with q^n & $Z-p'$

$$\begin{cases} Z_{11} = 12\Omega, Z_{12} = 5\Omega \\ Z_{21} = -6\Omega, Z_{22} = -4\Omega \end{cases} \text{ ans.}$$

Q.9 find Z-Parameters of given Network:

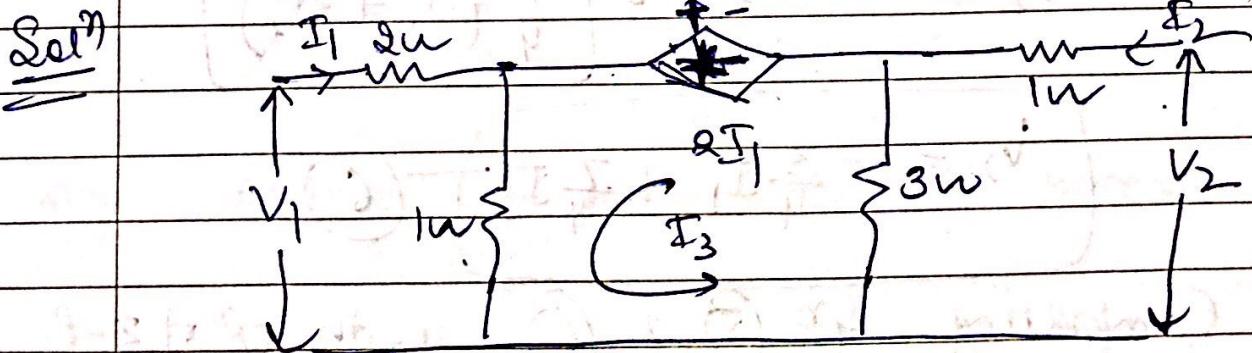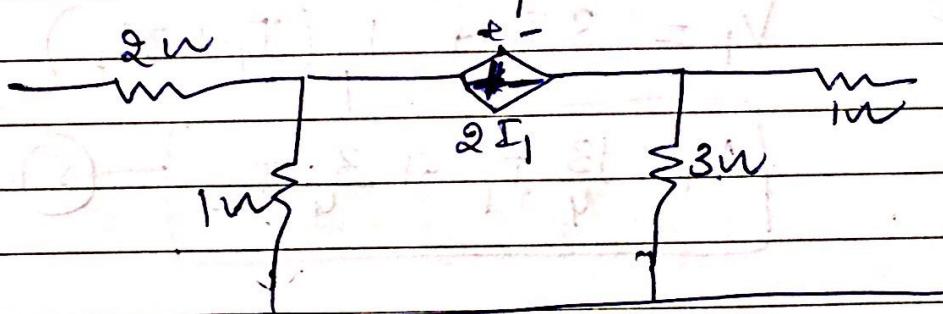

$$V_1 = 2I_1 + 1(I_1 + I_3)$$

$$\boxed{V_1 = 3I_1 + \frac{I_3}{3}} \quad \text{--- (1)}$$

DOMS

$$V_2 = 1 \cdot I_2 + 3(I_2 - I_3)$$

$$V_2 = 4I_2 - 3I_3 \quad \text{--- (2)}$$

$$2I_1 = 1 \cdot (I_1 + I_3) + 3(I_3 - I_2)$$

$$0 = -I_1 - 3I_2 + 4I_3 \quad \text{--- (3)}$$

from eqn (3): —

$$I_3 = \frac{1}{4}(I_1 + 3I_2) \quad \text{--- (4)}$$

so $V_1 = 3I_1 + \frac{1}{4}(I_1 + 3I_2)$

$$V_1 = \frac{13}{4}I_1 + \frac{3}{4}I_2 \quad \text{--- (5)}$$

$$V_2 = 4I_2 - 3\left[\frac{1}{4}(I_1 + 3I_2)\right]$$

$$V_2 = -\frac{3}{4}I_1 + \frac{7}{4}I_2 \quad \text{--- (6)}$$


Comparing eqn (5) & (6) with eqn 1 & 2-p.

$$Z_{11} = \frac{13}{4} \Omega, Z_{12} = \frac{3}{4} \Omega$$

$$Z_{21} = -\frac{3}{4} \Omega, Z_{22} = \frac{7}{4} \Omega.$$

DOMS

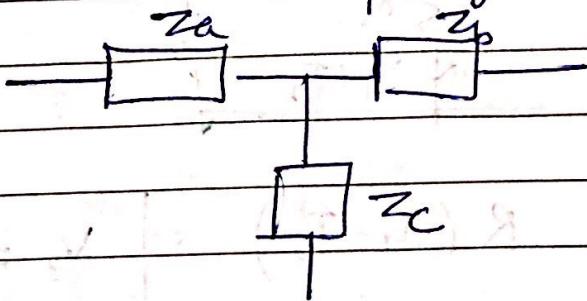Q.9 obtain Z-Parameters of given T-network:-




Soln

$$Z_{11} = (z_a + z_c), \quad Z_{22} = (z_b + z_c)$$

$$Z_{12} = Z_{21} = -z_c$$

Q.10

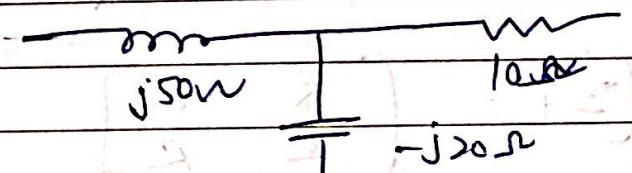


Soln

$$Z_{11} = j50 - j20 = j30 \Omega$$


$$Z_{12} = Z_{21} = -j20 \Omega$$

$$Z_{22} = (10 - j20) \Omega$$

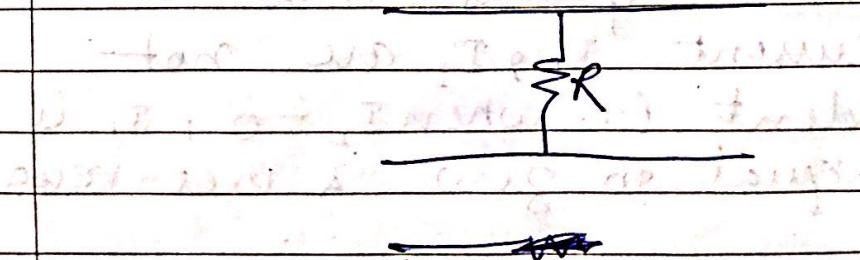Q.11 obtain Z-Parameters of given network



DOMS

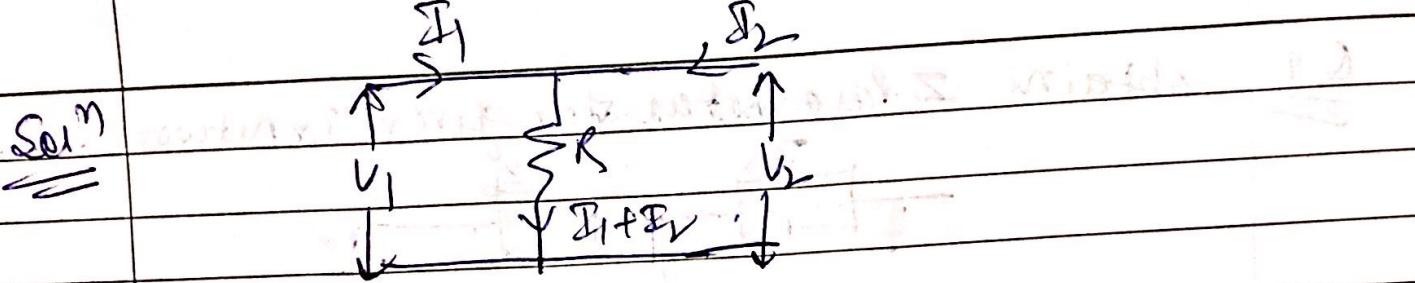

$$V_1 = R(I_1 + I_2)$$


$$V_1 = RI_1 + RI_2 \quad \text{--- (1)} \quad V_2 = RI_1 + R(I_1 + I_2) \quad \text{--- (2)}$$

$$\text{So } Z_{11} = R \quad \text{and} \quad Z_{12} = R$$

$$Z_{21} = R \quad \text{and} \quad Z_{22} = R$$

$$[Z] = \begin{pmatrix} R & R \\ R & R \end{pmatrix}$$

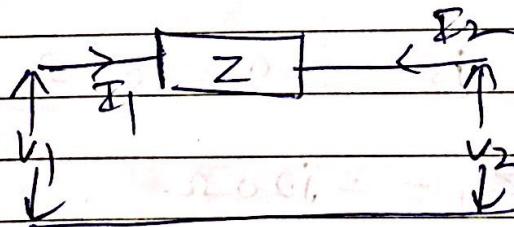Q. 12 obtain Z-Parameters of given network —




Solⁿ

$$V_1 = -I_1 Z + V_2$$



$$\text{while } I_1 = -I_2$$

Z-Parameters of this n/w don't exist, since current I_1 & I_2 are not independent i.e. when $I_2 = 0$, I_1 is also equal to zero & vice-versa.

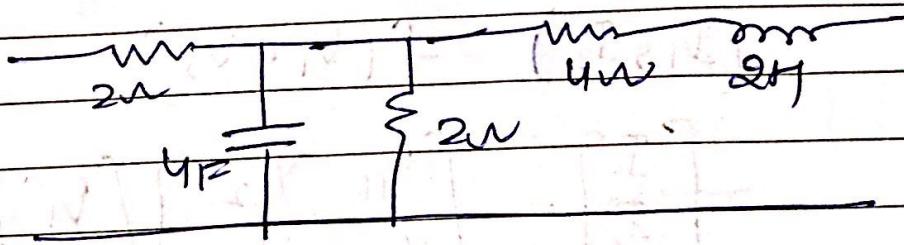Q.13 obtain z-Parameters of given network.



Sol:

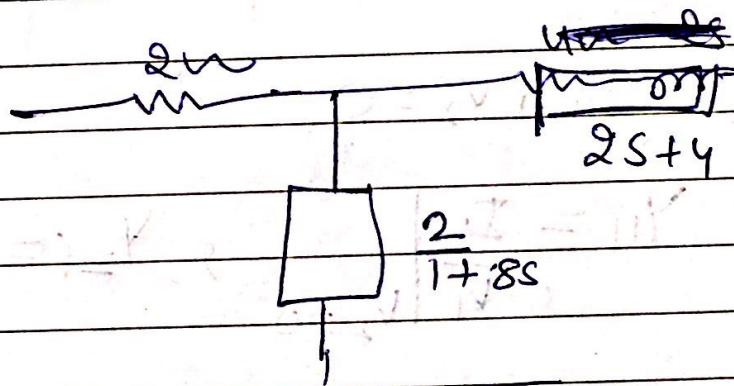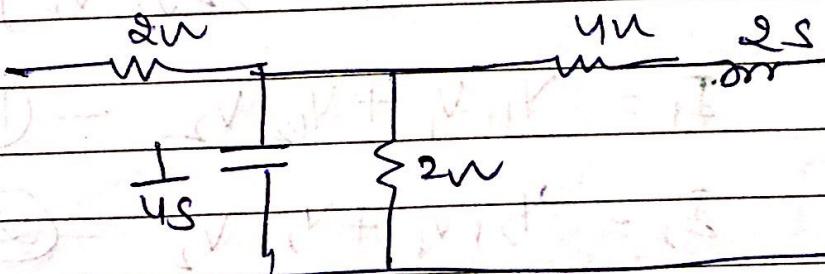

$$Z_{11} = 2 + \frac{2}{1+8s} = \frac{4+16s}{1+8s}$$

$$Z_{12} = Z_{21} = \frac{2}{1+8s}$$

$$Z_{22} = 2s + 4 + \frac{2}{1+8s} = \frac{6 + 34s + 16s^2}{1+8s}$$

⑤ Short Circuit | Admittance | Y- Parameters

In Y- Parameters:-

$$(I_1, I_2) = f(V_1, V_2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (2)}$$

Case 1 when $V_2 = 0$

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}, \quad Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

Case 2 when $V_1 = 0$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}, \quad Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$


$Y_{11} \rightarrow$ O/P Driving Point Admittance when o/p circuit is short circuited.

$Y_{21} \rightarrow$ forward transfer Admittance when o/p circuit is short circuited.


$Y_{12} \rightarrow$ O/P Driving Point Admittance with the o/p circuit short circuited.

$\gamma_{12} \rightarrow$ Reverse Transfer Admittance with the J1P short circuited.

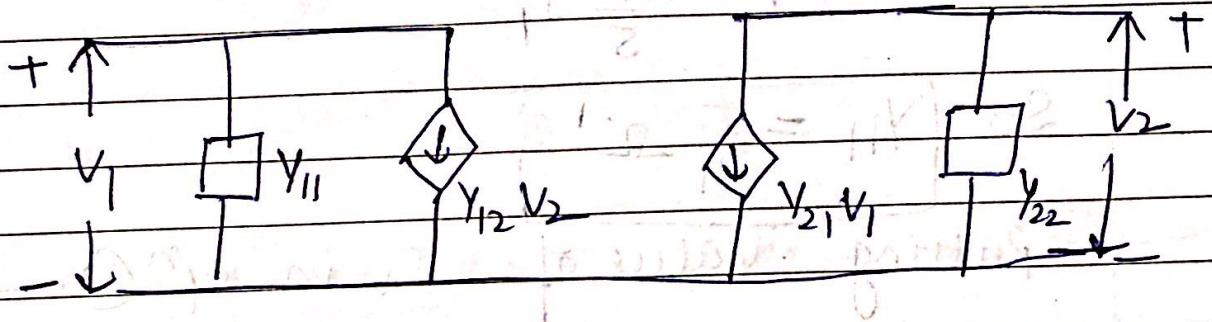
Equivalent circuit of 2-Port n/w in terms of Y-Parameters:-



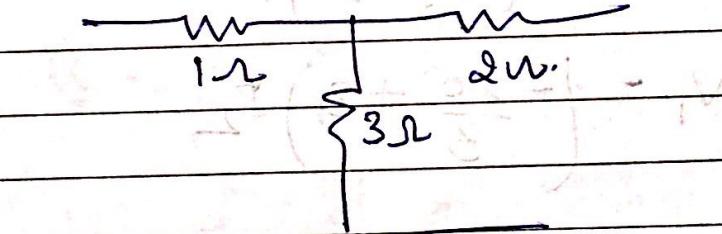Q.12 Obtain Y-Parameters of given network:-



Solⁿ

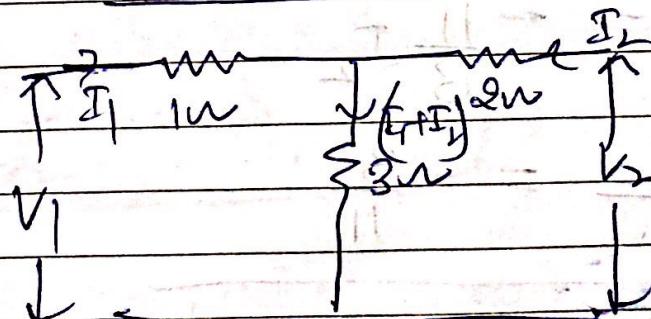

$$V_1 = 4I_1 + 3I_2 \quad (1)$$

$$V_2 = 3I_1 + 5I_2 \quad (2)$$

Case1:- when $V_2 = 0$

$$3I_1 = -5I_2$$

~~$I_1 = -\frac{5}{3}I_2$~~

$$I_1 = -\frac{5}{3}I_2$$

$$I_2 = -\frac{3}{5}I_1$$

Putting the value of I_2 in eqn ① :-

$$V_1 = 4I_1 + 3\left(-\frac{3}{5}I_1\right)$$

$$V_1 = 4I_1 - \frac{9}{5}I_1$$

$$V_1 = \frac{11}{5}I_1$$

So $\boxed{Y_{11} = \frac{5}{11} A^{-1}}$

Putting value of I_1 in eqn ① :-

$$V_1 = 4\left(-\frac{5}{3}I_2\right) + 3I_2$$

$$V_1 = \left(-\frac{20}{3} + 3\right)I_2$$

$$V_1 = -\frac{11}{3}I_2$$

So $\frac{I_2}{V_1} = -\frac{3}{11}$

So $\boxed{Y_{21} = -\frac{3}{11} A^{-1}}$

Case 2 : when $V_1 = 0$

$$4I_1 = -3I_2$$

$$I_1 = -\frac{3}{4}I_2 \quad \& \quad I_2 = -\frac{4}{3}I_1$$

DOMS

Putting the value of I_2 in eqⁿ Q:-

$$V_2 = 3I_1 + 5\left(-\frac{4}{3}I_1\right)$$

$$V_2 = 3I_1 - \frac{20}{3}I_1$$

$$V_2 = -\frac{11}{3}I_1$$

$$\boxed{Y_{12} = \frac{I_1}{V_2} = -\frac{3}{11} \text{ S}^{-1}}$$

Putting the value of I_1 in eqⁿ Q:-


$$V_2 = 3\left(-\frac{3}{4}I_2\right) + 5I_2$$

$$V_2 = \left(-\frac{9}{4} + 5\right) I_2$$

$$V_2 = \frac{11}{4}I_2$$


$$\boxed{Y_{22} = \frac{I_2}{V_2} = \frac{4}{11} \text{ S}^{-1}}$$

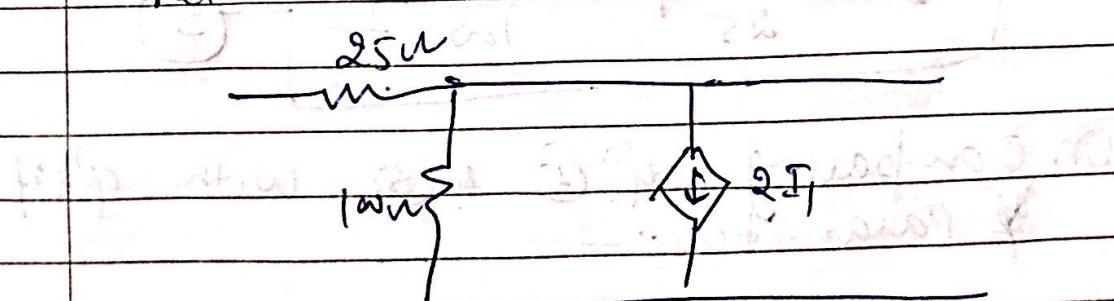Q.15 find the short circuit parameters of given network.



DOMS

Solⁿ

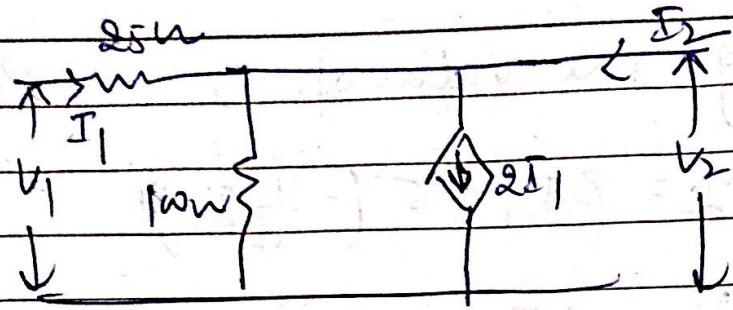

Applying KCL :-

$$I_1 + I_2 = \frac{V_2}{100} + 2I_1$$

$$I_1 = -\frac{V_2}{100} + I_2 \quad \text{--- (1)}$$

And Also

$$I_1 = \frac{V_1 - V_2}{25}$$

$$I_1 = \frac{1}{25}V_1 - \frac{1}{25}V_2 \quad \text{--- (2)}$$

Putting the value of I_1 in eqⁿ (1) :-

$$\frac{V_1 - V_2}{25} = -\frac{V_2}{100} + I_2$$


$$I_2 = \frac{1}{25}V_1 - \frac{3}{100}V_2 \quad \text{--- (3)}$$

On Comparing eqⁿ (2) & (3) with eqⁿ of
parameters:-

$$Y_{11} = \frac{1}{25}\omega^{-1}, \quad Y_{12} = -\frac{1}{25}\omega^{-1}$$

$$Y_{21} = \frac{1}{25}\omega^{-1}, \quad Y_{22} = -\frac{3}{100}\omega^{-1}$$

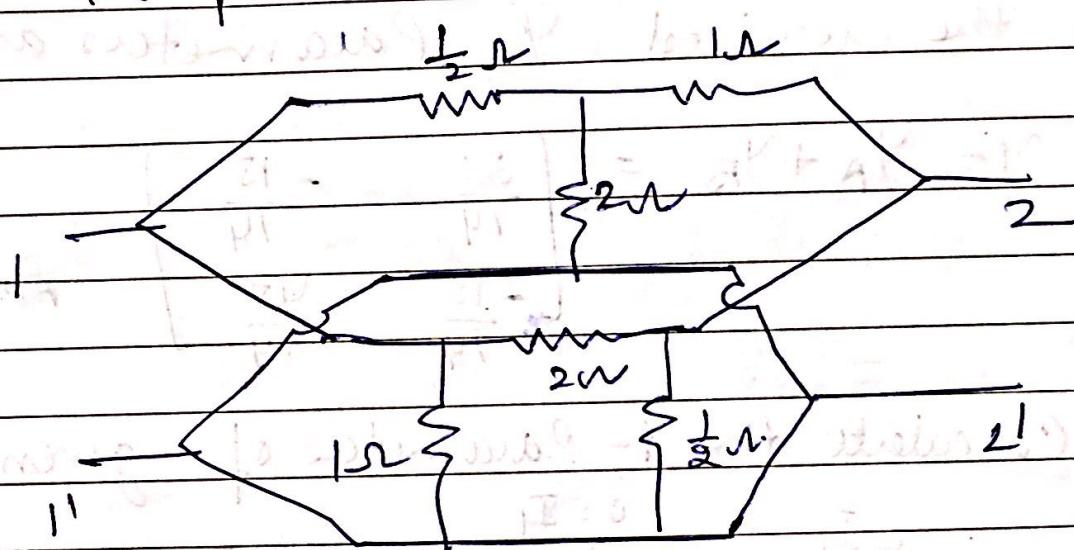Q.16 The given network consists of a resistive-T and a resistive-II network connected in parallel. Calculate Y-Parameters.



Soln Y-Parameter of "IT" network :-

$$Y_A = [Z_A]^{-1} = \begin{bmatrix} \frac{1}{2} + 2 & 2 \\ 2 & 2 + 1 \end{bmatrix}^{-1}$$

$$= \begin{bmatrix} \frac{5}{2} & 2 \\ 2 & 3 \end{bmatrix}^{-1}$$

$$= \begin{bmatrix} \frac{6}{7} & -\frac{4}{7} \\ -\frac{4}{7} & \frac{5}{7} \end{bmatrix}$$

$$Y_B = \begin{bmatrix} 1 + \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} + 2 \end{bmatrix}$$

$$Y_B = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{2} \end{bmatrix}$$


So the required Y-Parameters are:-

$$Y = Y_A + Y_B = \begin{bmatrix} \frac{33}{14} & -\frac{15}{14} \\ -\frac{15}{14} & \frac{45}{14} \end{bmatrix}$$

Ans.

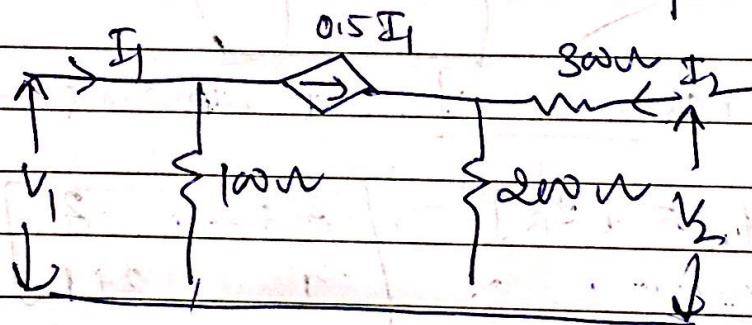Q.17

Calculate the Y-Parameters of given network



Soln)

$$V_1 = 100(I_1 - 0.5I_1)$$

$$\boxed{V_1 = 50I_1}, \quad \boxed{I_1 = \frac{V_1}{50}} \quad (1)$$

$$V_2 = 30I_2 + 20(I_2 + 0.5I_1)$$

$$\boxed{V_2 = 100I_1 + 500I_2} \quad (2)$$

Putting the value of I_1 from eqn (1) into (2).

DOMS

$$V_2 = 100 \left(\frac{V_1}{50} \right) + 500 I_2$$

$$V_2 = 2V_1 + 500 I_2$$

$$500 I_2 = -2V_1 + V_2$$

$$I_2 = -\frac{2}{500} V_1 + \frac{1}{500} V_2$$

$$I_2 = -\frac{1}{250} V_1 + \frac{1}{500} V_2$$

So

$$Y_{11} = \frac{1}{50} \Omega^{-1} \quad , \quad Y_{12} = 0$$

$$Y_{21} = -\frac{1}{250} \Omega^{-1} \quad , \quad Y_{22} = \frac{1}{500} \Omega^{-1}$$

Ans

③ h-Parameters (Hybrid Parameters).

hybrid parameters are widely used
in electronics circuit, especially in
constructing models for transistors

$$(V_1, I_2) = f(I_1, V_2)$$


$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

DOMS

Equivalent Circuit:-

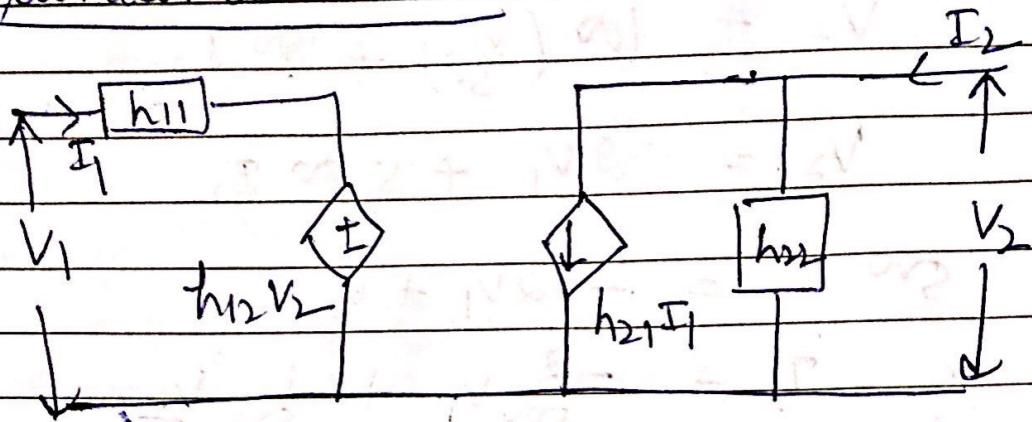

Case 1 :- when $V_2 = 0$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}, \quad h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

Case 2 when $I_1 = 0$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}, \quad h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

$h_{11} \rightarrow \text{ZIP impedance with O/P circuit}$


short circuited,

$h_{21} \rightarrow$ forward Current gain with o/p Port short circuited.


$h_{12} \rightarrow$ Reverse Voltage Gain with the ZIP Port open circuited.

$h_{22} \rightarrow$ output Admittance with the input port open circuited.

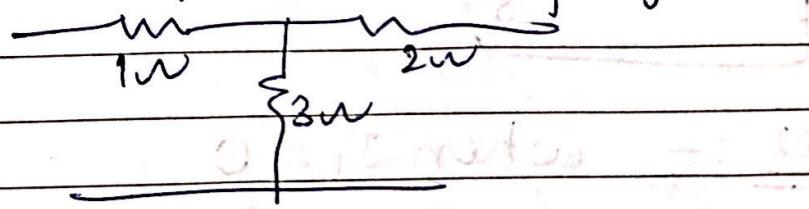Q.18 obtain h-parameters of given network.



Soln

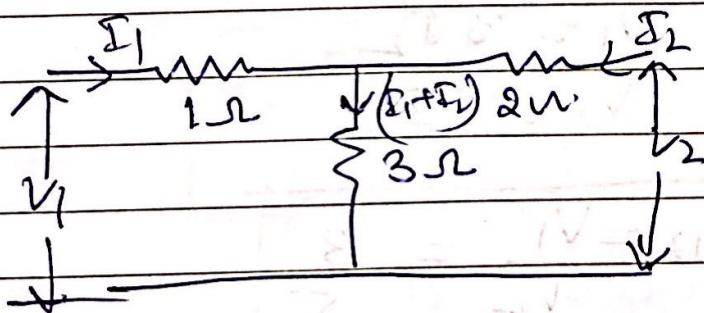

$$V_1 = 4I_1 + 3I_2 \quad \text{---} \textcircled{1}$$

$$V_2 = 3I_1 + 5I_2 \quad \text{---} \textcircled{2}$$

Case 1 when $V_2 = 0$

$$3I_1 = -5I_2$$

$$I_2 = -\frac{3}{5}I_1, \quad I_1 = -\frac{5}{3}I_2$$

Putting value of I_2 in eqⁿ $\textcircled{1}$:-

$$V_1 = 4I_1 + 3\left(-\frac{3}{5}I_1\right)$$

$$V_1 = 4I_1 - \frac{9}{5}I_1$$

$$\boxed{V_1 = \frac{11}{5}I_1}$$

So $\boxed{h_{11} = \frac{11}{5}\Omega}$

$$h_{21} = -\frac{3}{5}$$

Case 2 :- when $I_1 \neq 0$


$$V_1 = 3 I_2$$

$$V_2 = 5 I_2$$

so
$$h_{12} = \frac{V_1}{V_2} = \frac{3}{5}$$

$$h_{22} = \frac{I_2}{V_2} = \frac{1}{5} \text{ or } 1$$

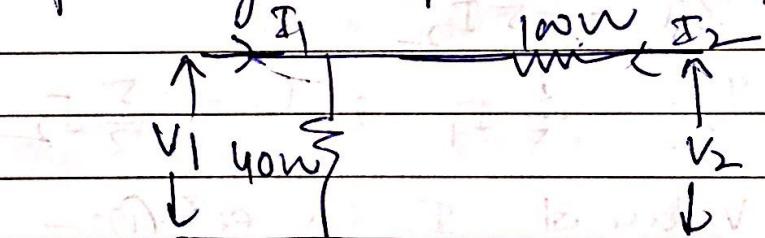Q. 19 find hybrid parameters of given network



Soln

$$V_1 = 40(I_1 + I_2)$$

$$V_1 = 40I_1 + 40I_2 \quad \text{--- (1)}$$

$$V_2 = 100I_2 + 40(I_1 + I_2)$$

$$V_2 = 40I_1 + 140I_2 \quad \text{--- (2)}$$

DOMS

Case 1 when $V_2 = 0$

$$40I_1 = -140I_2$$

$$I_1 = -\frac{7}{2}I_2 \quad \text{--- (3)}$$

$$I_2 = \frac{2}{7}I_1 \quad \text{--- (3)}$$

Putting value of I_2 from (3) in (1):-

$$V_1 = 40I_1 + 40\left(-\frac{2}{7}I_1\right)$$

$$V_1 = 40I_1 - \frac{80}{7}I_1$$

$$V_1 = \frac{200}{7}I_1$$

$$\text{So } h_{11} = \frac{200}{7} \text{ n}$$

$$h_{21} = \frac{I_2}{I_1} = -\frac{2}{7}$$

Case 2:- when $I_1 = 0$

$$V_1 = 40I_2$$

$$V_2 = 140I_2$$


$$h_{12} = \frac{40}{140} = \frac{2}{7}$$

Doms

$$h_{22} = \frac{140}{140} = 1$$

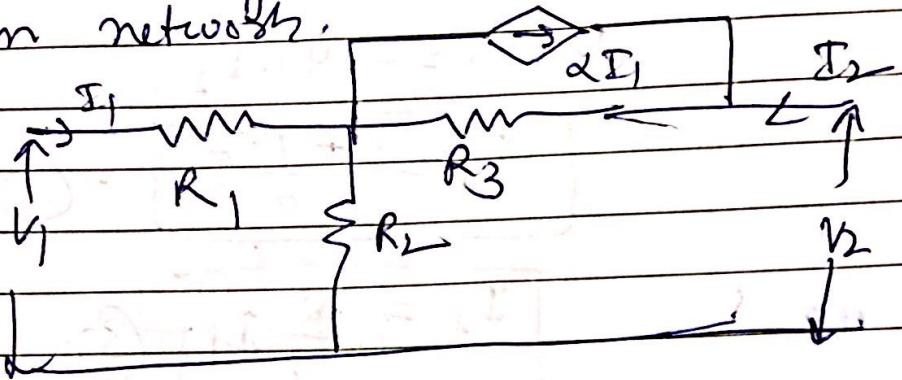
Q.20

find the hybrid parameters of the given network.



SOLN

Case 1: when $V_2 = 0$

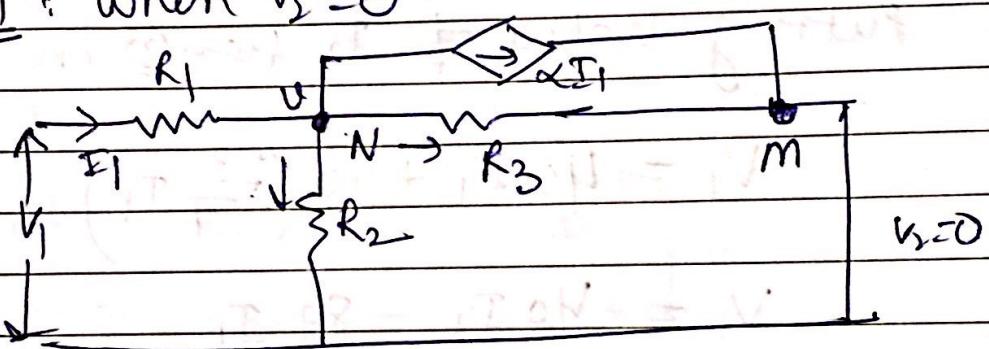

Let v be the voltage at the junction of R_1, R_2 & R_3 . Then applying KCL at node N :

$$I_1 = \frac{v}{R_2} + \frac{v}{R_3} + \alpha I_1$$

this gives:-

$$v = \frac{(1-\alpha) I_1 R_2 R_3}{R_2 + R_3}$$

Applying KVL:-

$$V_1 = I_1 R_1 + v$$

Putting value of v :-

DOMS

$$V_1 = I_1 \cdot R_1 + \frac{(1-\alpha) I_1 R_2 R_3}{R_2 + R_3}$$

$$V_1 = E_1 \left[R_1 + \frac{(1-\alpha) R_2 R_3}{R_2 + R_3} \right]$$

Applying KCL at node M:-

$$\frac{V}{R_3} + \alpha I_1 + I_2 = 0$$

$$E_2 = -\alpha I_1 - \frac{V}{R_3}$$

$$= -\alpha I_1 - \frac{1}{R_3} \left[\frac{(1-\alpha) I_1 R_2 R_3}{R_2 + R_3} \right]$$

$$I_2 = I_1 \left[-\alpha - \frac{(1-\alpha) R_2}{R_2 + R_3} \right]$$


$$= -I_1 \left[\frac{\alpha R_2 + \alpha R_3 - R_2 + \alpha R_2}{R_2 + R_3} \right]$$

$$I_2 = -I_1 \left[\frac{\alpha R_3 + R_2}{R_2 + R_3} \right]$$

$$\text{So } h_{11} = \frac{V_1}{I_1} = \left[R_1 + \frac{(1-\alpha) R_2 R_3}{R_2 + R_3} \right] \Omega$$

$$h_{21} = \frac{I_2}{I_1} = - \left[\frac{\alpha R_3 + R_2}{R_2 + R_3} \right]$$

case 2 :- when $I_1 = 0$

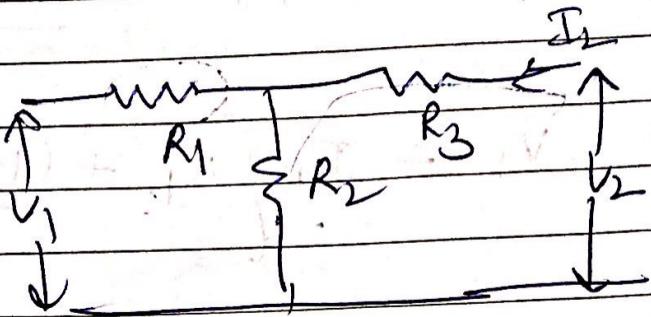


$$V_2 = I_2 R_2 + I_2 R_3$$

$$V_1 = I_2 R_2$$

$$\text{So } h_{12} = \frac{V_1}{V_2} = \frac{R_2}{R_2 + R_3}$$

$$h_{22} = \frac{I_2}{V_2} = \frac{1}{R_2 + R_3}$$

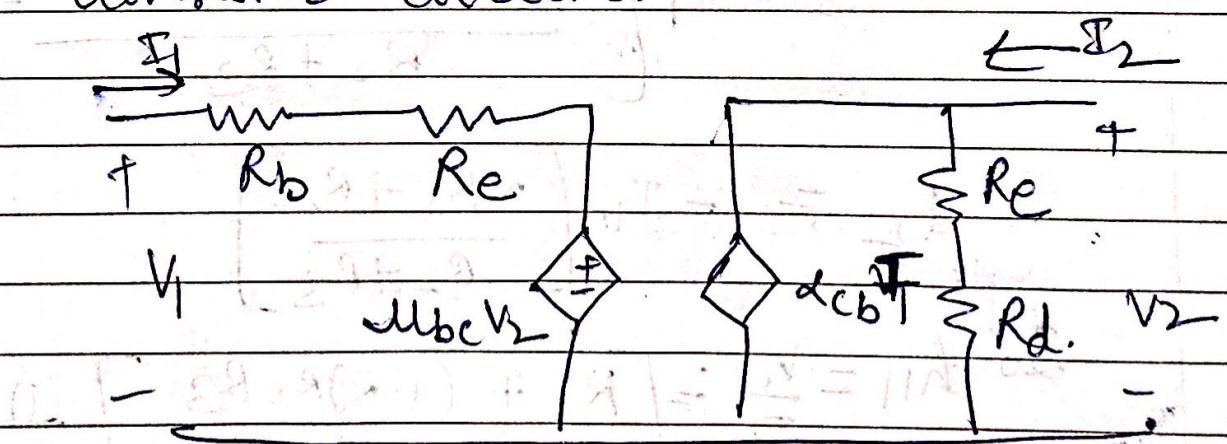Q.2) Calculate h - parameters of a model of a common-emitter connected transistor circuit.



Soln $V_1 = (R_b + R_e) I_1 + \mu_{bc} V_2$ → (1)


DOMS

$$V_2 = \alpha_{cb} I_1 + \frac{V_2}{R_e + R_d} \quad (2)$$

$$\text{So } h_{11} = R_b + R_e \quad h_{12} = \alpha_{bc}$$

$$h_{21} = \alpha_{cb} \quad h_{22} = \frac{1}{R_e + \frac{1}{R_d}}$$

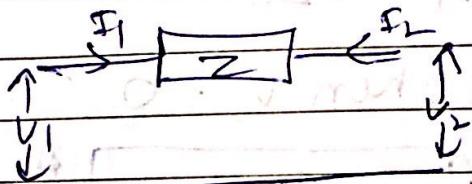Q.22 obtain h-parameters of given network:



$$V_1 = V_2 + I_1 Z \quad (1)$$

$$I_1 = -I_2$$

Case 1: when $V_2 = 0$

$$V_1 = I_1 Z$$

$$h_{11} = \frac{V_1}{I_1} = Z_L$$

$$h_{21} = \frac{I_2}{I_1} = -1$$

Case 2: when $I_1 = 0$

$$V_1 = V_2$$

$$I_1 = -I_2$$


$$h_{12} = \frac{V_1}{V_2} = 1$$

$$h_{22} = \frac{I_2}{V_2} = 0$$

DOMS

Q.23

obtain h-Parameters of given network!

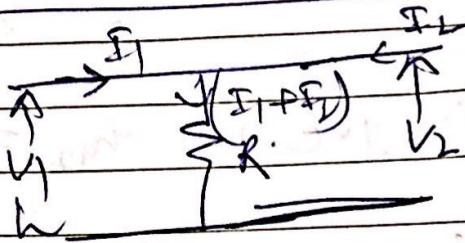

Soln

$$V_1 = RI_1 + RI_2$$

$$V_2 = RI_1 + RI_2$$

$$V_1 = V_2$$

Case 1:- when $V_2 = 0$

$$\boxed{h_{11} = \frac{V_1}{I_1} = 0 \Omega}$$

As ($V_1 = V_2 = 0$)

$$\boxed{h_{21} = \frac{I_2}{I_1} = -1 \Omega}$$

Case 2:- when $I_1 = 0$

$$V_1 = RI_2$$

$$V_2 = RI_2$$

$$\boxed{h_{12} = \frac{V_1}{V_2} = 1}$$

$$\boxed{h_{22} = \frac{V_2}{I_2} = \frac{1}{R} \Omega}$$

DOMS

(4) Transmission (T) or chain or ABCD Parameters:-

$$(V_1, I_1) = f (V_2, -I_2)$$

T-parameters are used in analysis of power transmission lines. The input and output ports are called the sending & receiving ends respectively.

(since in this case, output port current is considered outward, so the negative sign arises with I_2 .)

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

Case 1: when $I_2 = 0$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} \quad \& \quad C = \frac{I_1}{V_2} \Big|_{I_2=0}$$

Case 2: when $V_2 = 0$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} \quad \& \quad D = \frac{I_1}{-I_2} \Big|_{V_2=0}$$

A \rightarrow Reverse Voltage Ratio with o/p port open circuited

C \rightarrow Reverse Transfer Admittance with o/p port open circuited



B \rightarrow Reverse Transfer Impedance with o/p port short circuited.

D \rightarrow Reverse Current Ratio with o/p port short circuited.

DOMS

* The equivalent circuit of a two-port network is not possible in terms of T-parameters.

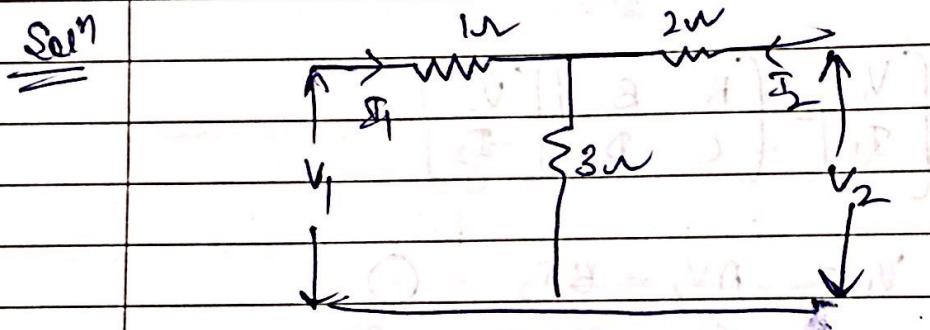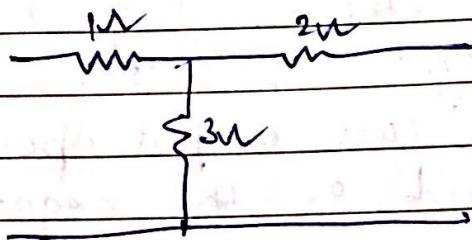Q.24 obtain T-parameters of a given network



$$V_1 = 4I_1 + 3\delta_2 \quad \text{---} \textcircled{1}$$

$$V_2 = 8I_1 + 5I_2 \quad \text{---} \textcircled{2}$$

Case 1: when $I_2 = 0$

$$V_1 = 4I_1$$

$$V_2 = 3\delta_1$$

$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{4}{3}, \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{3} \text{ ohm}^{-1}$$

Case 2: when $V_2 = 0$

$$3I_1 = -5I_2 \Rightarrow I_1 = -\frac{5}{3}\delta_2$$

$$V_1 = 4\left(-\frac{5}{3}\delta_2\right) + 3\delta_2$$


$$\text{DOMS} \quad \therefore V_1 = -\frac{11}{3}\delta_2$$

$$B = \frac{V_1}{-I_2} \Big|_{V_2=0} = \frac{1}{3} \Omega \quad \text{Ans}$$

$$D = \frac{I_1}{-I_2} \Big|_{V_2=0} = \frac{5}{3} \quad \checkmark$$

Q.25 obtain T-parameters of given network.

Q.

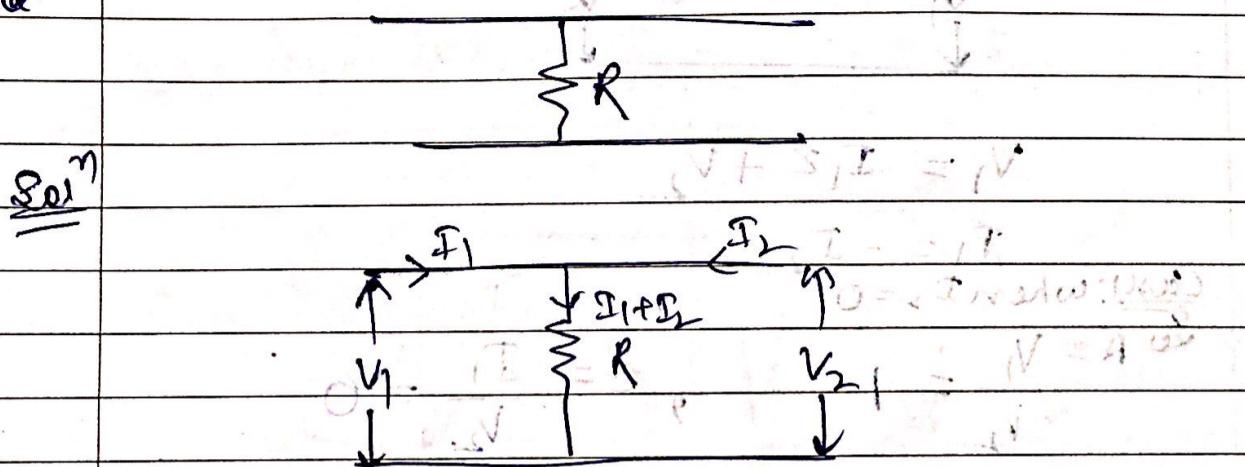

$$V_1 = RI_1 + RI_2 \quad \text{---(1)}$$

$$V_2 = RI_1 - RI_2 \quad \text{---(2)}$$

Case 1: when $I_2 = 0$

$$V_1 = RI_1 \quad \text{---(3)}$$

$$V_2 = RI_1 \quad \text{---(4)}$$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = 1 \quad , \quad C = \frac{V_1}{V_2} \Big|_{I_2=0} = \frac{1}{R}$$

Case 2: when $I_1 = 0$


$$RI_1 = V_1 - RI_2$$

$$\boxed{I_1 = -I_2}$$


$$V_1 = R(-I_2) + RI_2 = 0 \quad , \quad D = \frac{I_1}{-I_2} \Big|_{V_1=0} = 1$$

$$\text{So } B = \frac{V_1}{-I_2} = 0 \quad \text{DOMS} \quad \text{So } [T] = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \text{ Ans.}$$

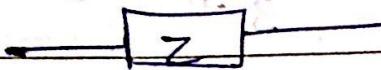Q.26 obtain T-parameters of given network



Soln

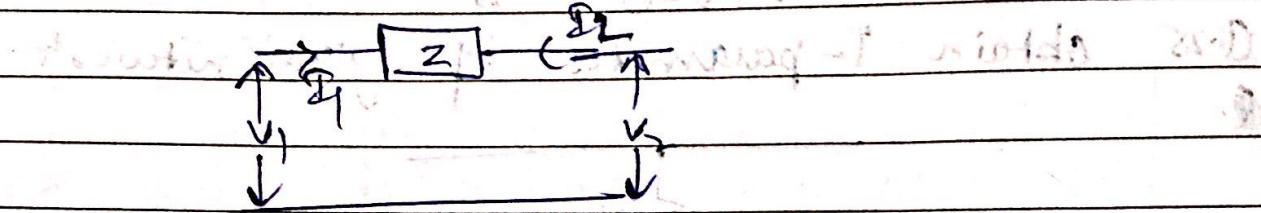

$$V_1 = I_1 Z + V_2$$

$$I_1 = -I_2$$

Case 1: when $I_2 = 0$

$$\text{So } A = \frac{V_1}{V_2} = 1, \quad B = \frac{I_1}{V_2} = 0$$


Case 2: when $V_2 = 0$


$$B = \frac{V_1}{-I_2} = Z, \quad D = \frac{I_1}{-I_2} = 1$$

So

$$[T] = \begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$

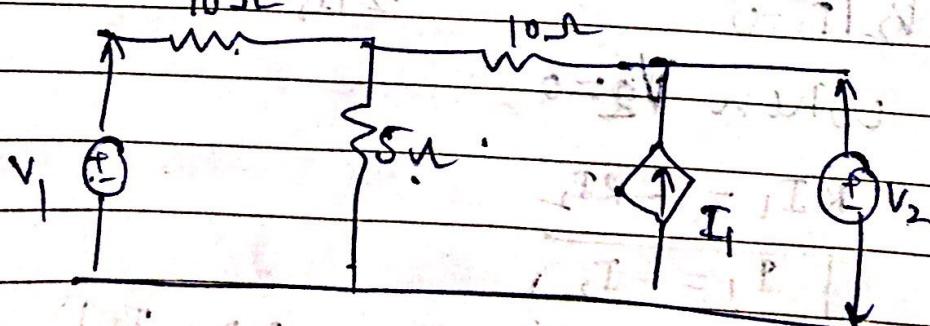Q.27 obtain ABCD parameters of the given circuit



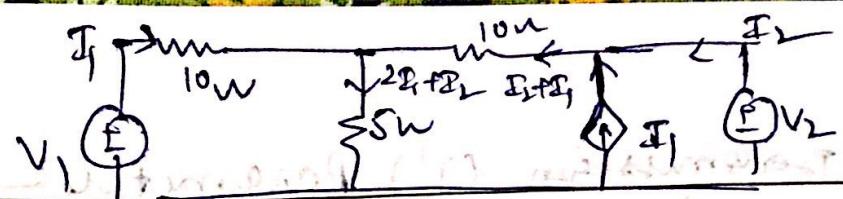

Ques

Applying KV2 :- $V_1 = 10(I_1 + I_2)$

$$V_1 = 10I_1 + 5(2I_1 + I_2) \quad (1)$$

$$V_1 = 20I_1 + 5I_2 \quad (1)$$

$$V_2 = 10(I_2 + I_1) + 5(2I_1 + I_2)$$

$$V_2 = 10I_2 + 10I_1 + 10I_1 + 5I_2 \quad (2)$$

$$V_2 = 20I_1 + 15I_2 \quad (2)$$

Case 1 : when $I_2 = 0$

$$A = \frac{V_1}{V_2} = 1, \quad C = \frac{I_1}{V_2} = \frac{1}{20} \text{ ohm}^{-1}$$

Case 2 : when $V_2 = 0$

$$B = \frac{V_1}{-I_2}, \quad I_1 = -\frac{15}{20}I_2$$

$$B = \frac{10I_2}{-I_2}, \quad I_1 = -\frac{3}{4}I_2$$

$$V_1 = 20\left(-\frac{3}{4}I_2\right) + 5I_2$$

$$V_1 = -15I_2 + 5I_2$$

$$V_1 = -10I_2$$

$$D = \frac{3}{4}$$

* Inverse Transmission (T') Parameters

$$(V_2, I_2) = f(V_1, -I_1)$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}$$

$$V_2 = A'V_1 - B'I_1 \quad \text{--- (1)}$$

$$I_2 = C'V_1 - D'I_1 \quad \text{--- (2)}$$

Case 1: when $I_1 = 0$

$$V_2 = A'V_1$$

$$I_2 = C'V_1$$

$$A' = \frac{V_2}{V_1} \Big|_{I_1=0}$$

$$C' = \frac{I_2}{V_1} \Big|_{I_1=0}$$

Case 2: when $V_1 = 0$

$$V_2 = -B'I_1$$

$$I_2 = -D'I_1$$

$$B' = \frac{V_2}{-I_1} \Big|_{V_1=0}$$

$$D' = \frac{I_2}{-I_1} \Big|_{V_1=0}$$

A' \rightarrow forward voltage Ratio with F/P Port open
circuited.

C' \rightarrow Transfer Admittance with F/P port open
circuited.

B' \rightarrow Transfer Impedance with F/P port
short circuited.

D' \rightarrow forward current Ratio with F/P port
short circuited.

* Inverse Hybrid (g) Parameters :-

From $\frac{V_2}{I_2} = \frac{1}{g_{11}}$


$$[g] = [h]^{-1}$$

Impedance $Z = (I_1, V_2) = f(V_1, I_2)$

Assume $I_1 = g_{11}V_1 + g_{12}I_2$ - (1)

$V_2 = g_{21}V_1 + g_{22}I_2$ - (2)

Equivalent ckt of 2-port in terms of g- parameters:-

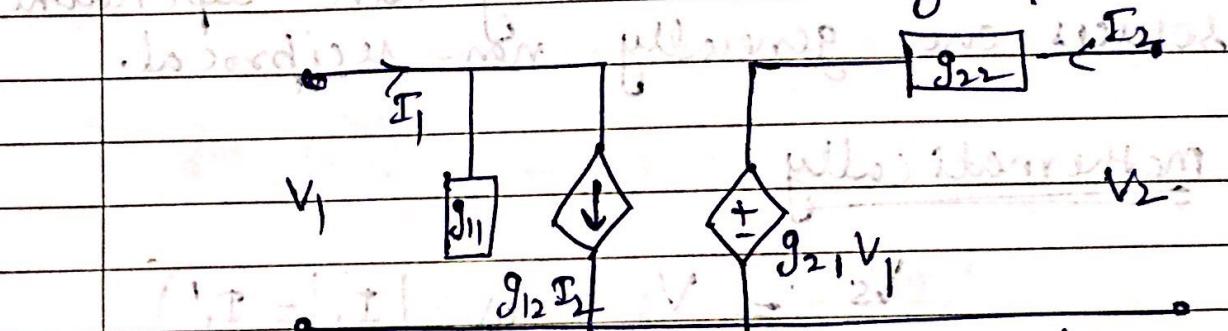

Case 1: when $I_2 = 0$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

Case 2: when $V_1 = 0$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$

$g_{11} \rightarrow \text{I/P Admittance with o/p Port open circuited}$

$g_{21} \rightarrow \text{forward Voltage Gain with o/p Port open circuited}$

$g_{12} \rightarrow \text{Reverse Current Gain with I/P Port short circuited}$

$g_{22} \rightarrow \text{o/p Impedance with I/P Port short Circuited}$

* Condition for Reciprocity :- A two port network is said to be reciprocal, if the ratio of the excitation to response is invariant to an interchange of the position of excitation and response in the network.

- Networks containing resistors, inductors & capacitors are generally reciprocal.
- Networks that additionally have dependent sources are generally non-reciprocal.

Mathematically :

$$\frac{V_s}{I_2} = \frac{V_s}{I'_1} \quad \text{or} \quad I'_2 = I'_1$$

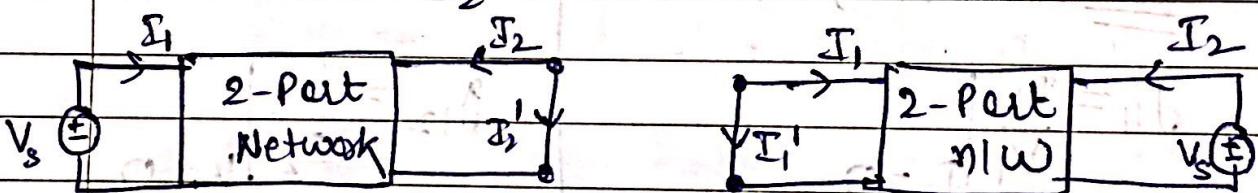


fig (a)

fig (b)

$$V_1 = V_s$$

$$I_1 = I_2$$

$$V_2 = 0$$

$$I_2 = -I'_1$$

$$V_2 = V_s$$

$$I_2 = I'_2$$

$$I_1 = -I'_1$$

$$V_1 = 0$$

① condition for Reciprocity in terms of Z-Parameters:-

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (2)}$$

from fig(a)

$$V_1 = V_s, \quad I_1 = I_1, \quad V_2 = 0, \quad I_2 = -I_2$$

Putting these values in eqn (1) & (2) :-

$$V_s = Z_{11} I_1 - Z_{12} I_2' \quad \text{--- (3)}$$

$$0 = Z_{21} I_1 - Z_{22} I_2' \quad \text{--- (4)}$$

from eqn (4) :- $-Z_{21} I_1 = Z_{22} I_2'$

$$I_1 = \frac{Z_{22} I_2'}{Z_{21}}$$

Putting value of I_1 in eqn (3) :-

$$V_s = Z_{11} \left(\frac{Z_{22} I_2'}{Z_{21}} \right) - Z_{12} I_2'$$

$$= Z_{11} Z_{22} I_2' - Z_{12} Z_{21} I_2'$$

$$V_s = (Z_{11} Z_{22} - Z_{12} Z_{21}) I_2'$$

$$\boxed{\frac{V_s}{I_2'} = \frac{\Delta Z}{Z_{21}}} \quad \text{--- (5)}$$

DOMS

from fig(b) :-

$$V_2 = V_S, I_2 = I_1', V_1 = 0, I_1 = -I_1'$$

So from eqn (6) & (7) :-

$$0 = -Z_{11} I_1' + Z_{12} I_2 \quad \text{--- (6)}$$

$$V_S = -Z_{21} I_1' + Z_{22} I_2 \quad \text{--- (7)}$$

So from eqn (6) :-

$$Z_{12} I_2 = Z_{11} I_1'$$

$$I_2 = \frac{Z_{11}}{Z_{12}} I_1' \quad \text{--- (8)}$$

Putting value of I_2 in eqn (7) :-

$$V_S = -Z_{21} I_1' + Z_{22} \left(\frac{Z_{11}}{Z_{12}} I_1' \right)$$

$$V_S = -Z_{12} Z_{21} I_1' + Z_{11} Z_{22} I_1'$$

$$V_S = (Z_{11} Z_{22} - Z_{12} Z_{21}) I_1'$$

$$\boxed{\frac{V_S}{I_1'} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{12}}} \quad \text{--- (8)}$$

Now from eqn (5) & (8) :-

$$\boxed{Z_{12} = Z_{21}} \quad \text{DOMS}$$

② Condition of Reciprocity in terms of Y-Parameters

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- (1)}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- (2)}$$

from fig.(a)

$$V_1 = V_S, I_1 = I_1, V_2 = 0, P_2 = -I_2'$$

$$I_1 = Y_{11}V_S$$

$$-I_2' = Y_{21}V_S$$

$$\boxed{\frac{V_S}{I_2'} = -Y_{21}} \quad \text{--- (3)}$$

from fig(b):—

$$V_2 = V_S, I_2 = I_2, V_1 = 0, I_1 = -I_1'$$

$$-I_1' = Y_{12}V_S$$

$$I_2 = Y_{22}V_S$$

$$\boxed{\frac{V_S}{I_1'} = Y_{12}} \quad \text{--- (4)}$$

on comparing eqn (3) & (4):—

$$\boxed{Y_{12} = Y_{21}}$$

This is the condition of reciprocity in terms of Y-parameters.

3) In terms of T-Parameters: → (3)

$$V_1 = AV_2 - BS_2 \quad (1)$$

$$I_1 = CV_2 - DS_2 \quad (2)$$

from fig(a):— $V_1 = V_s$, $I_1 = I_1$, $V_2 = 0$, $I_2 = -S_2$

$$V_s = BS_2$$

$$\frac{V_s}{S_2} = B \quad (3)$$

from fig(b):— $V_2 = V_s$, $I_2 = S_2$, $V_1 = 0$, $I_1 = -S_1$

$$0 = AV_s - BS_2 \quad (4)$$

$$-I_1' = CV_s - DS_2 \quad (5)$$

from eqⁿ(4):—

$$AV_s = BS_2$$

$$S_2 = \left(\frac{A}{B}\right)V_s$$

Putting value of S_2 in eqⁿ(5):—

$$-I_1' = CV_s - B \left(\frac{A}{B}V_s\right)$$

$$-I_1' = \left(\frac{BC - AB}{B}\right)V_s$$

$$I_1' = \left(\frac{AB - BC}{B}\right)V_s$$

$$\boxed{\frac{V_S}{I'}} = \boxed{\frac{AB - BC}{AD - BC}} \quad \text{--- (6)}$$

on comparing eqⁿ (3) & (6): →

$$B \Rightarrow \underline{B}$$

$$AD - BC \quad [AD = ad]$$

$$\boxed{AD - BC = 1} \quad \text{or} \quad \boxed{AT = 1}$$

← this is the condition of reciprocity in terms of T-parameters, (2)

(4) In terms of h-Parameters: →

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- (2)}$$

from fig (a): $V_1 = V_S, I_1 = I_1, V_2 = 0, I_2 = -I_2'$

$$V_S = h_{11} I_1$$

$$-I_2' = h_{21} I_1$$

$$\boxed{\frac{V_S}{I_2'} = -\frac{h_{11}}{h_{21}}} \quad \text{--- (3)}$$

from fig (b): $V_2 = V_S, I_2 = I_2, V_1 = 0, I_1 = -I_1'$

$$0 = -h_{11} I_1' + h_{12} V_S \quad \text{--- (4)}$$

$$I_2 = -h_{21} I_1' + h_{22} V_S \quad \text{--- (5)}$$

$$h_{11} I_1' = h_{12} V_S$$

$$\boxed{\frac{V_S}{I'} = \frac{h_{11}}{h_{12}}} \quad \text{--- (6)}$$

on comparing eqⁿ (3) & (6) :-

$$-\frac{h_{11}}{h_{21}} = \frac{h_{11}}{h_{12}}$$

So
$$h_{12} = -h_{21}$$

Similarly

(5) In terms of T Parameters :-

$$\Delta T^T = 1$$

(6) In terms of g Parameters :-

$$g_{12} = -g_{21}$$

* Condition of Symmetry :-

A 2-Port network is said to be symmetrical if the ports can be interchanged without changing the port voltages and currents.

Mathematically,

$$\left| \frac{V_2}{I_1} \right|_{I_2=0} = \left| \frac{V_1}{I_2} \right|_{I_1=0}$$

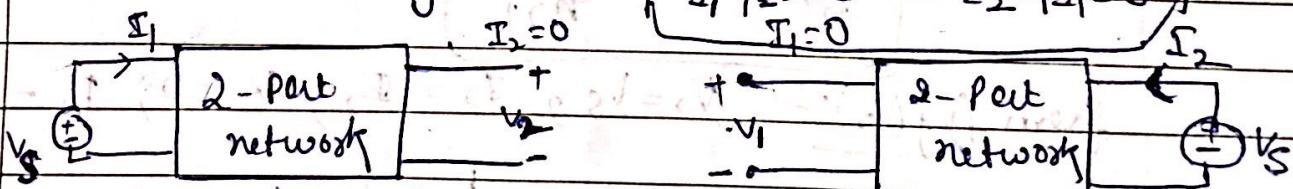


fig.(a)

$$V_1 = V_S, I_1 = I_1$$

$$I_2 = 0, V_2 = V_2$$

$$V_2 = V_S, I_1 = 0$$

$$I_2 = I_2, V_1 = V_1$$

DOMS

i) In terms of Z-parameters:-

from fig.(a) $V_1 = V_S$, $I_2 = 0$

$$I_1 = I_1 \quad , \quad V_2 = V_2$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$V_S = Z_{11} I_1$$

$$V_2 = Z_{21} I_1$$

So $\boxed{\begin{array}{|c|c|} \hline V_S & = Z_{11} \\ \hline I_1 & I_2 = 0 \\ \hline \end{array}}$

from fig.(b) :-

$$V_2 = V_S, \quad I_1 = 0$$

$$I_2 = I_2 \quad , \quad V_1 = V_1$$

$$V_1 = Z_{12} I_2$$

$$V_S = Z_{22} I_2$$

So $\boxed{\begin{array}{|c|c|} \hline V_S & = Z_{22} \\ \hline I_2 & I_1 = 0 \\ \hline \end{array}}$

from the definition of Symmetry

$$\boxed{\frac{V_S}{I_1} \Big|_{I_2=0} = \frac{V_S}{I_2} \Big|_{I_1=0}} \quad \text{made to}$$

$$\boxed{Z_{11} = Z_{22}}$$

DOMS

ii) In terms of γ -Parameters -

from fig.(a) :- $V_1 = V_S$, $I_1 = I_1$, $I_2 = 0$, $V_2 = V_2$

eqn of $\gamma = P$

$$I_1 = \gamma_{11} V_1 + \gamma_{12} V_2 \quad \text{--- (1)}$$

$$I_2 = \gamma_{21} V_1 + \gamma_{22} V_2 \quad \text{--- (2)}$$

$$I_1 = \gamma_{11} V_S + \gamma_{12} V_2 \quad \text{--- (3)}$$

$$0 = \gamma_{21} V_S + \gamma_{22} V_2 \quad \text{--- (4)}$$

$$V_2 = -\frac{\gamma_{21} V_S}{\gamma_{22}}$$

Putting value of V_2 in eqn (3) :-

$$I_1 = \gamma_{11} V_S + \gamma_{12} \left[-\frac{\gamma_{21} V_S}{\gamma_{22}} \right]$$

$$I_1 = \left[\gamma_{11} \gamma_{22} - \gamma_{12} \gamma_{21} \right] V_S$$

$$\frac{V_S}{I_1} = \frac{\gamma_{22}}{\gamma_{11} \gamma_{22} - \gamma_{12} \gamma_{21}}$$

$$\boxed{\frac{V_S}{I_1} = \frac{\gamma_{22}}{\Delta Y}} \quad \text{--- (5)}$$

from fig. (b) $V_2 = V_S$, $I_2 = I_2$, $I_1 = 0$, $V_1 = V_1$

$$0 = Y_{11}V_1 + Y_{12}V_S$$

$$\Sigma_2 = Y_{21}V_1 + Y_{22}V_S.$$

$$\boxed{\frac{V_S}{\Sigma_2} = \frac{Y_{11}}{Y_{11}Y_{22} - Y_{12}Y_{21}}} \quad \textcircled{6}$$

equating eqn ⑤ & ⑥:-

$$\boxed{Y_{11} = Y_{22}}$$

iii) In terms of T-parameters:-

from fig(a):

$$V_1 = V_S$$

$$\Sigma_2 = 0$$

$$\Sigma_1 = I_1$$

$$V_2 = V_2$$

eqn of T-Parameters:-

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

$$V_S = AV_2$$

$$I_1 = CV_2$$

so

$$\boxed{\frac{V_S}{\Sigma_1} = \frac{A}{C}} \quad \textcircled{1}$$

from fig(b) : $V_2 = V_S \Rightarrow \Sigma_2 = \Sigma_1, I_1 = 0, V_1 = V_1$

$$V_1 = AV_S - BI_2$$

$$0 = CV_S - DI_2$$

DOMS

So

$$\boxed{\frac{V_s}{I_2} = \frac{D}{C}} \quad (2)$$

from eqn (1) & (2): -

$$\frac{A}{C} = \frac{D}{C}$$

$$\boxed{A = D}$$

(iv)

In terms of h-Parameters:-

from fig. (a) $V_1 = V_s$, $I_1 = I_1$, $I_2 = 0$, $V_2 = V_2$

$$V_s = h_{11} I_1 + h_{12} V_2$$

$$0 = h_{21} I_1 + h_{22} V_2$$

$$\boxed{\frac{V_s}{I_1} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}}} \quad (1)$$

from fig (b) :- $V_2 = V_s$, $I_2 = I_2$, $I_1 = 0$, $V_1 = V_1$

$$V_1 = h_{12} V_s$$

$$I_2 = h_{22} V_s$$

a

$$\boxed{\frac{V_s}{I_2} = \frac{1}{h_{22}}}$$

Therefore the condition for Symmetry :-

DOMS

$$\frac{V_s}{I_1} \Big|_{I_2=0} = \frac{V_s}{I_2} \Big|_{I_1=0} \quad \text{leads to}$$

$$h_{11}h_{22} - h_{12}h_{21} = 1$$

$$\boxed{\Delta h = 1}$$

v) In terms of g - Parameters:-

$$g_{11}g_{22} - g_{12}g_{21} = 1$$

$$\text{or } \boxed{\Delta g = 1}$$

vi) In terms of inverse T Parameters:-

$$\boxed{A' = D'}$$

Relationships Between Parameter Sets:-

If we want to express α -parameters in terms of β -Parameters, we have to write β -parameter equations and then by algebraic manipulation, rewrite the equations as needed for α -parameters.

① Z-Parameters in terms of Y-Parameters:-

$$[I] = [Y][V]$$

$$[V] = [Z][I]$$

$$\text{So } [Z] = [Y]^{-1}$$

$$\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1} = \frac{1}{\Delta Y} \begin{bmatrix} Y_{22} & -Y_{12} \\ -Y_{12} & Y_{11} \end{bmatrix}$$

DOMS

$$\text{So } Z_{11} = \frac{Y_{22}}{\Delta Y}, \quad Z_{12} = -\frac{Y_{12}}{\Delta Y}$$

$$Z_{21} = -\frac{Y_{21}}{\Delta Y}, \quad Z_{22} = \frac{Y_{11}}{\Delta Y}$$

(2) Z-Parameters in terms of T-Parameters:-

$$\begin{aligned} V_1 &= AV_2 + BI_2 \quad \text{--- (1)} \\ I_1 &= CV_2 - DI_2 \quad \text{--- (2)} \end{aligned} \quad \left[\begin{array}{l} V_1 = Z_{11}I_1 + Z_{12}I_2 \\ V_2 = Z_{21}I_1 + Z_{22}I_2 \end{array} \right]$$

Rewriting eqn (2):-

$$V_2 = \frac{1}{C}I_1 + \frac{D}{C}I_2 \quad \text{--- (3)}$$

Putting the value of V_2 from eqn (3) into eqn (1):-

$$V_1 = A \left[\frac{1}{C}I_1 + \frac{D}{C}I_2 \right] - BI_2$$

$$V_1 = \frac{A}{C}I_1 + \frac{AD-BC}{C}I_2$$

$$V_1 = \frac{A}{C}I_1 + \frac{\Delta T}{C}I_2 \quad \text{--- (4)}$$

Comparing eqn (3) & (4) with eqn's of Z-Parameters:-

$$Z_{11} = \frac{A}{C}, \quad Z_{21} = \frac{1}{C}$$

$$Z_{12} = \frac{\Delta T}{C}, \quad Z_{22} = \frac{D}{C}$$

③ z-parameters in terms of h-parameters :-

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad (1) \quad \left[\begin{array}{l} V_1 = Z_{11} I_1 + Z_{12} I_2 \\ V_2 = Z_{21} I_1 + Z_{22} I_2 \end{array} \right]$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad (2)$$

Rewriting eqⁿ (2) :-

$$V_2 = -\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \quad (3)$$

Putting value of V_2 from eqⁿ (3) into eqⁿ (1) :-

$$V_1 = h_{11} I_1 + h_{12} \left[-\frac{h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right]$$

$$V_1 = \left[h_{11} - \frac{h_{12} h_{21}}{h_{22}} \right] I_1 + \frac{h_{12}}{h_{22}} I_2$$

$$V_1 = \frac{\Delta h}{h_{22}} I_1 + \frac{h_{12}}{h_{22}} I_2 \quad (4)$$

Comparing eqⁿ (3) & (4) with eqⁿs of Z-Parameters :-

$$Z_{11} = \frac{\Delta h}{h_{22}}, \quad Z_{12} = \frac{h_{12}}{h_{22}}$$

$$Z_{21} = -\frac{h_{21}}{h_{22}}, \quad Z_{22} = \frac{1}{h_{22}}$$

(4) z-parameters in terms of g-parameters :-

$$Z_{11} = \frac{1}{g_{11}}, \quad Z_{12} = -\frac{g_{12}}{g_{11}}, \quad Z_{21} = \frac{g_{21}}{g_{11}} \quad \& \quad Z_{22} = \frac{\Delta g}{g_{11}}$$

* Y-Parameters in terms of other Parameters:-

(3) Y-Parameters in terms of Z-Parameters:-

$$[Y] = [Z]^{-1}$$

$$Y_1 = \frac{z_{22}}{\Delta z}, Y_{12} = -\frac{z_{12}}{\Delta z}, Y_{21} = -\frac{z_{21}}{\Delta z} \text{ & } Y_{22} = \frac{z_{11}}{\Delta z}.$$

(6) Y-Parameters in terms of T-Parameters:-

$$V_1 = AV_2 - BV_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DV_2 \quad \text{--- (2)}$$

Rewriting eqⁿ (1):-

$$I_2 = -\frac{1}{B}Y_1 + \frac{A}{B}V_2 \quad \text{--- (3)}$$

Putting the value of I_2 in eqⁿ (2):-

$$I_1 = CV_2 - D\left[-\frac{1}{B}Y_1 + \frac{A}{B}V_2\right]$$

$$I_1 = CV_2 + \frac{D}{B}Y_1 - \frac{AD}{B}V_2$$

$$I_1 = \frac{D}{B}Y_1 + \left(C - \frac{AD}{B}\right)V_2$$

$$I_1 = \frac{D}{B}Y_1 + \frac{AT}{B}V_2 \quad \text{--- (4)}$$

on comparing eqⁿ (3) & (4) with eqⁿs of Y-P:-

$$Y_{11} = \frac{D}{B}; \quad Y_{12} = -\frac{AT}{B}$$

$$Y_{21} = -\frac{1}{B}, \quad Y_{22} = \frac{A}{B}$$

DOMS

7 Y-Parameters in terms of h- Parameters:-

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad (1)$$

$$\begin{aligned} V_1 &= Y_{11} V_1 + Y_{12} V_2 \\ V_2 &= Y_{21} V_1 + Y_{22} V_2 \end{aligned}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad (2)$$

Rewriting the eqn (1) :-

$$I_1 = \frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \quad (3)$$

$$I_2 = h_{21} \left[\frac{1}{h_{11}} V_1 - \frac{h_{12}}{h_{11}} V_2 \right] + h_{22} V_2$$

$$I_2 = \frac{h_{21}}{h_{11}} V_1 + \frac{\Delta h}{h_{11}} V_2 \quad (4)$$

on comparing eqn (3) & (4) with eqns of Y-P:-

$$Y_{11} = \frac{1}{h_{11}}, \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

$$Y_{21} = \frac{h_{21}}{h_{11}}, \quad Y_{22} = \frac{\Delta h}{h_{11}}$$

8 Y-Parameters in terms of g- Parameters:-

$$Y_{11} = \frac{\Delta g}{g_{22}}, \quad Y_{12} = \frac{g_{12}}{g_{22}}$$

$$Y_{21} = -\frac{g_{21}}{g_{22}}, \quad Y_{22} = \frac{1}{g_{22}}$$

* T-Parameters in terms of other Parameters:-

(Q) T-Parameters in terms of Z-Parameters:-

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (1) \quad [V_1 = AV_2 - BV_2]$$
$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (2) \quad [V_2 = CV_2 - DV_2]$$

Rewriting eqn (2) :-

$$I_1 = \frac{1}{Z_{21}} V_2 + \frac{Z_{22}}{Z_{21}} (-I_2)$$

$$\boxed{I_1 = \frac{1}{Z_{21}} V_2 + \left(\frac{Z_{22}}{Z_{21}} \right) (-I_2)} \quad (3)$$

Putting value of I_1 in eqn (1) :-

$$V_1 = Z_{11} \left[\frac{1}{Z_{21}} V_2 - \frac{Z_{22}}{Z_{21}} I_2 \right] + Z_{12} I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{Z_{11} Z_{22}}{Z_{21}} I_2 + Z_{12} I_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}} V_2 + \left(\frac{Z_{12} Z_{21} - Z_{11} Z_{22}}{Z_{21}} \right) I_2$$

$$\boxed{V_1 = \frac{Z_{11}}{Z_{21}} V_2 - \frac{\Delta Z}{Z_{21}} I_2} \quad (4)$$

Comparing eqn (3) & (4) with eqns of Z-p :-

$$C = \frac{1}{Z_{21}} \quad , \quad D = \frac{Z_{22}}{Z_{21}}$$

$$A = \frac{Z_{11}}{Z_{21}}, \quad B = \frac{\Delta Z}{Z_{21}}$$

DOMS

(10) T-Parameters in terms of γ -Parameters:

$$A = -\frac{\gamma_{22}}{\gamma_{21}}, \quad B = -\frac{1}{\gamma_{21}}$$

$$C = -\frac{\Delta\gamma}{\gamma_{21}}, \quad D = -\frac{\gamma_{11}}{\gamma_{21}}$$

(11) T-Parameters in terms of h -Parameters:

$$\begin{aligned} V_1 &= h_{11}I_1 + h_{12}V_2 \quad \text{--- (1)} \\ I_2 &= h_{21}I_1 + h_{22}V_2 \quad \text{--- (2)} \end{aligned} \quad \left[\begin{array}{l} V_1 = AV_2 - BS_2 \\ I_1 = CV_2 - DS_2 \end{array} \right]$$

Rewriting eqⁿ (2):—

$$\left[I_1 = -\frac{h_{22}}{h_{21}}V_2 + \left(-\frac{1}{h_{21}}\right)(-S_2) \right] \quad \text{--- (3)}$$

Putting value of I_1 from eqⁿ (3) into eqⁿ (1):—

$$V_1 = h_{11} \left(-\frac{h_{22}}{h_{21}}V_2 + \left(-\frac{1}{h_{21}}\right)(-S_2) \right) + h_{12}V_2$$

$$\left[V_1 = -\frac{\Delta h}{h_{21}}V_2 - \left(\frac{h_{11}}{h_{21}}\right)(-S_2) \right] \quad \text{--- (4)}$$

On Comparing eqⁿ (3) & (4) with eqⁿs of T-Parameters:

$$A = -\frac{\Delta h}{h_{21}}, \quad B = -\frac{h_{11}}{h_{21}}$$

$$C = -\frac{h_{22}}{h_{21}}, \quad D = -\frac{1}{h_{21}}$$

(12) T-Parameters in terms of g-Parameters:

$$A = \frac{1}{g_{21}}, B = \frac{g_{22}}{g_{21}}, C = \frac{g_{11}}{g_{21}}, D = \frac{A \cdot g}{g_{21}}$$

* h-Parameters in terms of other Parameters:

(13) h-Parameters in terms of Z-Parameters:

$$\begin{aligned} V_1 &= Z_{11} I_1 + Z_{12} I_2 \quad (1) & V_1 &= h_{11} I_1 + h_{12} V_2 \\ V_2 &= Z_{21} I_1 + Z_{22} I_2 \quad (2) & I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

Rewriting the eqⁿ (2) :-

$$I_2 = -\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \quad (3)$$

Putting value of I_2 from eqⁿ (3) into (1) :-

$$V_1 = Z_{11} I_1 + Z_{12} \left(-\frac{Z_{21}}{Z_{22}} I_1 + \frac{1}{Z_{22}} V_2 \right)$$

$$V_1 = \left(Z_{11} - \frac{Z_{12} Z_{21}}{Z_{22}} \right) I_1 + \frac{Z_{12}}{Z_{22}} V_2 \quad (4)$$

Comparing eqⁿ (3) & (4) with eqⁿs of h-Parameters

$$h_{11} = \frac{\Delta Z}{Z_{22}}, \quad h_{12} = \frac{Z_{12}}{Z_{22}}$$

$$h_{21} = -\frac{Z_{21}}{Z_{22}}, \quad h_{22} = \frac{1}{Z_{22}}$$

DOMS

(M) h -Parameters in terms of γ -Parameters:-

$$h_{11} = \frac{1}{\gamma_{11}}, h_{12} = -\frac{\gamma_{12}}{\gamma_{11}}, h_{21} = \frac{\gamma_{21}}{\gamma_{11}} \text{ & } h_{22} = \frac{\Delta \gamma}{\gamma_{11}}$$

(15) h -Parameters in terms of T -Parameters:-

$$V_1 = AV_2 - BI_2 \quad \text{--- (1)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (2)}$$

Rewriting eqn (2):-

$$I_2 = -\frac{1}{D} I_1 + \left(\frac{C}{D} V_2 \right) \quad \text{--- (3)}$$

Putting value of I_2 in eqn (1):-

$$V_1 = AV_2 + B \left[\frac{1}{D} I_1 - \frac{C}{D} V_2 \right]$$

$$\boxed{V_1 = \frac{B}{D} I_1 + (A - BC) V_2} \quad \text{--- (4)}$$

On comparing eqn (3) & (4) with eqn's of h -parameters:

$$h_{11} = \frac{B}{D}, h_{12} = \frac{\Delta T}{D}$$

$$h_{21} = -\frac{1}{D}, h_{22} = \frac{C}{D}$$

(16) h -Parameters in terms of g -Parameters:-


$$[h] = [g]^{-1}$$

$$h_{11} = \frac{g_{22}}{\Delta g}, h_{12} = -\frac{g_{12}}{\Delta g}, h_{21} = -\frac{g_{21}}{\Delta g}, h_{22} = \frac{g_{11}}{\Delta g}$$

* Interconnections of Two Port Networks:-

Two port networks may be interconnected in various configurations, such as series, parallel, cascade, series-parallel, parallel-series connection, resulting in new 2-Port networks.

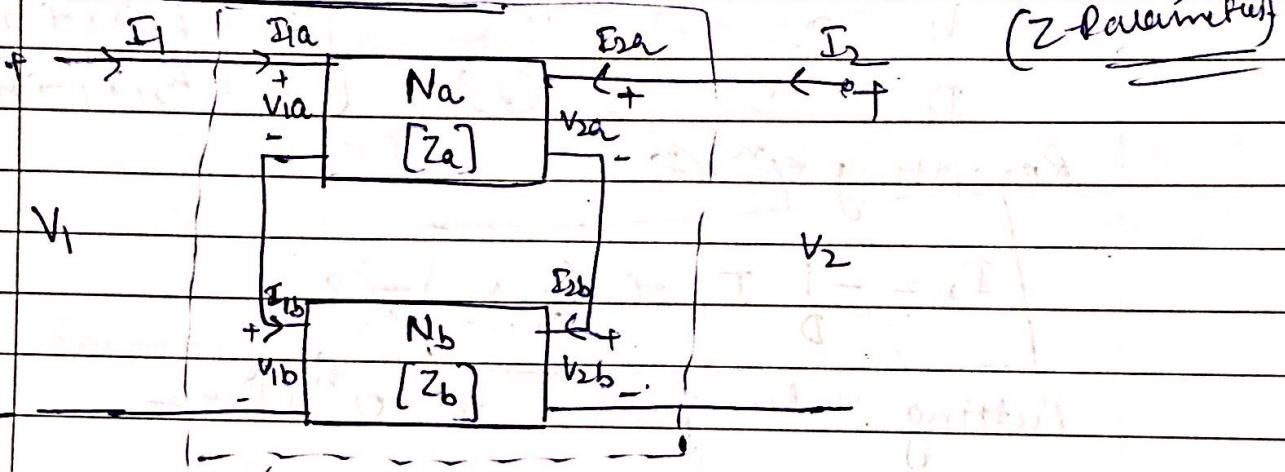① Series Connection:- (Series-Series Connection).



for Network, N_A :

$$\begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix} = \begin{bmatrix} Z_{11a} & Z_{12a} \\ Z_{21a} & Z_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix}$$

for Network, N_B :

$$\begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix} = \begin{bmatrix} Z_{11b} & Z_{12b} \\ Z_{21b} & Z_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix}$$

then, Series Connection requires that:-

$$I = I_{1a} = I_{1b}, \quad I_2 = I_{2a} = I_{2b}$$

$$V_1 = V_{1a} + V_{1b} \quad , \quad V_2 = V_{2a} + V_{2b}$$

$$V_1 = (Z_{11a} I_{1a} + Z_{12a} I_{2a}) + (Z_{11b} I_{1b} + Z_{12b} I_{2b})$$

$$V_2 = (Z_{21a} I_{1a} + Z_{22a} I_{2a}) + (Z_{21b} I_{1b} + Z_{22b} I_{2b})$$

DOMS

Since $I_1 = I_{1a} = I_{1b}$ &

$I_2 = I_{2a} = I_{2b}$.

$$V_1 = (Z_{11a} + Z_{11b}) I_1 + (Z_{12a} + Z_{12b}) I_2$$

$$V_2 = (Z_{21a} + Z_{21b}) I_1 + (Z_{22a} + Z_{22b}) I_2$$

$$\text{So } Z_1 = Z_{11a} + Z_{11b}$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$


or in matrix form:-

$$[Z] = [Z_a] + [Z_b]$$

So,

The overall Z -parameter matrix for series connected π -port networks is simply the sum of Z -parameter matrices of each individual π -port network connected in series.

② Parallel Connection: - (Y-Parameters)

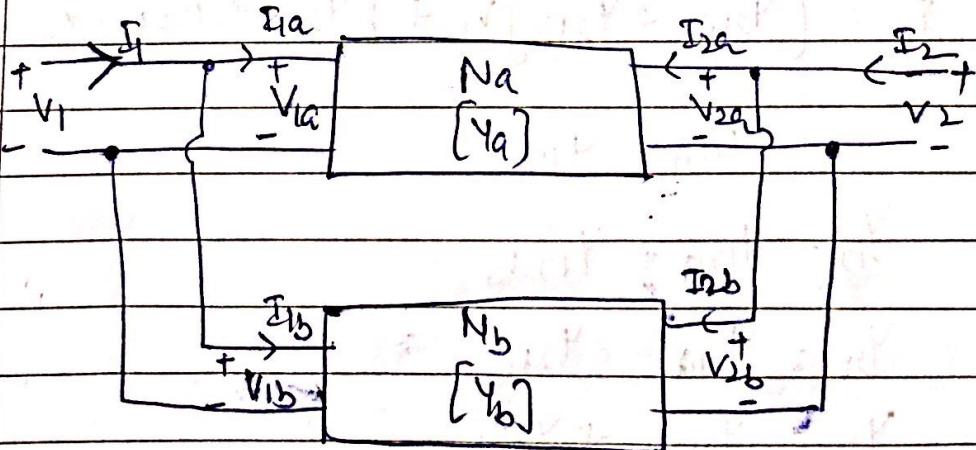

for Network N_a :

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

DOMS

for Network N_b:-

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$

for Parallel Connection:-

$$V_1 = V_{1a} = V_{1b} \quad | \quad I_1 = I_{1a} + I_{1b}$$

$$V_2 = V_{2a} = V_{2b} \quad | \quad I_2 = I_{2a} + I_{2b}$$

Now

$$I_1 = I_{1a} + I_{1b}$$

$$I_1 = [Y_{11a} V_{1a} + Y_{12a} V_{2a}] + [Y_{11b} V_{1b} + Y_{12b} V_{2b}]$$

$$I_2 = I_{2a} + I_{2b}$$

$$I_2 = [Y_{21a} V_{1a} + Y_{22a} V_{2a}] + [Y_{21b} V_{1b} + Y_{22b} V_{2b}]$$

Since

$$V_1 = V_{1a} = V_{1b}, \& V_2 = V_{2a} = V_{2b}.$$

$$I_1 = [Y_{11a} + Y_{11b}] V_1 + [Y_{12a} + Y_{12b}] V_2$$

$$I_2 = [Y_{21a} + Y_{21b}] V_1 + [Y_{22a} + Y_{22b}] V_2$$

$$\text{So } Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

So

$$[Y] = [Y_a] + [Y_b]$$


Hence,

The overall Y-Parameters matrix for
DOMS

Parallel connected 2-Port networks is simply the sum of Y-parameter matrices of each individual 2-Port network connected in parallel.

③ Cascade Connection :- (Tandem Connection)

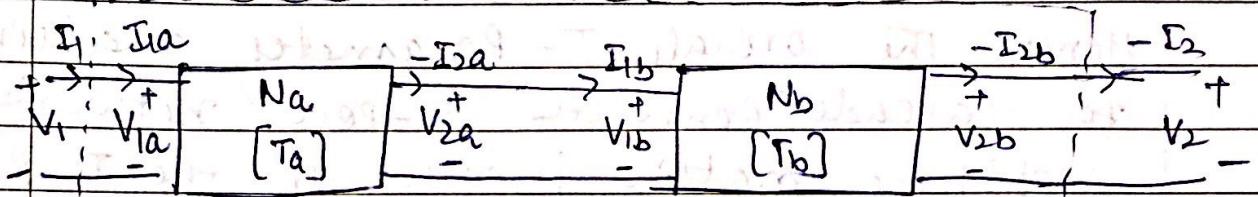Two two port networks are said to be connected in cascade if the o/p port of first becomes the I/P port of the second.



for Na

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

for Nb

$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

Cascade Connection Requires that:-

$$I_1 = I_{1a} \quad -I_{2a} = I_{1b} \quad I_{2b} = I_2$$

$$V_1 = V_{1a} \quad V_{2a} = V_{1b} \quad V_{2b} = V_2$$

Now,

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\text{so } \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

DOMS

or in eqⁿ form:-

$$A = A_a A_b + B_a C_b$$

$$B = A_a B_b + B_a D_b$$

$$C = C_a A_b + D_a C_b$$

$$D = C_a B_b + D_a D_b$$


a in the matrix form:-

$$[T] = [T_a] \cdot [T_b]$$

Hence, The overall T-Parameter matrix for cascade connected 2-port networks is simply the matrix product of the T-Parameter matrices of each individual two port network in cascade.

(4)

Series - Parallel Connection:-

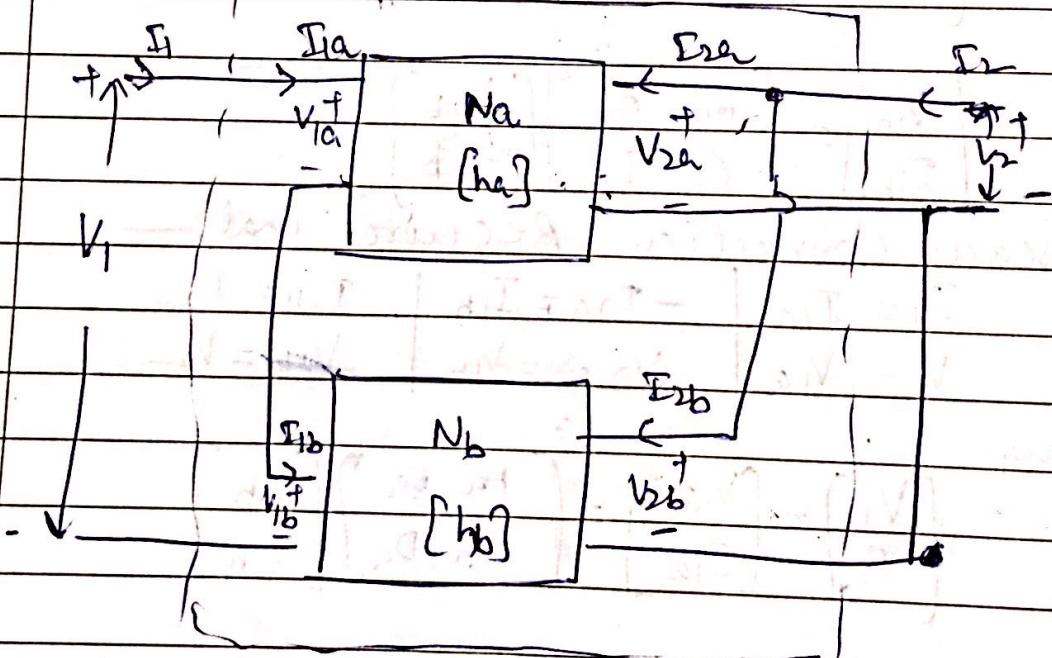

Series - Parallel Connection Requirements:-

$$V_1 = V_{1a} + V_{1b} \quad | \quad V_2 = V_{2a} \pm V_{2b}$$

$$I_1 = I_{1a} = I_{1b} \quad | \quad I_2 = I_{2a} + I_{2b}$$

DOMS

for Network N_a:-

$$\begin{bmatrix} V_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix}$$

for Network N_b:-

$$\begin{bmatrix} V_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \begin{bmatrix} I_{1b} \\ V_{2b} \end{bmatrix}$$

$$V_1 = V_{1a} + V_{1b}$$

$$V_1 = [h_{11a}I_{1a} + h_{12a}V_{2a}] + [h_{11b}I_{1b} + h_{12b}V_{2b}]$$

$$I_2 = I_{2a} + I_{2b}$$

$$I_2 = [h_{21a}I_{1a} + h_{22a}V_{2a}] + [h_{21b}I_{1b} + h_{22b}V_{2b}]$$

$$\text{As } I_1 = I_{1a} = I_{1b}$$

$$V_2 = V_{2a} = V_{2b}$$

$$V_1 = (h_{11a} + h_{11b})I_1 + (h_{12a} + h_{12b})V_2$$

$$I_2 = (h_{21a} + h_{21b})I_1 + (h_{22a} + h_{22b})V_2$$

$$\text{So } h_{11} = h_{11a} + h_{11b}$$

$$h_{12} = h_{12a} + h_{12b}$$


$$h_{21} = h_{21a} + h_{21b}$$

$$h_{22} = h_{22a} + h_{22b}$$

$$\text{or } [h] = [h_a] + [h_b]$$

So, the overall h-Parameter matrix for series-parallel connected 2-Port networks is simply the sum of h-Parameter matrices for each individual 2-Port network connected in series-parallel connection.

(5) Parallel-Series Connection:-

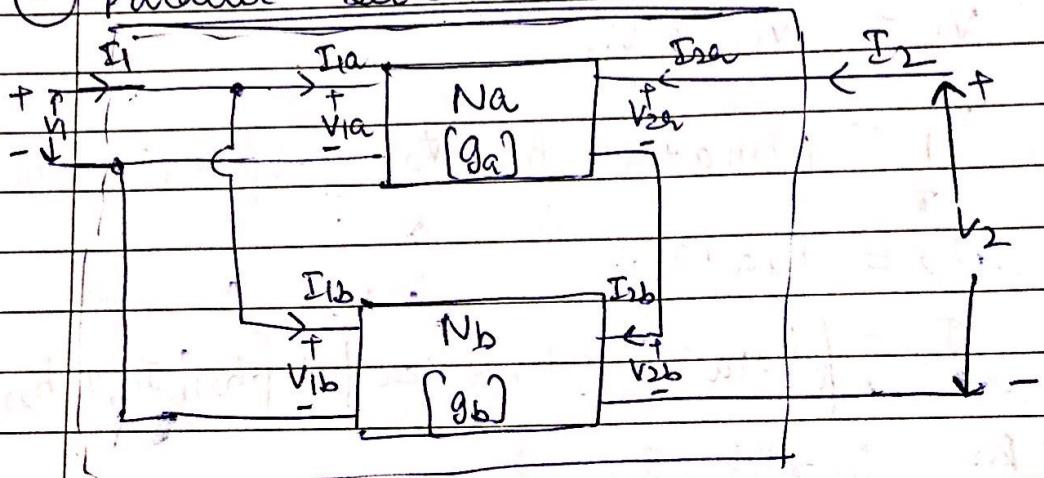

The connection requires that :-

$$V_1 = V_{1a} \pm V_{1b}$$

$$I_1 = I_{1a} + I_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$I_2 = I_{2a} = I_{2b}$$

Similar to previous case:-

$$g_{11} = g_{11a} + g_{11b}$$

$$g_{12} = g_{12a} + g_{12b}$$

$$g_{21} = g_{21a} + g_{21b}$$

$$g_{22} = g_{22a} + g_{22b}$$

DOMS

or in the matrix form:-


$$\{g\} = [g_a] + [g_b]$$

So


The overall g-parameter matrix for parallel-series connected 2-port networks is simply the sum of g-parameter matrices of each individual 2-port network connected in parallel series connection.

Q.28

obtain z-parameter of given network.

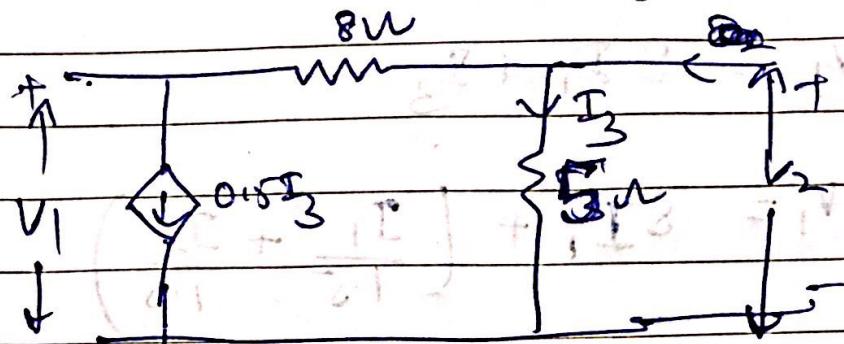

Soln

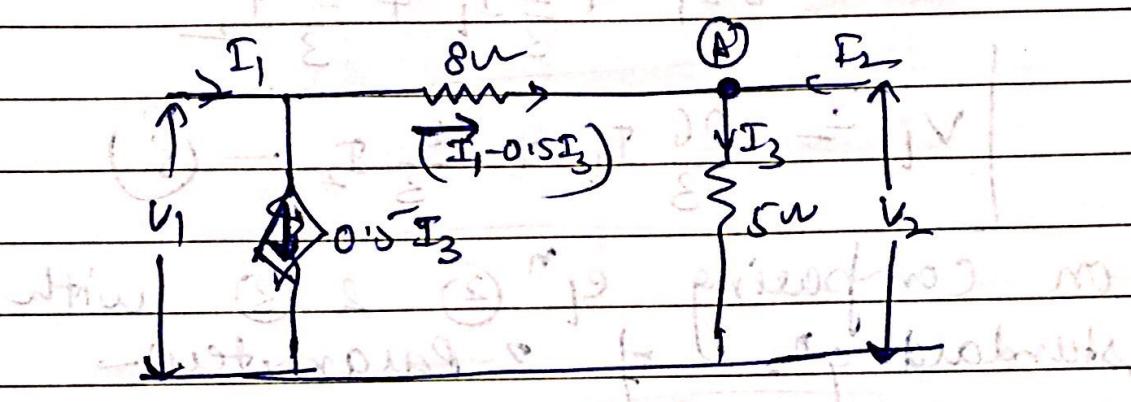

Applying KCL at node (A):—

$$I_1 - 0.5I_3 + I_2 = I_3$$

$$1.5I_3 = I_1 + I_2$$

$$I_3 = \frac{1}{1.5} [I_1 + I_2]$$

$$\boxed{I_3 = \frac{1}{1.5} I_1 + \frac{1}{1.5} I_2} \rightarrow \textcircled{1}$$

DOMS

$$V_2 = 5 I_3$$

$$= 5 \left[\frac{I_1}{1.5} + \frac{I_2}{1.5} \right]$$

$$V_2 = \frac{10}{3} I_1 + \frac{10}{3} I_2 \quad \text{--- (2)}$$

$$V_1 = 8(I_1 - 0.5 I_3) + 5 I_3$$

$$= 8 I_1 - 4 I_3 + 5 I_3$$

$$V_1 = 8 I_1 + I_3$$

$$V_1 = 8 I_1 + \left(\frac{I_1}{1.5} + \frac{I_2}{1.5} \right)$$

$$= 8 I_1 + \frac{2}{3} I_1 + \frac{2}{3} I_2$$

$$V_1 = \frac{26}{3} I_1 + \frac{2}{3} I_2 \quad \text{--- (3)}$$

on comparing eqn (2) & (3) with standard eqns of 2-parameters

$$Z_{11} = \frac{26}{3} = 8.67 \Omega$$


$$Z_{12} = \frac{2}{3} = 0.67 \Omega$$

$$Z_{21} = \frac{10}{3} = 3.33 \Omega$$


$$Z_{22} = \frac{10}{3} = 3.33 \Omega$$

Q.29 for the given network find.

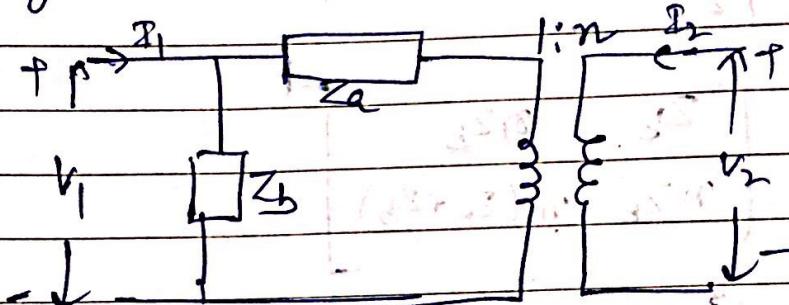- 1.) Impedance and admittance parameters.
- 2.) transmission and inverse-transmission parameters.
- 3.) Hybrid & inverse hybrid parameters.



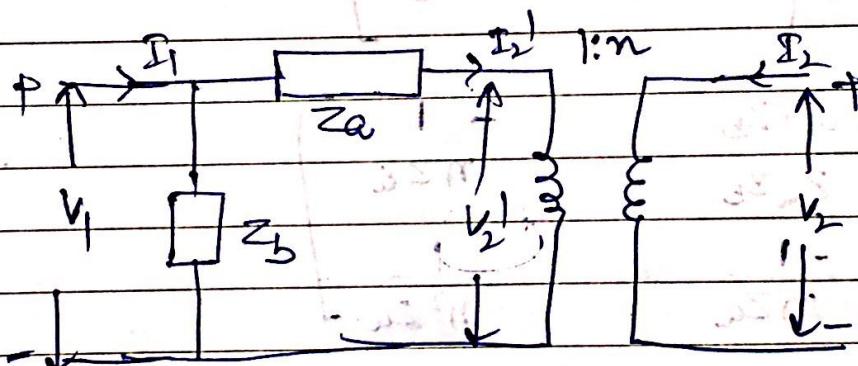Soln let V_2' & I_2' be the ZP voltage and ZP current of the transformer respectively.



$$V_1 = Z_b(I_1 - I_2') \quad \text{--- (1)}$$

$$V_2 = nV_2' \quad \text{and} \quad I_2 = -\frac{1}{n}I_2'$$

$$V_2 = n[V_1 - Z_a I_2']$$

$$\text{So } V_1 = Z_b(I_1 + nI_2)$$

$$\boxed{V_1 = Z_b I_1 + n Z_b I_2} \quad \text{--- (2)}$$

$$V_2 = n[Z_b I_1 + n Z_b I_2 + n Z_b I_2]$$

$$\boxed{V_2 = n Z_b I_1 + n^2 (Z_a + Z_b) I_2} \quad \text{--- (3)}$$

$$\textcircled{1} \quad \text{So } z_{11} = z_b, z_{12} = nz_b, z_{21} = nz_b, z_{22} = n^2(z_a + z_b)$$

$$[y] = [z]^{-1}$$

$$= \begin{bmatrix} z_b & nz_b \\ nz_b & n^2(z_a + z_b) \end{bmatrix}^{-1}$$

$$= \frac{1}{n^2 z_a z_b} \begin{bmatrix} n^2(z_a + z_b) & -nz_b \\ -nz_b & z_b \end{bmatrix}$$

$$[y] = \begin{bmatrix} z_a + z_b & -\frac{1}{n z_a} \\ z_a z_b & \frac{1}{n^2 z_a} \end{bmatrix}$$

$$y_{11} = \frac{z_a + z_b}{z_a z_b} \quad \textcircled{1} \rightarrow y_{12} = -\frac{1}{n z_a} \quad V = 1V$$

$$y_{21} = -\frac{1}{n z_a}, \quad y_{22} = \frac{1}{n^2 z_a} \quad V = 1V$$

$$\textcircled{2} \quad A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = \frac{1}{n}, \quad C = \left. \frac{I_1}{V_2} \right|_{I_2=0} = \frac{1}{n z_b}$$

$$B = \left. \frac{V_1}{V_2} \right|_{I_1=0} = n z_a, \quad D = \left. \frac{I_1}{V_2} \right|_{V_2=0} = n \left(\frac{z_a + z_b}{z_b} \right)$$

$$A' = \frac{D_0}{\Delta T} \cdot \sin(z_a + z_b)$$

(1) da ΔT mit z_b bringt keinen Einfluss auf A'

$$B' = \frac{\partial B_{DC}}{\Delta T} = n z_a$$

$$C' = \frac{C}{\Delta T} = \frac{1}{n z_b}$$

$$D' = \frac{D}{\Delta T} = \frac{1}{n}$$

$$(3) \cdot h_{11} = \frac{v_1}{\Sigma I} \Big|_{v_2=0} = \frac{z_a z_b}{z_a + z_b}$$

$$h_{21} = \frac{I_2}{\Sigma I} \Big|_{v_2=0} = \frac{-1}{n} \left(\frac{z_b}{z_a + z_b} \right)$$

$$h_{12} = \frac{v_1}{v_2} \Big|_{I_2=0} = \frac{z_b}{n(z_a + z_b)}$$

$$h_{22} = \frac{I_2}{v_2} \Big|_{I_1=0} = \frac{1}{n^2(z_a + z_b)}$$

and

$$g_{11} = \frac{h_{22}}{\Delta h} = \frac{1}{z_b}$$


$$g_{12} = \frac{-h_{21}}{\Delta h} = -n$$

$$g_{21} = \frac{-h_{12}}{\Delta h} = n$$

$$g_{22} = \frac{h_{11}}{\Delta h} = n^2 z_a$$

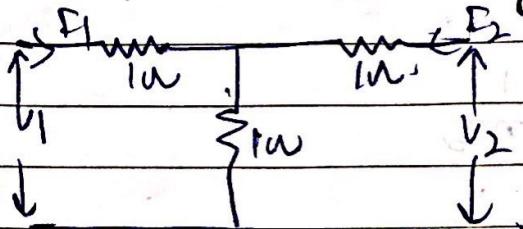Q.30

Two Identical sections of the n/w shown in figure are cascaded. Calculate the AB CD parameters of the resulting network.



Soln

for one network:-

$$V_1 = 1 \cdot I_1 + 1 \cdot (I_1 + I_2)$$

$$V_1 = 2I_1 + I_2 \quad \text{--- (1)}$$

$$V_2 = 1 \cdot I_2 + 1 \cdot (I_1 + I_2)$$

$$V_2 = 2I_2 + I_1 \quad \text{--- (2)}$$

Case 1: when $I_2 = 0$

$$V_1 = 2I_1$$

$$V_2 = I_1$$

$$\text{So } A = \left. \frac{V_1}{V_2} \right|_{I_2=0} = 2$$

$$C = \frac{I_1}{V_2} = 1 \text{ ohm}^{-1}$$

Case 2: when $V_2 = 0$

$$2I_2 = -I_1$$

$$I_2 = -\frac{I_1}{2} \text{ and } I_1 = -2I_2$$

$$B = \left. \frac{V_1}{-I_2} \right|_{V_2=0} = 3$$

$$D = \left. \frac{V_1}{I_2} \right|_{V_2=0} = 2$$

$$\text{So } [Y] = \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$$


Similarly, for second network, parameters will be $\begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix}$

So, The overall T-parameters of the cascaded network is given by:

$$T = \begin{bmatrix} A & B \\ C & D \end{bmatrix}, \begin{bmatrix} A & B \\ C & D \end{bmatrix}$$

$$= \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix} \begin{bmatrix} 2 & 3 \\ 1 & 2 \end{bmatrix} = \begin{bmatrix} 7 & 12 \\ 4 & 7 \end{bmatrix} \text{ Ans}$$

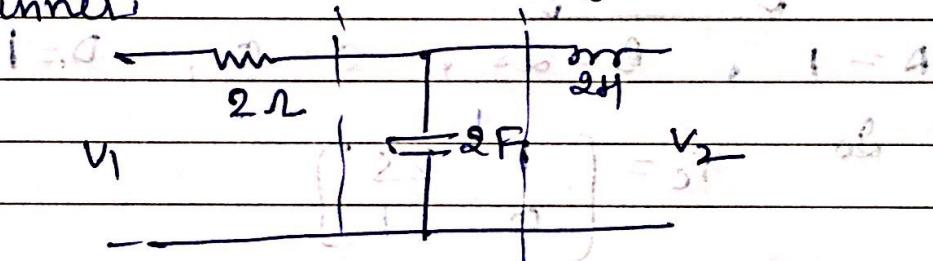- Q.31 Determine the transmission of a T-network as shown in figure. Considering three sections as shown in fig, assuming connected in cascade manner.



for N_a $\frac{V_1}{V_2} = \frac{I_1 + I_2}{I_2} = 1 + \frac{I_1}{I_2}$ $V_1 = 2I_1 + V_2$


$$\underline{V_1 = 2I_1 + V_2} \quad \underline{I_1 = -I_2}$$

case 1: when $I_2 = 0$ case 2: when $V_2 = 0$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = 1 \quad B = \frac{V_1}{V_2} \Big|_{V_2=0} = 2$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = 0 \quad D = \frac{I_1}{V_2} \Big|_{V_2=0} = 1$$
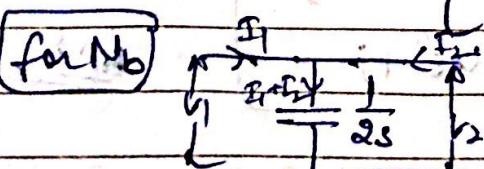
$$\therefore T_a = \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix}$$



$$V_1 = \frac{1}{2s} I_1 + \frac{1}{2s} I_2$$

$$V_2 = \frac{1}{2s} I_1 + \frac{1}{2s} I_2$$

DOMS

Case 1: when $V_1 = 0$

$$A = \frac{V_1}{V_2} \Big|_{V_2 \neq 0} = 1 \quad \text{and} \quad C = \frac{I_1}{V_2} \Big|_{V_2 \neq 0} = 2s$$

Case 2: when $V_2 = 0$


$$B = 0 \quad \therefore D = 1$$

So

$$T_B = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix}$$

Structure FD for $\begin{bmatrix} 2s & 1 \end{bmatrix}$ and example 11.8

(Ans)

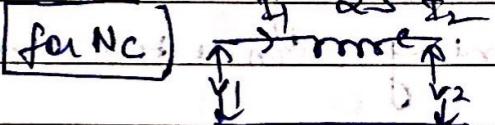

$$A = 1, \quad B = 2s, \quad C = 0, \quad D = 1$$

So

$$T_C = \begin{bmatrix} 1 & 2s \\ 0 & 1 \end{bmatrix}$$

So, the overall parameters of given network

$$T = \begin{bmatrix} 1 & 2 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 2s & 1 \end{bmatrix} \begin{bmatrix} 1 & 2s \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1+2s & 2 \\ -2s & 1 \end{bmatrix} \begin{bmatrix} 1 & 2s \\ 0 & 1 \end{bmatrix}$$


$$= \begin{bmatrix} 1+2s & 2s(1+2s)+2 \\ 2s & 2s(2s)+1 \end{bmatrix}$$

$$T = \begin{bmatrix} 4s^2+1 & 2(4s^2+s+1) \\ 2s & 4s^2+s \end{bmatrix}$$

DOMS

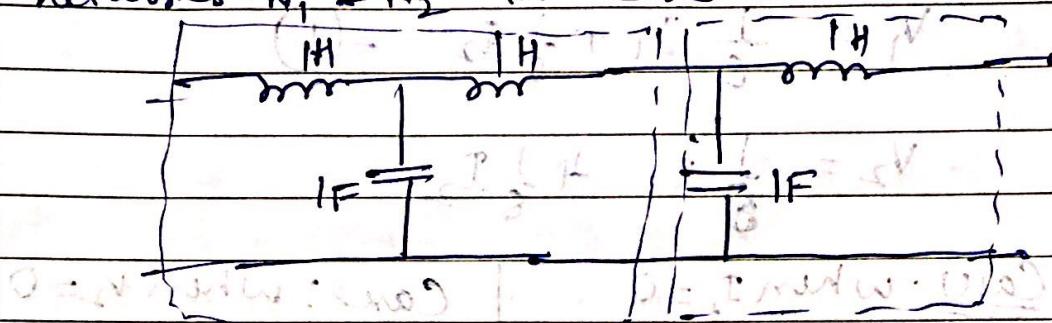
Q.32

Determine the transmission parameters of the given network as shown in figure, using the concept of interconnection of two two-port networks N_1 & N_2 in cascade.



Soln for Network N_1 :-

$$T^2 + B + 1 = 0$$

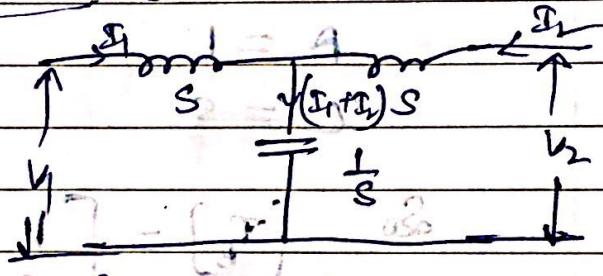

$$V_1 = S I_1 + \frac{1}{s} (I_1 + I_2)$$

$$V_1 = \left(\frac{s^2 + 1}{s} \right) I_1 + \frac{1}{s} I_2 \quad \text{--- (1)}$$

$$V_2 = 3 I_2 + \frac{1}{s} (I_1 + I_2)$$

$$V_2 = \frac{1}{s} I_1 + \left(\frac{s^2 + 1}{s} \right) I_2 \quad \text{--- (2)}$$

Case 1: when $I_2 = 0$

$$A = \frac{V_1}{V_2} \Big|_{I_2=0} = s^2 + 1$$

$$C = \frac{I_1}{V_2} \Big|_{I_2=0} = s$$

$$[T_A] = \begin{bmatrix} 1+s^2 & 2s+s^3 \\ s & 1+s^2 \end{bmatrix}$$


DOMS

Case 2: when $V_2 = 0$

$$B = \frac{V_1}{V_2} \Big|_{V_2=0} = 2s + s^3$$

$$D = \frac{I_1}{V_2} \Big|_{V_2=0} = 1+s^2$$

for Network N₂

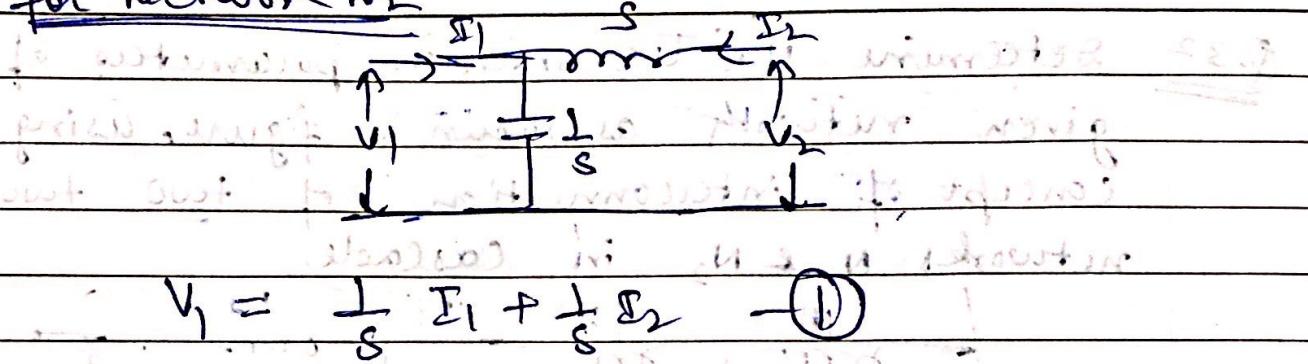

$$V_2 = \frac{1}{s} I_1 + \frac{1}{s} I_2$$

Case 1: when $I_2 = 0$

$$\begin{aligned} A &= 1 \\ C &= s \end{aligned}$$

Case 2: when $V_2 = 0$

$$\begin{aligned} B &= s+1 \\ D &= 1+s^2 \end{aligned}$$

$$\text{So } [T_B] = \begin{bmatrix} 1 & s \\ s & 1+s^2 \end{bmatrix}$$

So overall parameters:-

$$T = [T_A] \cdot [T_B]$$

$$= \begin{bmatrix} 1+s^2 & 2s+s^3 \\ s & 1+s^2 \end{bmatrix} \begin{bmatrix} 1 & s \\ s & 1+s^2 \end{bmatrix}$$

$$T = \begin{bmatrix} 1+3s^2+s^4 & 2s^3+4s^4+s^5 \\ s^2+s^3 & 1+3s^2+s^4 \end{bmatrix}$$

Ans.