

Graph Theory

(1)

- When all the elements (e.g. resistors, inductors, capacitors etc) in a network are replaced by lines with circles, or dots at both ends, the configuration is then called graph of n/w.

The graph of any network is drawn by keeping all the points of intersection of two or more branches and representing the network element as lines, voltages and current sources by their internal impedances. The point of intersection of two or more branches is called a node.

Terminology used in Network Graph:

- **Branch:-** A branch is a line segment representing one network element or combination of elements connected between two points. Though the line segment with two distinct end points represents a branch, it does not indicate anything about the type of element.
- **Node:-** A node point is defined as end point of a line segment and exists at the junction between two branches or at ends of an isolated branch.
- **Tree:-** It is an interconnected open set of branches which include all the nodes of given graph. In a tree of graph there can not be any closed loop.
- **Twig (Tree branch):-** It is any branch of a tree.
- **Tree link or chord:-** It is that branch of the graph that does not belong to the particular tree. It is simply called link.

Ex:-

(2)

→ Loop:-

This is the closed contour selected in graph.

→ Cut set:-

It is that set of element or branches of a graph that separates two main part of a network.

→ Tie set:- It is a unique set with respect to a given tree of a connected graph containing one link.

→ Directed or oriented graph:-

A graph is said to be directed or oriented when all nodes and branches are numbered and direction are assigned to the branches by arrow.

→ Relation between twig and links

No. of twigs in a particular tree = $N-1$

No. of link in " " " " = $B-N+1$

Where B = Branches of graph

N = Nodes " "

→ Properties of a Tree in a Graph:-




(1) It consists of all the nodes of graph

(2) If the graph has ' N ' no. of nodes the tree will have $(N-1)$ branches

(3) There will be no closed path in the tree.





(4) There can be many possible different tree for a given graph depending on the no. of nodes and branches.

Ex:-

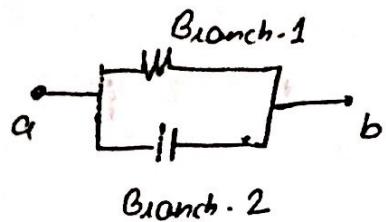
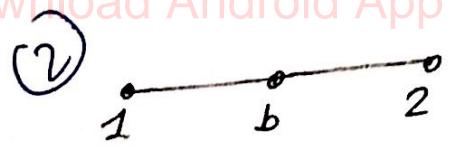
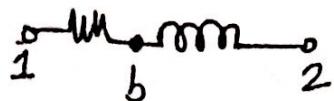


Node - 3
Branch - 2

Node - 2
Branch - 2

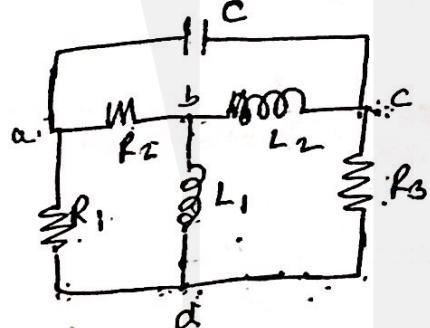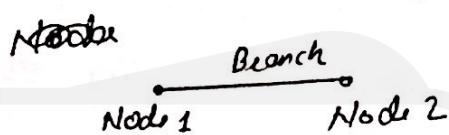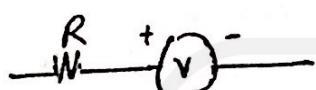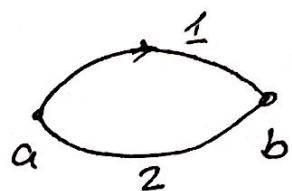


Node 4
Branch - 6

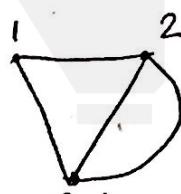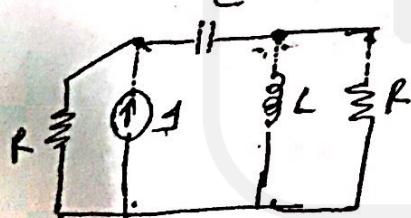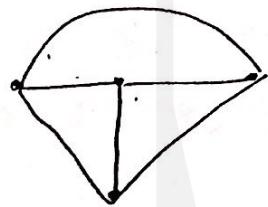

Here current source is present so it is open circuit so no branch is drawn for current source

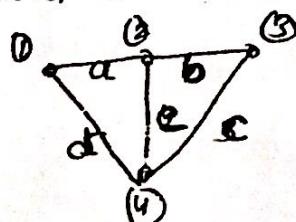
(2) Fig showing the graph of a network. Show the tree, bridge and links.




Incidence Matrix

a.

Tree :-



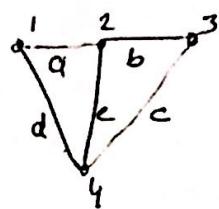


(3)

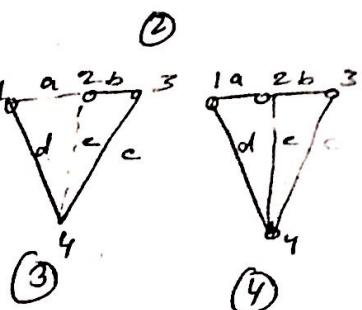

b.

Fo

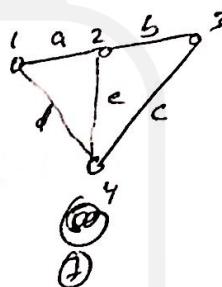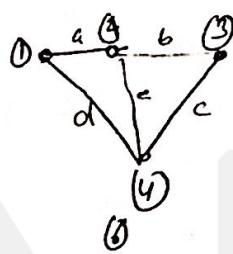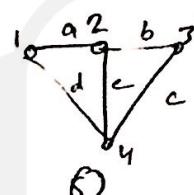

c.

Tree (Twigs)

1. [b e d]
2. [c e d]
3. [d c b]
4. [d a b]
5. [a e c]
6. [a d c]
7. [a b c]
8. [a b e]

link [co-tree]


- [a, c]
- [a, b]
- [a, e]
- [e, c]
- [b, d]
- [b, e]
- [d, e]
- [c, d]

Tie set or Fundamental loop (Circuit) - B_f (4)

→ loop which contain only one link are independent
are called basic fundamental loop or tie set.

→ No. of fundamental loop or tie set is equal to
No. of links i.e. $b-n+1$ Imp


Ex:-

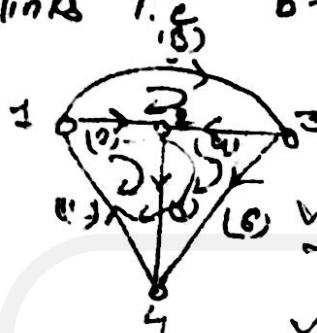




Procedure for obtaining Tie set matrix [fundamental loop matrix]:

Step 1:- Arbitrarily a tree is selected in the graph

Step 1:- A tree is selected;

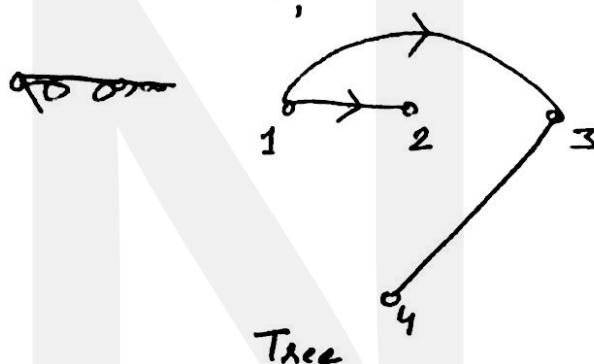

Step 2:- Fundamental loop

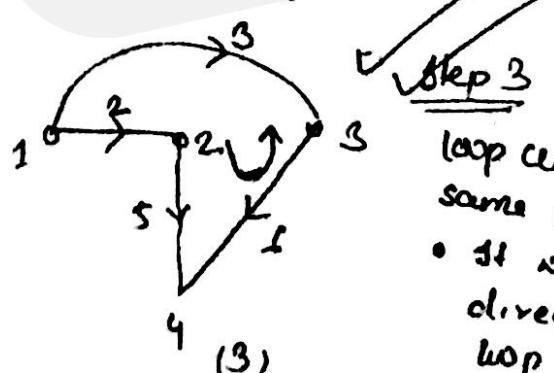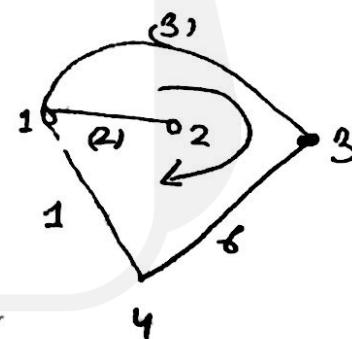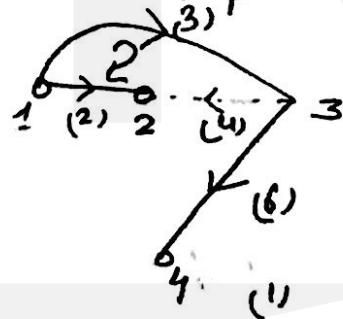

Step 3 (2)
Assume direction of
loop current oriented in the
same direction
• It will be +1, so that if link
direction will be same
loop direction will be same as
will be -1, else it

Graph Theory

①

- When all elements [e.g. resistors, inductors, capacitors etc] in a network are replaced by lines with circle or dots at both ends, the configuration is then called the graph of network.

Terminology used in Graph:-

Branch → A branch is a line segment representing one network element or a combination of element connected between two points

Node → A node point is defined as an end point of a line segment and exist at the junctⁿ between two branches or at the ends of an isolated branch.

Path — Path in a network constitute a set of element traversed such that no node is passed through again

Tree — It is any an interconnected open set of branches which include all nodes of given graph. In a tree of graph there cannot be any closed loop.
Each tree has $(n-1)$ branch where n : no. of nodes


Twigs :— The tree branches are called twigs.
No. of twigs = $n-1$

Dink — It is that branch of graph that does not belong to a particular tree

$$\text{No. of links} = b - n + 1$$

loop — closed contour selected in a graph.

Ex:-

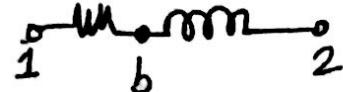


(2)




Node - 3

Branch - 2

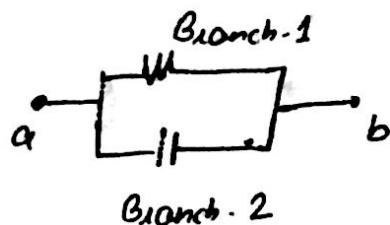

Node - 2



Branch - 2

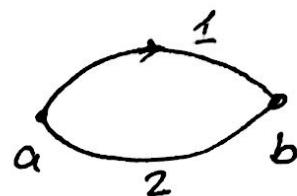



Branch - 2



Node

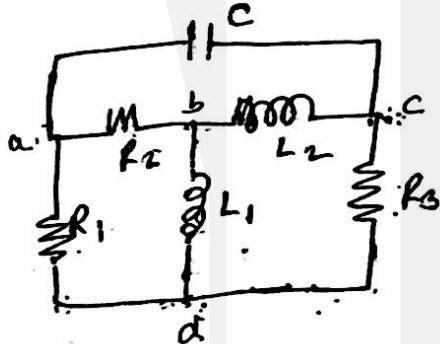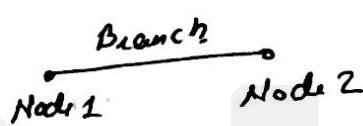


Node 4
Branch - 6

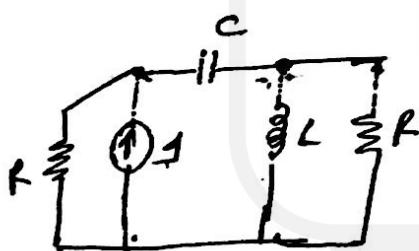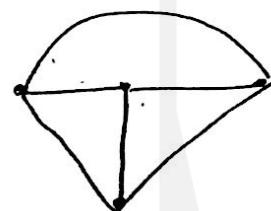

Here current source is present so it is open circ so no branch is drawn for current source

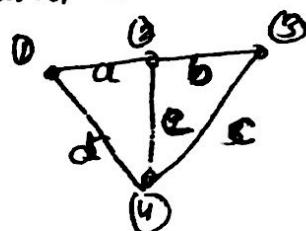Q) Fig showing the graph of a network. Show the tree, twigs and links.



Any oriented graph can be described completely in a compact matrix form. Here we specify the orientation of each branch in graph and nodes at which this branch is incident. This matrix is called incidence matrix.

- When one row is deleted from the complete incidence matrix, the remaining matrix are termed as reduced incidence matrix.


Formation of Incidence matrix - $[A_i]$

- This matrix shows which branch is incident to which node.

Each row of matrix being representing the corresponding node and each column of matrix represent the branch.

- If branch 'j' is incident at node 'i' but oriented away from node then matrix element will be '1' and if oriented toward nodes then it will be '-1'.

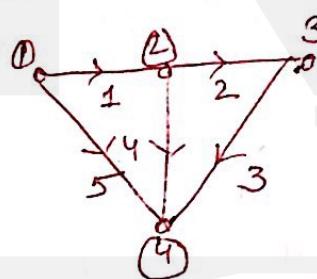- Obtain the incidence matrix of given graph.



Node	Branch				
	1	2	3	4	5
1	1	0	0	0	1
2	-1	1	0	1	0
3	0	-1	1	0	0
4	0	0	-1	-1	-1

- ① Algebraic sum of the column entries of an incidence matrix is 340.
- ② Determinant of incidence matrix of a closed loop is 340.

Reduced Incidence Matrix [A]:-


When one row is deleted from complete incidence matrix $[A_i]$ the remaining matrix is called a reduced incidence matrix $[A]$.

Q) An incidence matrix is given by

$$[A_i] = \begin{bmatrix} 1 & 0 & 0 & 1 \\ -1 & 1 & 1 & 0 \\ 0 & -1 & -1 & -1 \end{bmatrix}$$

Draw the graph corresponding to this matrix.

Node	Branch			
1	1	2	3	4
2	1	0	0	1
3	-1	1	1	0
4	0	-1	-1	-1

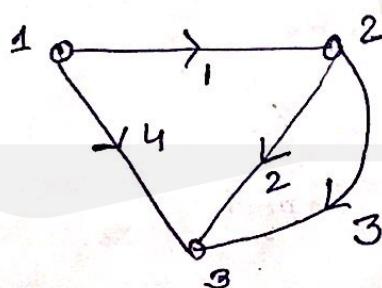

Develop the reduced matrix from given incidence matrix.

$$[A] = \begin{bmatrix} 1 & 0 & 0 & 1 \\ -1 & 1 & 1 & 0 \end{bmatrix}$$

For reduce matrix
delete one row.
from given
incidence matrix

Provided by NotesHub.co.in | Download Android App


(4)

the directed graph


Branch

Node	1	2	3	4	5	6	7
1	-1	0	-1	1	0	0	1
2	0	-1	0	-1	0	-1	0
3	1	1	0	0	-1	1	0
4	0	0	1	0	1	0	-1

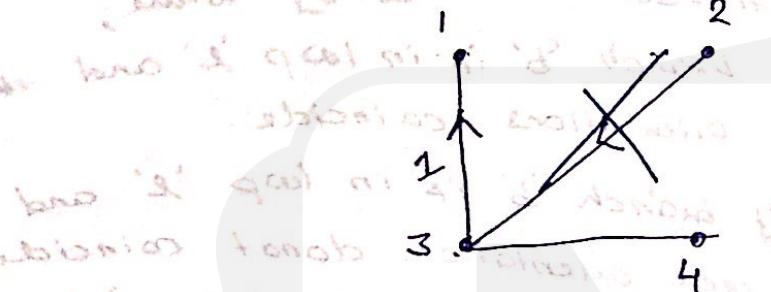[Ans] At node 1 branch '1' and branch '3' is incident



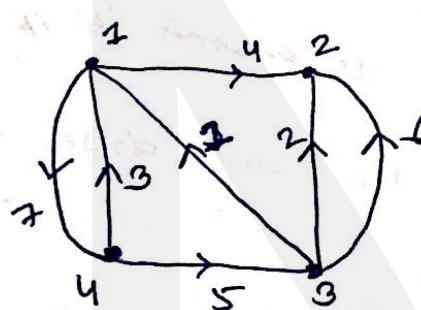At node '2' branch 2 and 3 is incident
similarly draw for another nodes



At node '2' branch 2 and 3 is incident
similarly draw for another nodes

* Fundamental Tie-set Matrix or Fundamental loop matrix
[B]:-

→ A fundamental loop or a fundamental tie-set of a graph with respect to a tree is a loop formed by only one link associated with other tie-set.

No. of fundamental loop or Tie-set

$$= B - (N-1)$$


where B = Branch

N = Nodes

Q) Incidence matrix of a graph is given below. Draw the directed graph.

(4)

Node	1	2	3	4	5	6	7
Branch	-1	0	-1	1	0	0	1
1							
2	0	-1	0	-1	0	-1	0
3	1	1	0	0	-1	1	0
4	0	0	1	0	1	0	-1

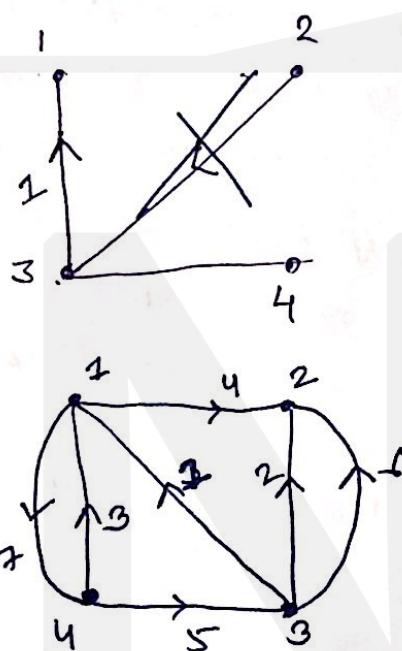

At node 1 branch '1' and branch '3' is incident

At node '2' branch 2 and 3 is incident
similarly draw for another nodes

* Fundamental Tie-set Matrix or Fundamental loop matrix
[B]:-

→ A fundamental loop or a fundamental tie-set of a graph with respect to a tree is a loop formed by only one link associated with other twigs.


$$\text{No. of fundamental loop or Tie-set} = B - (N-1)$$

where B = Branch
 N = Nodes



* Procedure of obtaining Fundamental Tie-Set matrix or loop matrix:-

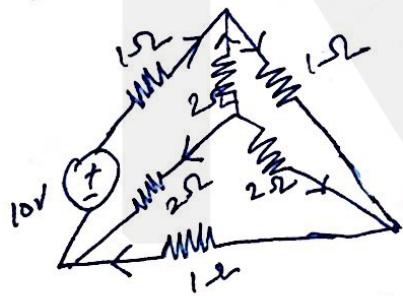- 1) Arbitrarily a tree is selected in the graph.
- 2) Form fundamental loop with each links in the graph for entire tree.
- 3) Assume direction of loop current oriented in the same direction as that of link.
- 4) Form fundamental tie-set matrix $[b_{lb}]$ where;
 $b_{lb} = 1$; if branch 'b' is in loop 'l' and their orientations coincide.
 $= -1$; if branch 'b' is in loop 'l' and their orientation do not coincide.
 $= 0$; if branch 'b' is not in loop 'l'.

Draw the graph and work down the tie-set matrix





Sol:-

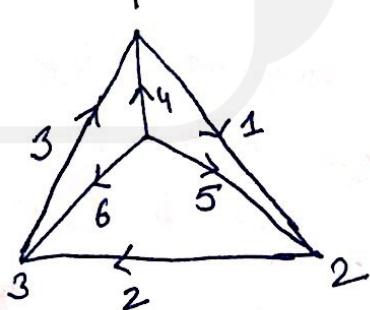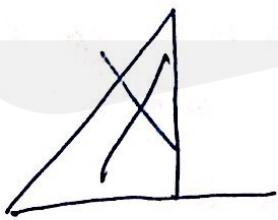



Oriented Graph

Step 1:- Randomly select a tree

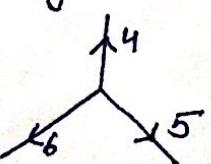


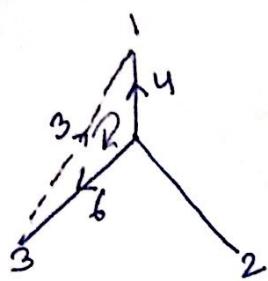

Tie-set-1

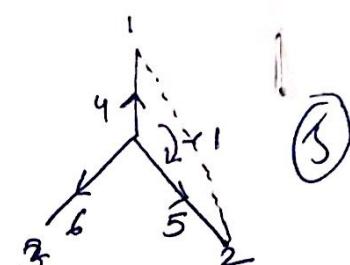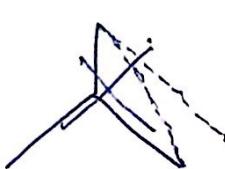

Tie-set-2

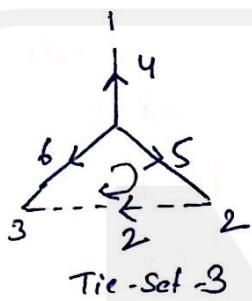

Tie-set-3



Tie-set 1 [4 6 3] Tie-set 2 [1 4 5] Tie-set 3 [6 5 2]

Branch		1	2	3	4	5	6	
Tie-set		1	0	0	1	-1	0	1
		2	1	0	0	1	-1	0
		3	0	1	0	0	1	-1


* Cutset Matrix:- $[Q_s]$

- A fundamental cutset of a graph with respect to a tree is a cutset formed by one and only one twig and a set of links.
- For a graph having 'n' nodes there will be $(N-1)$ fundamental cutset.
- ⇒ Orientation of cutset is so chosen that it coincides with orientation of its twig.
- ⇒ cutset is a minimal set of branches of graph, removal of which cuts the graph into two part. It separate the node of graph into two graph each being in one of two parts.

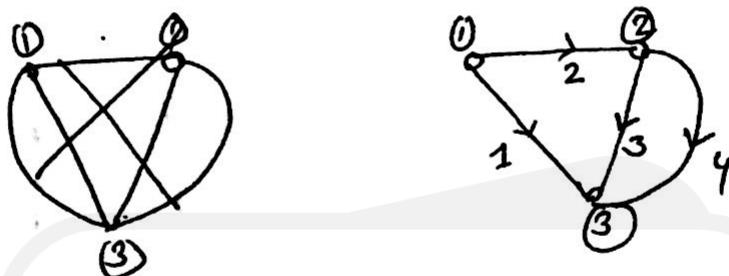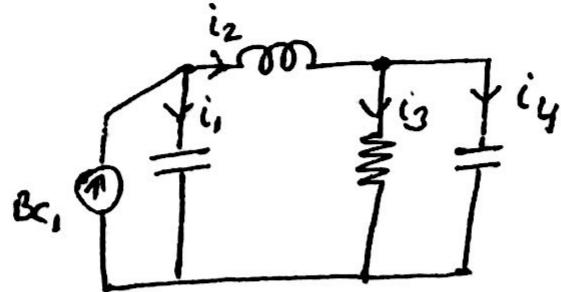Q1 Develop the fundamental cutset matrix (5)



Select a tree:-

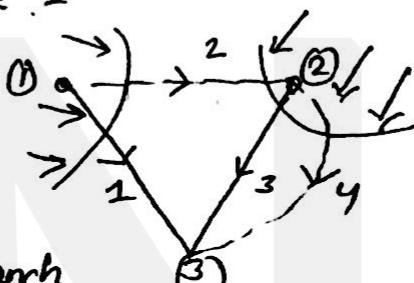

subset	Branch	1	2	3	4
1		1	1	0	0
2		0	-1	1	1

Procedure of forming Fundamental cutset matrix:-

Step 1:- Arbitrarily a tree is selected in [the] graph.

Step 2:- Form fundamental cutset with each twig in the graph for entire tree.

Step 3:- Assume direction of cutset current in the same direction of concerned twig.

→ If direction of links is same as that of concerned twig then it will be +1 else opposite then -1.

Fundamental loop or tie set B_f

$$\text{Tie set } 1 = [2 \ 3 \ 4]$$

$$\text{Tie set } 2 = [1 \ 3 \ 6]$$

$$\text{Tie set } 3 = [2 \ 3 \ 5 \ 6].$$

Tie set Matrix

		Branches \rightarrow					
		1	2	3	4	5	6
Tie set	1	0	-1	1	1	0	0
	2	0	0	1	0	0	1
	3	0	1	-1	0	1	-1


Cut set matrix :- $[Q_f]$

→ A fundamental cut set of a graph with respect to a tree is a cutset formed by one and only one twig and a set of links.

→ For a graph having 'N' nodes there will be $(N-1)$ fundamental cutset.



→ Orientation of cutset is so chosen that it coincides with orientation of its twigs.

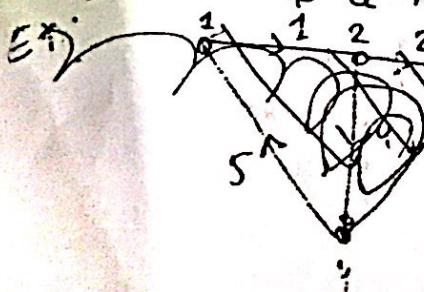→ Cutset is a minimal set of branches of graph, removal of which cuts the graph into two parts. These separate the node of graph into two groups each being in one of two parts.



Q) For a given graph, find out the cutset matrix
Ans - Select a tree - for given tree $[1, 2, 5]$

(6)

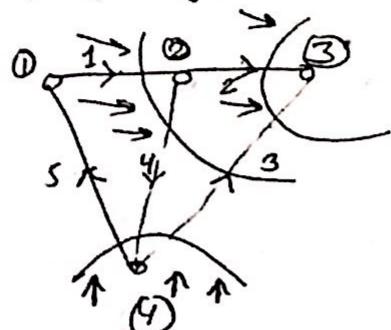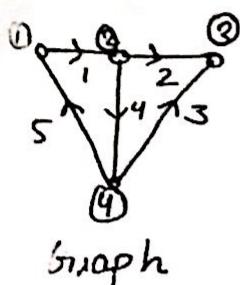

Twig $\Rightarrow 3$

Dink $\Rightarrow 2$

Cutset 1 $[2, 3]$



Cutset 2 $[1, 4]$

Cutset 3 $[5, 3, 4]$

Branches

Cutset	1	2	3	4	5
1	0	1	1	0	0
2	1	0	1	-1	0
3	0	0	1	-1	1

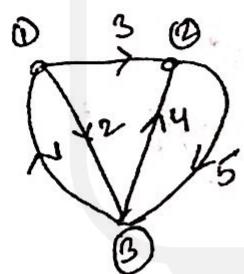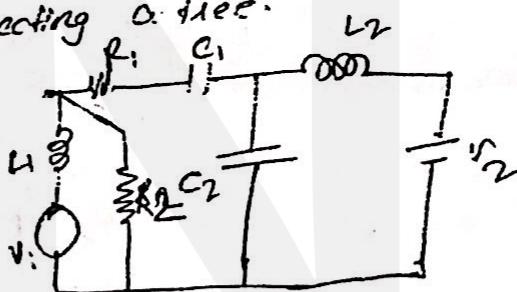Develop the graph of network shown and obtain the
tie set matrix selecting a tree.



Select Tree $[3, 2]$ is selected




Tie set 1 $[1, 2]$

Tie set 2 $[2, 3, 4]$


Tie set 3 $[2, 3, 5]$

Tie set	1	2	3	4	5
1	1	1	0	0	0
2	0	1	-1	1	0
3	0	-1	1	0	1

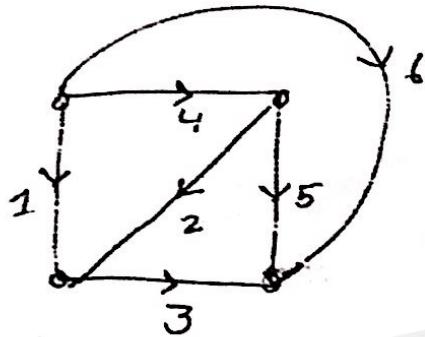
An oriented graph of a certain circuit shown in fig.
For tree $[2, 4, \{1\}]$, Find $[Q_f]$ and B_f and hence show that
 $[Q_f][B_f]^T = 0$




For tree

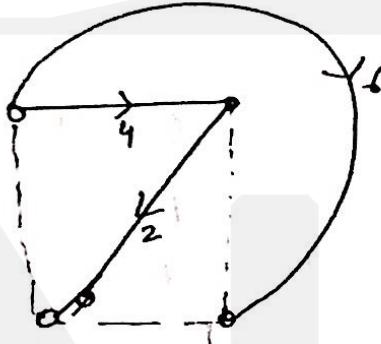


Fundamental TieSet matrix:-

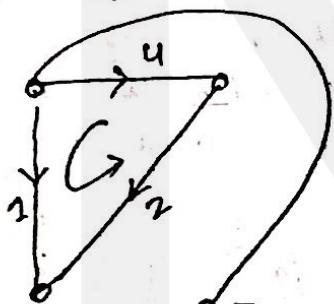

TieSet 1 $[1, 2, 4]$

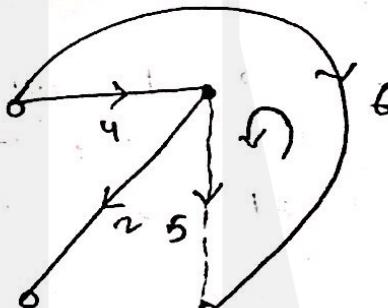

TieSet 2 $[4, 5, 6]$

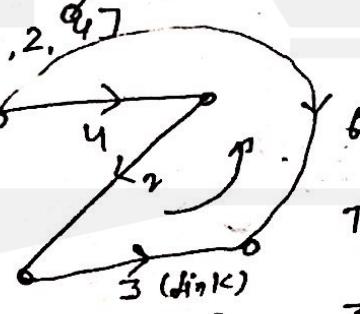


TieSet 3 $[2, 3, 4]$

B_f :- TieSet 1

$$\begin{bmatrix} 1 & -1 & 0 & -1 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & -1 \\ 0 & 1 & 0 & 1 & 0 & -1 \end{bmatrix}$$

(7)

Cutset matrix :-

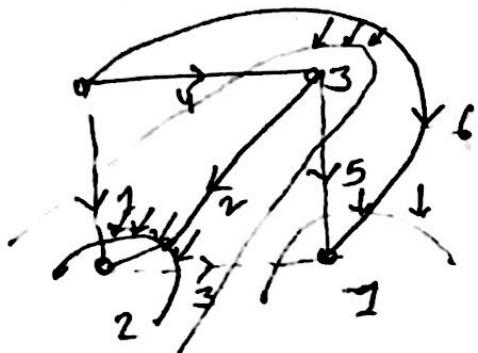


Cutset 1 [3 5 6]

Cutset 2 [1 2 3]

Cutset 3 [1 4 5 3]

$$Q_3 = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} 1 \\ 2 \\ 3 \end{matrix} & \left[\begin{matrix} 0 & 0 & 1 & 0 & 1 & 1 \\ 1 & 1 & -1 & 0 & 0 & 0 \\ -1 & 0 & 1 & -1 & -1 & 0 \end{matrix} \right] \end{matrix}$$

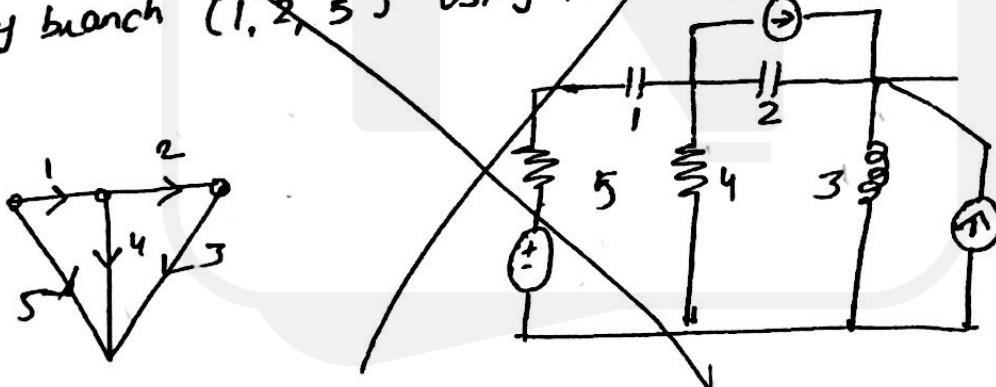Q) For the n/w determine a " tree and corresponding
 (o-tree form) network and consider the tree formed
 by branch (1, 2, 5) using tree walk A, B_j and Q_j



B-tree form

Q) The reduced incidence matrix of a graph is given by (7)


Nodes / Branches →	1	2	3	4	5	6
↓	1	0	0	-1	+1	1
a	0	1	0	0	0	0
b	0	-1	1	0	1	0
c	1	0	-1	0	0	0

Draw the oriented graph. Select a tree and find
j-cutset matrix.

	1	2	3	4	5	6
a	0	1	0	-1	-1	1
b	0	-1	1	0	1	0
c	1	0	-1	0	0	0

Incidence Matrix

	1	2	3	4	5
a	0	1	0	-1	-1
b	0	-1	1	0	1
c	1	0	-1	0	0
d	-1	0	0	1	0

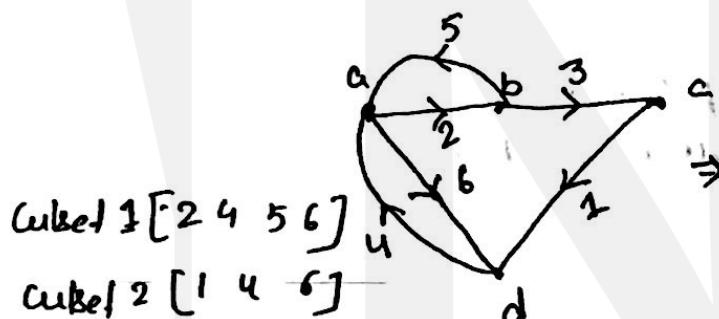

Cutset 1 [2 4 5 6]


Cutset 2 [1 4 6]

Cutset 3 [3 4 6]

Branches


Cutset	1	2	3	4	5	6
1	0	1	0	-1	-1	1
2	1	0	0	-1	0	1
3	0	0	1	-1	0	1

Select a tree

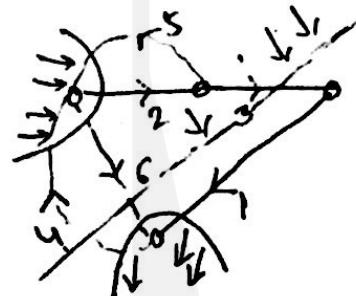


Show the cutset for the graph and develop the fundamental cutset matrix

(Q)

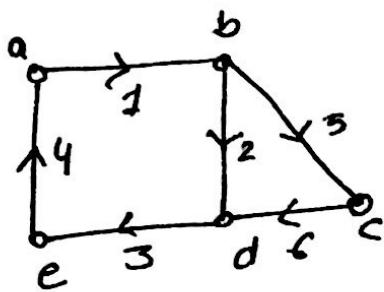

Step 1:- First select an arbitrary tree.

Tree $[1 \ 2 \ 3 \ 6]$ is selected


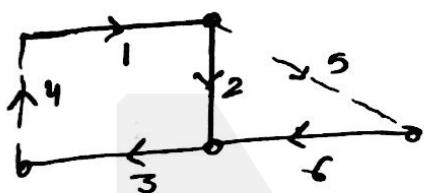


Twigs $[1 \ 2 \ 3 \ 6]$
Link $[4 \ 5]$



Step 2:- Form fundamental cutset with single link removed

branch and no. of links.
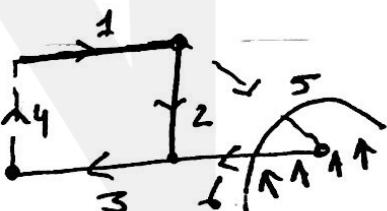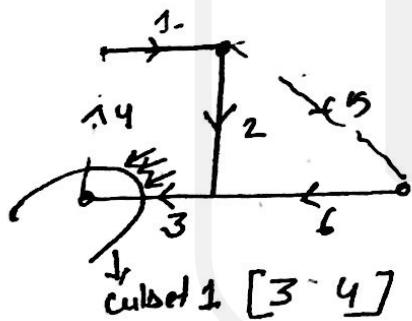
$$\text{Total no. of cutset} = N-1 \\ = 5-1 = 4$$



Cutset 2 $[6 \ 5]$

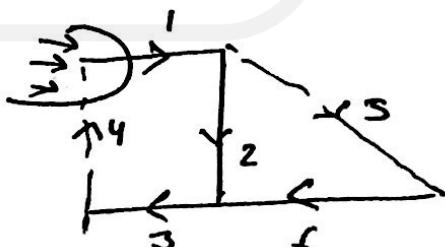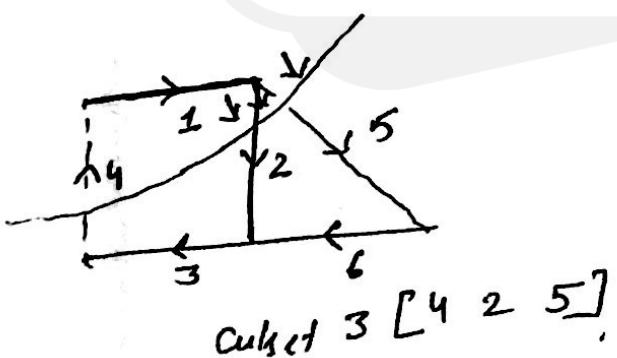


Cutset 4 $[1 \ 4]$


Cutset Matrix :- Branch

Cutset	1	2	3	4	5	6
1	0	0	1	-1	0	0
2	0	0	0	0	-1	1
3	0	1	0	-1	1	0
4	1	0	0	-1	0	0

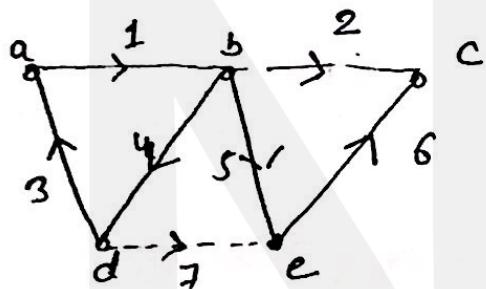Q) Find the cutset and tie-set matrix of given graph.



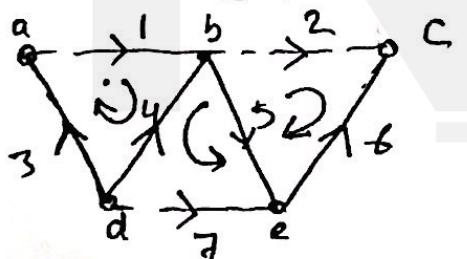For Cut set :- $B - N + 1 = 7 - 5 + 1 = 3$



Tie-set 1 [1 3 4]

Tie-set 2 [4 5 7]

Tie-set 3 [2 5 6]

Tie-set matrix :-

Tie-set	1	2	3	4	5	6	7
1	1	0	1	-1	0	0	0
2	0	0	0	-1	-1	0	1
3	0	1	0	0	0	-1	1

Q1 The reduced incidence matrix of a graph is given by

Nodes / Branches


$$\begin{array}{c|cccccc} & 1 & 2 & 3 & 4 & 5 & 6 \\ \hline a & 0 & 1 & 0 & -1 & -1 & 1 \\ b & 0 & -1 & 1 & 0 & 1 & 0 \\ c & 1 & 0 & -1 & 0 & 0 & 0 \end{array}$$

(9)

Draw the oriented graph . Select a tree and find f-cutset matrix.

Soln:- Incidence Matrix:-

$$\begin{array}{c|cccccc} & 1 & 2 & 3 & 4 & 5 & 6 \\ \hline a & 0 & 1 & 0 & -1 & -1 & 1 \\ b & 0 & -1 & 1 & 0 & 1 & 0 \\ c & 1 & 0 & -1 & 0 & 0 & 0 \\ d & 1 & 0 & 0 & 1 & 0 & -1 \end{array}$$

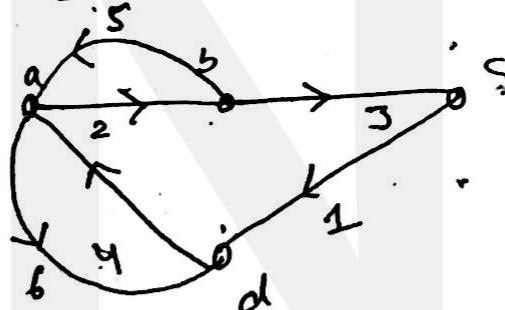


Cutset matrix :- Select a tree :-

Cutset 1 :- Cutset 1 [4 5 2 6]

Cutset 2 [1 4 6]

Cutset 3 [3 4 6]

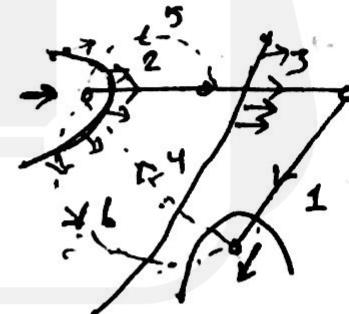

Branch

$$\begin{array}{c|cccccc} \text{Cutset} & 1 & 2 & 3 & 4 & 5 & 6 \\ \hline 1 & & & 1 & -1 & -1 & 1 \\ 2 & & 1 & & & -1 & 1 \\ 3 & & & & 1 & -1 & 1 \end{array}$$

Two Port Network

→ Port → If the current entering one terminal of a pair is equal and opposite to the current leaving the other terminal of the pair, then this type of terminal pair is called as a "port".

→ Two port network:-



→ Each port consists of two terminals, one for entering the current and other for leaving.
So two port network represented by a box assumed to consist of a passive network of linear resistor, inductors, capacitor and dependent source.

→ In order to describe the relationship between the port voltage and port current of a linear port n/w, two linear eqⁿ are required among the four variables.

Relationship of two port variables:-

of open ckt impedance [Z] Express function
 v_1, v_2 in terms of
 J_1, J_2

matrix eq"

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} J_1 \\ J_2 \end{bmatrix}$$

b) Short ckt admittance [Y]

$$J_1, J_2 \quad v_1, v_2 \quad \begin{bmatrix} J_1 \\ J_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$

$$\text{Transmission or chain } [T] \quad v_1, i_1 \quad v_2, -i_2 \quad \begin{bmatrix} v_1 \\ i_1 \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} \text{ Delimited}$$

$$\text{Inverse Transmission } [T] \quad v_2, i_2 \quad v_1, -i_1 \quad \begin{bmatrix} v_2 \\ i_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} v_1 \\ i_1 \end{bmatrix}$$

$$\text{Hybrid } (h) \quad v_1, i_2 \quad i_1, v_2 \quad \begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$


$$\text{Inverse hybrid } (g) \quad i_1, v_2 \quad v_1, i_2 \quad \begin{bmatrix} i_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

Open Ckt Impedance $[z]$ Parameters:-

$$(v_1, v_2) = f(i_1, i_2)$$


$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$
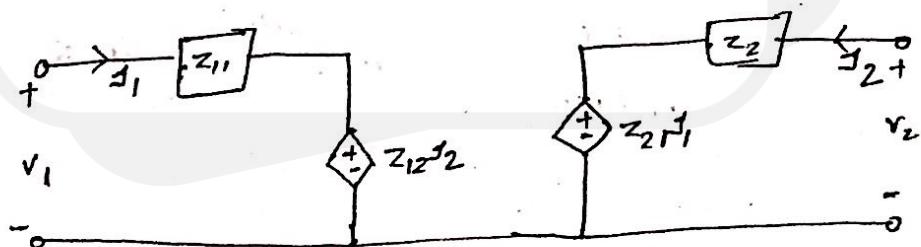
$$\begin{aligned} v_1 &= z_{11}i_1 + z_{12}i_2 \\ v_2 &= z_{21}i_1 + z_{22}i_2 \end{aligned} \quad \rightarrow (a)$$



Equivalent ckt of a two port network in terms of Z-parameters.

Determination of Z-parameter:-

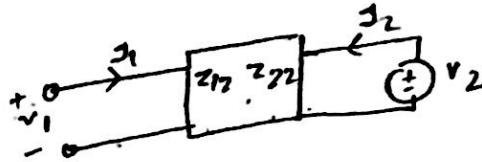

$$v_1 = g_1 z_{11} + g_2 z_{21}$$

$$v_2 = g_1 z_{21} + g_2 z_{22}$$

When $g_2 = 0$ [O/p port open circ'd]

Case 1:-

$$v_1 = g_1 z_{11} + 0$$

$$\frac{v_1}{g_1} \Big|_{g_2=0} = z_{11} \rightarrow \text{S/I P driving point impedance with O/p port open circ'd.}$$

$$v_2 = g_1 z_{21} + g_2 z_{22}$$

$$\frac{v_2}{g_1} \Big|_{g_2=0} = z_{21} \Rightarrow \text{Forward transfer impedance with the O/p port open circ'd.}$$

Case 2:- when $g_1 = 0$ [S/I P. port open circ'd]

$$v_1 = g_2 z_{12}$$

$$\frac{v_1}{g_2} \Big|_{g_1=0} = z_{12} \rightarrow \text{Reverse transfer impedance with S/I P. port open circ'd}$$

$$v_2 = g_2 z_{22}$$

$$\frac{v_2}{g_2} \Big|_{g_1=0} = z_{22} \rightarrow \text{O/p driving point impedance with S/I P. port open circ'd.}$$

by short ckt Admittance [Y] parameter:-

$$(I_1, I_2) = f(v_1, v_2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix}$$


$$[f] \sim [Y] [v]$$

where $[Y]$ = Short ckt admittance parameter.

where $Y_{12} v_2$ and $Y_{21} v_1$ are voltage controlled current source

$$I_1 = Y_{11} v_1 + Y_{12} v_2$$

$$I_2 = Y_{21} v_1 + Y_{22} v_2$$

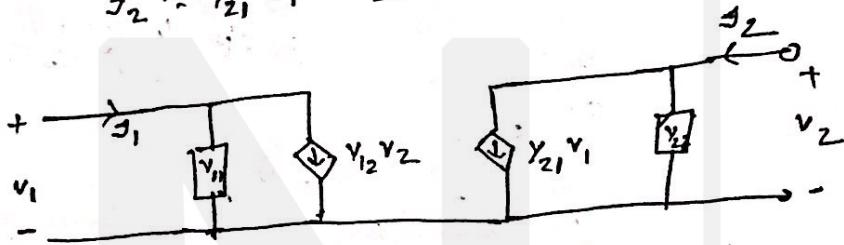

Case 1 :- $v_2 = 0$ [o/p port short circuited]

$$I_1 = Y_{11} v_1$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{v_2=0} \rightarrow \text{[d/p driving point admittance with the o/p port short circuited]}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{v_2=0} \rightarrow \text{[forward transfer admittance with o/p port short circuited]}$$

Case 2 :- $v_1 = 0$ [s/p port short ckt'd]

$$Y_{12} = \frac{I_1}{V_2} \Big|_{v_1=0} \rightarrow \text{[reverse transfer admittance with s/p port short ckt'd]}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{v_1=0} \rightarrow \text{[o/p driving point admittance with the s/p port short ckt'd]}$$

short circuit admittance matrix = [open circuit impedance matrix]⁻¹ 3]

$$[Y] = [Z]^{-1}$$

And $Y_{ij} \neq \frac{1}{Z_{ij}}$ i.e. $Y_{11} \neq \frac{1}{Z_{11}}$ and

$$Y_{12} \neq \frac{1}{Z_{12}} \text{ etc.}$$

Transmission (T) or chain or $ABCD$ -parameters;

Expressing one port variables in terms of other port variables i.e.

$$(V_1, I_1) = f(V_2, -I_2)$$

- T -parameters are used in the analysis of power transmission line
- the SIP and OIP ports are called sending and receiving end respectively.

- OIP port current is considered outward, therefore negative sign arises with I_2 .


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

- the matrix equation defined A, B, C, D parameters, where matrix is known as Transmission (T) or $ABCD$ matrix.

$$V_1 = A V_2 - B I_2$$

$$I_1 = C V_2 - D I_2$$

Determination of T -parameters:-

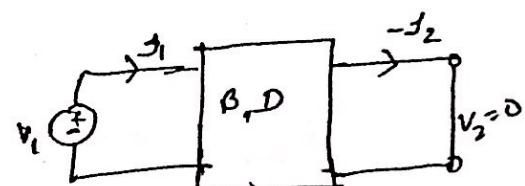

- In order to determine the T -parameters, open and short the OIP port (receiving end) and apply some voltage ' V_1 ' to SIP port to obtain A, C and B, D

$$\text{Case 1:- } g_2 = 0 \quad [\text{o/p port open ckt'd}]$$

$$A = \frac{V_1}{V_2} \Big|_{g_2=0} \quad [\text{reverse voltage ration with receiving end open ckt'd}]$$

$$C = \frac{J_1}{V_2} \Big|_{g_2=0} \quad [\text{reverse transfer admittance with receiving end open ckt'd}]$$

$$\text{Case II:- } V_2 = 0 \quad [\text{o/p short ckt'd}]$$

$$B = \frac{V_1}{-J_2} \Big|_{V_2=0} \quad [\text{reverse branch impedance with receiving end short ckt'd}]$$

$$D = \frac{J_1}{-J_2} \Big|_{V_2=0} \quad [\text{reverse current ration with receiving end short ckt'd}]$$

Inverse Transmission (T') parameter:-

Expressing o/p port variables in terms of I/p port variables;

$$(V_2, J_2) = f(V_1, -J_1)$$



$$\begin{bmatrix} V_2 \\ J_2 \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} V_1 \\ -J_1 \end{bmatrix}$$

where matrix consisting of A', B', C', D' is called as inverse transmission matrix,

$$V_2 = A'V_1 + B'(-J_1)$$

$$J_2 = C'V_1 + D'(-J_1)$$

Determination of T' parameters:-

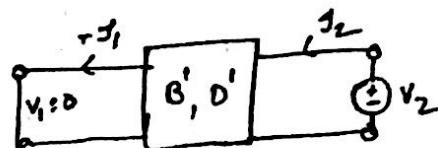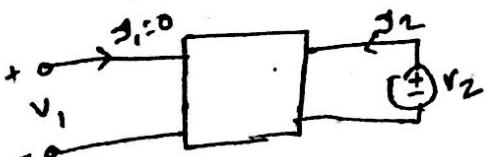

$\mathfrak{I}_1 = 0$ import port is open circled

$$\mathfrak{V}_2 = A'V_1 + B'(-\mathfrak{I}_1)$$

$$\mathfrak{I}_2 = C'V_1 + D'(-\mathfrak{I}_1)$$

$A' = \frac{\mathfrak{V}_2}{V_1} \Big|_{\mathfrak{I}_1=0}$ \Rightarrow forward voltage ratio with sending end open circled

$D' = \frac{\mathfrak{I}_2}{V_1} \Big|_{\mathfrak{I}_1=0} \Rightarrow$ Transfer admittance

Case 2: $V_1 = 0 \Rightarrow S/P$ is short circled

$B' = \frac{\mathfrak{V}_2}{-\mathfrak{I}_1} \Big|_{V_1=0} \Rightarrow$ Transfer impedance with sending end short circled

$D' = \frac{\mathfrak{I}_2}{-\mathfrak{I}_1} \Big|_{V_1=0} \Rightarrow$ forward current ratio.



Hybrid (h) Parameters:-
In this case, voltage of S/P port and ~~voltage of~~ current of S/P port and ~~voltage of~~ current of O/P port are expressed in terms of current of S/P port and voltage of O/P port.

$$(V_1, \mathfrak{I}_2) = f(\mathfrak{I}_1, V_2)$$

$$\begin{bmatrix} V_1 \\ \mathfrak{I}_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} \mathfrak{I}_1 \\ V_2 \end{bmatrix}$$

$$V_1 = h_{11}\mathfrak{I}_1 + h_{12}V_2$$
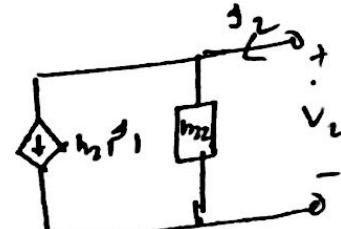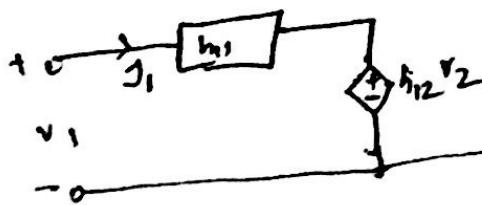
$$\mathfrak{I}_2 = h_{21}\mathfrak{I}_1 + h_{22}V_2$$




Determination of h-parameter :-

$$\text{Case I} \quad v_1 = h_{11} i_1 + h_{12} v_2$$

$$i_2 = h_{21} i_1 + h_{22} v_2$$

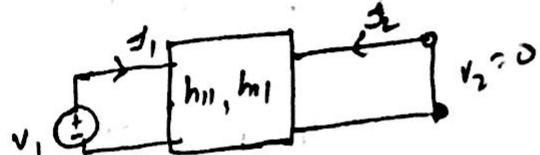Case I:- $v_2 = 0 \rightarrow \text{o/p port short circ'd}$




$$h_{11} = \left. \frac{v_1}{i_1} \right|_{v_2=0} \rightarrow \text{o/p impedance}$$

$$h_{21} = \left. \frac{i_2}{v_1} \right|_{v_2=0} \rightarrow \text{forward current gain}$$

Case II

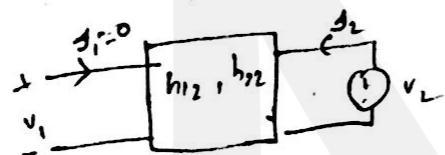$i_1 = 0 \rightarrow \text{o/p port open circ'd}$



$$h_{12} = \left. \frac{v_1}{v_2} \right|_{i_1=0} \Rightarrow \text{reverse voltage gain}$$

$$h_{22} = \left. \frac{i_2}{v_2} \right|_{i_1=0} \Rightarrow \text{o/p admittance}$$


Inverse hybrid parameter [g] :-

$$[g] = [h]^{-1}$$

$$\begin{bmatrix} i_1 \\ v_2 \end{bmatrix} \sim \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ i_2 \end{bmatrix}$$

$$i_1 = g_{11} v_1 + g_{12} i_2$$

$$v_2 = g_{21} v_1 + g_{22} i_2$$

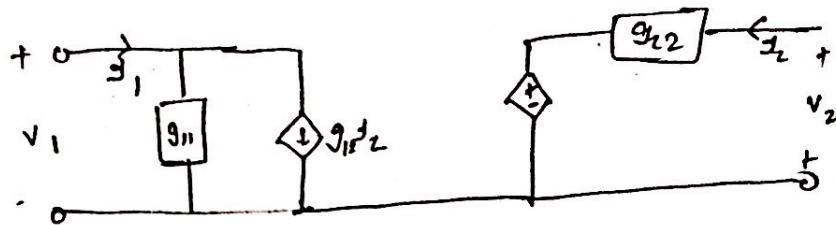

a) Z parameter
Case I:

Determination of g. parameters :-

Case I: $j_2 = 0 \Rightarrow$ O/p port open ckt/d.


$$g_{11} = \left. \frac{j_1}{v_1} \right|_{j_2=0} \Rightarrow \text{O/p admittance}$$

$$g_{21} = \left. \frac{v_2}{v_1} \right|_{j_2=0} \Rightarrow \text{forward voltage gain}$$


Case II: $v_1 = 0 \Rightarrow$ O/p port short ckt/d

$$g_{12} = \left. \frac{j_1}{j_2} \right|_{v_1=0} \Rightarrow \text{reverse current gain}$$

$$g_{22} = \left. \frac{v_2}{j_2} \right|_{v_1=0} \Rightarrow \text{O/p impedance}$$

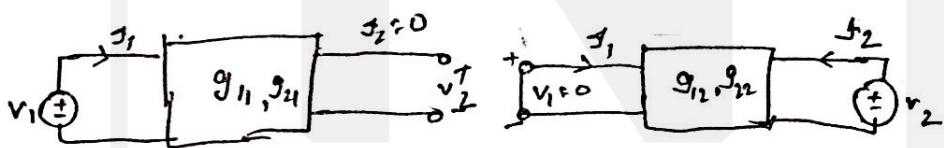

Ex:-

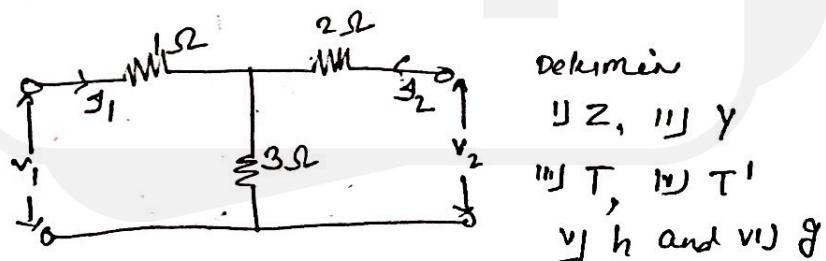

Determine
i) Z, ii) Y
iii) T, iv) T'
v) h and vi) g

$$v_1 = j_1 x 1 + 3(j_1 + j_2)$$

$$v_1 = 4j_1 + 3j_2 \quad \text{(I)}$$

$$v_2 = g_21 + 3(j_1 + j_2)$$

$$v_2 = 3j_1 + 5j_2 \quad \text{(II)}$$

$$\text{a) } z\text{-parameters} \vdash (v_1, v_2) = f(s_1, s_2)$$

Case I :- $s_2 = 0$ and Case II :- $s_1 = 0$

$$z_{11} = \frac{v_1}{s_1} \Big|_{s_2=0} = \frac{v_1}{v_2} = 4\Omega$$

$$z_{21} = \frac{v_2}{s_1} \Big|_{s_2=0} \Rightarrow 3\Omega.$$

Case II :- $s_1 = 0$

$$v_1 = 3s_2$$

$$z_{12} = \frac{v_1}{s_2} = 3\Omega$$

$$z_{22} = \frac{v_2}{s_2} = 5\Omega$$

$$Y\text{-parameters} - (s_1, s_2) = f(v_1, v_2)$$

Case I :- $v_2 = 0$ Case II $v = 0$

$$v_1 = 4s_1 + 3s_2$$

$$v_2 = 3s_1 + 5s_2 \Rightarrow 3s_2 = -5s_1$$

$$v_1 = \frac{11}{5}s_1$$

$$v_1 = -\frac{11}{3}s_2$$


$$y_{11} = \frac{s_1}{v_1} \Big|_{v_2=0} \Rightarrow \frac{5}{11} V$$

$$y_{21} = \frac{s_2}{v_1} \Big|_{v_2=0} \Rightarrow -\frac{3}{11} V$$

$$s_1 = v_{11}v_1 + v_{12}v_2$$

$$s_2 = v_{21}v_1 + v_{22}v_2$$

Q1

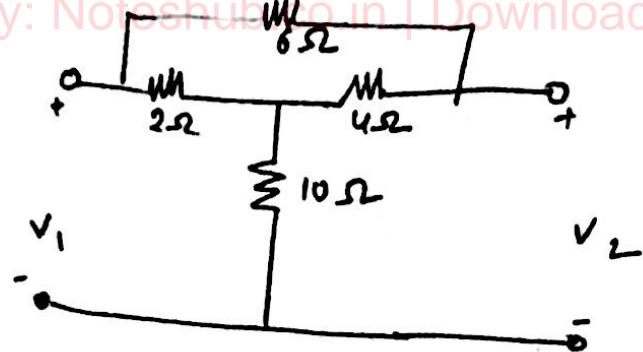


Obtain the open-circuit 2-parameter of the network;

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

Case: $I_2 = 0$
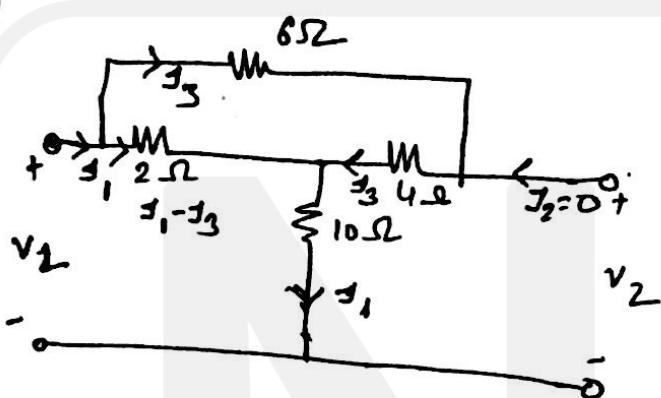
$$\begin{aligned} -6 &= 2I_1 + 10I_1 \\ -12 &= 4I_1 + 10I_1 \end{aligned}$$



$$\begin{aligned} V_1 &= 2(I_1 - I_3) + 10I_1 \Rightarrow V_1 = 12I_1 - 2I_3 \quad (1) \\ V_2 &= 4I_3 + 10I_1 \quad (2) \end{aligned}$$

$$-6I_3 - 4I_3 - 2(I_3 - I_1) = 0$$

$$-12I_3 + 2I_1 = 0$$

$$12I_3 = 2I_1$$

$$\boxed{I_3 = \frac{I_1}{6}}$$


$$V_1 = 12I_1 - \frac{I_1}{3}$$

$$V_2 = \frac{2I_1}{3} + 10I_1 = \frac{32I_1}{3}$$

$$Z_{11} = \frac{35}{3} \Omega$$

$$Z_{21} = \frac{32}{3} \Omega$$

Case II :- $I_1 = 0$

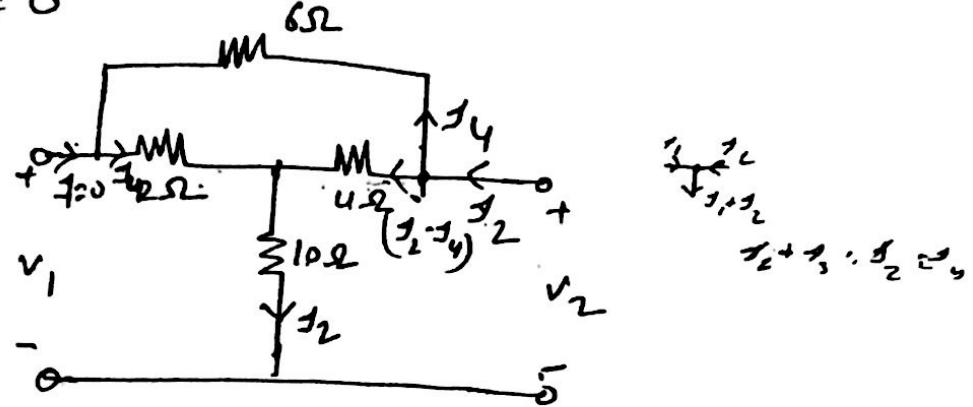

$$V_1 = 2I_4 + 10I_2 \quad (1)$$

$$V_2 = 4(I_2 - I_4) + 16I_2 \quad -6I_2 - 2I_4 - 4(I_2 - I_4) = 0$$

$$V_2 = 14I_2 - 4I_2 \quad +12I_2 \quad (II)$$

$$-6I_2 - 2I_4 - 4(I_2 - I_4) = 0$$

$$-2I_2 - 6I_4 = 0$$

$$-2I_2 = 6I_4$$

$$\frac{I_2}{3} = I_4$$

$$8I_4 + 4(I_2 - I_4) = 0$$

$$12I_4 + 4I_2 = 0$$

$$-6I_4 - 2I_4 - 4(I_4 - I_2) = 0$$

$$-12I_4 + 4I_2 = 0$$

$$14I_4 = 12I_2$$

$$3I_4 = I_2$$

$$-6I_4 - 2I_4 - 4(I_2 - I_4) = 0$$

$$-4I_4 + 4I_2 = 0$$



$$-6I_4 - 2I_4 - 4(I_4 - I_2) = 0$$

$$-12I_4 + 4I_2 = 0$$

$$12I_4 = 4I_2$$

$$3I_4 = I_2$$

$$I_4 = \frac{I_2}{3}$$

$$V_1 = 2 \frac{I_2}{3} + 10 I_2 = \frac{32}{3} I_2$$

$$V_2 = 14 I_2 - 4 \frac{I_2}{3} = \frac{38}{3} I_2$$



$$Z_{12} = \frac{32}{3} \Omega$$

$$Z_{22} = \frac{38}{3} \Omega$$

Condition for Reciprocity:-

Reciprocal:- A two port network is said to be reciprocal if ratio of excitation to response is invariant to an interchange of position of excitation and response in the n/p.

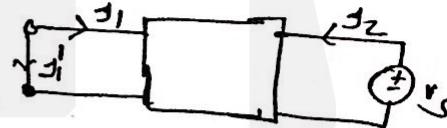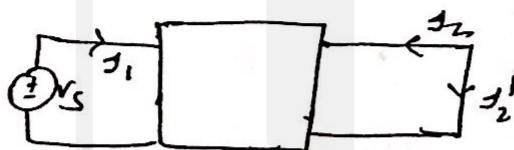- Network containing resistors, inductors, and capacitors are generally reciprocal.
- Network additionally have dependent source are generally non-reciprocal.



$$[V_1 = V_S, I_1 = I_1, V_2 = 0, I_2 = -I_2']$$

In terms of Z-parameter:-

$$\boxed{Z_{12} = Z_{21}}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\text{From fig 01} \quad V_S = Z_{11} I_1 - Z_{12} I_2'$$

$$0 = Z_{21} I_1 - Z_{22} I_2'$$

$$\Rightarrow Z_{21} I_1 = Z_{22} I_2'$$

on solving ; $\mathfrak{I}_2' = \frac{V_S Z_{21}}{Z_{11} Z_{22} - Z_{21} Z_{12}}$

From fig b) ; $V_2 = V_S$, $\mathfrak{I}_2 = \mathfrak{I}_2'$, $V_1 = 0$, $\mathfrak{I}_1 = -\mathfrak{I}_1'$

$$\left. \begin{aligned} 0 &= -Z_{11} \mathfrak{I}_1' + Z_{12} \mathfrak{I}_2 \\ V_S &= -Z_{21} \mathfrak{I}_1' + Z_{22} \mathfrak{I}_2 \end{aligned} \right] \rightarrow b)$$

on solving b)

$$\mathfrak{I}_1' = \frac{V_S Z_{12}}{Z_{11} Z_{22} - Z_{21} Z_{12}}$$

comparing \mathfrak{I}_1' and \mathfrak{I}_2' ,

$$\boxed{Z_{12} = Z_{21}} \rightarrow \text{condition of reciprocity}$$

\rightarrow In terms of Y-parameter :-

$$\boxed{Y_{12} = Y_{21}}$$

$$\mathfrak{I}_1 = Y_{11} V_1 + Y_{12} V_2$$

$$\mathfrak{I}_2 = Y_{21} V_1 + Y_{22} V_2$$

In same manner in Z-parameters

\rightarrow In terms of T-parameters :-

$$V_1 = A V_2 + B (-\mathfrak{I}_2)$$

$$\mathfrak{I}_2 = C V_2 + D (-\mathfrak{I}_2)$$

From fig. a) $V_1 = V_S$, $\mathfrak{I}_1 = \mathfrak{I}_1'$, $V_2 = 0$, $\mathfrak{I}_2 = -\mathfrak{I}_2'$

$$\mathfrak{I}_2' = \frac{V_S}{B}$$

From fig b) ; $V_2 = V_S$, $\mathfrak{I}_2 = \mathfrak{I}_2'$, $V_1 = 0$, $\mathfrak{I}_1 = -\mathfrak{I}_1'$

$$-\mathfrak{I}_1' = C V_S - D \mathfrak{I}_2'$$

$$= C V_S + D \mathfrak{I}_2'$$

$$\begin{aligned} -\mathfrak{I}_1' &= C V_S + D \frac{V_S}{B} \\ -B \mathfrak{I}_1' &= C V_S + D \frac{V_S}{B} \end{aligned}$$

From fig by $v_2 = v_s, g_2 = g_s, v_o = 0, g_o = g_1$

$$0 = Av_s - Bg_2$$

$$\frac{Av_s}{B} = g_2$$

$$-g'_1 = Cv_s - Dg_2$$

$$-g'_1 = Cv_s - \frac{DAv_s}{B}$$

$$-g'_1 = \left(BC - \frac{AD}{B} \right) v_s$$

$$g'_1 = \frac{(AD \cdot BC)}{B} v_s$$

on comparing g'_1 and g'_2 :

$$AD \cdot BC : 1 \text{ or } \Delta T = 1$$

$$\begin{vmatrix} A & B \\ C & D \end{vmatrix} = 1$$

In terms of T-parameter:-

$$A'D' - B'C' = 1 \text{ or } \Delta T' = 1$$

$$\begin{vmatrix} A' & B' \\ C' & D' \end{vmatrix} = 1$$

* In terms of h-parameter:-


$$h_{12} = -h_{21}$$

Similarly find g'_1 and g'_2 and compare


* In terms of g-parameter:-

$$g_{12} = -g_{21}$$

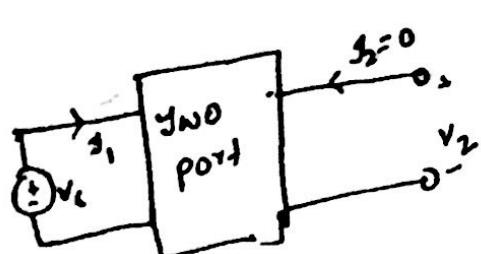A two port network is said to be symmetrical if the ports can be interchanged without changing the port voltage and current.


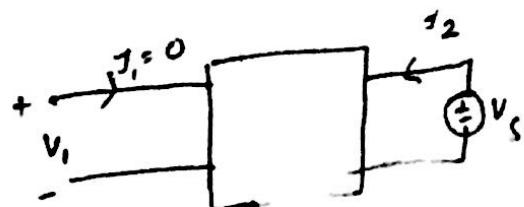
$$V_1 = V_S, \quad g_1 = g_1, \quad g_2 = 0, \quad V_2 = V_S.$$



$$V_1 = V_S, \quad g_1 = 0, \quad V_S = V_2, \quad I_2 = I_1$$

$$\left. \frac{V_S}{I_1} \right|_{g_2=0} = \left. \frac{V_S}{I_2} \right|_{g_1=0}$$

In terms of Z-parameter:

$$\boxed{Z_{11} = Z_{22}}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\text{From fig a)} \quad V_S = Z_{11} I_1$$

$$\left. \frac{V_S}{I_1} \right|_{g_2=0} = Z_{11}$$

$$\text{From fig b)} \quad V_S = Z_{22} I_2.$$

$$\left. \frac{V_S}{I_2} \right|_{g_1=0} = Z_{22}$$

$$\therefore Z_{11} = Z_{22}$$

In terms of Y-parameter:

$$\boxed{Y_{11} = Y_{22}}$$

in terms of T

$$A = D$$

in terms of H

$$A = D$$

$$\begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 2$$

$$\begin{vmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{vmatrix} = 2$$

In terms of T-parameter :-

$$\boxed{A = D}$$

In terms of T' parameter :-

$$\boxed{A' = D'}$$

In terms of h-parameter :-

$$h_{11}h_{22} - h_{12}h_{21} = 1; \Delta h = 1$$

$$\begin{vmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{vmatrix} = 1$$

In terms of g-parameter :-

$$g_{11}g_{22} - g_{12}g_{21} = 1; \Delta g = 1$$

$$\begin{vmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{vmatrix} = 1$$

Relation b/w Parameter sets :-

Table no - 8.3, Page no - 282 From KM Soni.

In Interconnections of TWO Port Networks :-

Two port network may be interconnected in various config.
such as series, parallel, cascade, series-parallel and
parallel-series connection.

Series Connection :-

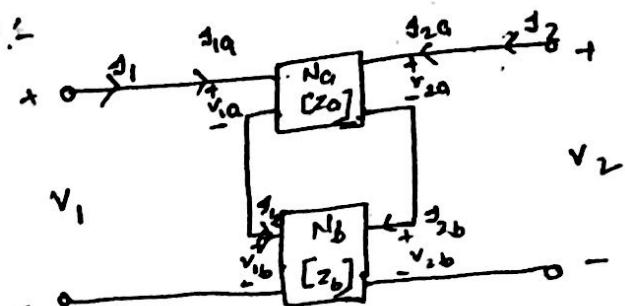


Fig showing connection of two two port network N_a and N_b with open circuit z-parameter z_{1a} and z_{2a} for network N_g

$$\begin{bmatrix} v_{1a} \\ v_{2a} \end{bmatrix} = \begin{bmatrix} z_{11a} & z_{12a} \\ z_{21a} & z_{22a} \end{bmatrix} \begin{bmatrix} s_{1a} \\ s_{2a} \end{bmatrix}$$

For Network N_b :

$$\begin{bmatrix} v_{1b} \\ v_{2b} \end{bmatrix} = \begin{bmatrix} z_{11b} & z_{12b} \\ z_{21b} & z_{22b} \end{bmatrix} \begin{bmatrix} s_{1b} \\ s_{2b} \end{bmatrix}$$

Then their series connection requires that;

$$s_1 = s_{1a} = s_{1b}, \quad s_2 = s_{2a} = s_{2b}$$

$$v_1 = v_{1a} + v_{1b}$$

$$v_2 = v_{2a} + v_{2b}$$

$$v_1 = v_{1a} + v_{1b} = (z_{11a}s_{1a} + z_{12a}s_{2a}) + (z_{11b}s_{1b} + z_{12b}s_{2b}) \\ = (z_{11a} + z_{11b})s_1 + (z_{12a} + z_{12b})s_2$$

$$[\text{Since } s_1 = s_{1a} = s_{1b} \text{ and } s_2 = s_{2a} = s_{2b}]$$

and similarly; $v_2 = v_{2a} + v_{2b}$

$$= (z_{21a}s_{1a} + z_{22a}s_{2a}) + (z_{21b}s_{1b} + z_{22b}s_{2b})$$

$$= (z_{21a} + z_{21b})s_1 + (z_{22a} + z_{22b})s_2$$

$$= (z_{21a} + z_{21b})s_1 + (z_{22a} + z_{22b})s_2$$

In matrix form;

$$\begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} s_1 \\ s_2 \end{bmatrix}$$

$$z_{11} = z_{11a} + z_{11b}$$

$$z_{12} = z_{12a} + z_{12b}$$

$$z_{21} = z_{21a} + z_{21b}$$

$$z_{22} = z_{22a} + z_{22b}$$

or in matrix form;

$$[Z] = [Z_a] + [Z_b]$$

Thus, the overall Z-parameter matrix for series connected two port n/w is simply the sum of Z-parameter matrices of each individual two port n/w connected in series.


Parallel connection:-

Fig. shows a parallel connection of two port n/w N_a and N_b with short circ. Y-parameter Y_a and Y_b respectively i.e. for network N_a;

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} Y_{11a} & Y_{12a} \\ Y_{21a} & Y_{22a} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$

Similarly for network N_b;
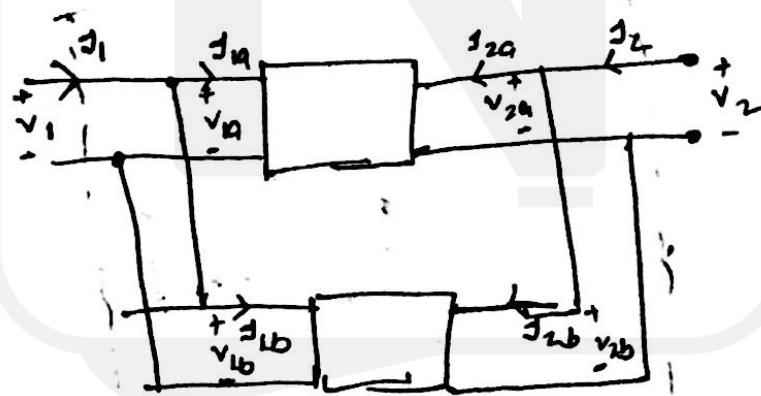
$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} Y_{11b} & Y_{12b} \\ Y_{21b} & Y_{22b} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$



$$\begin{aligned}
 V_{1a} &= V_1 - V_{1b} \\
 V_2 &= V_{2a} + V_{2b} \\
 V_1 &= V_{1a} = V_{1b} \\
 V_2 &= V_{2a} = V_{2b} \\
 I_1 &= I_{1a} + I_{1b} \\
 I_2 &= I_{2a} + I_{2b}
 \end{aligned}$$

$$= (Y_{11a} v_{1a} + Y_{12a} v_{2a}) + (Y_{11b} v_{1b} + Y_{12b} v_{2b})$$

and $v_{1a} = v_{1b} = v_1$ and $v_{2a} = v_{2b} = v_2$

$$\Rightarrow (Y_{11a} + Y_{11b})v_1 + (Y_{12a} + Y_{12b})v_2$$

$$\therefore \boxed{Y_{11} = Y_{11a} + Y_{11b}}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$\text{and } I_2 = I_{2a} + I_{2b}$$

$$= (Y_{21a} v_{1a} + Y_{22a} v_{2a}) + (Y_{21b} v_{1b} + Y_{22b} v_{2b})$$


$$= (Y_{21a} + Y_{21b})v_1 + (Y_{22a} + Y_{22b})v_2$$

$$\therefore \boxed{Y_{21} = Y_{21a} + Y_{21b}}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

Cascade connection:- (Tandem connection)

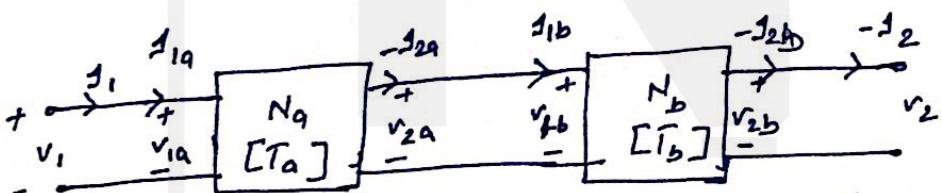Two port network are said to be connected in cascade if output port of first becomes the input port of second



$$\begin{bmatrix} v_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} v_{2a} \\ -I_{2a} \end{bmatrix} \quad \text{and} \quad \begin{bmatrix} v_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} v_{2b} \\ -I_{2b} \end{bmatrix}$$

$$\text{and } I_{1a} = I_1, \quad -I_{2a} = I_{1b}, \quad I_2 = I_{2b}$$

$$v_1 = v_{1a}, \quad v_{2a} = v_{1b}, \quad v_{2b} = v_2.$$

$$\begin{bmatrix} v_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} v_{2a} \\ -I_{2a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} v_{1b} \\ I_{1b} \end{bmatrix}$$

and value of $\begin{bmatrix} v_{1b} \\ I_{1b} \end{bmatrix}$ from eqn (b)

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} v_{2b} \\ -I_{2b} \end{bmatrix}$$

Provided by: NotesHub.co.in | Download Android App

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$\therefore \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

$$\therefore A = A_a A_b + B_a C_b$$

$$B = A_b B_b + B_a D_b$$

$$C = C_a A_b + D_a C_b$$


$$D = C_a B_b + D_a D_b$$

$$\therefore [T] = [T_a] \cdot [T_b]$$

∴ therefore the overall T-parameter matrix for cascade connected two port network is simply the matrix product of the T-parameter matrices of each individual two port network in cascade.

Series - Parallel connection :-

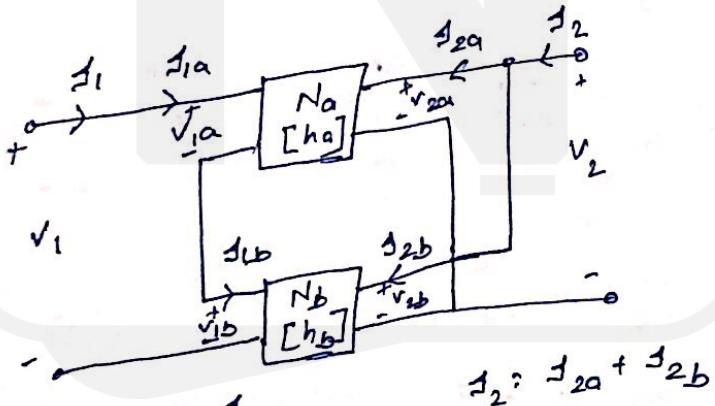Two two port networks are said to be connected in series - parallel if the input ports are connected in series while output ports are connected in parallel.



$$I_1 = I_{1a} = I_{1b}$$

$$V_1 = V_{1a} + V_{1b}$$

$$I_2 = I_{2a} + I_{2b}$$

$$V_2 = V_{2a} = V_{2b}$$

For network N_a :

$$\begin{bmatrix} V_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} h_{11a} & h_{12a} \\ h_{21a} & h_{22a} \end{bmatrix} \begin{bmatrix} I_{1a} \\ V_{2a} \end{bmatrix}$$

$$\begin{bmatrix} v_{1b} \\ i_{2b} \end{bmatrix} = \begin{bmatrix} h_{11b} & h_{12b} \\ h_{21b} & h_{22b} \end{bmatrix} \begin{bmatrix} i_{1b} \\ v_{2b} \end{bmatrix}$$

$$\begin{bmatrix} v_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} v_{1a} \\ i_{2a} \end{bmatrix} + \begin{bmatrix} v_{1b} \\ i_{2b} \end{bmatrix}$$

$$= \begin{bmatrix} h_{11a} + h_{11b} \\ h_{21a} + h_{21b} \end{bmatrix} \begin{bmatrix} i_1 \\ v_2 \end{bmatrix}$$

$$\therefore h_{11} = h_{11a} + h_{11b}$$

$$h_{12} = h_{12a} + h_{12b}$$


$$h_{21} = h_{21a} + h_{21b}$$

$$h_{22} = h_{22a} + h_{22b}$$

$$\therefore [h] = [h_a] + [h_b]$$

Therefore the overall h-parameter matrix for series-parallel connected two port network is simply the sum of h-parameter matrix of each individual two port network connected in series parallel.

* Parallel-Series Connection:-

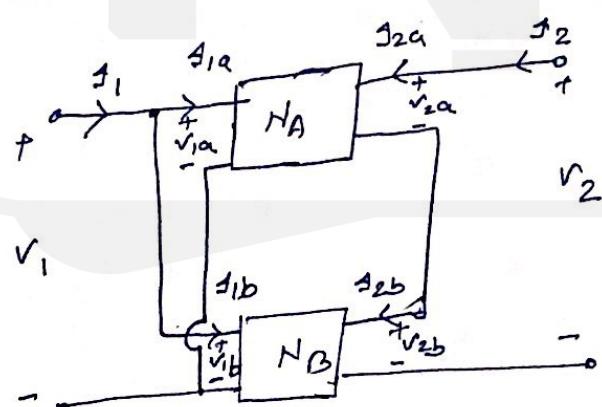

As similar to previous case;

$$g_{11} = g_{11a} + g_{11b}$$


$$g_{12} = g_{12a} + g_{12b}$$

$$g_{21} = g_{21a} + g_{21b}$$

$$g_{22} = g_{22a} + g_{22b}$$

$$[g] = [g_a] + [g_b]$$

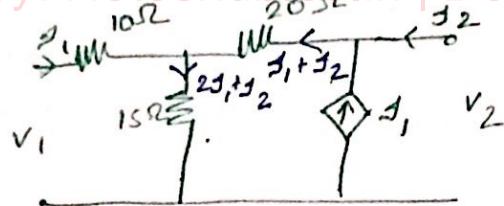Q) Determine the Z-parameter of the network.



$$v_1 = 10I_1 + 15(2I_1 + I_2)$$

$$v_1 = 10I_1 + 30I_1 + 15I_2$$

$$v_1 = 40I_1 + 15I_2 \quad \text{--- (1)}$$

$$v_2 = 20(I_1 + I_2) + 15(2I_1 + I_2)$$


$$v_2 = 50I_1 + 35I_2 \quad \text{--- (11)}$$

Comparing eqn (1) and (11) with $v_1 = z_{11}I_1 + z_{12}I_2$
 $v_2 = z_{21}I_1 + z_{22}I_2$


$$\therefore z_{11} = 40 \Omega \quad z_{21} = 50 \Omega$$

$$z_{12} = 50 \Omega \quad z_{22} = 35 \Omega$$

Q) Obtain the open circuit Z-parameter of network.

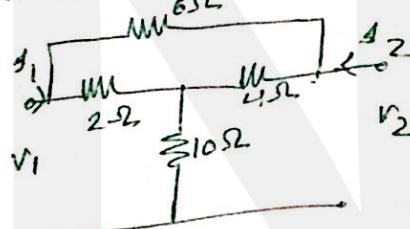

Case 1 :-

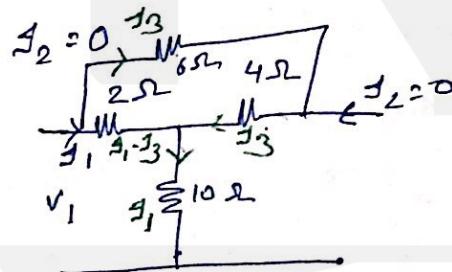



$$v_1 = 2(I_1 - I_3) + 10I_1 = 12I_1 - 2I_3$$

$$v_2 = 4I_3 + 10I_1$$

$$I_3 = I_1 \times \frac{2}{2+6+4} = \frac{I_1}{6} \quad [\text{Using current division rule}]$$

$$\therefore v_1 = 12I_1 - 2 \times \frac{I_1}{6} \Rightarrow v_1 = \frac{35}{3}I_1$$
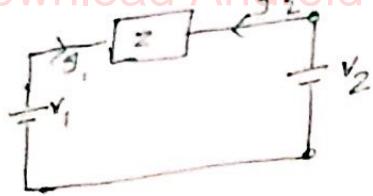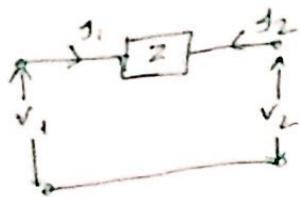
$$v_2 = 4 \times \frac{I_1}{6} + 10I_1 = \frac{32}{3}I_1$$



$$\text{Soln: } v_1 = z_1 z + v_2$$

$$j_1 = -j_2$$

and For z -parameters;

$$v_1 = z_{11} j_1 + z_{12} j_2$$

$$v_2 = z_{21} j_1 + z_{22} j_2$$

For finding the z_{11} and $z_{21} \rightarrow j_2 = 0$

$$\text{but } j_1 = -j_2 = 0$$

and similarly z_{12} and $z_{22} \rightarrow j_1 = 0$

$$\text{but } j_1 = -j_2 = 0$$

so z -parameters don't exist, as j_1 and j_2 are not independent.

→ For y -parameters;

$$z_1 = y_{11} v_1 + y_{12} v_2$$

$$z_2 = y_{21} v_1 + y_{22} v_2$$

For finding y_{11} and $y_{21} \rightarrow v_2 = 0$

$$v_1 = z_1 z + v_2 \quad \text{and } j_1 = -j_2$$

$$v_2 = 0 \Rightarrow v_1 = z_1 z$$

$$\text{and } y_{11} = \frac{j_1}{v_1} = \frac{1}{z}$$

$$y_{21} = \frac{j_2}{v_1} \text{ and } j_2 = -j_1$$

$$= \frac{-j_1}{v_1} = -\frac{1}{z}$$

For finding y_{12} and $y_{22} \rightarrow v_1 = 0$

$$v_1 = z_1 z + v_2 \Rightarrow 0 = z_1 z + v_2$$

$$y_{12} = \frac{j_1}{v_2} = \cancel{\frac{1}{z}}$$

$$\Rightarrow z_1 z = -v_2$$

$$\Rightarrow \frac{z_1}{v} = -\frac{v_2}{z} = y_{12}$$

$$v_1 = v_2 + j_1 z \Rightarrow 0 = v_2 + j_1 z$$

$$j_1 = -j_2 \Rightarrow 0 = v_2 - j_2 z$$

$$\Rightarrow v_2 = +j_2 z$$


$$= +\frac{1}{2} = \frac{j_2}{v_2} = Y_{22} = \frac{1}{2}$$

$$Y = \begin{bmatrix} k & -k \\ -1/2 & 1/2 \end{bmatrix}$$

Q) Find short circuit parameters of the circuit;

~~Applying KCL;~~

$$j_1 + j_2 = \frac{v_2}{100} + 2j_1$$

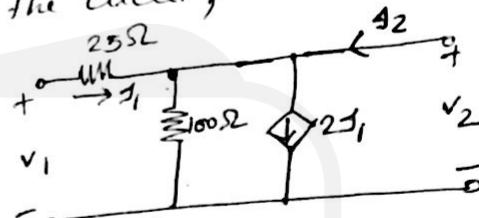

$$\Rightarrow -j_1 + j_2 = \frac{v_2}{100} \quad (i)$$

$$j_1 = \frac{v_1 - v_2}{25}$$

$$\text{so, } j_1 = \frac{v_1}{25} - \frac{v_2}{25} \quad (ii)$$

~~$j_2 = \frac{v_2}{100}$~~

$$\text{from eqn (i)} \quad -j_1 + j_2 = \frac{v_2}{100}$$

$$-\left[\frac{v_1 - v_2}{25}\right] + j_2 = \frac{v_2}{100}$$

$$j_2 = \frac{v_2}{100} + \frac{v_1 - v_2}{25}$$

$$= \frac{v_2 + 4v_1 - 4v_2}{100}$$

$$j_2 = \frac{1}{25}v_1 - \frac{3}{100}v_2 \quad (iii)$$

Comparing eqn (ii) and eqn (iii) with

$$j_1 = Y_{11}v_1 + Y_{12}v_2$$

$$j_2 = Y_{21}v_1 + Y_{22}v_2$$

$$Y_{11} = \begin{bmatrix} \frac{1}{25} & -\frac{1}{25} \\ \frac{1}{100} & -\frac{3}{100} \end{bmatrix}$$

$$\begin{aligned}
 I_1 &= I_{1a} + I_{1b} \\
 &= (Y_{11a}V_{1a} + Y_{12}V_{2a}) + (Y_{11b}V_{1b} + Y_{12b}V_{2b}) \\
 &= (Y_{11a} + Y_{11b})V_1 + (Y_{12a} + Y_{12b})V_2 \\
 \text{Since } V_1 &= V_{1a} = V_{1b} \quad \text{and } V_2 = V_{2a} = V_{2b}
 \end{aligned}$$

and similarly;

$$\begin{aligned}
 I_2 &= I_{2a} + I_{2b} \\
 &= (Y_{21a} + Y_{21b})V_1 + (Y_{22a} + Y_{22b})V_2
 \end{aligned}$$

In matrix form;

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$Y_{11} = Y_{11a} + Y_{11b}$$

$$Y_{12} = Y_{12a} + Y_{12b}$$

$$Y_{21} = Y_{21a} + Y_{21b}$$

$$Y_{22} = Y_{22a} + Y_{22b}$$

or in matrix form;


$$[Y] = [Y_a] + [Y_b]$$

The overall y -parameter matrix for parallel connected two port network is simply the sum of y -parameter matrices of each individual two port networks connected in parallel.

→ Parallel connection is called as parallel-parallel connection since both s/p and o/p ports are parallel connected.

Cascade Connection:-

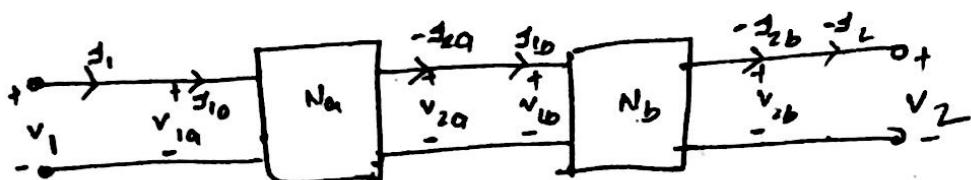Two two port n/p are said to be connected in cascade if the o/p port of the first becomes the i/p port of second.



If the T_a and T_b are T-parameters of n/p N_a and N_b;

For network N_a:

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

For network N_b:

$$\begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

Then their cascade connection requires that.

$$I_1 = I_{1a}$$

$$-I_{2a} = I_{1b}$$

$$I_{2b} = I_2$$

$$V_1 = V_{1a}$$

$$V_{2a} = V_{1b}$$

$$V_{2b} = V_2$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} V_{1b} \\ -I_{1b} \end{bmatrix}$$

So after putting the value of V_{1b} and I_{1b}

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

and $v_{2b} = v_2$ and $I_{2b} = I_2$

$$= \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$

In matrix form;

$$\begin{bmatrix} v_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} v_2 \\ -I_2 \end{bmatrix}$$

$$= \begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A_a & B_a \\ C_a & D_a \end{bmatrix} \begin{bmatrix} A_b & B_b \\ C_b & D_b \end{bmatrix}$$

In T form;

$$A = A_a A_b + B_a C_b$$

$$B = A_a B_b + B_a D_b$$

$$C = C_a A_b + D_a C_b$$

$$D = C_a B_b + D_a D_b$$

or in matrix form;

$$[T] = [T_a] \cdot [T_b]$$

The overall T -parameter matrix for cascade connected two port n/w is simply the matrix product of T -parameters in matrix of each individual two port network in cascade.

Note:- For T' parameter overall T' parameter matrix for cascade two port n/w is simply the matrix product of


T' parameter matrices for each individual two port n/w in reverse order.

$$[T] = [T'_b] [T'_a]$$

TWO port networks are said to connected in series. parallel if input ports are connected in series while o/p port are connected in parallel;

$$\begin{aligned} V_1 &= V_{1a} + V_{1b} \\ I_1 &= I_{1a} = I_{1b} \end{aligned} \quad] \rightarrow S/I/P$$
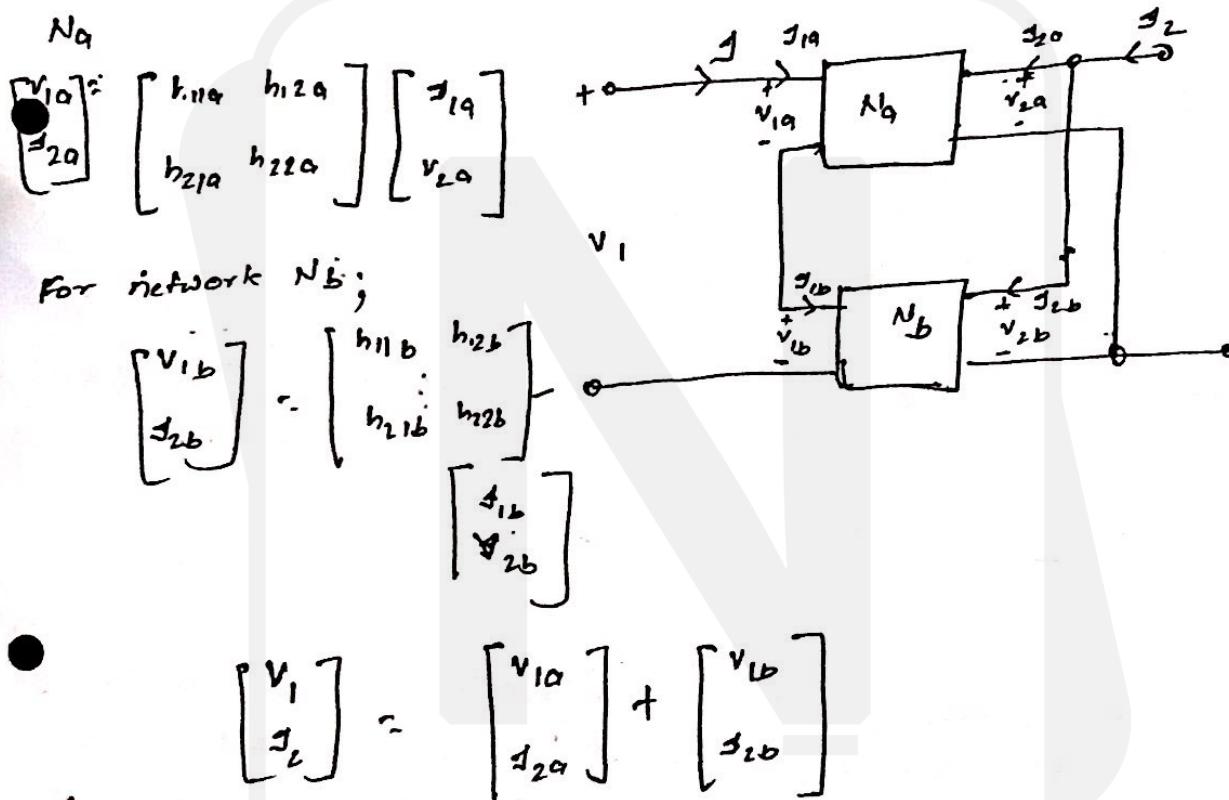
$$\begin{aligned} V_2 &= V_{2a} = V_{2b} \\ I_2 &= I_{2a} + I_{2b} \end{aligned} \quad] \rightarrow O/P$$



Relations:

$$\begin{cases} h_{11} = h_{11a} + h_{11b} \\ h_{12} = h_{12a} + h_{12b} \\ h_{21} = h_{21a} + h_{21b} \\ h_{22} = h_{22a} + h_{22b} \end{cases}$$

in matrix form;

$$[h] = [h_a] + [h_b]$$

Parallel - series connection :-
 If p ports are connected in parallel, while o/p ports are connected in series.

$$\therefore V_1 = V_{1a} = V_{1b}$$


$$I_1 = I_{1a} + I_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$\therefore \begin{cases} g_{11} = g_{1a} + g_{1b} \\ g_{21} = g_{21a} + g_{21b} \\ g_{12} = g_{12a} + g_{12b} \\ g_{22} = g_{22a} + g_{22b} \end{cases}$$

$$\text{or } [g] = [g_a] + [g_b]$$

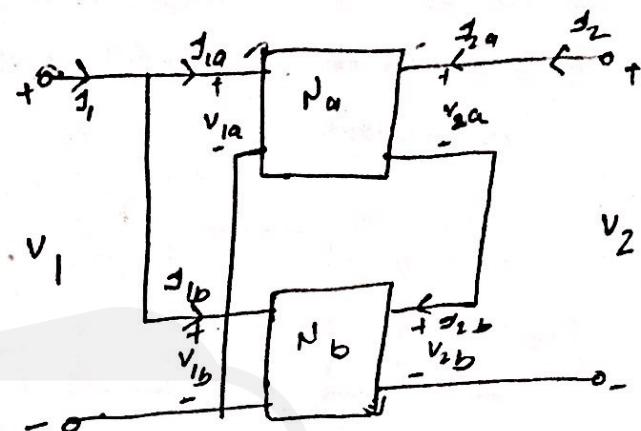


$$V_1 = N_a = V_1$$

$$= Z_1$$

$$V_2 = N_b = V_2$$

$$= Z_2$$

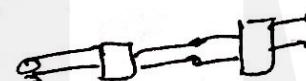

$$Z_{eq} = Z_1 + Z_2$$

$$I_1 =$$

$$V_1 \quad V_2$$

$$I_1 \quad I_2$$



$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2}$$

$$Y_{eq} = Y_1 + Y_2$$

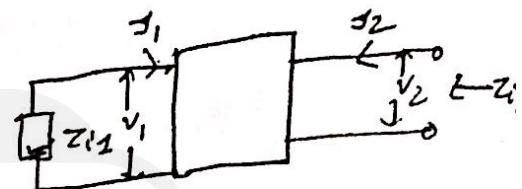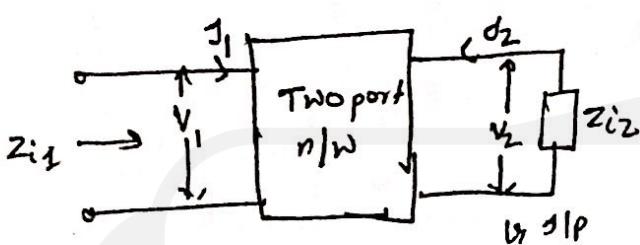- **Image Impedance :-**
In a two port n/w, if the impedance at S/p port with input z_{i2} connected across o/p port be z_{i1} and the impedance at o/p port with impedance z_{i1} connected across S/p port be z_{i2} then z_{i1} and z_{i2} are known as image impedances of the network.



- For symmetrical n/w, image impedances are equal to each other i.e. $z_{i1} = z_{i2}$ and is called characteristic or intrinsic impedance z_c ;

$$z_{i1} = \frac{V_1}{J_1} \quad (\text{driving point impedance at S/p port})$$

$$z_{i2} = \frac{V_2}{J_2} \quad (\text{driving point impedance at o/p port})$$

- \rightarrow Image impedances in terms of S/p and o/p impedances:
 $z_{i1} = z_{ip}$ and $z_{i2} = z_{op}$

\rightarrow Image impedance in term of T-parameters:

$$z_{op} : z_{i1} = z_{ip}$$

$$z_{i1} = \frac{A z_{i2} + B}{C z_{i2} + D}$$


$$z_{i2} = z_{op}$$

$$z_{i2} = \frac{D z_{i1} + B}{C z_{i1} + A}$$

$$V_1 = AV_2 + B(-I_2)$$

$$I_1 = CV_2 + D(-I_2)$$

$$\therefore V_2 = z_{i2}x - I_2$$

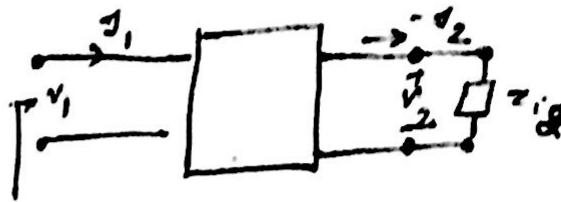

$$V_1 = A(z_{i2}x - I_2) + B(-I_2)$$

$$= -(A z_{i2} + B) I_2$$

$$I_1 = C(z_{i2}x - I_2) - D I_2$$

$$= -(C z_{i2} + D) I_2$$

$$\frac{V_1}{I_1} = \frac{A z_{i2} + B}{C z_{i2} + D}$$

$$z_{i1} = \frac{V_1}{I_1} = \frac{A z_{i2} + B}{C z_{i2} + D} \quad (A)$$

$$z_{i2} = \frac{V_2}{I_2} = \frac{D z_{i1} + B}{C z_{i1} + A} \quad (B)$$

Solving eqⁿ (A) and (B);

$$z_{i1} = \sqrt{\frac{AB}{CD}}; \text{ and } z_{i2} = \sqrt{\frac{BD}{AC}}$$

→ Derivation of voltage and current ratios as follows:-

T-parameter eqⁿ :-

$$V_1 = AV_2 - BI_2$$


$$I_1 = CV_2 - DI_2$$

$$\text{and } z_{i2} = -\frac{V_2}{I_2} \Rightarrow I_2 = -\frac{V_2}{z_{i2}}$$

Incident

Reduced Incidence matrix :-

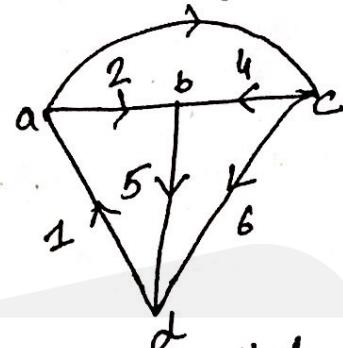If in the all incidence matrix, the information about a particular node is completely omitted i.e one of the rows is eliminated, it is called Reduced incidence matrix.




Incidence matrix :

$$A_C = \begin{matrix} & \text{Branch} \\ \text{Nodes} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} a \\ b \\ c \\ d \end{matrix} & \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 0 \\ 1 & 0 & 0 & 0 & -1 & -1 \end{bmatrix} \end{matrix}$$

If information about node 'd' is omitted, fourth row is eliminated, it results in reduced incidence matrix.

$$A_C = \begin{matrix} & \text{Branch} \\ \text{Nodes} & \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \\ \begin{matrix} a \\ b \\ c \end{matrix} & \begin{bmatrix} -1 & 1 & 1 & 0 & 0 & 0 \\ 0 & -1 & 0 & -1 & 1 & 0 \\ 0 & 0 & -1 & 1 & 0 & 1 \end{bmatrix} \end{matrix}$$

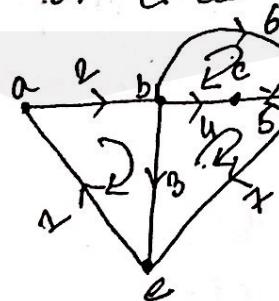loop matrix or circuit Matrix [BJ]:-

loop 1 :- [1, 2, 3]

loop 2 :- (4, 1, 5)

loop 3 :- (3, 4, 5, 7)

loop 4 :- (1, 2, 6, 7)

loop 5 :- (3, 6, 7)


loop 6 :- (1, 2, 4, 5, 7)

Incidence Matrix:- [A] Incidence matrix of a particular graph, is a matrix which gives complete information regarding the connection of various branches to the nodes and orientation of those branches towards the node.

The procedure for drawing incidence matrix is; for a graph with 'n' nodes and 'b' branches, the complete incidence matrix A_C is an $n \times b$ matrix whose elements are defined by;

$$a_{nb} = \begin{cases} +1 & \text{if branch 'b' leaves node 'n'} \\ -1 & \text{if 'b' enters 'n'} \\ 0 & \text{" " " is not incident with 'n' } \end{cases}$$

For ex:-

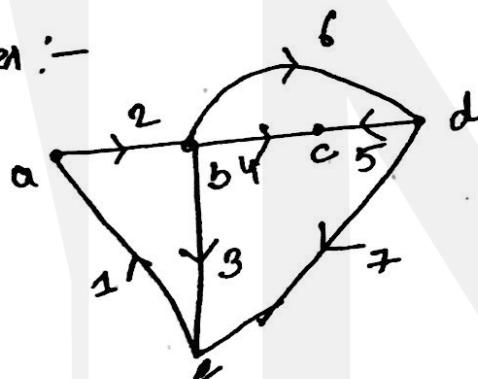

$A_C =$


Nodes/Branch	1	2	3	4	5	6	7
a	-1	1	0	0	0	0	0
b	0	-1	1	1	0	1	0
c	0	0	0	-1	-1	0	0
d	0	0	0	0	1	-1	1
e	1	0	-1	0	0	0	-1

Properties of Complete Incidence Matrix:-


- The sum of the entries in any column is zero.
- The determinant of complete incidence matrix is always zero.
- Rank of a complete incidence matrix of a connected graph is " $n-1$ ".

→ Another feature of all incidence matrix is that the determinant of the incidence matrix of a particular loop which is called sub-matrix is always zero.

Q1

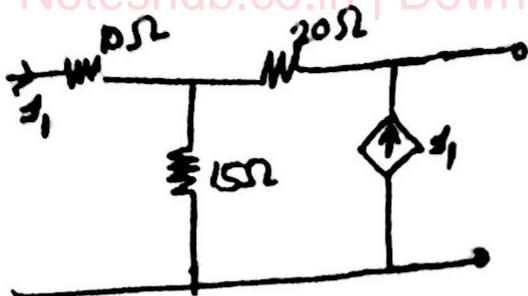

Determine the Z-parameter
of network

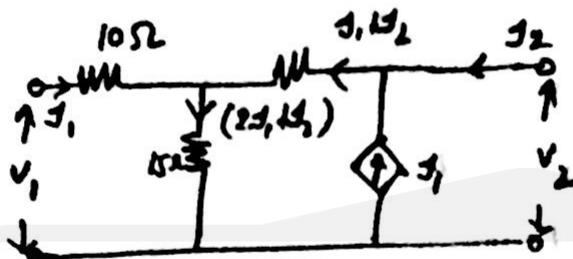

$$v_1 = 10g_1 + (2g_1 + g_2) \times 15$$

$$v_1 = 40g_1 + 15g_2 \quad \text{--- (i)}$$

$$v_2 = (20g_1 + g_2) \times 15 + 20(g_1 + g_2)$$

$$v_2 = 50g_1 + 35g_2 \quad \text{--- (ii)}$$

Now Comparing eqn (i) and (ii) we get

$$v_1 = z_{11}g_1 + z_{12}g_2$$

$$v_2 = z_{21}g_1 + z_{22}g_2$$

$$\therefore z_{11} = 40\Omega \quad z_{21} = 50\Omega$$


$$z_{12} = 15\Omega \quad z_{22} = 35\Omega$$

Q1



Calculate Z-parameter
of the n/w.

Solⁿ:

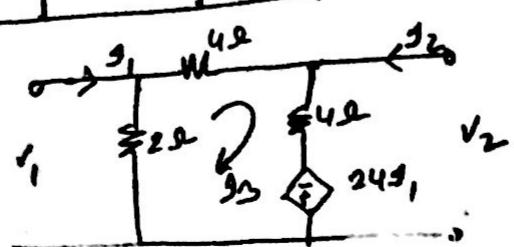

$$V_1 = 2(I_1 - I_3) \quad (D)$$

$$24I_1 = 2(I_3 - I_1) + 4I_3 + 4(I_3 + I_2)$$

$$\Rightarrow 26I_1 - 4I_2 - 10I_3 = 0 \quad (II)$$

$$V_2 = 4(I_2 + I_3) - 24I_1$$

$$V_2 = -24I_1 + 4I_2 + 4I_3 \quad (III)$$

Put the value of I_3 from eqⁿ (II) in eqⁿ (I)
and (III)

$$I_3 = \frac{26I_1 - 4I_2}{10}$$

$$\therefore V_1 = 2I_1 - 2\left(\frac{26I_1 - 4I_2}{10}\right)$$

$$V_1 = 2I_1 - 5.2I_1 + 0.8I_2$$

$$V_1 = -3.2I_1 + 0.8I_2 \quad (IV)$$

$$V_2 = -24I_1 + 4I_2 + 4I_3$$

$$= -24I_1 + 4I_2 + 4\left(\frac{26I_1 - 4I_2}{10}\right)$$

$$V_2 = -13.6I_1 + 2.4I_2 \quad (V)$$

from eqⁿ (V) and (IV) comparing with the

$$\text{eq}^n; \quad V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$


$$z_{11} = -3.2 \Omega$$

$$z_{21} = -13.6 \Omega$$

$$z_{12} = 0.8 \Omega$$


$$z_{22} = 2.4 \Omega$$

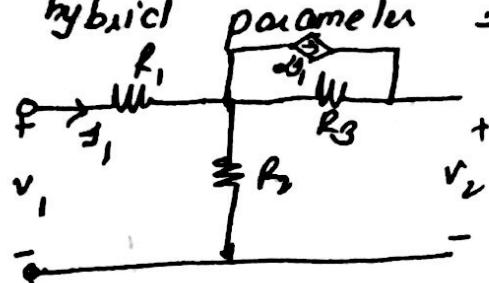Q] Find the hybrid parameter for the n/w.



$$\text{Sol :- Case 1 :- } V_2 = 0; \quad h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

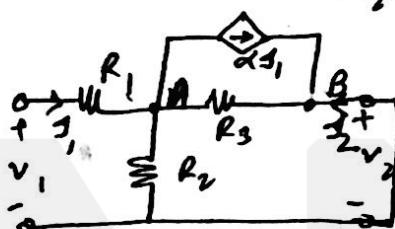

Applying KVL at node A;

At node A; 'V' potential is developed

$$\therefore I_1 = \frac{V}{R_2} + \frac{V}{R_3} + \alpha I_1$$

$$\Rightarrow V = \frac{(1-\alpha) I_1 R_2 R_3}{R_2 + R_3}$$

~~KCL~~ Applying KVL;

$$V_1 = I_1 R_1 + V$$

$$= I_1 R_1 + \frac{(1-\alpha) I_1 R_2 R_3}{R_2 + R_3}$$

$$\therefore \frac{V_1}{I_1} = R_1 \frac{(R_2 + R_3) + (1-\alpha) R_2 R_3}{R_2 + R_3}$$

$$\therefore \boxed{h_{11} = \frac{V_1}{I_1} = \frac{R_1 (R_2 + R_3) + (1-\alpha) R_2 R_3}{R_2 + R_3}}$$

KCL at node B;

$$\frac{V}{R_3} + \alpha I_1 + I_2 = 0$$

$$I_2 = -\frac{V}{R_3} + \alpha I_1$$

Putting the value of V;

$$I_2 = -\left[\frac{(1-\alpha) I_1 R_2 R_3}{R_2 + R_3} \right] - \alpha I_1$$

$$I_2 = \frac{I_1}{R_3} \left[-\frac{(1-\alpha) R_2 R_3}{R_2 + R_3} \right] - \alpha$$

~~$$\frac{I_2}{I_1} = \left[\frac{R_2 R_3 + \alpha R_2 R_3}{R_2 + R_3} \right]$$~~

$$\frac{I_2}{I_1} = \frac{-R_2 + \alpha R_2 - \alpha R_2 - \alpha R_3}{R_2 + R_3}$$

$$b_{21} = \frac{I_2}{I_1} = -\frac{(R_2 + \alpha R_3)}{R_2 + R_3}$$

On 2! $I_1 = 0$;

$$V_2 = I_2 (R_2 + R_3)$$

$$V_2 = I_2 R_2 + I_2 R_3 \quad (1)$$

$$V_1 = I_2 R_2 \quad (1')$$

$$\therefore b_{12} = \frac{V_1}{V_2} = \frac{I_2 R_2}{I_2 (R_2 + R_3)} = \frac{R_2}{R_2 + R_3}$$

$$b_{22} = \frac{I_2}{V_2} = \frac{R_2}{R_2 + R_3} \frac{I_2}{I_2 R_3 + I_2 R_2}$$

$$b_{22} = \frac{1}{R_2 + R_3}$$

Note:— No. 10. The Open circuit & short circuit Impedance
[Derivation], Input and output impedance,
and input impedance by yourself

[Page no - 301]
K.H. Soni.

→ It is necessary to convert from one set of parameters to another; for ex - all transformer problem cannot be solved by using h-parameters such as if we want to express α -parameters in terms of β -parameters we have to write β -parameters equation and then by algebraic manipulation, rewrite the eqⁿ as needed for α -parameters.

Z -parameters in term of other parameters:-

a) 'Z' in terms of 'Y'.

$$[z] = [y][v]$$

$$[v] = [z][\beta]$$

$$\text{therefore } [z] = [y]^{-1}$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1}$$

$$= \frac{1}{\Delta Y} \begin{bmatrix} y_{22} & -y_{12} \\ -y_{21} & y_{11} \end{bmatrix}$$

$$\therefore z_{11} = \frac{y_{22}}{\Delta Y} ; \quad z_{12} = \frac{-y_{12}}{\Delta Y}$$

$$z_{21} = \frac{-y_{21}}{\Delta Y} ; \quad z_{22} = \frac{y_{11}}{\Delta Y}$$

b) 'Z' in terms of T-parameters:-

$$v_1 = z_{11} i_1 + z_{12} i_2 \quad (a)$$

$$v_2 = z_{21} i_1 + z_{22} i_2 \quad (b)$$

$$\text{and } v_1 = A v_2 + B(-i_2) \quad (c)$$

$$i_1 = C v_2 + D(-i_2) \Rightarrow v_2 = \frac{1}{C} i_1 + \frac{D}{C} i_2 \quad (d)$$

on comparing (d) and (b) we will get;

$$z_{21} = \frac{1}{C} \quad \text{and} \quad z_{22} = \frac{D}{C}$$

and on putting the value of ' v_2 ' in eqⁿ (c)

$$v_1 = A\left(\frac{1}{C} i_1 + \frac{D}{C} i_2\right) + B(-i_2)$$

$$v_1 = \frac{A}{C} i_1 + \frac{AD - CB}{C} i_2 \quad (e)$$

$$Z_{11} = \frac{A}{C}, \quad Z_{12} = \frac{AD - BC}{C}$$

$$Z_{12} = \frac{\Delta T}{C}$$

Parameter
As si

Z-parameter in terms of T'-parameter:-

similarly to previous conversion;

$$Z_{11} = \frac{D'}{C'}, \quad Z_{12} = \frac{I}{C'}$$

$$Z_{21} = \frac{\Delta T'}{C'}, \quad Z_{22} = \frac{A'}{C'}$$

Z-parameter in terms of h-parameter:-

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad (a) \quad V_1 = Z_{11} I_1 + Z_{12} I_2 \quad (c)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad (b) \quad V_2 = Z_{21} I_1 + Z_{22} I_2 \quad (d)$$

$$\text{from (b); } V_2 = \frac{-h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \quad (e)$$

on comparing (d) and (e)

$$Z_{21} = \frac{-h_{21}}{h_{22}} \quad \text{and} \quad Z_{22} = \frac{1}{h_{22}}$$

and putting the value of V_2 in eqⁿ (a)

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} \left[\frac{-h_{21}}{h_{22}} I_1 + \frac{1}{h_{22}} I_2 \right] \\ &= \left(h_{11} - \frac{h_{12} h_{21}}{h_{22}} \right) I_1 + \frac{h_{12}}{h_{22}} I_2 \end{aligned} \quad (f)$$

on comparing eqⁿ (f) and (c)

$$Z_{11} = \frac{h_{11} h_{22} - h_{12} h_{21}}{h_{22}} = \frac{\Delta h}{h_{22}}$$

$$Z_{12} = \frac{h_{12}}{h_{22}}$$

parameters in terms of g -parameters:-
As similar to above case.

$$Z_{11} = \frac{1}{g_{11}} \quad Z_{12} = -\frac{g_{12}}{g_{11}}$$

$$Z_{21} = \frac{g_{21}}{g_{11}} \quad Z_{22} = \frac{Ag}{g_{11}}$$

Y -parameters in terms of other parameters:-

* In terms of Z -parameters;

$$Y_{11} = \frac{Z_{22}}{\Delta Z} \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z} \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

* In terms of T -parameters;

$$Y_{11} = \frac{D}{B} \quad Y_{12} = -\frac{AT}{B}$$

$$Y_{21} = -\frac{1}{B} \quad Y_{22} = \frac{A}{B}$$

In terms of T' parameters

$$Y_{11} = \frac{A'}{B'} \quad Y_{12} = -\frac{1}{B}$$

$$Y_{21} = -\frac{AT'}{B'} \quad Y_{22} = \frac{D'}{B'}$$

* In terms of h -parameters

$$Y_{11} = \frac{1}{h_{11}} \quad Y_{12} = -\frac{h_{12}}{h_{11}}$$

$$Y_{21} = \frac{h_{21}}{h_{11}} \quad Y_{22} = \frac{Ah}{h_{11}}$$

* In terms of g -parameters

$$Y_{11} = \frac{Ag}{g_{22}} \quad Y_{12} = \frac{g_{12}}{g_{22}}$$

$$Y_{21} = -\frac{g_{21}}{g_{22}} \quad Y_{22} = \frac{1}{g_{22}}$$

T -parameters in term of other parameters:-

* In terms of Z -parameters;

$$V_1 = AV_2 - BZ_2 \quad (i)$$

$$J_1 = CV_2 - DZ_2 \quad (ii)$$

$$V_1 = Z_{11}J_1 + Z_{12}J_2 \quad (iii)$$

$$V_2 = Z_{21}J_1 + Z_{22}J_2 \quad (iv)$$

$$\Rightarrow J_1 = \frac{1}{Z_{21}}V_2 - \frac{Z_{22}}{Z_{21}}J_2 \quad (v)$$

on comparing (i) and (iv)

$$C = \frac{1}{Z_{21}} \quad D = \frac{Z_{22}}{Z_{21}}$$

putting the value of J_1 from eqⁿ (v) to eqⁿ (ii)

$$V_1 = Z_{11} \left[\frac{1}{Z_{21}}V_2 - \frac{Z_{22}}{Z_{21}}J_2 \right] + Z_{12}J_2$$

$$V_1 = \frac{Z_{11}}{Z_{21}}V_2 + \left(Z_{12} - \frac{Z_{22}}{Z_{21}} \right) J_2$$

$$\frac{V_1 - V_2}{Z_{21}} = \frac{Z_{11} Z_{22} - Z_{12} Z_{21}}{Z_{21}} \quad \text{for the Applying v.}$$

$$A = \frac{Z_{11}}{Z_{21}} \quad \text{and} \quad B = \frac{\Delta Z}{Z_{21}}$$

* T-parameter in terms of Y-parameter;

As similar to above case;

$$A = -Y_{22} : B = -\frac{1}{Y_{21}}$$

$$C = -\frac{\Delta Y}{Y_{21}}, \quad D = -\frac{Y_{11}}{Y_{21}}$$

* T-parameter in terms of T-parameter:-

$$V_1 = AV_2 + BC(-J_2)$$

$$J_1 = CV_2 + D(-J_2)$$

$$V_2 = A'V_1 + B'(-J_1) \quad (a)$$

$$J_2 = C'V_1 + D'(-J_1) \quad (b)$$

$$J_1 = \frac{C'}{D'}V_1 - \frac{1}{D'}J_2$$

Putting the value of J_1 in eqn (b)

$$V_2 = A'V_1 - B'\left(\frac{C'}{D'}V_1 - \frac{1}{D'}J_2\right)$$

$$V_2 = \left(A' - \frac{B'C'}{D'}\right)V_1 + \frac{B'}{D'}J_2$$

$$V_2 = \left(\frac{A'D' - B'C'}{D'}\right)V_1 + \frac{B'}{D'}J_2$$

$$V_1 = \frac{D'}{A'D' - B'C'} V_2 - \frac{B'}{A'D' - B'C'} J_2$$

$$\therefore A = \frac{D'}{\Delta T'}, \quad B = \frac{B'}{\Delta T'}$$

$$\text{Similarly } C = \frac{C'}{\Delta T'}, \quad D = \frac{A'}{\Delta T'}$$

* T-parameter in terms of h-parameter:-

$$V_1 = h_{11}J_1 + h_{12}V_2 \quad (a)$$

$$J_2 = h_{21}J_1 + h_{22}V_2 \quad (b)$$

$$J_1 = -\frac{h_{22}}{h_{21}}V_2 + \left(-\frac{1}{h_{21}}\right)(-J_2)$$

$$V_1 = AV_2 - BJ_2$$

$$J_1 = CV_2 - DJ_2$$

T-parameter in terms of g-parameter; $C = -\frac{h_{22}}{h_{21}}, \quad D = -\frac{1}{h_{21}}$

$$A = \frac{1}{g_{21}}, \quad B = \frac{g_{22}}{g_{21}}$$

Putting the value of J_1 in eqn (a)

$$V_1 = h_{11} \times \left[\left(-\frac{h_{22}}{h_{21}} \right) V_2 + \left(-\frac{1}{h_{21}} \right) (-J_2) \right] + h_{12}V_2$$

$$C = \frac{g_{11}}{g_{21}}, \quad D = \frac{g_{12}}{g_{21}}$$

$$V_1 = \left(\frac{h_{11}h_{22} + h_{12}h_{21}}{h_{21}} \right) V_2 + \left(-\frac{h_{11}}{h_{21}} \right) C(-J_2)$$

$$\therefore A = -\frac{h_{11}}{h_{21}} \quad \text{and} \quad B = -\frac{h_{12}}{h_{21}}$$

For the network calculate Π , Z and Y -parameters


Applying KVL eqⁿ,

$$V_1 = 1I_1 + 3(I_1 + I_2)$$

$$V_1 = 4I_1 + 3I_2 \quad \text{--- (i)}$$

$$V_2 = 2I_2 + 3(I_1 + I_2) \quad \text{--- (ii)}$$
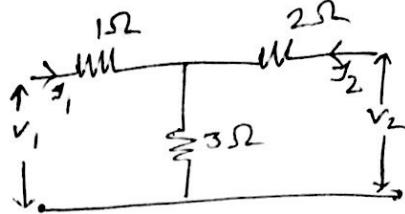
$$V_2 = 3I_1 + 5I_2 \quad \text{--- (iii)}$$



For Z -parameters;

$$\left. \begin{aligned} V_1 &= Z_{11}I_1 + Z_{12}I_2 \\ V_2 &= Z_{21}I_1 + Z_{22}I_2 \end{aligned} \right\} \quad \text{--- (iv)}$$

on comparing eqⁿ (i) and (ii) with eqⁿ (iv)

$$Z_{11} = 4\Omega, \quad Z_{12} = 3\Omega$$

$$Z_{21} = 3\Omega, \quad Z_{22} = 5\Omega$$

For Π -parameters;

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$\text{when } V_2 = 0; \quad V_1 = 4I_1 + 3I_2 \quad \text{--- (b)}$$

$$V_2 = 3I_1 + 5I_2 \quad \text{--- (c)}$$

$$\text{then } 3I_1 = -5I_2 \Rightarrow I_2 = -\frac{3}{5}I_1$$

putting the value of I_2 in eqⁿ (b)

$$V_1 = 4I_1 - 3 \times \frac{3}{5}I_1$$

$$V_1 = \left(\frac{20-9}{5} \right) I_1 \Rightarrow V_1 = \frac{11}{5}I_1$$

$$\text{and } Y_{11} = \frac{I_1}{V_1} = \frac{5}{11}\Omega$$

$$\text{and for } Y_{21} = \frac{I_2}{V_1}$$

$$\text{and } V_1 = 4I_1 + 3I_2 \quad \Rightarrow \quad V_1 = 4x - \frac{5}{3}I_2 + 3I_2$$

$$V_1 = -\frac{11}{3}I_2$$

$$\text{So, } Y_{21} = \frac{z_2}{v_1} = -\frac{3}{11} \text{ V}$$

$$\text{When } v_1 = 0; \quad v_1 = 4z_1 + 3z_2 \\ v_2 = 3z_1 + 5z_2$$

$$v_1 = 0 \Rightarrow 4z_1 = -3z_2$$

$$v_2 = 3z_1 + 5z_2$$

$$Y_{12} = \frac{z_1}{v_2}$$

so putting the value of $z_2 = -\frac{4}{3}z_1$,

$$v_2 = 3z_1 + 3 \times \frac{4}{3}z_1$$

$$v_2 = -11z_1$$

$$Y_{12} = \frac{z_1}{v_2} = -\frac{3}{11} \text{ V}$$

$$\text{and } Y_{22} = \frac{z_2}{v_2}$$

$$v_2 = 3z_1 + 5z_2$$

$$\text{and } z_1 = -\frac{3}{4}z_2$$

$$v_2 = 3 \times -\frac{3}{4}z_2 + 5z_2$$

$$v_2 = +11z_2$$



$$\text{So, } Y_{22} = \frac{z_2}{v_2} = \frac{4}{11} \text{ V}$$

$$\text{So } Z = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} 4 & 3 \\ 3 & 5 \end{bmatrix}$$

$$Y = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} = \begin{bmatrix} \frac{5}{11} & -\frac{3}{11} \\ -\frac{3}{11} & \frac{4}{11} \end{bmatrix}$$

Q) For the T-network, obtain the Z-parameters.

Soln:- on comparing the circuit

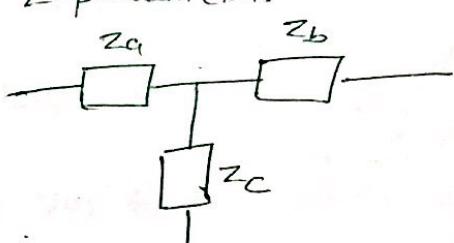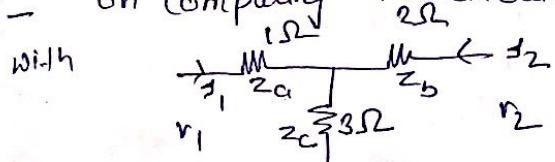

$$g_1 = Y_{11} v_1 + Y_{12} v_2$$

$$g_2 = Y_{21} v_1 + Y_{22} v_2$$

Case I :- $v_2 = 0$

$$v_1 = (g_1 + g_2) \times \frac{1}{Y_a}$$

and also,

$$v_1 = -\frac{g_2}{Y_c}$$

$$g_2 = -v_1 Y_c$$

$$\therefore v_1 = (g_1 - v_1 Y_c) \times \frac{1}{Y_a}$$

$$v_1 + v_1 Y_c = \frac{g_1}{Y_a} \Rightarrow \frac{g_1}{v_1} = Y_{11} = \left(1 + \frac{Y_c}{Y_a}\right) \times Y_a$$

$\boxed{Y_{11} = (Y_a + Y_c)}$

$$Y_{21} = \frac{g_2}{v_1} \Rightarrow -Y_c$$

Case II $v_1 = 0$

$$v_2 = \frac{1}{Y_b} (g_1 + g_2)$$

$$\text{and } v_2 = -\frac{g_1}{Y_c}$$

$$Y_{12} = \frac{g_1}{v_2} = -Y_c$$

$$Y_{22} = \frac{g_2}{v_2}$$

$$v_2 = \frac{1}{Y_b} (g_1 + g_2)$$




$$\text{and } g_1 = -v_2 Y_c$$


$$v_2 = \frac{1}{Y_b} (-v_2 Y_c + g_2)$$

$$v_2 \left(1 + \frac{Y_c}{Y_b}\right) = \frac{g_2}{Y_b}$$

$$\Rightarrow Y_b + Y_c = \frac{g_2}{v_2} = Y_{22}$$
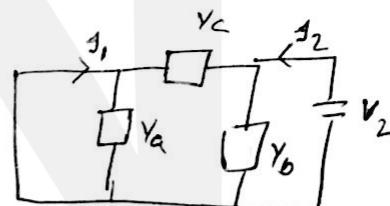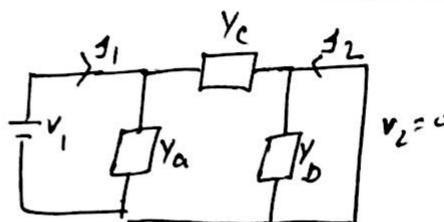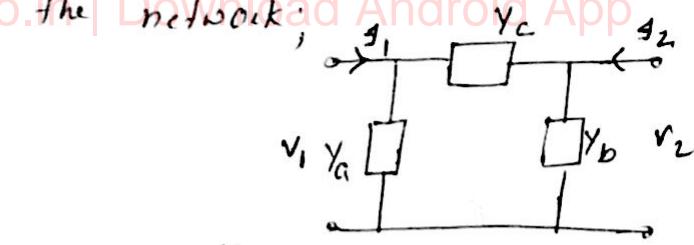
$$Y = \begin{bmatrix} Y_a + Y_c & -Y_c \\ -Y_c & Y_b + Y_c \end{bmatrix}$$



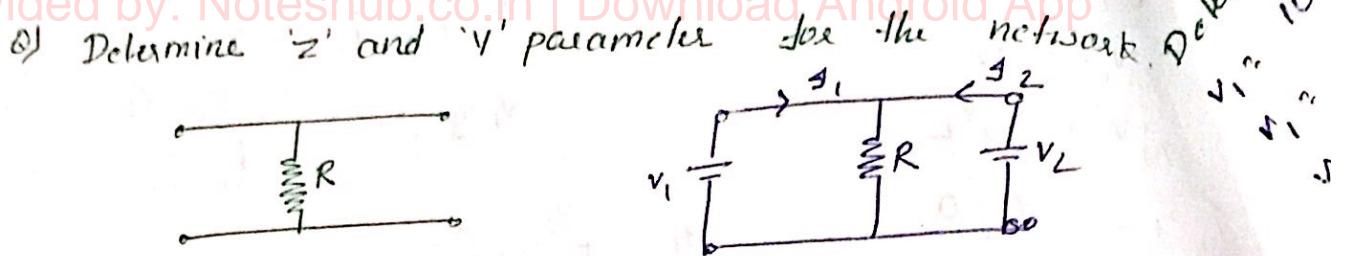

$$V_1 = R(I_1 + I_2)$$

$$V_2 = R(I_1 + I_2)$$

$$\therefore V_1 = V_2$$

For Z-parameter; $V_1 = Z_{11}I_1 + Z_{12}I_2$

$$V_2 = Z_{21}I_1 + Z_{22}I_2$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad \text{and} \quad Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0}$$

$$Z_{11} = \frac{V_1}{I_1} = R \quad Z_{21} = R$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0} \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$

$$= R \quad = R$$

$$Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} R & R \\ R & R \end{bmatrix}$$

For Y-parameter; $I_1 = Y_{11}V_1 + Y_{12}V_2$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0} \quad \text{but when } V_2 \neq 0$$

then $V_1 = V_2 = 0$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0} \quad \text{similarly for } Y_{12} \text{ and } Y_{22}$$

$$V_1 \neq 0 \quad \text{and} \quad V_2 \neq 0$$

So in this case Y-parameter don't exist.


Determine the transmission parameters of circuit (3)

$$v_1 = 10j_1 + 5(j_1 + j_2)$$

$$v_1 = 20j_1 + 5j_2 \quad (1)$$

$$v_2 = 10(j_1 + j_2) + 5(2j_1 + j_2)$$

$$v_2 = 20j_1 + 15j_2 \quad (2)$$

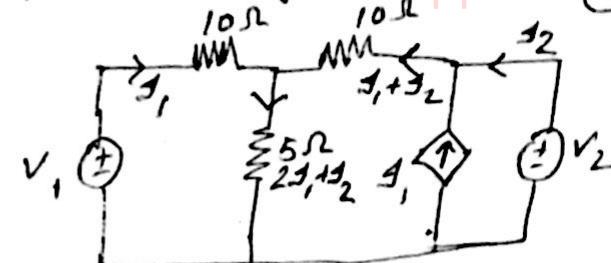

$$\text{Case 1: } j_2 = 0, \quad A = \frac{v_1}{v_2}$$

$$C = \frac{j_1}{v_2}$$

$$\begin{aligned} v_1 &= 20j_1 \\ v_2 &= 20j_1 \end{aligned} \quad \Rightarrow A = \frac{v_1}{v_2} = 1$$

$$\Rightarrow C = \frac{j_1}{v_2} = \frac{1}{20} \text{ S}$$

$$\text{Case 2: } v_2 = 0$$

$$B = \frac{v_1}{-j_2}$$

$$D = -\frac{j_1}{j_2}$$

$$v_1 = 20j_1 + 5j_2$$

$$0 = 20j_1 + 15j_2 \Rightarrow -20j_1 = 15j_2$$

$$\Rightarrow -\frac{j_1}{j_2} = \frac{15}{20} = D$$


$$\Rightarrow D = \frac{3}{4}$$

$$\text{and } A = -\frac{3}{4} j_2$$

$$v_1 = 20x - \frac{3}{4} j_2 + 5j_2$$

$$v_1 = -10j_2 \Rightarrow \frac{v_1}{j_2} = -10 = B$$

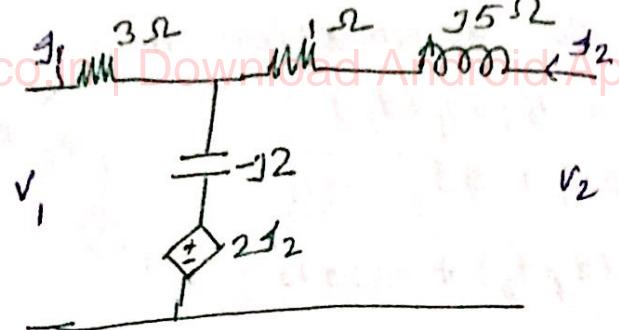Q) Calculate the z-parameter of network and show that network is neither reciprocal nor symmetrical.



$$V_1 = 3j_2 - j_2 \times (j_1 + j_2) + 2j_2$$

$$V_1 = (3-j2)j_1 + (2-j2)j_2 \quad (i)$$

$$V_2 = j5 \times j_2 + 1 \times j_2 - j2(j_1 + j_2) - 2j_2$$

$$V_2 = -j2 \times j_1 + (3+j3)j_2 \quad (ii)$$

from eqn (i) and (ii)

$$\therefore Z_{11} = (3-j2)\Omega$$

$$Z_{12} = (2-j2)\Omega$$

$$Z_{21} = -j2\Omega$$

$$Z_{22} = (3+j3)\Omega$$


For network to be reciprocal, $Z_{12} = Z_{21}$

and $Z_{12} \neq Z_{21}$ so network is not reciprocal.

For network to be symmetric, $Z_{11} = Z_{22}$.

Q1 Determine the transmission parameters of network shown in fig using concept of interconnection of two port networks N_1 and N_2 in cascade.

For N_1 network:

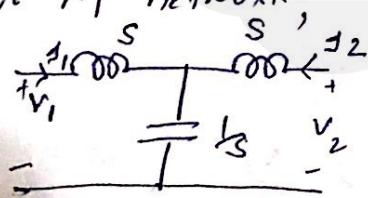


$$V_1 = Sj_1 + \frac{1}{S}(j_1 + j_2)$$

$$V_1 = (S + \frac{1}{S})j_1 + \frac{1}{S}j_2 \quad (i)$$

$$V_2 = Sj_2 + \frac{1}{S}(j_1 + j_2) \quad (ii)$$
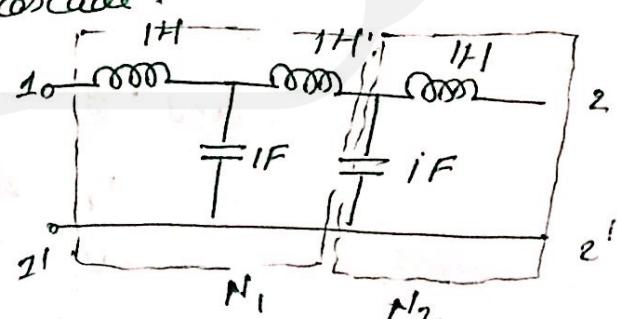
$$V_2 = \frac{1}{S}j_1 + (S + \frac{1}{S})j_2 \quad (iii)$$



$$v_1 = \left(\frac{s^2+1}{s}\right) f_1 + \frac{1}{s} f_2$$

$$\begin{aligned} v_1 &= \left(-\frac{(s^2+1)^2+1}{s}\right) f_2 \\ &\approx \left(-\frac{(s^4+1+2s^2)+1}{s}\right) f_2 \end{aligned}$$

$$v_1 \approx \left(-\frac{s^4+1+2s^2+1}{s}\right) f_2$$

$$\Rightarrow v_1 \approx -\frac{s(s^3+2s)}{s} f_2$$

$$\Rightarrow -\frac{v_1}{f_2} \approx B \approx (s^3+2s)$$

For network 1;

$$\begin{bmatrix} A_a & B_R \\ C_a & D_a \end{bmatrix} = \begin{bmatrix} 1+s^2 & 2s+s^3 \\ s & 1+s^2 \end{bmatrix}$$

For network 2;

$$v_1 = \frac{1}{s}(f_1 + f_2)$$

$$v_2 = s f_2 + (f_1 + f_2) \frac{1}{s}$$

$$v_1 = \frac{1}{s} f_1 + \frac{1}{s} f_2 \quad (1)$$

$$v_2 = \cancel{s f_2} + \left(\frac{1}{s} f_1 + (s + \frac{1}{s}) f_2 \right) \frac{1}{s} \quad (II)$$

$$\begin{bmatrix} 1 & s \\ s & 1+s^2 \end{bmatrix}$$

Case 1: $f_2 = 0$:

$$v_1 = \frac{1}{s} f_1 \quad (a) \text{ (from eqn (I))}$$

$$v_2 = \frac{1}{s} f_1 \quad (b) \text{ (from eqn (II))}$$

$$\therefore C = \frac{f_1}{v_2} = \frac{1}{s} \quad (\text{from (b)})$$

$$\text{and } A = \frac{v_1}{v_2} = 1 \quad (\text{from (a)})$$

For T-network; Case 1: $\frac{I_2}{s} = 0$

$$V_1 = \left(s + \frac{1}{s}\right) I_1 + \frac{1}{s} I_2$$

$$V_1 = \left(s + \frac{1}{s}\right) I_1 \quad \text{--- (a)}$$

$$V_2 = \frac{1}{s} I_1 \quad \text{--- (b)}$$

$$\Rightarrow \boxed{\frac{I_2}{V_2} = \frac{I_1}{s}}$$

and (a) \div (b)

$$A = \frac{V_1}{V_2} = \frac{s + \frac{1}{s}}{\frac{1}{s}} = s^2 + 1$$

Case 2:- $\frac{I_2}{s} \neq 0$

$$V_1 = \frac{1}{s} I_2 + \left(s + \frac{1}{s}\right) I_1$$

$$V_2 = \left(s + \frac{1}{s}\right) I_2 + \frac{1}{s} I_1$$

$$\Rightarrow 0 = \left(s + \frac{1}{s}\right) I_2 + \frac{1}{s} I_1$$

$$\left(s + \frac{1}{s}\right) I_2 = -\frac{1}{s} I_1$$

$$\text{and } D = \frac{-I_1}{I_2} = \frac{\cancel{I_1}}{\cancel{I_2}} = \frac{s^2 + 1}{s^2 - 1}$$

$$\text{and } B = \frac{V_1}{I_2}$$

~~$$V_1 = \frac{1}{s} I_2 + \left(\frac{s^2 + 1}{s}\right) I_1$$~~

~~$$\text{and } I_1 = -\frac{s^2 + 1}{s} I_2$$~~

~~$$V_1 = \left(\frac{s^2 + 1}{s}\right) I_2 + \frac{1}{s} I_1$$~~

~~$$\text{and } I_1 = (s^2 + 1) I_2$$~~

~~$$V_1 = \left(\frac{s^2 + 1}{s}\right) I_2 + \frac{1}{s} \times (s^2 + 1) I_2$$~~

~~$$= \frac{1}{s} I_2 - \frac{(s^2 + 1)(s^2 + 1)}{s} I_2 = \left(\frac{2s^2 + 2}{s}\right) I_2$$~~

~~$$= s^4 + 2s^2 + 1$$~~

$$V_1 = \left(s + \frac{1}{s}\right) I_1 + \frac{1}{s} I_2$$

$$\text{and } \left(s + \frac{1}{s}\right) I_2 = -\frac{1}{s} I_1$$

$$\Rightarrow -(s^2 + 1) I_2 = I_1$$

Putting the value of I_1 ; ~~$\frac{1}{s} \times (s^2 + 1) \neq \frac{1}{s} \times (s^2 + 1)$~~

(5)

$$V_1 = \frac{1}{s} I_1 + \frac{1}{s} I_2 \quad \text{--- (I)}$$

$$V_2 = \frac{1}{s} I_1 + \left(s + \frac{1}{s}\right) I_2 \quad \text{--- (II)}$$

$$0 = \frac{1}{s} I_1 + \left(s + \frac{1}{s}\right) I_2 \quad \text{--- (III)}$$

and $D = -\frac{I_1}{I_2}$

$$\Rightarrow -\frac{I_1}{I_2} = \left(\frac{s^2 + 1}{s}\right) I_2$$

$$\therefore \boxed{-\frac{I_1}{I_2} = s^2 + 1 = D}$$

and $B = -\frac{V_1}{I_2}$

$$V_1 = \frac{1}{s} I_1 + \frac{1}{s} I_2$$

and from eqn (III)

$$I_1 = -(s^2 + 1) I_2$$

$$\therefore V_1 = \frac{(s^2 + 1)}{s} I_2 + \frac{1}{s} I_2$$

$$= \underbrace{\left\{ \frac{(s^2 + 1) + 1}{s} \right\}}_{s} I_2$$

$$V_1 = -\frac{s^2}{s} I_2$$

and $B = -\frac{V_1}{I_2}$

$$= +s$$

\therefore for N/O


$$\begin{bmatrix} 1 & s \\ s & 1+s \end{bmatrix}$$

and overall T-parameter:

$$[T] = [T_1][T_2] = \begin{bmatrix} 1+s^2 & 2s+s^3 \\ s & 1+s^2 \end{bmatrix} \begin{bmatrix} 1-s & s \\ s & 1+s^2 \end{bmatrix} = \begin{bmatrix} 1+3s^2+s^4 & 3s+4s^3+s^5 \\ 2s+s^3 & 1+3s^2+s^4 \end{bmatrix}$$

Provided by NotesHub Download Android App

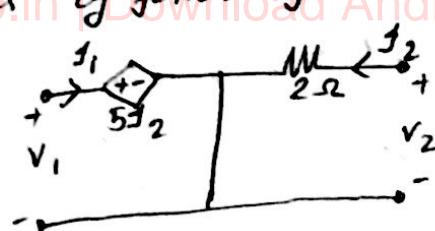Q) Find the Z-parameter of following circuit



Soln:- Applying KVL in left hand side;

$$v_1 = 5I_2 \quad (1)$$

Applying KVL in right hand side;

$$v_2 = 2I_2 \quad (2)$$

and we know;


$$v_1 = z_{11}I_1 + z_{12}I_2$$

$$v_2 = z_{21}I_1 + z_{22}I_2$$

$$\therefore z_{11} = 0, \quad z_{12} = 5\Omega$$

$$z_{21} = 0, \quad z_{22} = 2\Omega$$

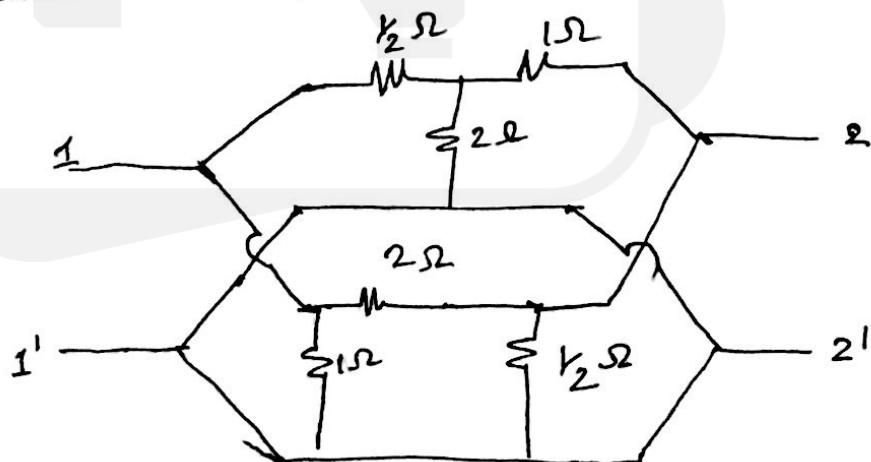Q) The n/w shown in fig. consist of resistive T' and a resistive π -n/w connected in parallel. For the element values given, determine the Y-parameter.



(6)

Provided by: Noteshub.co.in | Download Android App

For n/w A:
previous ques; (page no. 1)

$$[Z] = \begin{bmatrix} z_a + z_c & z_c \\ z_c & z_b + z_c \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{2} + 2 & 2 \\ 2 & 2+1 \end{bmatrix} = \begin{bmatrix} \frac{5}{2} & 2 \\ 2 & 3 \end{bmatrix}$$

and for Y-n/w:

$$[Y] = [Z]^{-1} = \begin{bmatrix} \frac{5}{2} & 2 \\ 2 & 3 \end{bmatrix}^{-1}$$


For inverse of Z; first transpose the given matrix

$$[Z^{-1}] = \frac{[Z]^T}{|Z|} = \frac{\begin{bmatrix} 3 & -2 \\ -2 & \frac{5}{2} \end{bmatrix}}{\frac{15}{2} - 4} = \begin{bmatrix} 3 & -2 \\ -2 & \frac{5}{2} \end{bmatrix} \times \frac{2}{7}$$

$$[Y_n] = [Z^{-1}] = \begin{bmatrix} \frac{6}{7} & -\frac{4}{7} \\ -\frac{4}{7} & \frac{10}{7} \end{bmatrix}$$

For B-n/w:

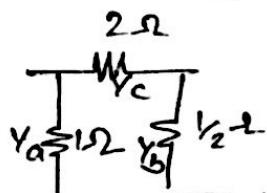In previous ques it has been found
(page no. 2)



$$[Y_B] = \begin{bmatrix} y_a + y_c & -y_c \\ -y_c & y_b + y_c \end{bmatrix}$$

$$= \begin{bmatrix} 1 + \frac{1}{2} & -2 \\ -2 & 2 + \frac{1}{2} \end{bmatrix} = \begin{bmatrix} \frac{3}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{5}{2} \end{bmatrix}$$

Network function:-

A network function exhibit the relationship between the form of source or excitation to the transform of the response for an electrical network.

②

Driving point Impedance and Admittance:-

Driving point impedance of a one port network is defined as;

$$Z(s) = \frac{V(s)}{I(s)}$$

while driving point admittance is given as;

$$Y(s) = \frac{I(s)}{V(s)}$$

⇒ For two port network, the driving point impedance and admittance at port 1 is defined as;

$$[Z_{11}(s) = \frac{V_1(s)}{I_1(s)}]$$

$$[Y_{11}(s) = \frac{I_1(s)}{V_1(s)}]$$

while driving point impedance and admittance at post 2 is defined as;

$$[Z_{22}(s) = \frac{V_2(s)}{I_2(s)}]$$

$$[Y_{22}(s) = \frac{I_2(s)}{V_2(s)}]$$

Provide by: impedance and admittance. Android App

Because
X₁₂
A₁₂

→ Transfer impedance is defined as ratio of voltage at the output port to the transformed current at the input port of two port network.

Thus;

$$[Z_{12}(s) = \frac{V_2(s)}{I_1(s)}]$$

ratio of one voltage to another current or one current to other voltage

→ Transfer admittance is defined as ratio of current transform at output to the voltage transform at input port.

Thus;

$$[Y_{12}(s) = \frac{I_2(s)}{V_1(s)}]$$

$$Y_{12} = \frac{I_2}{V_1}$$

Voltage and Current Transfer Ratio:-

voltage transfer ratio is the ratio of voltage transform at output port to the voltage transform at the input port. It is usually denoted by $G(s)$

$$[G_{12}(s) = \frac{V_2(s)}{V_1(s)}]$$

→ Current transfer ratio is the ratio of transform of current at output port to that at the input port of two port network gives the current transfer ratio and denoted by $\alpha(s)$

$$[\alpha_{12}(s) = \frac{I_2(s)}{I_1(s)}]$$

Because of similarity of impedance and admittance these two quantities are assigned as immittance.

An immittance is thus an impedance or an admittance.

Immittance function for circuit element

Elements	Impedance func ⁿ $Z(s)$	Admittance func ⁿ $Y(s)$
----------	---------------------------------------	--

$$\textcircled{1} \quad R \quad R \quad \frac{1}{R} = G_R$$

$$\textcircled{2} \quad L \quad sL \quad \frac{1}{sL}$$

$$\textcircled{3} \quad C \quad \frac{1}{sC} \quad sC$$

Concept of poles and zeros in a Network funcⁿ:-
A network funcⁿ $H(s)$ may be written as;

$$H(s) = \frac{A(s)}{B(s)} = \frac{a_0 s^n + a_1 s^{n-1} + \dots + a_{n-1} s + a_n}{b_0 s^m + b_1 s^{m-1} + \dots + b_{m-1} s + b_m}$$

where a_0, a_1, \dots, a_n and b_0, b_1, \dots, b_m are the coefficients of polynomial $A(s)$ and $B(s)$.

Factoring the numerator and denominator, the network funcⁿ can be;

$$H(s) = \frac{A(s)}{B(s)} = \frac{a_0 (s-z_1)(s-z_2) \dots (s-z_n)}{b_0 (s-p_1)(s-p_2) \dots (s-p_m)}$$

where z_1, z_2, \dots, z_n are n-roots for $A(s)=0$

p_1, p_2, \dots, p_m are m-roots for $B(s)=0$

Provided by: NotesLuv.com | Download Android App

$\frac{A_0}{B_0}$ is a constant called scale factor.

- z_1, z_2, \dots, z_n are called zeros and denoted by a "smiley" circle in the complex freq. diagram while p_1, p_2, \dots, p_m are called poles and denoted by "cross" on the plot.
- The network funcⁿ $H(s)$ becomes zero if "s" is equal to any of the zeros and become infinity when 's' is equal to any of the poles.

Note:- (1) When " $n > m$ " we have poles at infinity of multiplicity or degree $(n-m)$.

(2) When " $n < m$ " we have zeros at infinity of multiplicity or degree of $(m-n)$.

Ex:- $T(s) = \frac{(2s+4)(s+4)}{(s+2)(s^2+2s+2)}$

Poles ~~s~~ $s_1 = -2$

Pole will be

$$(s+2) = 0 \Rightarrow s = -2$$

$$(s^2+2s+2) = 0 \Rightarrow s = -1 \pm j$$

Zeros will be

$$(2s+4) = 0 \Rightarrow s = -2$$

$$(s+4) = 0 \Rightarrow s = -4$$

Poles; $s_1 = -2, s_2 = -1 + j, s_3 = -1 - j$

Zeros $s_1 = -2, s_2 = -4, s_3 = \infty$

Driving point impedance funcⁿ:-

The following list provides the listing of restrictions of location of poles and zeros in driving point impedance funcⁿ:

$$H(s) = \frac{A(s)}{B(s)}$$

- (1) Coefficient of $A(s)$ and $B(s)$ = real and positive
- (2) poles and zeros if complex must occur in conjugate pairs.
- (3) Real parts of poles and zeros must be zero or negative.
- (4) Polynomial $A(s)$ or $B(s)$ cannot have any missing term between those of highest and lowest ~~order~~ value unless all even order or all ~~even~~ odd order terms are missing
- (5) Degree of $A(s)$ and $B(s)$ may differ by zero or one only.
- (6) Lowest degree in $A(s)$ and $B(s)$ may differ in degree by at most one.

Q) check whether driving point impedance $Z(s)$ is suitable for representing a passive network.

$$Z(s) = \frac{s^4 - s^3 + 2s^2}{(s+5)} = \frac{A(s)}{B(s)} = \frac{s^2(s^2 - s + 2)}{(s+5)}$$

Solⁿ:- ① One coeff. in $A(s)$ is -ve.


$$\begin{aligned} \textcircled{2} \quad s &= -5, \\ s &= 0, -0.5 \pm \sqrt{7/4} \end{aligned}$$

- ③ degree of numerator = 4 and degree of denominator = 2
 difference of 3 exist between degree of numerator and denominator and it is not permitted.
- ④ degree in numerator is 2 and in denominator is 3rd and difference is 2 \Rightarrow not permitted.
 So given funcⁿ is not suitable for representing the driving point impedance.

\Rightarrow Necessary condition for Transfer function :-

The limitation on poles and zero location in transfer function are as follows:-


- ① Coefficient of $B(s)$ must be true and coeff. of $A(s)$ may or may not be true.
- ② poles and zeros if complex must be conjugate.
- ③ Real part of poles must be negative or zero
- ④ Polynomial $A(s)$ may have missing term between lowest and highest degree but $B(s)$ should not have any missing term b/w highest and lowest degree unless all even or odd terms are missing
- ⑤ Degree of $A(s)$ may be zero, independent of degree of $B(s)$
- ⑥ For voltage or current ratio, max^m degree of $A(s)$ must equal the degree of $B(s)$
- ⑦ For transfer impedance and admittance, the max^m degree of $A(s)$ must equal the degree of $B(s)$ plus one

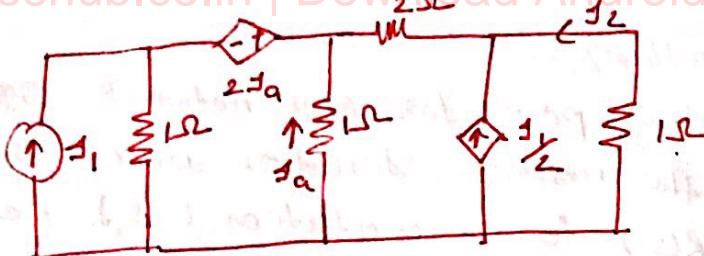

Q1 Find current ratio transfer funcⁿ (α).

Solⁿ: current ratio transfer funcⁿ

$$\alpha = \frac{I_2}{I_1}$$

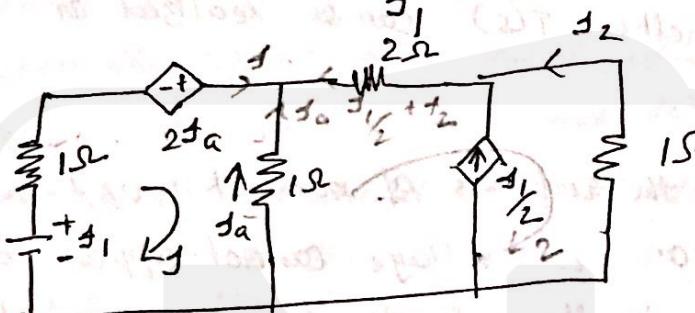

$$I_1 = I - 2I_a - I_{12}$$

$$I_1 = I - 3I_a$$

$$\text{and } I + I_{12} + I_{12} + I_2 = 0$$

$$I = -(I_a + I_{12} + I_2)$$

$$I_1 = -(I_a + I_{12} + I_2) - 3I_a$$

$$I_a = -\frac{1}{4}(3I_{12} + I_2)$$

KVL in loop 2;

$$-I_a \times 1 + 2(I_{12} + I_2) + I_2 \times 1 = 0$$

$$\Rightarrow 3I_2 + I_1 - I_a = 0$$

$$\Rightarrow 3I_2 + I_1 + \frac{1}{4}(3I_{12} + I_2) = 0$$

$$= 3I_2 + \frac{1}{4}I_2 + \frac{3}{4}I_2 + I_2 = 0$$

$$\frac{13}{8}I_2 + \frac{11}{8}I_1 = 0$$

$$\therefore I_2 = -\frac{11}{26}I_1$$

Network Synthesis:-

The starting point for any network synthesis problem is the network function which is the ratio of response $R(s)$ to the excitation $E(s)$ i.e.,

$$T(s) = \frac{R(s)}{E(s)}$$

→ The first step in a synthesis procedure is to determine whether $T(s)$ can be realized as a physical passive network.

a) Causality:- The response of network must be zero for $t < 0$ i.e. voltage cannot appear between any pair of terminal in the network before a current is impressed.

b) Stability:-

For the network to be stable, the following conditions must be satisfied:-

a) $T(s)$ cannot have poles in the right half of s-plane.

b) $T(s)$ should not have any multiple poles in the jω-axis.

c) The degree of numerator of $T(s)$ cannot exceed the degree of denominator by more than unity.

Hurwitz Polynomial:-

The denominator polynomial $p(s)$ of the system function is termed as Hurwitz polynomial.

~~Roots of polynomial~~ P(s) is real when s is real

- (1) The roots of P(s) have real parts which are to be zero or negative.

Properties of Hurwitz Polynomial:-

$$P(s) = a_n s^n + a_{n-1} s^{n-1} + \dots + a_1 s + a_0$$

- (2) All coeff. 'a_i' must be positive.
 Between the highest and lowest order term, none of coefficients may be zero. [unless the polynomial is even or odd). [Should not be missing terms in 's']
- (3) $P(s) = H(s) + N(s)$

where $H(s)$ = even part of $P(s)$

$N(s)$ = odd part of $P(s)$

Both $H(s)$ and $N(s)$ should have roots on jw-axis only.

- (4) If $P(s)$ is either even or odd, all its roots are on the jw-axis including origin.

- (5) The continued fraction expansion of ratio of odd to even part or even to odd part of Hurwitz polynomial yield all positive quotient terms.

$$\psi(s) \sim \frac{N(s)}{M(s)} \text{ or } \frac{H(s)}{N(s)}$$

$$\sim q_1 s + \frac{1}{q_2 s + \frac{1}{q_3 s + \frac{1}{\dots}}} + \frac{1}{q_n s}$$

(6) In case if polynomial is either even or only odd it is not possible to obtain continued fraction expansion. In such cases, the polynomial $P(s)$ is Hurwitz if ratio of $P(s)$ and its derivative $P'(s)$ gives a continued fraction expansion.

Conditions to check polynomial is Hurwitz or not:-

i) All coeff. of polynomial should be +ve, no missing terms except all even or odd.

(ii) $P(s) = M(s) + N(s)$

All continued fraction of $M(s)$ or $N(s)$ should be +ve.

Q) $P(s) = s^4 + s^3 + 2s^2 + 3s + 2$

check whether Hurwitz or not.

i) $P(s) = s^4 + s^3 + 2s^2 + 3s + 2$

All coeff are +ve, no missing term.

ii) Even part $M(s) = s^4 + 2s^2 + 2$

Odd part $N(s) = s^3 + 3s$

so, $\frac{M(s)}{N(s)} = \frac{s^4 + 2s^2 + 2}{s^3 + 3s}$

Non continued fraction of $\frac{M(s)}{N(s)}$

A

②

Only odd order expansion

$$\frac{H(s)}{N(s)} = \frac{s^4 + 2s^2 + 2}{s^3 + 3s}$$

$$\begin{array}{r} s^3 + 3s \\) s^4 + 2s^2 + 2 \\ s^4 + 3s^2 \\ \hline -s^2 + 2 \\) s^3 + 3s \\ s^3 - 2s \\ \hline - + \\ 5s) -s^2 + 2 \\ -s^2 \\ \hline + \\ 2 \end{array} \quad \left(\begin{array}{l} s \\ -s \\ \hline s/5 \end{array} \right)$$

Quotient of continued fraction is negative.
so it is not Hurwitz polynomial.

Note:- ① For pure even Hurwitz polynomial means all roots are on JN axis

② For pure odd Hurwitz polynomial means all roots are on JN-axis including origin.

(Q) $P(s) = s^6 + 6s^4 + 11s^2 + 6$ check Hurwitz or not.

$$P(s) = s^6 + 6s^4 + 11s^2 + 6$$

- ① All coeff. are +ve and pure even.
- ② so continued fraction; $\frac{P(s)}{P'(s)}$

All
Huntwiz

$$\frac{P(s)}{P'(s)} = \frac{s^6 + 6s^4 + 11s^2 + 6}{6s^5 + 24s^3 + 22s}$$

$$\begin{array}{r} 6s^5 + 24s^3 + 22s \\) s^6 + 6s^4 + 11s^2 + 6 \\ - - - \\ s^6 + 4s^4 + 11s^2 \end{array} \quad \left(\frac{s}{6} \right)$$

$$\begin{array}{r} 2s^4 + 22s^2 + 6 \\) 6s^5 + 24s^3 + 22s \\ - - - \\ 6s^5 + 22s^3 + 16s \end{array} \quad \left(\frac{3s}{2} \right)$$

$$\begin{array}{r} 2s^3 + 4s \\) 2s^4 + 22s^2 + 6 \\ - - - \\ 2s^4 + 4s^2 \end{array} \quad \left(3 \right)$$

$$\begin{array}{r} 10s^2 + 6 \\) 2s^4 + 22s^2 + 6 \\ - - - \\ 2s^4 + 18s^2 \end{array} \quad \left(+ \right)$$

$$\begin{array}{r} 10s^2 + 6 \\) 2s^4 + 4s \\ - - - \\ 2s^4 + 18s^2 \end{array} \quad \left(\frac{3s}{5} \right)$$

$$\begin{array}{r} 2s \\) \frac{10s^2 + 6}{3} \\ - - - \\ \frac{10s^2 + 6}{3} \end{array} \quad \left(\frac{2s}{3} \right) \quad \cancel{\times}$$

All quotient of $\frac{P(s)}{P'(s)}$ is +ve. So it is huntwiz.

Hurwitz or not.

① All coeff. are +ve and no missing b/w them.

$$\text{② } H(s) = s^4 + 3s^2 + 2$$

$$N(s) = s^3 + 2s$$

$$\frac{H(s)}{N(s)} = \frac{s^4 + 3s^2 + 2}{s^3 + 2s}$$

$$\begin{array}{r} s^3 + 2s \\ \overline{s^4 + 3s^2 + 2} \\ - - \\ s^2 + 2 \end{array} \left| \begin{array}{l} s^4 + 3s^2 + 2 \\ s^4 + 2s^2 \\ \hline s^2 + 2s \end{array} \right| \begin{array}{l} s \\ s \\ \hline s \end{array}$$

It is said premature termination.

Note:- In Premature Termination there are roots on jw-axis given by last divisor.

$$\text{if } N(s) = s^2 + 2$$

$$N'(s) = 2s$$

$N(s)$ = quotient should be positive
 $N'(s)$ = then polynomial will be Hurwitz.

$$2s \left| \begin{array}{l} s^2 + 2 \\ s^2 \end{array} \right| \begin{array}{l} (s_1) \\ (s_2) \end{array}$$

$$\overline{x^2} \left| \begin{array}{l} 2s \\ 2s \end{array} \right| \begin{array}{l} (s) \\ (s) \end{array}$$

quotient of $\frac{N(s)}{N'(s)}$ is positive so it is Hurwitz

Driving point impedance funcⁿ $Z(s)$ as well as driving admittance $Y(s)$ of one port network can be represented in the form of :

$$F(s) = \frac{A(s)}{B(s)}$$

PRF represent physically realizable and stable passive driving point impedance function

$$= \frac{a_0 s^n + a_1 s^{n-1} + \dots + a_{n-1} s + a_n}{b_0 s^m + b_1 s^{m-1} + \dots + b_{m-1} s + b_m}$$

The function $F(s)$ is called a positive Real function if

- a) $F(s)$ is real for 's' real
- b) $B(s)$ is Hurwitz polynomial
- c) If $F(s)$ has poles on jw-axis, the poles are simple and residues therefore are real and true.
- d) Real $F(jw) \geq 0$ for all values of w.

Procedure for testing PRF:-

① $F(s) = \frac{A(s)}{B(s)}$ if PRF if

- ① $F(s)$ is real for 's' real

- ② $B(s)$ is Hurwitz polynomial and $T(s)$ have no poles on right half of s-plane.

- ③ If $T(s)$ have poles on jw-axis then poles are simple and residues there are of real and positive.

④ $F(s) = \frac{A(s)}{B(s)} = \frac{H_1 + N_1}{H_2 + N_2}$

N_1, N_2 = odd part of $F(s)$

determine $M_1, M_2 - N_1, N_2$ and put $s = j\omega$ and it
 $A(\omega^2) \geq 0$ for all ω $0 \leq \omega < \infty$. so it is

PRF.

Q) $H(s) = \frac{s^2 + 10s + 4}{s + 2}$ check PRF or not.

$$H(s) = \frac{s^2 + 10s + 4}{s + 2}$$

$$N(s) = s^2 + 10s + 4$$

$$D(s) = s + 2$$

$$= s = -2$$

(1) $D(s)$ is having 3 polynomial(2) No poles on $j\omega$ axis.

(3) $H(s) = \frac{N(s)}{D(s)} = \frac{s^2 + 10s + 4}{s + 2} = \frac{M_1 + N_1}{M_2 + N_2}$

even part $\begin{bmatrix} M_1(s) = s^2 + 4 \\ M_2(s) = s + 2 \end{bmatrix}$ odd part $\begin{bmatrix} N_1(s) = 10s \\ N_2(s) = s \end{bmatrix}$

$$M_1 M_2 - N_1 N_2 = (s^2 + 4) \times 2 - 10s \times s \\ = -8s^2 + 8$$

put $s = j\omega$
 $= -8(j\omega)^2 + 8$

$$A(\omega^2) = 8\omega^2 + 8 > 0 \text{ for every value of } \omega.$$

so it is PRF

$$s(s^2 + 1)$$

$$\textcircled{I} \quad D(s) = s(s^2 + 1)$$

$$s=0, \pm J \Rightarrow \text{Hurwitz}$$

\textcircled{II} Poles on jn-axis $s = \pm J$

so residue on these poles;

$$H(s) = \frac{2s^2 + 5}{s(s^2 + 1)} = \frac{2s^2 + 5}{s^3 + s}$$

$$= \frac{2s^2 + 5}{s(s-J)(s+J)}$$

$$= \frac{A}{s} + \frac{B}{s-J} + \frac{C}{s+J}$$

Residue of $H(s)$ at a pole $s = J$

$$\frac{2s^2 + 5}{s(s-J)(s+J)} = \frac{A}{s} + \frac{B}{s-J} + \frac{C}{s+J}$$

$$\text{Res } [f(s), J] = \lim_{s \rightarrow J} (s-J) \times F(s)$$

$$= \lim_{s \rightarrow J} (s-J) \times \frac{2s^2 + 5}{s(s-J)(s+J)}$$

$$= \frac{2(J)^2 + 5}{J(J+J)} = -\frac{2+5}{J \times 2J}$$

$$= \frac{3}{2J^2} = \frac{-3}{2}$$

Residue of $H(s)$ at a pole $s = -J$

$$\text{Res } [f(s), -J] = \lim_{s \rightarrow -J} (s+J) \times \frac{2s^2 + 5}{s(s-J)(s+J)}$$

$$= \frac{2(-J)^2 + 5}{-J \times -2J} = \frac{-3}{2}$$

so it is not PTF.

$$H(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

(I) For D(s) to Hurwitz;

$$s^3 + 2s^2 + s + 2 = D(s)$$

$$H(s) = \frac{s^3 + s^2 + s + 2}{2s^2 + 2}$$

$$N(s) = s^3 + s$$

$$\frac{N(s)}{M(s)} = \frac{s^3 + s}{2s^2 + 2}$$

$$\begin{array}{r} 2s^2 + 2 \\ \overline{) s^3 + s} \end{array} \quad \left(\frac{s}{2} \right) \quad \text{X premature termination}$$

$$\therefore w(s) = 2s^2 + 2$$

$$w'(s) = 4s$$

$$\frac{w(s)}{w'(s)} = \frac{2s^2 + 2}{4s}$$

$$\begin{array}{r} 4s \\ \overline{) 2s^2 + 2} \end{array} \quad \left(\frac{s}{2} \right)$$

$$\begin{array}{r} 2 \\ \overline{) 4s} \end{array} \quad (2s)$$

$$\overline{\quad X \quad}$$

Quotient is +ve so it is Hurwitz

(II) For poles; $s^3 + 2s^2 + s + 2 = (s^2 + 1)(s + 2)$

$$s = \pm j, -2$$

Poles are on jw axis;

Therefore residue at $s = J$:

$$F(s) \text{ at } s = J = \frac{(s-J) \times 2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

$$= (s-J) \times \frac{2s^2 + 2s + 1}{(s^2 + 1)(s + 2)}$$

$$= (s-J) \frac{2s^2 + 2s + 1}{(s+J)(s+1)(s+2)}$$

$$= \frac{2(J)^2 + 2J + 1}{(J+J)(J+2)}$$

$$= \frac{-2 + 2J + 1}{2J \times (J+2)}$$

$$= \frac{2J - 1}{2J^2 + 4J} = \frac{2J - 1}{-1 + 2}$$

$$= \frac{2J - 1}{-2 + 4J} = \frac{2J - 1}{2(2J - 1)}$$

$$= \frac{1}{2}$$

at $s = -J$

Residue will be:

$$F(s) \text{ at } s = -J = (s+J) \times \frac{2s^2 + 2s + 1}{(s+J)(s+J)(s+2)}$$

$$= \frac{2(-J)^2 + 2(-J) + 1}{(-J-J)(-J+2)}$$

$$\begin{aligned} &= \frac{-2 - 2J}{-2 - 2J} = \frac{2 \times -1 - 2J + 1}{-2J(-J+2)} \\ &= \frac{-1 - 2J}{-2J} = \frac{-1 - 2J}{2J^2 - 4J} = \frac{\cancel{-1}}{\cancel{2J}} \end{aligned}$$

$$\frac{-1 - 2j}{-2 - 4j}$$

$$= \frac{j(1 + 2j)}{j^2 + 2(1 + 2j)} = \frac{1}{2}$$

So residues are real and P.R.C.

$$(11) \quad F(s) = \frac{2s^2 + 2s + 1}{s^3 + 2s^2 + s + 2}$$

$$H_1(s) = 2s^2 + 1 \quad N_1(s) = 2s$$

$$H_2(s) = 2s^2 + 2 \quad N_2(s) = s^3 + s$$

$$A(\omega^2) = H_1 H_2 - N_1 N_2 \geq 0$$

$$= (2s^2 + 1)(2s^2 + 2) - 2s(s^3 + s)$$

$$= 4s^4 + 6s^2 + 2 - 2s^4 - 2s^2$$

$$= 2s^4 + 4s^2 + 2$$

$$\text{Put } \omega = j\omega = 2(j\omega)^2 + 4(j\omega)^2 + 2$$

$$= 2j^4\omega^4 + 4j^2\omega^2 + 2$$

$$= 2\omega^4 - 4\omega^2 + 2$$

$$= 2(\omega^4 - 2\omega^2 + 1)$$

$$= 2(\omega^2 - 1)^2 \geq 0 \text{ for all } \omega.$$

$\begin{matrix} z^2 - x \\ z^2 - 2z + 1 \\ (z-1)^2 \end{matrix}$

Therefore $F(s)$ is always P.R.F.

Properties of Positive Real funcⁿ:-

① $T(s)$ is P.R.F then $\frac{1}{T(s)}$ is also P.R.F. If $Z(s)$ is

P.R.F then $\frac{1}{Z(s)} = Y(s)$ is also P.R.F

② ~~is too important~~

③ sum of P.R.F function is also P.R.F i.e. sum of two

impedance connected in series or two admittances in parallel, resultant admittance or impedance PRF.

Synthesis of Network:-

For the synthesis of one port network with two kind of element either LC, RL or RC network has to choose.

→ There are a number of methods of synthesizing (or realizing) a one port network:-

- (I) Foster - I form] \Rightarrow by partial fraction
- (II) Foster - II Form
- (III) Cauer - I form] \Rightarrow by continued fraction.
- (IV) Cauer - II form.

① LC Impedance Function:-

Properties:-

- ① $Z(s) = \frac{\text{even}}{\text{odd}}$ or $\frac{\text{odd}}{\text{even}}$
- ② All the poles and zeros of $Z(s)$ are on JN- axis including origin
- ③ Poles and zeros are intertwined so residues alternate.

② RC impedance (Z_{RC}) or RL admittance (Y_{RL}) function:

Properties:-

- ① All poles and zeros are on real axis including origin and intertwined with first singularity is pole

Provider by: Notchuck on YRC(s) and +ve App

RL impedance (Z_{RL}) or RC admittance (Y_{RC}) function:

Properties:-

- ① All the poles and zeros are on -ve real axis including origin and included with first singularity is zero.
- ② Residue of $\frac{Y_{RC}}{s}$ or $\frac{Z_{RL}}{s}$ are positive.

Fogku-1 form:-

$$Z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$$

- ① First check whether LC or RL or RC immittance using properties.
- ② This one is LC immittance function.
- ③ Second step is to do partial fraction of $Z(s)$.

$$Z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$$

or;

$$\frac{Z(s)}{s} = \frac{s^2+4}{2(s^2+1)(s^2+9)}$$

$$\text{let } s^2 = x$$

$$\frac{Z(s)}{s} = \frac{(x+4)}{2(x+1)(x+9)}$$

$$\frac{Z(s)}{s} = \frac{1}{2} \left[\frac{(x+4)}{(x+1)(x+9)} \right]$$

$$50, \frac{x+4}{(x+1)(x+9)} = \frac{A}{x+1} + \frac{B}{x+9}$$

$$x+4 = A(x+9) + B(x+1)$$

$$A + B = 1$$

$$9A + B = 4$$

$$\begin{array}{r} - \\ - \\ \hline -8A = -3 \end{array}$$

$$A = \frac{3}{8}; B = 1 - \frac{3}{8} = \frac{5}{8}$$

$$\therefore \frac{x+4}{(x+9)(x+1)} = \frac{3}{8(x+1)} + \frac{5}{8(x+9)}$$

Therefore final eqn will be:

$$Z(s) = \frac{1}{2} \left[\frac{3}{8(s+1)} + \frac{5}{8(s+9)} \right]$$

$$\text{and } x = s^2$$

$$Z(s) = \frac{1}{2} \times s \left[\frac{3}{8(s^2+1)} + \frac{5}{8(s^2+9)} \right]$$

or

$$Z(s) = \frac{3s}{16(s^2+1)} + \frac{5s}{16(s^2+9)}$$

$$Z(s) = \frac{3s}{16s^2+16} + \frac{5s}{16s^2+144}$$

$$\Rightarrow Z(s) = \frac{1}{\left(\frac{16s^2}{3s} + \frac{16}{3s}\right)} + \frac{1}{\left(\frac{16s^2}{5s} + \frac{144}{5s}\right)}$$

$$\Rightarrow Z(s) = \frac{1}{\left(\frac{16s}{3s} + \frac{16}{3s}\right)} + \frac{1}{\left(\frac{16s}{5} + \frac{144}{5s}\right)}$$

$$(CS) = \left[\frac{1}{\left(\frac{16}{3}\right)s + \frac{1}{\left(\frac{3}{16}\right)s}} \right] + \left[\frac{1}{\left(\frac{16}{5}\right)s + \frac{1}{\left(\frac{5}{144}\right)s}} \right]$$

\Downarrow
 z_1 z_2

$$z_1 = \frac{1}{y_1}$$

$$z_2 = \frac{1}{y_2}$$

$$y_1 = \left(\frac{16}{3}\right)s + \frac{1}{\left(\frac{3}{16}\right)s}$$

$$y_2 = \left(\frac{16}{5}\right)s + \frac{1}{\left(\frac{5}{144}\right)s}$$

$$\boxed{z_L = sL \quad \text{or} \quad y_L = \frac{1}{sL}}$$

$$\quad \quad \quad \quad \quad \quad \boxed{z_C = \frac{1}{sC} \quad \text{or} \quad y_C = sC}$$

$$\Rightarrow y_1 = \frac{16}{3}s + \frac{1}{\left(\frac{3}{16}\right)s}$$

$$= y_{11} + y_{12}$$

$$y_{11} = \frac{16}{3}s \Rightarrow C = \frac{16}{3}F$$

$$y_{12} = \frac{1}{\left(\frac{3}{16}\right)s} \Rightarrow L = \frac{3}{16}H$$

$$y_2 = \frac{16}{5}s + \frac{1}{\left(\frac{5}{144}\right)s}$$


$$= y_{21} + y_{22}$$

$$\text{so, } y_{21} = \frac{16}{5}s \Rightarrow C = \frac{16}{5}F$$

$$\gamma_{22} = \frac{1}{\left(\frac{5}{144}\right)s}$$

So, $L = \frac{5}{144} H$

Therefore; Network;

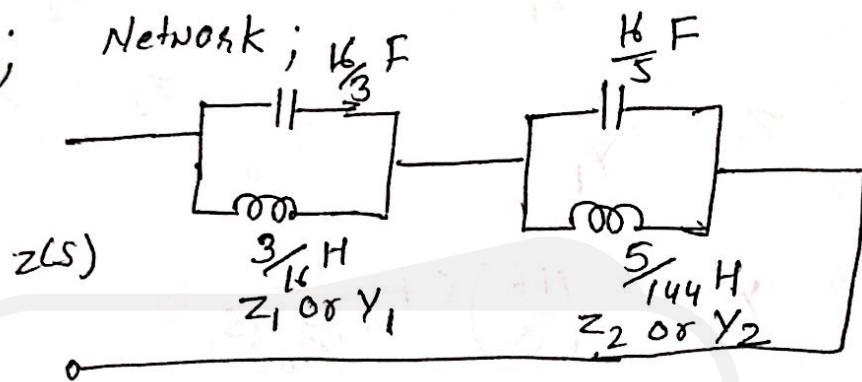

Note; Z_1 and Z_2 will be in series
 Y_1 and Y_2 will be in parallel.

For II form:-

$$z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$$

$$y(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+4)}$$

$$\Rightarrow \frac{y(s)}{s} = 2 \left[\frac{(s^2+1)(s^2+9)}{s^2(s^2+4)} \right]$$

$$\det s^2 = \infty$$

$$\Rightarrow \frac{y(s)}{s} = 2 \left[\frac{(s^2+1)(s^2+9)}{s^2(s^2+4)} \right]$$

$$Y(s) = \frac{(x+1)(x+9)}{x(x+4)}$$

$$\frac{(x+1)(x+9)}{x(x+4)} = \frac{x^2 + 10x + 9}{x^2 + 4x}$$

$$\begin{aligned} & x^2 + 4x) x^2 + 10x + 9 \\ & \quad - \frac{x^2 + 4x}{6x + 9} \end{aligned}$$

$$\Rightarrow \frac{(x+1)(x+9)}{x(x+4)} = 1 + \frac{6x+9}{x^2 + 4x}$$

$$\frac{6x+9}{x(x+4)} = \frac{A}{x} + \frac{B}{x+4}$$

$$A = \frac{9}{4}, B = \frac{15}{4}$$

$$\therefore \frac{(x+1)(x+9)}{x(x+4)} = 1 + \frac{9}{4x} + \frac{15}{4(x+4)}$$

$$\frac{Y(s)}{s} = 2 \left[1 + \frac{9}{4x} + \frac{15}{4(x+4)} \right]$$

$$Y(s) = 2s + \frac{9s}{4x} + \frac{15s}{4(x+4)}$$

$$x = s^2$$

$$Y(s) = 2s + \frac{9s}{4s^2} + \frac{15s}{24(s^2+4)}$$

$$Y(s) = 2s + \frac{9}{2s} + \frac{15s}{2(s^2+4)}$$

$$Y(s) = 2s + \frac{9}{2s} + \frac{1}{(\frac{2}{15})s + \frac{8}{15s}}$$

$$Y(s) = \left[\frac{2s}{1} \right] + \left[\frac{1}{\frac{2}{9}s} \right] + \left[\frac{1}{\frac{2}{15}s + \frac{1}{(\frac{15}{8})s}} \right]$$

$\downarrow \quad \downarrow \quad \downarrow$
 $y_1 \quad y_2 \quad y_3$

$$Y = CS$$

$$Y = \frac{1}{LS}$$

$$y_1 = CS = 2s$$

$$C = 2F$$


$$y_2 = \frac{1}{\left(\frac{2}{9}\right)s} \Rightarrow L = \frac{2}{9} H$$


$$y_3 = \frac{1}{\frac{2}{15}s + \frac{1}{(\frac{15}{8})s}}$$

$$y_3 = \frac{1}{z_{31} + z_{32}}$$

$$z_{31} = \frac{2}{15}s \Rightarrow C = \frac{2}{15} F$$
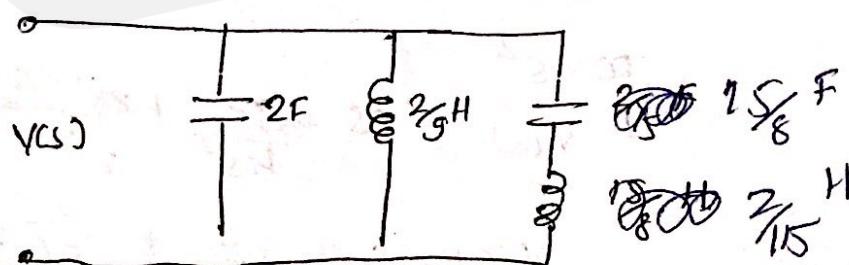
$$z_{32} = \frac{1}{(\frac{15}{8})s} \Rightarrow C = \frac{15}{8} F$$



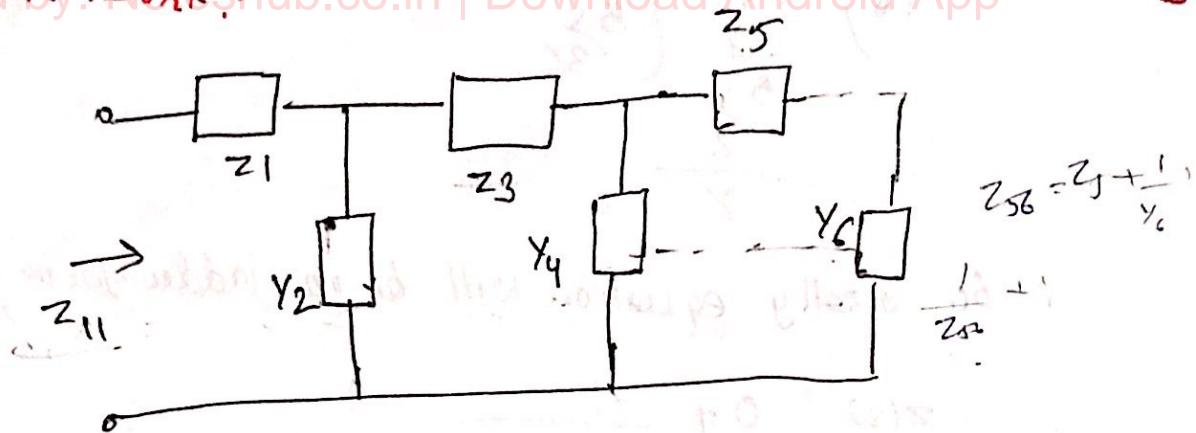

$$z = z_1 + \frac{1}{y_2 + \frac{1}{z_3 + \frac{1}{y_4 + \frac{1}{z_5 + \frac{1}{y_6 + \dots}}}}}$$

This equation is known as continued fraction.

It may be simplified to determine z' for a given ladder network.

Case 1-form: Continued fraction of $z(s)$

1st type Question:-

$$z(s) = \frac{s(s^2+4)}{2(s^2+1)(s^2+9)}$$

$$= \frac{s^3+4s}{2s^4+2s^2+18}$$

$$\text{so, } z(s) = \frac{1}{\frac{2s^4+2s^2+18}{s^3+4s}}$$

Note:- this eqn is in the form of $\frac{1}{\frac{2s^4+2s^2+18}{s^3+4s}}$

therefore $z_1 = 0$ as

$$z(s) = z_1 + \frac{1}{y_2}$$

$$= 0 + \frac{1}{2s + \frac{s^3+4s}{12s^2+18}}$$

$$= \frac{1}{2s + \frac{s^3+4s}{12s^2+18}}$$

$$= \frac{1}{2s + \frac{s^3+4s}{12s^2+18}} = \frac{1}{2s + \frac{s^3+4s}{12s^2+18}} = \frac{1}{2s + \frac{s^3+4s}{12s^2+18}}$$

$$= \frac{1}{2s + \frac{s^3+4s}{12s^2+18}} = \frac{1}{2s + \frac{s^3+4s}{12s^2+18}} = \frac{1}{2s + \frac{s^3+4s}{12s^2+18}}$$

$$\begin{array}{r} 18) \quad 5\frac{s}{2} \\ \quad \quad \quad \left(\frac{5s}{36} \right) \\ \quad \quad \quad \frac{5s}{2} \\ \hline \quad \quad \quad x \end{array}$$

so finally equation will be in ladder form;

$$z(s) = 0 + \frac{1}{2s + \frac{1}{\frac{s_{12}}{y_2} + \frac{1}{\frac{24}{5}s + \frac{1}{\left(\frac{5s}{36}\right)}}}}$$

$\downarrow \quad \downarrow \quad \downarrow \quad \downarrow \quad \downarrow$

$z_1 \quad y_2 \quad z_3 \quad y_4 \quad z_5$

$$z_1 = 0$$


$$y_2 = 2s \Rightarrow C = 2F$$

$$z_3 = \frac{s_{12}}{y_2} \Rightarrow L = \frac{1}{12} H$$

$$y_4 = \frac{24}{5}s \Rightarrow C = \frac{24}{5} F$$

$$z_5 = \frac{5s}{36} \Rightarrow L = \frac{5}{36} H$$

so ckt is

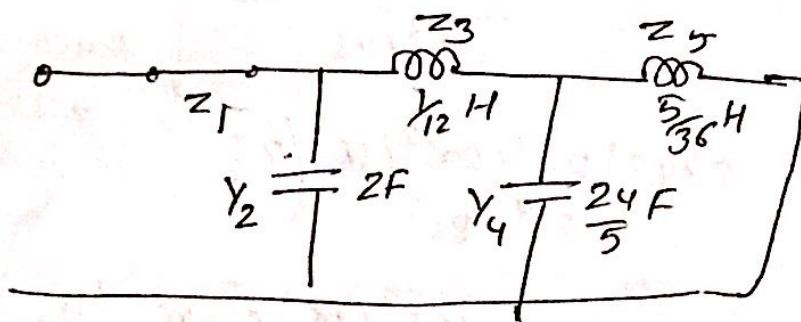

$$Q) \quad Z(s) = \frac{8s^5 + 5s^3 + 4s}{s^4 + 3s^2 + 1}$$

$$s^4 + 3s^2 + 1 \Big) s^5 + 5s^3 + 4s \quad (s \rightarrow z)$$

$$\overbrace{2s^3 + 5s} s^4 + 3s^2 + 1 \left(\frac{s}{2} \rightarrow y_2 \right)$$

$$\overline{\frac{3}{2}s^2 + 1} \Big) 2s^3 + 3s \left(\frac{4}{3}s \right) \rightarrow 3$$

$\underbrace{2s^3 + \frac{4}{3}s}$

$$\frac{5}{3}s \left(\frac{3}{2}s^2 + 1 \right) \left(\frac{9}{10}s^2 - \frac{3}{2}s^2 \right)$$

$$\cdot 1) \overline{5} \overline{3} s \left(\begin{matrix} \overline{5} s \\ \overline{3} s \end{matrix} \right) \overline{z} \overline{5}$$

$$Z(\zeta) = Z_1 + \frac{1}{\gamma_1 + \frac{1}{Z_2 + \frac{1}{\gamma_3 + \dots}}}$$

$$= s + \frac{1}{s_2} + \frac{1}{s_3} s + \frac{1}{s_{10}} s + \frac{1}{s_3} s$$

$$z_1 = s = LS \Rightarrow L = 1H$$


$$y_2 = s_2 = CS \Rightarrow C = \frac{1}{2} F$$
~~$$z_3 = \frac{4S}{3S} \Rightarrow C = \frac{3}{4} F$$~~

Provided by: Noteshub | Android App

$$Y_4 = \frac{g}{10} s \Rightarrow C = \frac{g}{10} F$$

$$Z_5 = \frac{5}{3} s \Rightarrow L = \frac{5}{3} H$$

ckt network:-

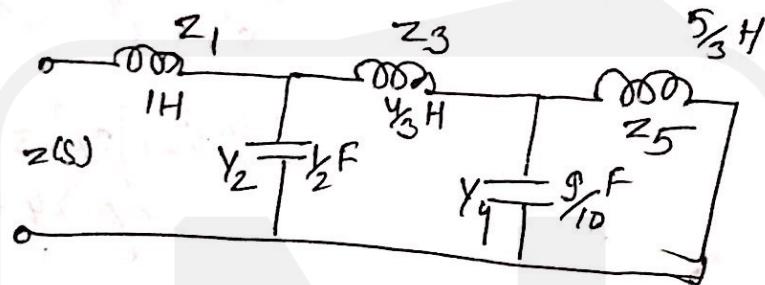

* Layer II - form:-

Continued fraction of $Z(s)$ when $s = \frac{1}{p}$

Type 1 question:-

$$Z(s) = \frac{s^4 + 9s^2 + 8}{s^3 + 4s}$$

$$\text{put } s = \frac{1}{p}$$

$$Z(s) = \frac{\frac{1}{p^4} + \frac{8}{p^2} + 8}{\frac{1}{p^3} + \frac{4}{p}}$$

$$Z(s) = \frac{\frac{8p^4 + 8p^2 + 1}{p^4}}{\frac{4p^3 + 1}{p^3}}$$

$$\Rightarrow \frac{8p^4 + 8p^2 + 1}{P(4p^2 + 1)}$$

$$\therefore \frac{8p^4 + 8p^2 + 1}{4p^3 + p}$$

$$(Q) Z(s) = \frac{s^4 + 9s^2 + 8}{s^3 + 4s}$$

Type 1 :-

(1) Arrange in ascending order first.


$$Z(s) = \frac{8 + 9s^2 + s^4}{4s + s^3}$$

(2) Continued fraction expansion of

$$Z(s) = \frac{8 + 9s^2 + s^4}{4s + s^3}$$

$$\begin{aligned} & 4s + s^3) \frac{8 + 9s^2 + s^4}{8 + 9s^2} \\ & \quad - \frac{8 + 9s^2}{7s^2 + s^4}) 4s + s^3 \\ & \quad - \frac{4s + \frac{4}{7}s^3}{7s^2 + s^4}) \frac{4g}{3s} \rightarrow z_1 \\ & \quad - \frac{7s^2}{s^4}) \frac{3}{7}s^3 \\ & \quad - \frac{3}{7}s^3) \frac{3}{7}s^3 \rightarrow z_2 \\ & \quad - \frac{3}{7}s^3) \frac{3}{7}s^3 \rightarrow z_3 \\ & \quad - \frac{3}{7}s^3) \frac{3}{7}s^3 \rightarrow z_4 \\ & \quad - \frac{3}{7}s^3) \frac{3}{7}s^3 \rightarrow z_5 \end{aligned}$$

Therefore network would be

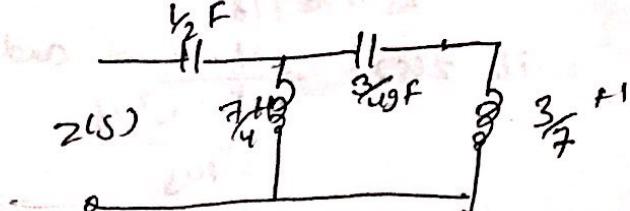

Note:-

for
Continue

- For synthesis of network, first check whether its LC, RC or RL imittance using the properties for each imittance defined
 - Then synthesize the networks using the method specify as for form-I form use partial fraction of $Z(s)$ and for form-II also use partial fraction of $Y(s)$ if $Z(s)$ is provided in question then find out the equation for $Y(s) = \frac{1}{Z(s)}$ then use form-II form.
 - For Case I and Case II form use continuous fraction and draw the ladder network. And for Case II form if numerator power is greater than denominator power then arrange in ascending form and then use continuous fraction and if numerator power is less than denominator power then put $s = \frac{1}{p}$ and then use continuous fraction. or if numerator power is less than denominator power arrange the $Z(s)$ or $Y(s)$ in terms of $\frac{1}{Z(s)}$
- For ex $Z(s) = \frac{s^3 + s}{2s^4 + 2s^2 + 18}$ is given then for Case-II form write $Z(s) = \frac{1}{\frac{2s^4 + 2s^2 + 18}{s^3 + s}}$ and then do the continued fraction.

continued fraction of $Z(s)$ when $s = \frac{1}{p}$

Type II question:-

(Q)

$$Z(s) \sim \frac{s(s^2+4)}{s(s^2+1)(s^2+9)}$$

$$Z(s) \sim \frac{s^3+4s}{2s^4+20s^2+18}$$

\Rightarrow Put $s = \frac{1}{p}$ we get;

$$Z(s) \sim \frac{\frac{1}{p^3} + \frac{4}{p}}{\frac{2}{p^4} + \frac{20}{p^2} + 18}$$

$$\Rightarrow Z(s) \sim \frac{4p^3 + p}{18p^4 + 20p^2 + 2}$$

$$\Rightarrow Z(s) \sim \frac{1}{\frac{18p^4 + 20p^2 + 2}{4p^3 + p}}$$

$$4p^3 + p \Big) \frac{18p^4 + 20p^2 + 2}{18p^4 + \frac{9}{2}p^2} \left(\frac{9}{2}p \right)$$

$$- \frac{-}{\frac{31}{2}p^2 + 2} \Big) 4p^3 + p \left(\frac{8}{31}p \right)$$

$$- \frac{-}{15_1p} \frac{\frac{31}{2}p^2 + 2}{\frac{31}{2}p^2} \left(\frac{(31)^2}{15}p \right)$$

$$- \frac{-}{2} \frac{15_1p}{15_1p} \left(\frac{15}{62}p \right)$$

Note:- Numerator power is $<$ denominator power so put $s = \frac{1}{p}$

Another method for this ques:-

$$Z(s) = \frac{s^3 + 4s}{2s^4 + 20s^2 + 18}$$

$$= \frac{1}{\frac{2s^4 + 20s^2 + 18}{s^3 + 4s}}$$

and now do the continued fraction

$$\text{of } \frac{2s^4 + 20s^2 + 18}{s^3 + 4s}$$

$$Z(s) = 0 + \frac{1}{\frac{9P}{2} + \frac{1}{\left(\frac{8P}{31}\right) + \frac{1}{\frac{961P}{30} + \frac{1}{\frac{15P}{62}}}}}$$

$\downarrow z_1 \quad \downarrow y_2 \quad \downarrow z_3 \quad \downarrow y_4 \quad \downarrow z_5$

As $s = \frac{1}{P}$

$$\Rightarrow P = \frac{1}{s}$$

$$z_1 = 0$$


$$y_2 = \frac{9P}{2} = \frac{9}{2s} = \frac{1}{(2g)}s \Rightarrow L = \frac{2}{g} H$$

$$z_3 = \frac{8P}{31} \Rightarrow \frac{8}{31s} \Rightarrow \frac{1}{\left(\frac{31}{8}\right)s} \Rightarrow C = \frac{31}{8} F$$

$$y_4 = \frac{961P}{30} \Rightarrow \frac{961}{30s} \Rightarrow \frac{1}{\frac{30}{961}s} \Rightarrow L = \frac{30}{961} H$$

$$z_5 = \frac{15P}{62} \Rightarrow \frac{15}{62s} \Rightarrow \frac{1}{\frac{62}{15}s} \Rightarrow C = \frac{62}{15} F$$

So ckt becomes;

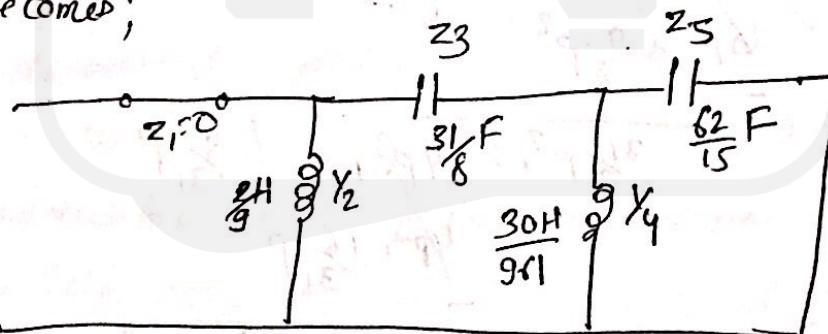

* Note:- if numerator power < denominator power
the $z_1 = 0$ for both case I and
case II form

* if numerator power > denominator power then there
will be value of z_1 for both case I and case II form

PQ And Impedance function is given by;

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

①

- Synthesize the network using
 i) Foster - I form
 ii) Foster - II form
 iii) Cauer - I form
 iv) Cauer - II form.


$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

Step 1:- check whether the network is LC impedance, RC or RL impedance.

→ $Z(s)$ is RC impedance.

$$\text{i) } P_1, P_2, P_3 = 0, -2, -5$$

$$Z_1, Z_2 = -1, -4$$

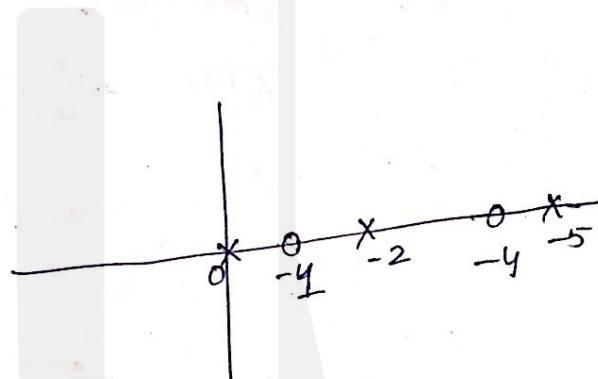

ii) Residue at $s=0, -2, -5$

$$\text{at } s=0; \text{ Residue} = \lim_{s \rightarrow 0} s \times \frac{(s+1)(s+4)}{s(s+2)(s+5)} = \frac{4}{10} = \frac{2}{5}$$

$$\text{Residue at } s=-2; \lim_{s \rightarrow -2} (s+2) \frac{(s+1)(s+4)}{s(s+2)(s+5)} = \frac{18}{3} = \frac{1}{3}$$

$$\text{Residue at } s=-5 \lim_{s \rightarrow -5} (s+5) \frac{(s+1)(s+4)}{s(s+2)(s+5)} = \frac{4}{15}$$

→ So poles and zeros lying in negative real axis with singularity is pole

→ Residue are real and positive
 therefore Network is RC impedance.

Step 2:- Partial fraction of $Z(s)$

$$\frac{A}{s} + \frac{B}{s+2} + \frac{C}{s+5}$$

on solving further we get the values of

$$A = \frac{2}{5}, \quad B = \frac{1}{3}, \quad C = \frac{4}{15}$$

$$\therefore Z(s) = \frac{2}{5s} + \frac{1}{3(s+2)} + \frac{4}{15(s+5)}$$


$$= \frac{1}{\frac{5}{2}s} + \frac{1}{3s+6} + \frac{1}{\frac{15}{4}s+\frac{75}{4}}$$

$$Y_1(s) = \frac{5}{2}s \Rightarrow C_1 = \frac{5}{2}F$$

$$Y_2(s) = 3s+6 \Rightarrow C_2 = 3F, R_1 = \frac{1}{6}\Omega$$

$$Y_3(s) = \frac{15}{4}s + \frac{75}{4} \Rightarrow C_3 = \frac{15}{4}F, R_2 = \frac{75}{4}\Omega, \frac{4}{75}\Omega$$

\therefore

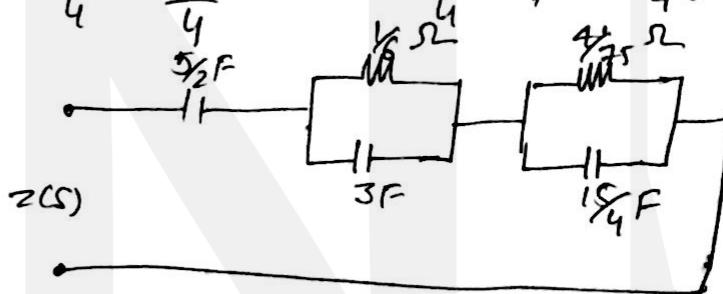

For II form:-

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

$$Y(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$$

$$\frac{Y(s)}{s} = \frac{(s+2)(s+5)}{(s+1)(s+4)}$$

\therefore This is RL admittance as all conditions are satisfied.

$$\frac{Y(s)}{s} = \frac{s^2 + 7s + 10}{s^2 + 5s + 4}$$

Step 2:- Partial fraction of $\frac{Y(s)}{s}$.

$$\text{Provided by Noteshun.co.in | Download Android App} \quad (2)$$

$$\frac{s^2 + 2s + 4}{s^2 + 5s + 4} = \frac{s^2 + 7s + 10}{s^2 + 5s + 4} - \frac{5s + 6}{s^2 + 5s + 4}$$

$$\frac{Y(s)}{s} = 1 + \frac{2s+6}{(s+1)(s+4)}$$

Now partial fraction of $\frac{2s+6}{(s+1)(s+4)}$

$$\frac{2s+6}{(s+1)(s+4)} = \frac{A}{(s+1)} + \frac{B}{(s+4)}$$

on solving we get the value of $A = \frac{4}{3}$, $B = \frac{2}{3}$

$$\frac{Y(s)}{s} \sim 1 + \frac{\frac{4}{3}(s+1)}{s+4} + \frac{\frac{2}{3}(s+4)}{s+1}$$

$$Y(s) \sim s + \frac{\frac{1}{3}s}{\frac{3}{4}s + \frac{3}{4}} + \frac{\frac{2}{3}s}{\frac{3}{2}s + 6}$$


$$Y(s) \sim s + \frac{1}{\frac{3}{4}s + \frac{3}{4}} + \frac{1}{\frac{3}{2}s + 6}$$

$$Y_1(s) \sim s \quad C_1 = 1F$$

$$Z_1(s) = \frac{3}{4}s + \frac{3}{4} \quad R_1 = \frac{3}{4}\Omega, \quad C_2 = \frac{4}{3}F$$

$$Z_2(s) = \frac{3}{2}s + \frac{6}{5} \quad R_2 = \frac{3}{2}\Omega, \quad C_3 = \frac{1}{6}F$$
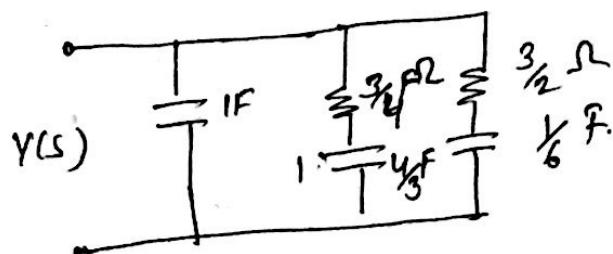
$$\therefore Y(s) = Y_1 + \frac{1}{Z_1} + \frac{1}{Z_2}$$



$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)} = \frac{s^2 + 5s + 4}{s^3 + 7s^2 + 10s}$$

$$Z(s) = \frac{\frac{1}{s^3 + 7s^2 + 10s}}{s^2 + 5s + 4}$$

Now continued fraction of $\frac{s^3 + 7s^2 + 10s}{s^2 + 5s + 4}$

$$s^2 + 5s + 4 \left| \begin{array}{l} s^3 + 7s^2 + 10s \\ s^3 + 5s^2 + 4s \end{array} \right. \quad (s \rightarrow y_1)$$

$$= \frac{-}{s^2 + 3s} \left| \begin{array}{l} s^2 + 5s + 4 \\ s^2 + 3s \end{array} \right. \quad (\frac{1}{2} \rightarrow z_2)$$

$$2s + 4 \left| \begin{array}{l} 2s^2 + 4s \\ 2s^2 + 4s \end{array} \right. \quad (2 \rightarrow x_3)$$

$$\frac{2s}{4} \left| \begin{array}{l} 2s \\ 2s \end{array} \right. \quad (2 \rightarrow x_3)$$


$$Y_1 = s \Rightarrow C_1 = 1F$$

$$Z_2 = \frac{1}{2} \Rightarrow R_2 = \frac{1}{2} \Omega$$

$$Y_3 = s \Rightarrow C_3 = 1F$$

$$Z_4 = 1 \Rightarrow R_4 = 1\Omega$$
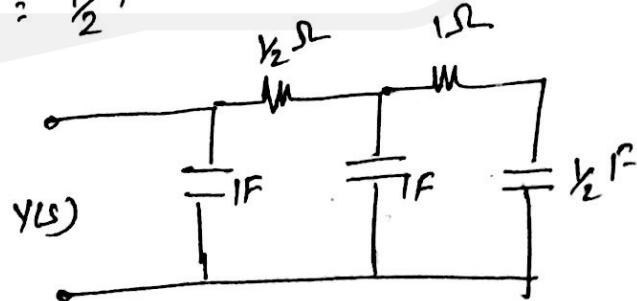
$$Y_5 = \frac{1}{2} \Rightarrow C_5 = \frac{1}{2} F$$



$$Z(s) = \frac{s^2 + 5s + 4}{s^3 + 7s^2 + 10s}$$

Numerator power < Denominator power.

$$\therefore Z(s) = \frac{1}{s} p$$

$$Z(s) = \frac{\frac{1}{p^2} + \frac{5}{p} + 4}{\frac{1}{p^3} + \frac{7}{p^2} + \frac{10}{p}}$$

$$\begin{aligned} Z(s) &= \frac{\frac{1 + 5p + 4p^2}{p^2}}{\frac{1 + 7p + 10p^2}{p^3 p}} \\ &= \frac{p + 5p^2 + 4p^3}{1 + 7p + 10p^2} \\ &= \frac{4p^3 + 5p^2 + p}{10p^2 + 7p + 1} \end{aligned}$$

$$\frac{10p^2 + 7p + 1}{4p^3 + 5p^2 + p} \left(\frac{4}{10} p \right)$$

$$= \frac{4p^3 + \frac{28}{10} p^2 + \frac{4}{10} p}{10p^2 + \frac{30}{10} p} \left(\frac{10}{22} p \right)$$

$$= \frac{\frac{22}{10} p^2 + \frac{6}{10} p}{10p^2 + \frac{12}{235} p} \left(\frac{11}{42} \times \frac{22}{10} p \right)$$


$$= \frac{\frac{22}{10} p^2 + \frac{6}{10} p}{10p^2 + \frac{12}{235} p} \left(\frac{22}{42} p \right)$$

$$Y_2 = \frac{100}{22} = \frac{50}{11} \Rightarrow R_2 = \frac{50}{11}$$

$$Z_3 = \frac{121}{235} P = \frac{121}{235} S \Rightarrow C_3 = \frac{235}{121} F$$

$$Y_4 = \frac{2209}{44} \Rightarrow R_4 = \frac{2209}{44} \Omega$$
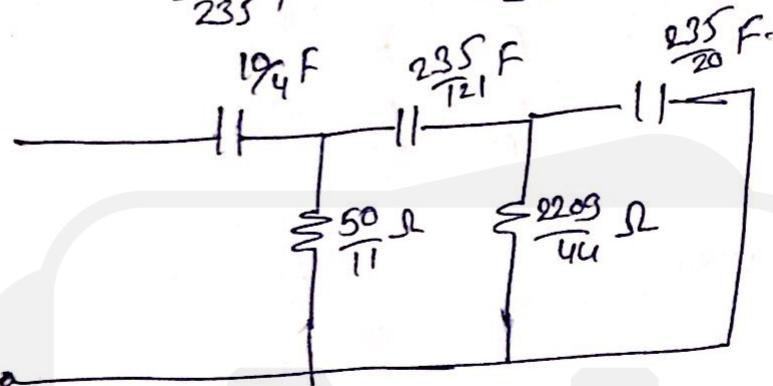
$$Z_5 = \frac{20}{235} P = \frac{20}{235} S \Rightarrow C_5 = \frac{235}{20} F$$



Q1 $Z(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$

Step 1:- checking of RC, RL and LC
• Poles and zeroes

provided by NotesHub.in at Download Android App 18

(1)

represented by;

$$Z(s) = \frac{s^2 + 5s + 4}{s^2 + 2s}$$

Express it in both the forms.


$$Z(s) = \frac{s^2 + 5s + 4}{s^2 + 2s} = \frac{(s+1)(s+4)}{s(s+2)}$$

Step 1:- check whether its RC , LC or RL impedance.

$$P_1, P_2 = 0, -2$$

$$z_1, z_2 = 1, -4$$

Poles are on negative real axis.

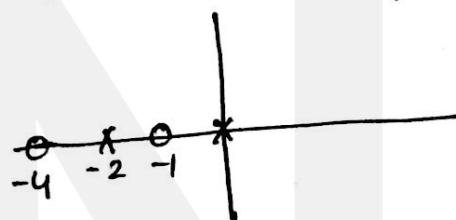

Poles are alternate and first singularity is pole

Residue of $Z(s)$ at $P_1 = 0, P_2 = -2$

$$\text{at } P_1 = 0 \Rightarrow \frac{(s-0) \times (s+4)(s+1)}{s(s+2)} = \frac{4}{2} = 2$$

$$\text{at } P_2 = -2 \quad \frac{(s+2)}{(s+2)} \frac{(s+1)(s+4)}{s(s+2)} = \frac{-1+2}{-2} = 1$$

Residue on Real and +ve.

Therefore it is RC impedance.

$$\text{Step 2:- } Z(s) = \frac{(s+1)(s+4)}{s(s+2)}$$

Partial fraction of $Z(s)$

$$\frac{s^2 + 5s + 4}{s^2 + 2s}$$

$$\frac{s^2 + 2s}{s^2 + 2s} \left(s^2 + 5s + 4 \right) / \frac{3s + 4}{s^2 + 2s}$$

$$\therefore Z(s) = 1 + \frac{3s + 4}{s(s+2)}$$

$$\text{Partial fraction of } Z(s) = \frac{3s + 4}{s(s+2)}$$

$$= \frac{A}{s} + \frac{B}{s+2}$$

On solving $A = 2, B = 1$

$$\therefore Z(s) = 1 + \frac{2}{s} + \frac{1}{s+2}$$

$$Z(s) = 1 + \frac{1}{s/2} + \frac{1}{s+2}$$

$$= z_1 + z_2 + z_3$$

$$z_1 = 1 \Rightarrow R = 1 \Omega$$


$$z_2 = \frac{1}{s/2} \Rightarrow C = \frac{1}{2} F$$

$$z_3 = \frac{1}{s+2} = \frac{1}{Y_3}$$

$$Y_3 = s+2$$

$$C_3 = 1 F$$

$$R_3 = \cancel{1/2} \Omega$$

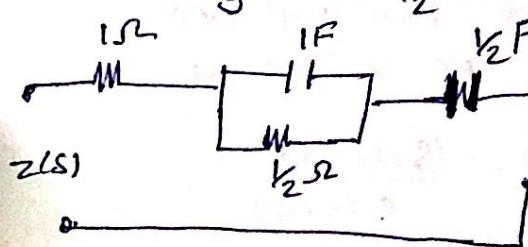



Fosku-II Form:

$$Z(s) = \frac{s^2 + 5s + 4}{s^2 + 2s} \quad [\text{Convert the } Z(s) \text{ into } Y(s)]$$

$$\Rightarrow Y(s) = \frac{s^2 + 2s}{s^2 + 5s + 4}$$

$$Y(s) = \frac{s(s+2)}{(s+1)(s+4)}$$

$$\Rightarrow \frac{Y(s)}{s} = \frac{s+2}{(s+1)(s+4)}$$

$$\frac{Y(s)}{s} = \frac{A}{s+1} + \frac{B}{s+4}$$

$$\Rightarrow A(s+4) + B(s+1) = s+2$$

$$A+B=1$$

$$4A+B=2$$

$$\frac{-3A = -1}{-3A = -1} \Rightarrow A = \frac{1}{3} \quad \text{and } B = \frac{2}{3}$$

$$\Rightarrow \frac{Y(s)}{s} = \frac{\frac{1}{3}}{s+1} + \frac{\frac{2}{3}}{s+4}$$

$$Y(s) = \frac{\frac{1}{3}s}{s+1} + \frac{\frac{2}{3}s}{s+4}$$

$$Y(s) = \frac{s}{3s+3} + \frac{2s}{3s+12}$$

$$Y(s) = \frac{1}{3s+3} + \frac{1}{3s+12}$$

$$Y(s) = Y_1 + Y_2$$

$$= \frac{1}{3s} + \frac{1}{12s}$$

$$Z_1 = 3 + \frac{3}{s}$$


$$R_1 = 3\Omega$$

$$C_1 = \frac{1}{3} F$$

$$Z_2 = \frac{3}{12} + \frac{1}{s}$$

$$R_2 = \frac{3}{12} \Omega$$

$$C_2 = \frac{1}{12} F$$

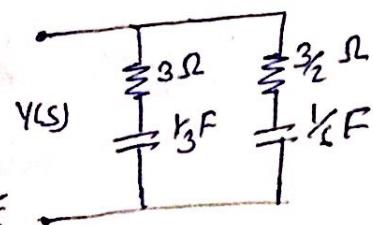

Fosku-II N/O

Circ. I form:-

$$Z(s) = \frac{s^2 + 5s + 4}{s^2 + 2s}$$

$$s^2 + 2s \Big) s^2 + 5s + 4 \quad (1 \rightarrow R_1)$$

$$\frac{3s + 4}{s^2 + 2s} \Big) s^2 + 2s \quad (s \rightarrow Y_2)$$

$$\frac{2s}{3s} \Big) 3s + 4 \quad (s \rightarrow R_3)$$


$$\frac{4}{2s} \Big) 2s \quad (s \rightarrow X_4)$$

$$R_1 = 1\Omega$$

$$Y_2 = CS = \frac{1}{3}F$$

$$R_3 = \frac{9}{2}\Omega$$

$$Y_4 = \frac{5}{6} = \frac{1}{6}F$$

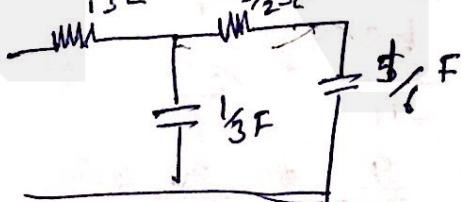Therefore ladder $\frac{n}{N}$.

Circ-II form:-

$$Z(s) = \frac{s^2 + 5s + 4}{s^2 + 2s}$$

Step 1:- Arrange in ascending order.

$$Z(s) = \frac{4 + 5s + s^2}{2s + s^2}$$

Step 2:- continued fractⁿ of $Z(s)$

$$\begin{aligned}
 & \frac{2s+s^2}{3s+s^2} \left| \begin{array}{l} 4+2s \\ 3s+2s^2 \end{array} \right. \xrightarrow{s \rightarrow z_1} \\
 & \frac{2s+s^2}{3s+s^2} \left| \begin{array}{l} 2s+s^2 \\ 2s+2s^2 \end{array} \right. \xrightarrow{s \rightarrow z_2} \\
 & \frac{2s+s^2}{3s+s^2} \left| \begin{array}{l} 3s+s^2 \\ 3s+2s^2 \end{array} \right. \xrightarrow{s \rightarrow z_3} \\
 & \frac{2s+s^2}{3s+s^2} \left| \begin{array}{l} 1s+s^2 \\ 1s+2s^2 \end{array} \right. \xrightarrow{s \rightarrow z_4} \\
 & \xrightarrow{x}
 \end{aligned}$$


$$z_1 = \frac{2s}{3s} \Rightarrow C_1 = \frac{1}{2} F$$

$$y_2 = \frac{2s}{3s} \Rightarrow R_2 = \frac{3}{2} \Omega \quad [z_1 = R]$$


$$z_3 = \frac{3s}{3s} \Rightarrow C_3 = \frac{1}{3} F$$

$$y_4 = \frac{1}{3} \Rightarrow R_4 = 3 \Omega$$

dadder structure:-

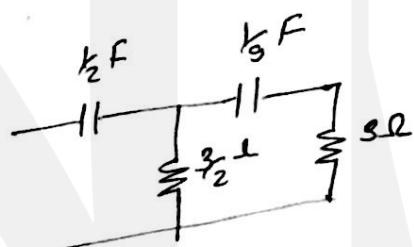

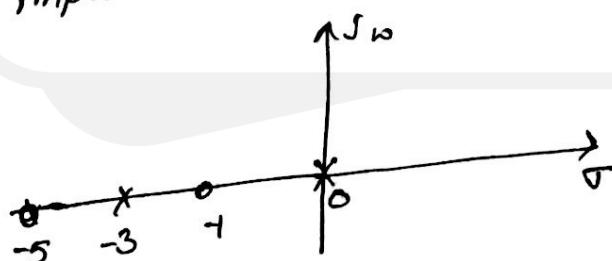- (Q) An impedance funct' has pole-zero pattern. If $z(-2) = 3$.
Synthesize the impedance in fulls-second form.



From pole zero pattern;

$$z(s) = \frac{k(s-z_1)(s-z_2)}{(s-p_1)(s-p_2)}$$

$$\begin{aligned}
 z_1 &= -1 & p_1 &= 0 \\
 z_2 &= -5 & p_2 &= -3
 \end{aligned}$$

$$Z(s) = \frac{k(s+1)(s+5)}{s(s+3)}$$

For value of k ; $Z(-2) = 3$

$$Z(-2) = \frac{k(-2+1)(-2+5)}{-2(-2+3)}$$

$$3 = \frac{k \times -1 \times 3}{-2 \times 1}$$

$$3 = \frac{k \times 3}{2}$$

$$\boxed{k = 2}$$

$$Z(s) = \frac{2(s+1)(s+5)}{s(s+3)}$$

Step 1:- check LC, RC, and RL immittance

By looking at pole-zero diag; first singularity is pole and initialized with $\angle 30^\circ$.

\therefore If it is RC immittance funcⁿ as all conditions are satisfied [check all three condition for RC immittance]

Step 2:- convert it into $Y(s)$

$$\therefore Y(s) = \frac{s(s+3)}{2(s+1)(s+5)}$$

$$\frac{Y(s)}{s} = \frac{(s+3)A}{2(s+1)(s+5)}$$

Step 3:- partial fractⁿ of $\frac{Y(s)}{s} = \frac{(s+3)A}{2(s+1)(s+5)}$

$$\therefore \frac{Y(s)}{s} = \frac{A}{s+1} + \frac{\beta}{s+5}$$

on solving $A = k_4$, $B = k_4$

$$\begin{aligned} \frac{Y(s)}{s} &= \frac{1}{4(s+1)} + \frac{1}{4(s+5)} \\ Y(s) &= \frac{s}{4(s+1)} + \frac{s}{4(s+5)} \end{aligned}$$

(1)

$$\frac{Y(s)}{S} = \frac{1}{4} \left[\frac{A}{S+1} + \frac{B}{S+5} \right]$$

$$\frac{Y(s+3)}{(S+1)(S+5)} = \frac{A(S+5) + B(S+1)}{(S+1)(S+5)}$$

$$Y(s+3) = (A+B)s + (5A+B)$$

$$A+B=3 \quad \text{--- (i)}$$

$$5A+B=0 \quad \text{--- (ii)}$$

-

$$\begin{array}{r} -4A \\ \hline A = 3 \end{array}$$

on solving eqn (i) & (ii)

$$A = \frac{1}{2}$$

$$B = \frac{1}{2}$$

$$\begin{array}{r} A+B=3 \\ -\frac{3}{4}+B=3 \Rightarrow B=\frac{8+3}{4} \\ \hline B=\frac{11}{4} \end{array}$$

$$\frac{Y(s)}{S} = \frac{1}{4} \left[\frac{-3}{S+1} + \frac{15}{S+5} \right] \quad \frac{Y(s)}{S} = \frac{1}{2} \left[\frac{\frac{1}{2}}{S+1} + \frac{\frac{1}{2}}{S+5} \right]$$

$$Y(s) = Y_1 + Y_2 = \frac{k_1 s}{S+1} + \frac{k_2 s}{S+5}$$

$$\Rightarrow Y(s) = \frac{1}{(4+\frac{1}{4}s)} + \frac{1}{(4+\frac{1}{4}s)}$$

$$Y(s) = Y_1 + Y_2$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{4+k_1 s}$$

$$Z_1 = 4 + \frac{1}{k_1 s} \Rightarrow R_1 = 4 \Omega$$


$$C_1 = \frac{1}{k_1} F$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{4 + \frac{20}{k_2 s}}$$

$$\therefore Z_2 = \frac{4 + \frac{20}{k_2 s}}{s}$$

$$R_2 = 4 \Omega$$

$$C_2 = \frac{1}{20} F$$

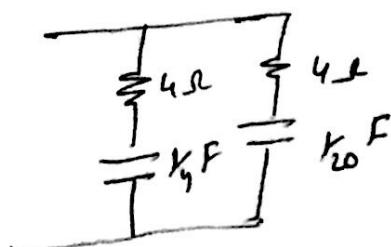

$$Y(s) = \frac{1}{(4+s)} + \frac{1}{(4+20/s)}$$

$$Y(s) = Y_1 + Y_2$$

$$Y_1 = \frac{1}{4+s} = \frac{1}{z_1}$$

$$z_1 = 4 + \frac{4}{s}$$

$$Y_2 = \frac{1}{4+20/s} = \frac{1}{z_2}$$

$$z_2 = 4 + \frac{20}{s}$$

$$\frac{k_4 s}{s+1}$$

$$\frac{k_4 s z_1}{(s+1)}$$

$$\frac{Y(s)}{s} = \frac{s(s+5)}{2(s+1)(s+5)}$$

$$\frac{A}{s+1} + \frac{B}{s+5}$$

$$= A(s+5) + B(s+1)$$

$$= (As+B)s + 5A+B$$

$$A+B=0$$

$$5A+B=0$$

$$-4A=0 \Rightarrow A = -\frac{3}{4}$$

$$\frac{k_4 s}{s+1}$$

$$\frac{1}{4+\frac{4}{s}} = \frac{1}{z_1}$$

$$\frac{k_4 s}{s+1}$$

$$Y_s \times \frac{1}{4}s$$

$$\frac{4s}{(s+1)} \left(4 + \frac{4}{s}\right)$$

$$Y = \frac{1}{z_1} =$$

$$z_1 = 4 + \frac{4}{s}$$

$$\frac{1}{cs} = \frac{1}{4s}$$

$$D = 4s$$

- A filter is electronic device that can remove specific range of freq. from signal. Resonant circuit in AC select narrow band of freq. and reject other. Reactive n/w are called filters.
- Filter n/w widely used in communication system to separate voice channel in carrier freq in telephone ckt.

Classification of filters:-

(1) Active Filter

(2) Passive Filter

- Passive filter:- Made up of entirely passive component such as resistors, capacitor, inductors.
- Active filter:- it is made up of active component such as op-amp in order to filter the signal.
- Active filter may contain active as well as passive component.
- passive filter can be used at high freq. by using inductors.
- For Active filter freq. range is dependent on bandwidth of amplifiers. Compared to active filter properties of passive filter may change when load is changed.

Parameters of Filters:-

(1) characteristic Impedance (Z_c or Z_0):-

The characteristic impedance of a filter must be chosen such that the filter may fit into a given line or between two type of equipment.

(2) Pass Band:-

Band in which filter have to pass all frequencies without reduction in magnitude are referred as pass band.

(3) Stop Band:-

Band in which filter have to attenuate frequencies

④ cut off freq (f_c):-

The frequency which separates the pass band and stop band is defined as cut off freq.

⑤ Attenuation:- It is a loss of signal.

→ It can be expressed in decibels (dB), or Neper or Bels.

$$\text{Attenuation in dB} = 10 \log_{10} \frac{P_i}{P_o}$$

$$= 20 \log_{10} \frac{V_i}{V_o}$$

$$= 20 \log_{10} \frac{Z_i}{Z_o}$$

$$\text{Attenuation in Neper} = \frac{1}{2} \log_e \frac{P_i}{P_o}$$

$$= \log_e \frac{V_i}{V_o}$$

$$= \log_e \frac{Z_i}{Z_o}$$

$$\text{Attenuation in Bels} = \log_{10} \frac{P_i}{P_o}$$

$$= 2 \log_{10} \frac{V_i}{V_o}$$


$$= 2 \log_{10} \frac{Z_i}{Z_o}$$

Attenuation in dB = $8.686 \times$ Attenuation in Neper

= $10 \times$ Attenuation in Bels.

Classification of Filter:-

① Low Pass filter:- AV(S)

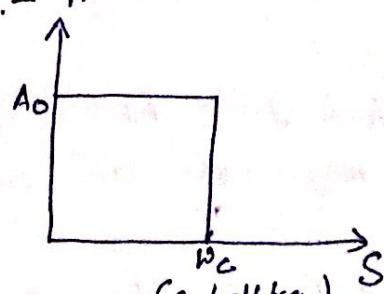


characteristic of LPF

LPF rejects all freq. above cut off freq. i.e. ω_c . Thus


(2)

the pass band for LPF is 0 to ω_c and stop band is the freq. range above ω_c .

T-n/w and π -n/w for LPF:-

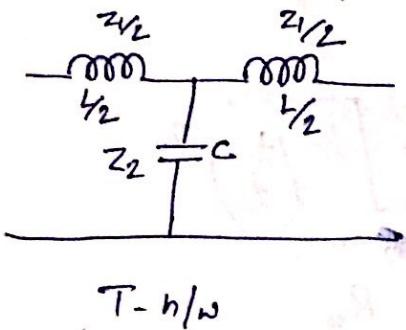

T-n/w.

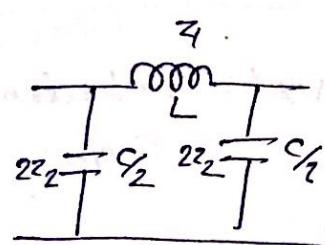

π -n/w.

Characteristic parameter for LPF:-

(1) Design impedance or load resistance;

$$Z_0 = \sqrt{R_0 C}$$

$$z_1 z_2 = k^2 = \frac{L}{C} = R_0^2$$

$$R_0 = \sqrt{\frac{L}{C}}$$

where z_1 = Series impedance

z_2 = shunt \rightarrow

(2) cut off freq:-

$$N_C = \frac{2}{\sqrt{LC}}$$

$$\omega_C = \frac{1}{\sqrt{LC}}$$

(3) Attenuation constant:-

$$\alpha = 2 \cosh^{-1} \left(\frac{1}{N_C} \right) \quad [\text{stop band}]$$

$$\alpha = 0 \quad [\text{pass band}]$$

(4) Phase constant:-

$$\beta = \pi \quad [\text{stop band}]$$

$$\beta = 2 \sin^{-1} \left(\frac{1}{N_C} \right) \quad [\text{pass band}]$$

(5) Filter component value:-

$$z_1 z_2 = k^2 \Rightarrow R_0 = \sqrt{\frac{L}{C}}$$

$$L = \frac{k}{\pi f_c} \quad C = \frac{1}{\pi f_c k}$$



⑥ characteristic impedance:

$$\text{For } T = n/\omega; \quad Z_{0T} = R_0 \sqrt{1 - \left(\frac{f}{f_c}\right)^2}$$

$$\text{For } \pi - N/\omega \quad Z_{0N} = \frac{R_0}{\sqrt{1 - \left(\frac{f}{f_c}\right)^2}}$$

Q) Design a LPF for both 'T' and π - n/ω having cut off freq. of 1kHz to operate with terminated load resistance of 2000Ω and find the freq. at which falls after attenuating 19.1 dB .

Sol:-

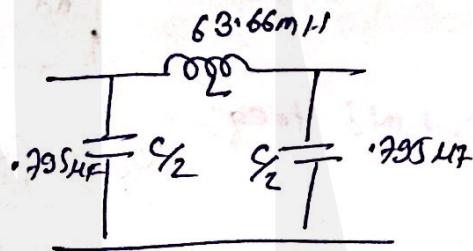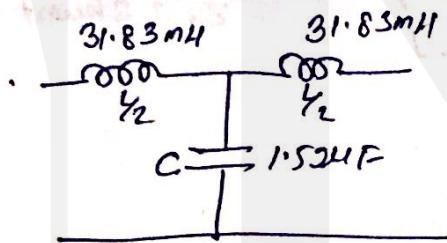

$$f_c = 1 \times 10^3 \text{ Hz}$$

$$R_0 = 2000 \Omega = K$$

$$L = \frac{k}{\pi f_c} = \frac{2000}{\pi \times 10^3} = 63.66 \text{ mH}$$

$$C = \frac{1}{\pi f_c k} = \frac{1}{30 \pi \times 10^3 \times 2000} \approx 1.59 \mu F$$

Attenuation in dB = 19.1


$$\therefore \text{dB loss} = \frac{19.1}{8.686} = 2.2 \text{ nepers}$$

$$\alpha = 2 \cosh^{-1} \left(\frac{f}{f_c} \right)$$



$$2.2 = 2 \cosh^{-1} \left(\frac{f}{1\text{kHz}} \right) \Rightarrow f = 1.67 \text{ kHz}$$

③

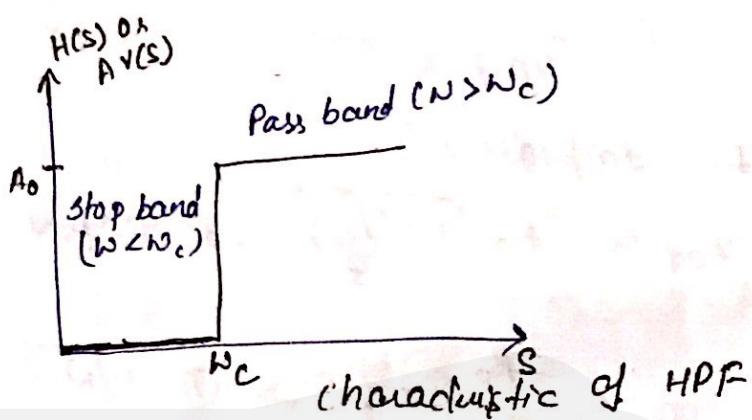High Pass filter :-
 HPF reject all frequencies below cut off freq. thus pass band and stop band of HP filter are the freq. range above f_c and below f_c .



Characteristic Parameters:-

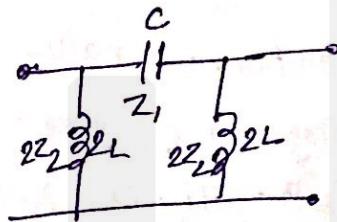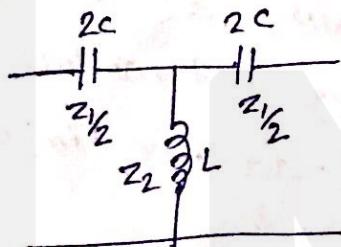

① Design impedance or load resistance:-

$$k^2 = R_0^2 = \frac{L}{C}$$

$$R_0 = \sqrt{\frac{L}{C}}$$

② Cut off freq :-

$$\omega_c = \frac{1}{2\pi\sqrt{LC}}$$

$$f_c = \frac{1}{4\pi\sqrt{LC}}$$

③ Attenuation constant:-

$$\alpha = 0 \rightarrow [\text{Pass band}]$$

$$\alpha = 2 \operatorname{cosec}^{-1} \left(\frac{f_c}{f} \right) [\text{Stop band}]$$

④ Phase constant:-

$$\beta = \pi [\text{Pass band}]$$

$$\beta = 2 \sin^{-1} \left(\frac{f_c}{f} \right) [\text{Stop band}]$$

Q5

Fill in component value:-

$$L = \frac{k}{4\pi f_c}$$

$$C = \frac{1}{4\pi f_c} k$$

Q6 characteristic impedance :-

$$Z_{0T} = R_0 \sqrt{1 - \left(\frac{f_c}{f}\right)^2} \rightarrow T - n/w$$

$$Z_{0n} = \frac{R_0}{\sqrt{1 - \left(\frac{f_c}{f}\right)^2}} \rightarrow T - n/w$$



Q7 Find the component value of $\pi - n/w$ constant ~~k~~ ^{is high} pass filter having cut off freq. of 8kHz and nominal characteristic impedance of 600Ω . Hence find its characteristic impedance and phase constant at $f = 12\text{kHz}$.

$$\text{Soln: } R_0 = k = \sqrt{\frac{L}{C}} = 600$$

$$f_c = 8000\text{Hz}$$


$$L = \frac{k}{4\pi f_c} = \frac{600}{4\pi \times 8000} = 397\text{ mH}$$

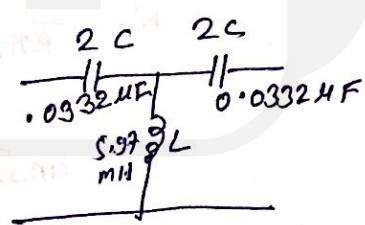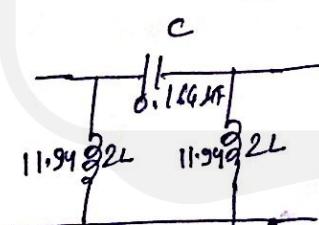
$$C = \frac{1}{4\pi k f_c} = \frac{1}{4\pi \times 600 \times 8000} = 0.0166\text{ nF}$$



Band Pass Filter:-

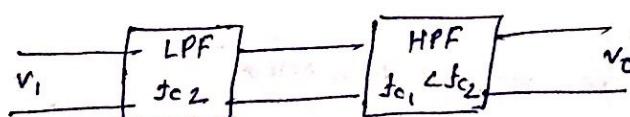
Band Pass filter is generally obtained by series or cascade connection of LPF and HPF



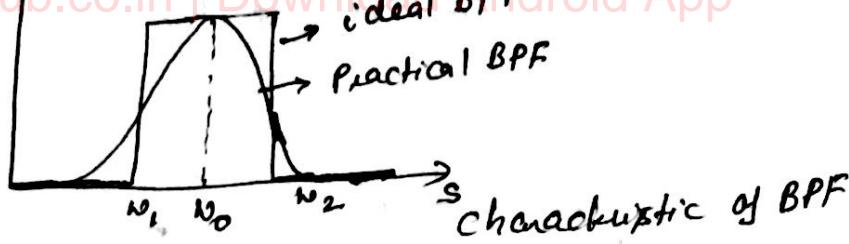

Pass band for BPF $\Rightarrow \omega_1 \rightarrow \omega_2$
 $f_{c1} \rightarrow f_{c2}$

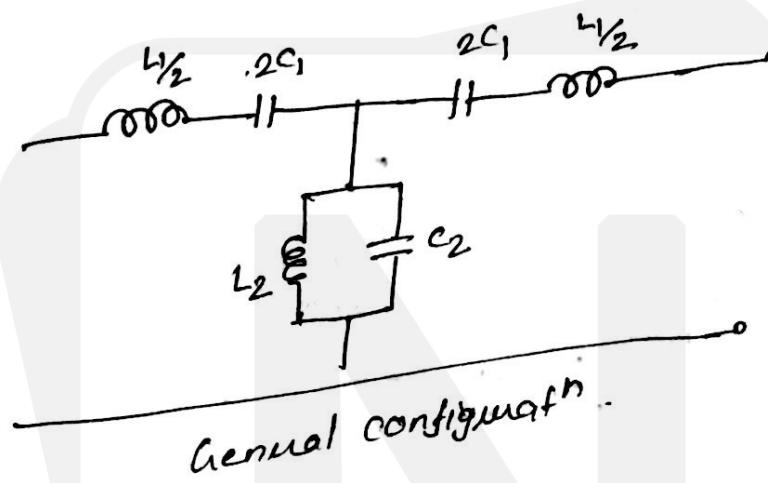Stop band for BPF $= 0 \rightarrow \omega_1, 0 \rightarrow f_{c1}$
 $\omega_2 \rightarrow \infty, f_{c2} \rightarrow \infty$



Characteristic Parameters:-

$$R_0 = K_0 = \sqrt{\frac{L_2}{C_1}} = \sqrt{\frac{L_1}{C_2}}$$

\rightarrow cut off freq; $f_0 = \sqrt{f_{c1} f_{c2}}$

cut off freq for BPF is equal to geometric mean of two cut off freq.

\rightarrow Filter component values:-

$$C_1 = \frac{f_{c2} - f_{c1}}{4\pi R_0 f_{c1} f_{c2}}$$



$$L_1 = \frac{R_0}{\pi (f_{c2} - f_{c1})}$$

$$C_2 = \frac{1}{\pi R_0 (f_{c2} - f_{c1})}$$

$$L_2 = \frac{(f_{c2} - f_{c1}) R_0}{4\pi f_{c1} f_{c2}}$$

Pr Board Shop Nitku! — Noteshub.co.in | Download Android App connection of Band Stop filter is obtained by parallel connection of LPF and HPF.


LPF and HPF.

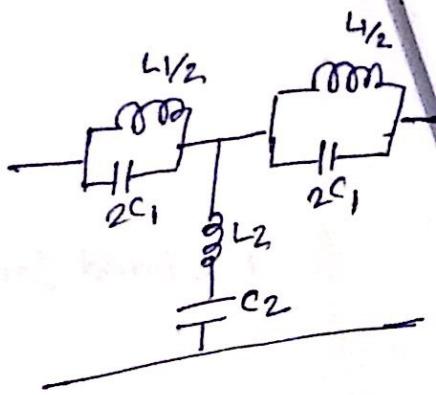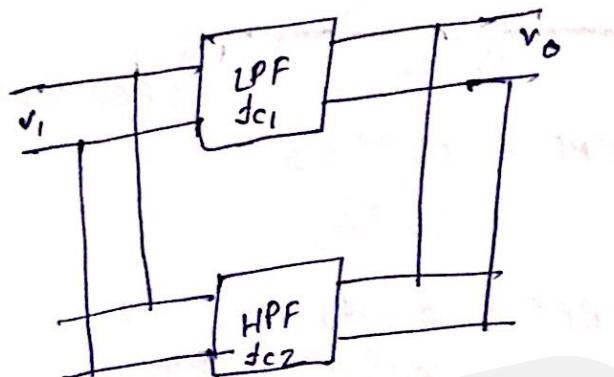

Pass band $\rightarrow 0 \rightarrow f_{c1}, f_{c2} \rightarrow \infty$

Stop band $\rightarrow f_{c1} \rightarrow f_{c2}$

ideal BSF.

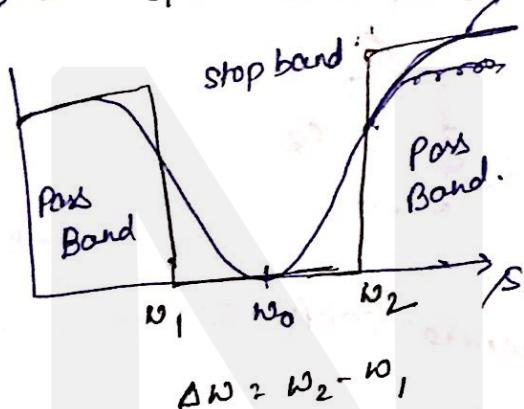

characteristic of BSF

Characteristic Parameters:-

(1) Design impedance or load impedance;

$$k = R_0 = \sqrt{\frac{L_1}{C_2}} = \sqrt{\frac{L_2}{C_1}}$$

(2) cut off freq:-

$$f_0 = \sqrt{f_{c1} f_{c2}}$$

(3) filter component values:

$$L_1 = \frac{R_0 (f_{c2} - f_{c1})}{\pi f_{c1} f_{c2}} \quad C_1 = \frac{1}{4\pi R_0 (f_{c2} - f_{c1})}$$

$$L_2 = \frac{R_0}{4\pi (f_{c2} - f_{c1})}$$

$$C_2 = \frac{f_{c2} - f_{c1}}{\pi R_0 f_{c1} f_{c2}}$$

Design by a Network Constant | Download Android App
 Design by a Network Constant | Download Android App

of a Band Pass filter with cut off freq. 3 kHz and 7.5 kHz and nominal characteristic impedance of 900 Ω

$$R_o = 900 \Omega$$

$$f_{c_1} = 3 \text{ kHz}$$

$$f_{c_2} = 7.5 \text{ kHz}$$

$$L_1 = \frac{R_o}{\pi(f_{c_2} - f_{c_1})}^2 \frac{900}{\pi(7.5 - 3) \times 10^3} = 63.66 \text{ mH}$$

$$C_1 = \frac{f_{c_2} - f_{c_1}}{4\pi R_o f_{c_1} f_{c_2}} = \frac{(7.5 - 3) \times 10^3}{4\pi \times 900 \times 7.5 \times 3 \times 10^6} = 0.017 \mu F$$

$$L_2 = \frac{(f_{c_2} - f_{c_1}) R_o}{4\pi f_{c_1} f_{c_2}} = \frac{(7.5 - 3) \times 10^3 \times 900}{4\pi \times 7.5 \times 3 \times 10^6} = 14.32 \text{ mH}$$

$$C_2 = \frac{1}{\pi R_o (f_{c_2} - f_{c_1})} = 0.078 \mu F$$

$$= \frac{1}{\pi \times 900 (7.5 - 3) \times 10^3}$$

