

Unit-II

Page _____ Date _____

25/Aug/17

→ Solⁿ of Differential Eqⁿs -I) First order & second order homogeneous eqⁿ -

$$\frac{dy(x)}{dt} + y(t) = 0$$

↓ ↓

$$\text{replace } D + 1 = 0$$

$$P_1 = -1$$

$$\begin{aligned} C.F. &= k e^{P_1 t} \\ C.F. &= k e^{-t} \end{aligned}$$

$$\frac{d^2 y(x)}{dt^2} + 3 \frac{dy(x)}{dt} + 2y(t) = 0$$

$$D^2 + 3D + 2 = 0$$

$$(D+1)(D+2) = 0$$

$$P_1 = -1, P_2 = -2$$

$$\begin{aligned} C.F. &= k_1 e^{P_1 t} + k_2 e^{P_2 t} \\ &= k_1 e^{-t} + k_2 e^{-2t} \end{aligned}$$

II) First/second order Non-homogeneous eqⁿ containing constant or exponential fn on right hand side -

Exponential fn

Case I: Constant on right side

Also put RHS = 0

Find P₁ and C.F.

$$\text{Sol}^n = P_1 + C.F.$$

$$\text{eg. } \frac{dy(t)}{dt} + y = 5e^{2t} / e^{at}$$

$$A.E. \quad D + 1 = 0$$

$$D = -1$$

$$1) C.F. = k e^{-t}$$

$$2) P.I. = \underline{5e^{2t}}$$

$$D + 1$$

Replace D by 2 (i.e. replace D by a for e^{at})

Date: _____

$$\Rightarrow P.I. = \frac{5e^{2t}}{D+1} = \frac{5e^{2t}}{3}$$

$$\text{Now, } y = CF + PI = ke^{-t} + \frac{5e^{2t}}{3}$$

$$\text{eg. } \frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = e^{2t}$$

$$A.E \Rightarrow D^2 + 3D + 2 = 0$$

$$(D+1)(D+2) = 0$$

$$D = -1, -2$$

$$\text{Now, } P.I. = \frac{e^{2t}}{D^2 + 3D + 2}$$

$$\text{Put } D =$$

II] Constant on RHS -

$$\text{eg. } \frac{dy}{dt} + y = 5$$

$$A.E] D+1=0$$

$$D = -1$$

$$C.F = k e^{-t}$$

$$P.I. = \frac{5}{D+1} e^{ot}$$

$$\text{eg.) } \frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = 5$$

$$A.E: D^2 + 3D + 2 = 0$$

$$D = -1, -2$$

$$P.I. = \frac{5}{D^2 + 3D + 2} e^{ot}$$

$$D^2 + 3D + 2$$

$$\text{Put } D=0$$

$$\Rightarrow P.I. =$$

Type 3: First & second order Non-homogeneous eqⁿ with:
RHS as a sine or cosine fn.

$$\text{eg. } \frac{dy}{dt} + yt = \sin 5t$$

$$A-E \Rightarrow D+1=0$$

$$D = -1$$

$$C.F. = K e^{-t}$$

$$P.I. = \frac{\sin 5t}{D+1}$$

Replace D^2 by $-a^2$,

To do so, we need to make $D \rightarrow D^2$,

\therefore Rationalizing the fraction,

$$= \frac{\sin 5t}{(D+1)(D-1)}$$

$$= \frac{(D-1) \sin 5t}{D^2 - 1}$$

$$\text{Put } D^2 = -a^2 = -(5)^2$$

$$= (D-1) \sin 5t$$

$$-25-1$$

$$= (D-1) \sin 5t$$

$$-26$$

Equating $D = \frac{d}{dt}$,

$$P.I. = \frac{d}{dt} \left(\frac{\sin 5t}{-26} \right) - \frac{\sin 5t}{(-26)}$$

$$= -\frac{1}{26} 5 \cos 5t + \frac{\sin 5t}{26}$$

$$P.I. = \frac{\sin 5t}{26} - \frac{5 \cos 5t}{26}$$

and, $\{y = C.F. + P.I.\}$

2nd Order - non-homogeneous differential equation
with constant coefficients

$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = \sin 5t$$

$$D^2 + 3D + 2 = 0$$

$$P.I. = \underline{\sin 5t}$$

$$D^2 + 3D + 2$$

$$\text{Put } D^2 = -(5)^2$$

$$= \underline{\sin 5t}$$

$$-25 + 3D + 2$$

$$= \underline{\sin 5t}$$

$$3D - 23$$

$$= \underline{\sin 5t} \times (3D + 23)$$

$$(3D - 23) (3D + 23) - C$$

$$= (3D + 23) \underline{\sin 5t} (1-C) (1+C)$$

$$9D^2 - 529$$

$$= (3D + 23) \underline{\sin 5t}$$

$$-225 - 529$$

Again equate $D = \frac{d}{dt}$ & solve $(1-C)$

→ Circuit Analysis by Classical Method-

Transient Response - Whenever a circuit is switched from one condition to another, then there is a transition period during which the current & voltage change from former values to new one. This period is known as 'Transition time' & the value of current & voltage are known as 'Transient Response'.

Steady State Response - When the transient period is over OR the transition has died out, the circuit is said to be in steady state.

Zero Input response

Zero Input Response - The value of current & voltage which results from initial condition when applied input is zero.

Zero State Response - The values of current & voltage for an input which is applied when all the initial conditions are zero. Such networks/circuits are said to be at rest.

→ Order of Differential Eqⁿ-

If a circuit contains only one storage element (L or C) \Rightarrow 1st order
 " two " \Rightarrow 2nd order

- The circuit changes are assumed to occur at time $t=0$ & represented by a switch.
- Switching ON/OFF at $t=0$ does not disturb the storage elements so that $I(0^-) = I(0^+)$.

In case of capacitor $V_C(0^-) = V_C(0^+)$

→ Voltage-current relationship for storage elements -

$$1) V = IR, I = \frac{V}{R}$$

$$2) V_L(t) = L \frac{dI_L(t)}{dt} \quad ; \quad I(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$

$$\text{or } I(t) = \frac{1}{L} \int_0^t V_L(t) dt + I_L(0^-)$$

$$3) V_C(t) = \frac{1}{C} \int_{-\infty}^t I_C(t) dt \quad ; \quad I_R(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$= \frac{1}{C} \int_0^t I_C(t) dt + V_C(t)$$

→ Initial / Boundary conditions in a circuit -


Circuit Element Eq. ckt at $t=0^+$ Eq. ckt. at $t=\infty$



$$\begin{array}{c} \bullet \\ \bullet \end{array} \text{ o/c}$$

$$\text{s/c}$$

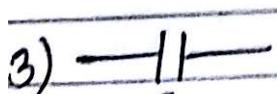
$$V_L = \infty \quad I = I_{\max}, \text{ Voltage drop} = 0$$




$$\text{s/c}$$

$$\begin{array}{c} \bullet \\ \bullet \end{array} \text{ o/c}$$

$$I_C = C \frac{dV_C(t)}{dt} \Big|_{t=0}$$

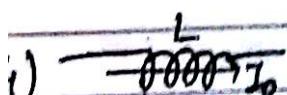

$$\text{ (clockwise arrow)}$$

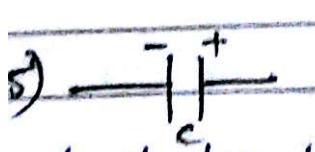


$$\begin{array}{c} \text{+} \\ \text{-} \end{array}$$

→ Circuit Analysis

Now calculate $i(0^+)$, $\frac{di}{dt}(0^+)$, $\frac{d^2i}{dt^2}(0^+)$, $i(t)$

transient response

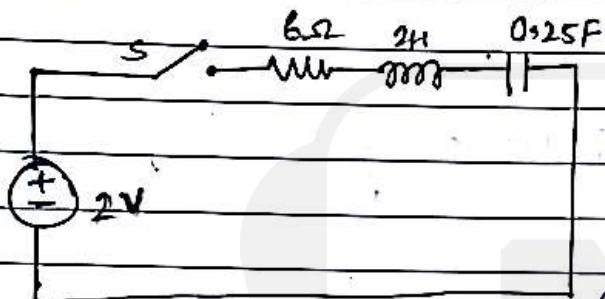of a given circuit where source is of 2V and resistance is of 6Ω.
 Inductor = 2H, capacitor = 0.25F when the switch S is closed at time $t=0$.



Applying KVL,

$$V_s = 6i(t) + 2\frac{di}{dt} + \frac{1}{C} \int_{0^+}^t i(t) dt + V_c(0^-)$$

$$2 = 6i(t) + 2\frac{di}{dt} + \frac{1}{0.25} \int_{0^+}^t i(t) dt + V_c(0^-)$$

— ① (no initial charge)

$$2 = v(t)16 + 16 \int_{0^+}^t v(t) dt + 4 \frac{dv(t)}{dt}$$

$$2 = 4 \frac{d(v(0^+))}{dt} \Rightarrow \frac{dv(0^+)}{dt} = \frac{1}{2}$$

Double diff.,

$$0 = 16 \frac{d^2v(t)}{dt^2} + 1 - v(t)dt + \frac{d^2v(t)}{dt^2}$$

$$0 = \frac{d^2v(t)}{dt^2} + 0 + 4 \cancel{\frac{d^2v(t)}{dt^2}} - 4 \frac{d^2v(t)}{dt^2}$$

$$\frac{d^2v(t)}{dt^2} = -2$$

Applying KVL,

$$V = R^i(t) + L \frac{di}{dt}$$

$$V = R^i + L D i$$

$$LD + R = 0$$

~~$$D = \frac{R}{L} - \frac{i}{L}$$~~

$$\Rightarrow i(t) = K e^{-\frac{Rt}{L}} + \frac{V}{R}$$

~~$$C.F. = K e^{\frac{Rt}{L}}$$~~

~~$$-Rt$$~~

~~$$K e$$~~

~~$$P.I. =$$~~

~~$$LD + R$$~~

~~$$\text{Put } D = 0$$~~

~~$$= \frac{V}{R + L} = \frac{V}{R}$$~~

XApplying $i(0^+) = 0$ Because at $t=0^+$, L behaves as open ckt. (initial cond'n)Putting $t = 0^+$,i.e. at $i(0^+)$

$$\text{eqn ① becomes, } 2 = 6i(0^+) + 4 \int_0^t i(0^+) dt + 2 \frac{di(0^+)}{dt}$$

$$2 = 2 \frac{di(0^+)}{dt}$$

$$\text{or } \boxed{\frac{di(0^+)}{dt} = 1} \quad \text{--- ②}$$

Double diff. of eqn ①,

$$0 = 6 \frac{di(t)}{dt} + 2 \frac{d^2 i(t)}{dt^2} + 4i(t) \quad \text{--- ③}$$

$$\text{Put } \frac{d}{dt} = D,$$

$$\text{Q3} \quad 6Di + 2D^2(i) + 4(i) = 0$$

$$\text{or} \quad 3D + D^2 + 2 = 0$$

$$D^2 + 3D + 2 = 0$$

$$(D+1)(D+2) = 0$$

$$D = -1, D = -2$$

Now, $C.F = k_1 e^{-D_1 t} + k_2 e^{-D_2 t}$
 $i(t) = k_1 e^{-t} + k_2 e^{-2t} \quad \text{--- (iv)}$

Apply initial condition in eqⁿ (iv), [To determine values of k_1 & k_2]

i.e. $t=0$

$$i(0^+) = k_1 + k_2 \quad \text{--- (v)}$$

Diff. eqⁿ (iv) w.r.t. t,

$$\frac{di(t)}{dt} = -k_1 e^{-t} - 2k_2 e^{-2t}$$

Put $t=0$,

$$\frac{di(0^+)}{dt} = -k_1 - 2k_2$$

→ L (from (v))

$$1 = -k_1 - 2k_2$$


$$\text{and, } \frac{0 = k_1 + k_2}{1 = -k_2}$$

$$\Rightarrow k_1 = 1, k_2 = -1$$

Putting these values in eqⁿ. (iv),

$$i(t) = e^{-t} - e^{-2t}$$

Date _____

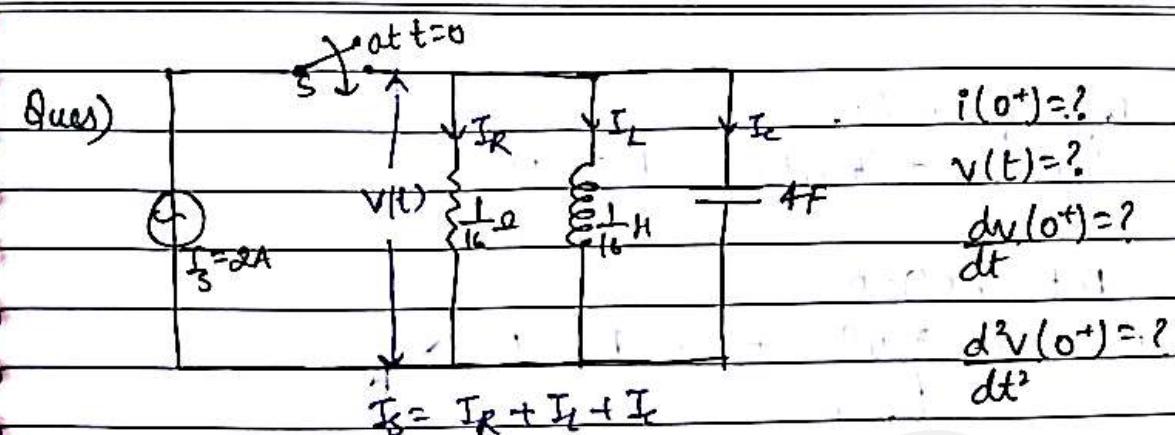

Applying KCL,

$$\frac{I}{I_s} = \frac{V(t)}{R} + \frac{1}{L} \int_0^t V(t) dt + I_c(0^+) + C \cdot \frac{dv(t)}{dt}$$

Since all three elements are connected in parallel, voltage across each is same.

$$\Rightarrow \frac{I}{I_s} = 16V(t) + 16 \int_0^t V(t) dt + 4 \frac{dv(t)}{dt} \quad \text{--- (1)}$$

At initial condⁿ, C acts as short circuited element.

$$\Rightarrow R_c = 0$$

 \Rightarrow entire current flows through this branch \Rightarrow Voltage across $s/c = 0$.

$$\Rightarrow v(0^+) = 0$$

Putting $v(0^+) = 0$ in eqⁿ (1),

$$I = 0 + 0 + 4 \frac{dv(0^+)}{dt}$$

or
$$\frac{dv(0^+)}{dt} = \frac{1}{2} \quad \text{--- (11)}$$

Date _____

Double diff. of eqⁿ ①,

$$0 = 16 \frac{dv(t)}{dt} + 16v(t) + \frac{4d^2v(t)}{dt^2}$$

$$\text{Put } v(0^+) = 0$$

$$0 = 16 \cdot \frac{dv(0^+)}{dt} + 0 + \frac{4d^2v(0^+)}{dt^2}$$

$$\frac{dv(0^+)}{dt} = \frac{1}{2}$$

$$0 = 8 + \frac{4d^2v(0^+)}{dt^2}$$

$$\Rightarrow \left[\frac{d^2v(0^+)}{dt^2} = -2 \right]$$

~~0 = 16~~ Diff. eqⁿ ①,

$$0 = 16 \frac{dv(t)}{dt} + 16v(t) + \frac{4d^2v(t)}{dt^2}$$

$$0 = 16D + 4D^2 + 16$$

$$\text{or } D^2 + 4D + 4 = 0$$

$$(D+2)^2 = 0$$

$$\text{or } D = -2$$

$$CF = k_1 e^{-Dt} + k_2 t e^{-Dt}$$

$$v(t) = k_1 e^{-Dt} + t k_2 e^{-Dt} \quad \text{(iii)}$$

Applying initial condⁿ, $t=0^+$ $v(0^+) = 0$

$$v(0^+) = k_1 + 0k_2$$

$$\boxed{k_1 = 0}$$

Diff. eqⁿ w.r.t. t,

$$\frac{dv(t)}{dt} = -2k_1 e^{-Dt} t + (k_2 e^{-Dt} + -2k_2 t e^{-Dt})$$

Date _____

Again put $t=0^+$,


$$\frac{dv(0^+)}{dt} = -\alpha k_1 + k_2$$

$$\text{or } \left| \frac{1}{2} = k_2 \right.$$

from (1) {

$$\Rightarrow v(t) = \frac{1}{2} t e^{-\alpha t}$$

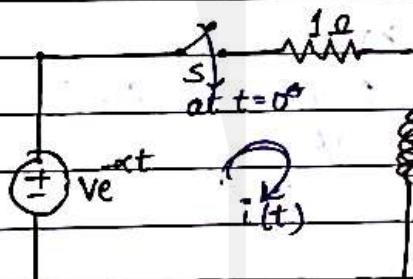Ques) For a given ckt., voltage source is an exponential fn $v(t) = ve^{-\alpha t}$
 where α is constant, the switch S is closed at $t=0$, $R=1\Omega$,
 $L=1H$. The ckt. is shown below. Calculate $i(t)$.



Applying KVL,

$$ve^{-\alpha t} = i(t)R + L \frac{di(t)}{dt}$$

$$\Rightarrow ve^{-\alpha t} = i(t) + \frac{di(t)}{dt} \quad \text{--- (1)}$$

$$\text{or } D = D + 1$$

$$D = -1$$

$$\therefore CF = ke^{-t}$$

$$\text{P.I.} = ve^{-\alpha t}$$

$$\text{or } i(t) = ke^{-t} + \frac{ve^{-\alpha t}}{1-\alpha} \quad \text{--- (II)}$$

Put $t=0$,

$$0 = K + V$$

$$\text{or } K = V$$

$$\Rightarrow i(t) = \frac{ve^t}{\alpha-1} + \frac{ve^{-t}}{1-\alpha}$$


Ques) Calculate the current i_1, i_2 and voltage v_i of the given network.

i) at $t=0^+$

iii) at $t=\infty$

ii) at $t=0^-$

iv) at $t=50\text{ms}$

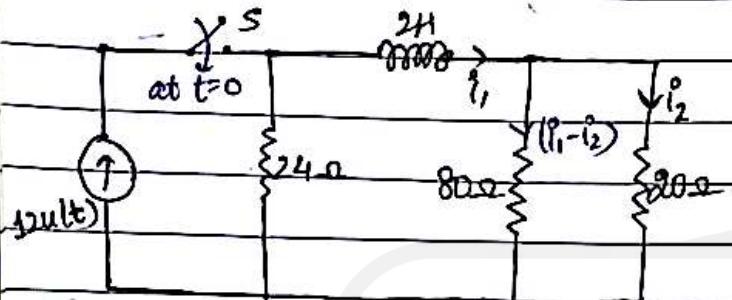


Since input voltage signal is an unit signal (which exists only for $t \geq 0$),

$$\Rightarrow i_1(0^-)=0, i_2(0^-)=0 \\ v_i(0^-)=0$$

Applying KVL, Also at $t=0^+$, L behaves as open ckt.

$$i_1(0^+)=0; i_2(0^+)=0$$

Simplified ckt:

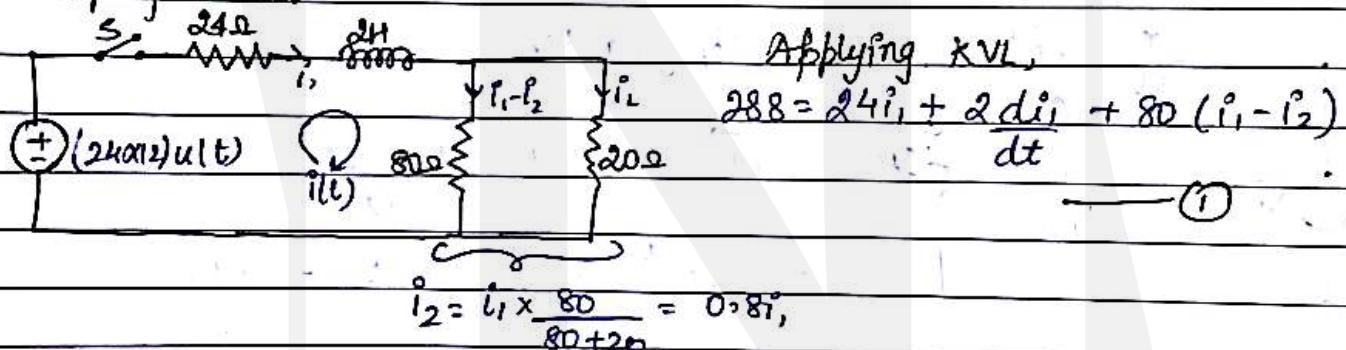

Applying KVL,

$$288 = 24i_1 + 2 \frac{di_1}{dt} + 80(i_1 - i_2) \quad \text{--- (1)}$$

$$i_2 = i_1 \times \frac{80}{80+20} = 0.8i_1$$

$$\Rightarrow \text{eqn (1)} \text{ becomes, } 288 = 24i_1 + 2 \frac{di_1}{dt} + 80(i_1 - 0.8i_1)$$

$$288 = 24i_1 + 2 \frac{di_1}{dt} + 16i_1$$

$$144 = 20i_1 + \frac{di_1}{dt}$$

$$\text{Now, } D + 20 = 0$$

$$D = -20$$

$$\text{Now, } \underline{\underline{i_1}} = k e^{-20t}$$

$$P.I. = \frac{144}{20} = 7.2$$

$$i(t) =$$

$$\text{Now, } i_1(t) = k e^{-20t} + 7.2$$

$$\text{at } t=0^+, i(0^+) = 0$$

$$0 = k + 7.2$$

$$\Rightarrow k = -7.2$$

$$i_1(t) = -7.2 e^{-20t} + 7.2$$

$$\text{Now, at } t=\infty, i_1(\infty) = -7.2 e^{-\infty} + 7.2 = 7.2$$


$$i_1(\infty) = 7.2 \text{ mA}$$

$$\text{and, } i_2(t) = \frac{4}{5} i_1$$

$$\therefore i_2(\infty) = \frac{4}{5} \times 7.2 = 5.76$$

Ques) Consider a series RL ckt. excited by sinusoidal voltage

$$v(t) = V_m \sin(\omega t + \phi)$$

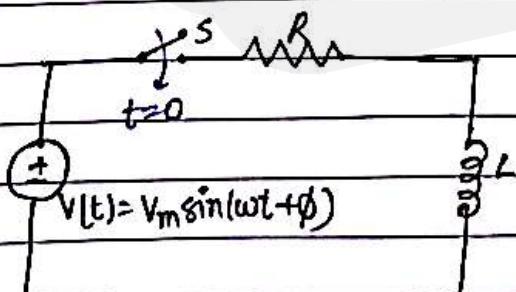

Applying KVL,

$$v(t) = iR + L \frac{di}{dt}$$

$$V_m \sin(\omega t + \phi) = R i + \frac{L}{L} \frac{di}{dt}$$

$$R i + D i = 0$$

$$\Rightarrow D = -R/L$$

Date: _____

$$CF = ke^{-\frac{R}{L}t}$$


$$P.I. = \frac{V(t)}{(D-R_L)} - \frac{(D-R_L)}{(D+R_L)}$$

$$= \frac{(D-R_L) V(t)}{D^2 - (R_L)^2}$$

Replace D^2 with $-w^2$,

$$i(t) = ke^{-\frac{R}{L}t} - \frac{V_m}{R^2 + w^2 L^2} [wL \cos(wt + \phi) - R \sin(wt + \phi)]$$

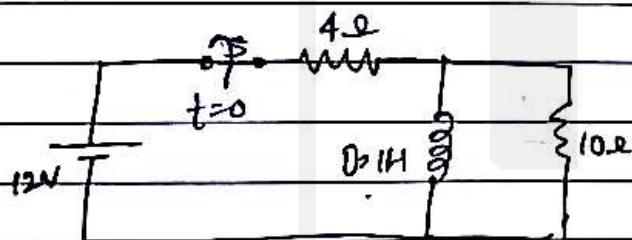(Ques) A 12V battery is suddenly disconnected at $t=0$. Find the inductor current at $t=0$ and $V_L(t)$.



at $t=\infty$, L behaves as short circuit
 \Rightarrow no current flows through 10Ω

$$\Rightarrow P = \frac{12}{4} = 3A$$

Applying KVL at $t=0^-$,

Ques)

→ Solutions of Circuits Using Laplace Transform

$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y(t) = 5u(t) \quad \text{--- (1)}$$

Taking Laplace transform on both sides,

$$L\left(\frac{d^2y}{dt^2}\right) = s^2Y(s) - sy(0^+) - y'(0^+)$$

$$L\left(\frac{dy}{dt}\right) = sY(s) - y(0^+)$$

$$Ly(t) = Y(s)$$

$$L\{5u(t)\} = \frac{5}{s}$$

∴ Eqⁿ (1) becomes,

$$s^2Y(s) - sy(0^+) - y'(0^+) + 3sY(s) - 3y(0^+) + 2Y(s) = \frac{5}{s}$$

--- (11)


Given that: Value of $y(0^+) = -1$

$$y'(0^+) = 2$$

∴ Eq^m (11) becomes,

$$s^2Y(s) - s(-1) - (2) + 3sY(s) + 2Y(s) = \frac{5}{s}$$

$$\text{or } Y(s)[s^2 + 3s + 2]$$

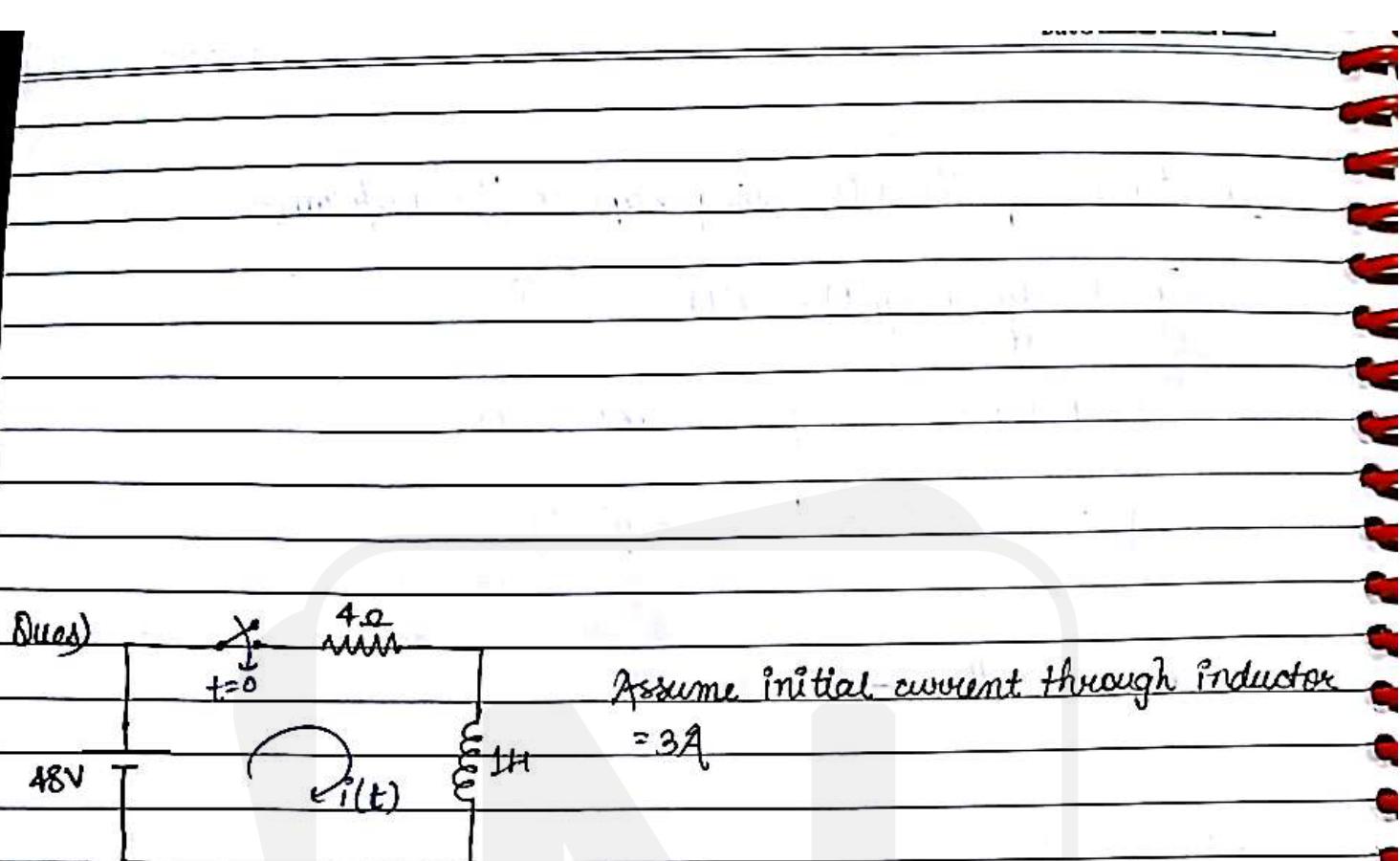

Applying KVL,

$$48 = 4i(t) + \frac{di(t)}{dt} \quad \text{--- (1)}$$

Taking Laplace on both sides,

$$\frac{48}{s} = 4I(s) + sI(s) - i(0^+)$$

$$\frac{48}{s} = (s+4)I(s) - 3$$

$$I(s) = \frac{3s+48}{s(s+4)}$$

$$= \frac{A}{s} + \frac{B}{s+4}$$


$$= \frac{12}{s} - \frac{9}{s+4}$$

$$I(t) = 12 - 9e^{-4t} \quad \rightarrow \text{Applying Inverse LT,}$$

Page _____

Date _____

Ques)

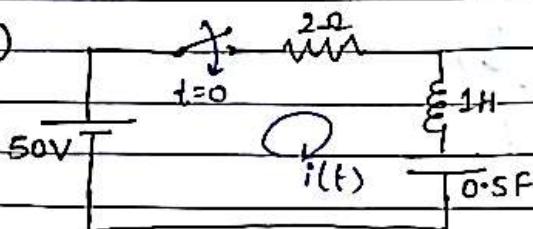

$$50 = 2i(t) + \frac{di(t)}{dt} + 2 \int_0^t i dt$$

Applying Laplace,

$$2I(s) + [sI(s) - i(0^+)] + 2 \frac{I(s)}{s} = 50$$

$$I(s) [2 + s + \frac{2}{s}] = \frac{50}{s}$$

$$I(s) [s^2 + 2s + 2] = 50$$


$$\text{or } I(s) = \frac{50}{s^2 + 2s + 2}$$

$$= \frac{50}{(s+1)^2 + 1^2}$$

Applying Inverse LT,

$$= 50(\sin t)e^{-t}$$

Ques)

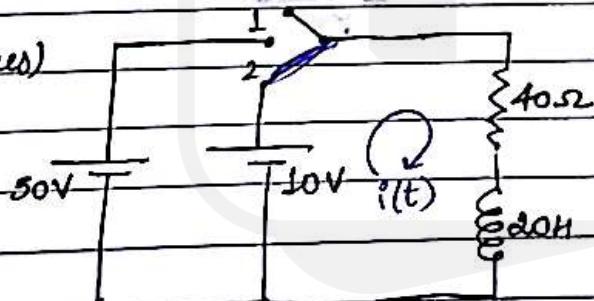

Switch is held in pos. 1 for a long time, then it is moved to pos. 2.

$$i(0^+) = i(0^-) = \frac{50}{4} = \frac{50}{4}$$

Applying KVL,

$$10 = 10i(t) + 10 \frac{di(t)}{dt}$$

Applying LT,

$$10 = \frac{10I(s)}{s} + 10[sI(s) - i(0^+)]$$

Date: _____

$$\frac{10}{s} = 40I(s) + 20sI(s) - 20\left(\frac{5}{4}\right)$$

$$\frac{10}{s} + 25 = I(s)[40 + 20s]$$

$$\frac{25s + 10}{20s^2 + 40s} = -I(s)$$

$$I(s) = \frac{5s + 2}{4s(s+2)}$$

Applying partial fraction,


$$I(s) = \frac{1}{4s} + \frac{1}{s+2}$$

Applying ILT,

$$i(t) = \frac{1}{4} + e^{-2t}$$

Ques) Find the current $i(t)$ if the voltage source is $v(t) = 2e^{-t/2}$
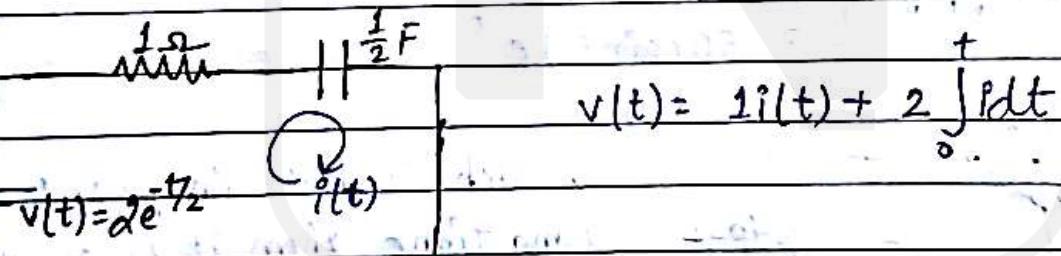
$$v_c(0^-) = 0, R = 1, C = \frac{1}{2} F$$



$$v(t) = 1i(t) + 2 \int_0^t i(t) dt$$