

Circuits & Systems

Page _____ Date _____
Page 1 Date 02 Aug 17

Signal - A physical quantity which can be a function of one or more variables like frequency, temp., pressure.
 It represents a physical phenomenon.

System - A physical entity which gives set of outputs after processing their input.
 System can be hardware or software.

→ Classification of signals -

I) Discrete time and Continuous time signal -

A signal is said to be continuous time signal if it is defined for all the continuous values of time variable ' t '

A discrete time signal is defined only for some specific instants of time variable ' n '.

It can have values only for integer instants of time variable ' n '.

II) Continuous value and Discrete value signals -

Continuous valued functions can have any value b/w $-\infty$ to $+\infty$; whereas discrete valued can have value within a particular specified range.

III) Deterministic and Random signals -


Deterministic signals are ones whose nature and amplitude can be predicted whereas this probable prediction is not possible for random signals. Only the probability function can be predicted.

Unit RAM signal - represented by g_u

$$g_u(t) = 0, \text{ for } t < 0 \\ = t, \text{ for } t \geq 0$$


GATE Signal - Rectangular pulse of unit height starting at $t=a$ and ending at $t=b$

$$G_{a,b}(t) =$$

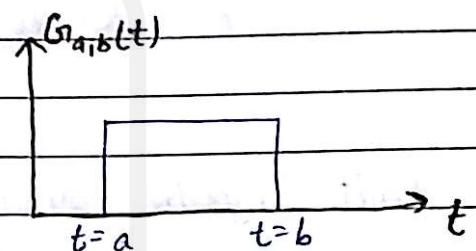

$$G_{a,b}(t) = u(t-a) - u(t-b)$$

end point

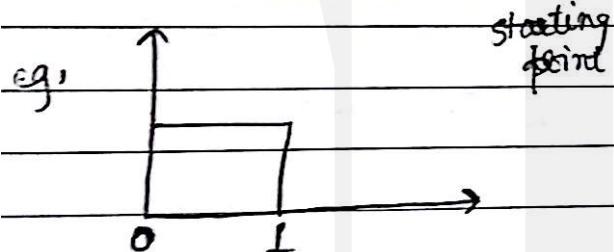

$$u(t-0) - u(t-1)$$

$$G(t) = u(t+4) - u(t-4)$$

→ Transformation of signals -



signals can be transformed by 3 processes -

- i) Time shifting
- ii) Time scaling
- iii) Time reversal

Time shifting - Signal can be time shifted by replacing time variable t with $(t-t_0)$, where t_0 is known as shifting factor

If $t_0 > 0$, signal is right-shifted and this operation results in delay of the signal by t_0 .

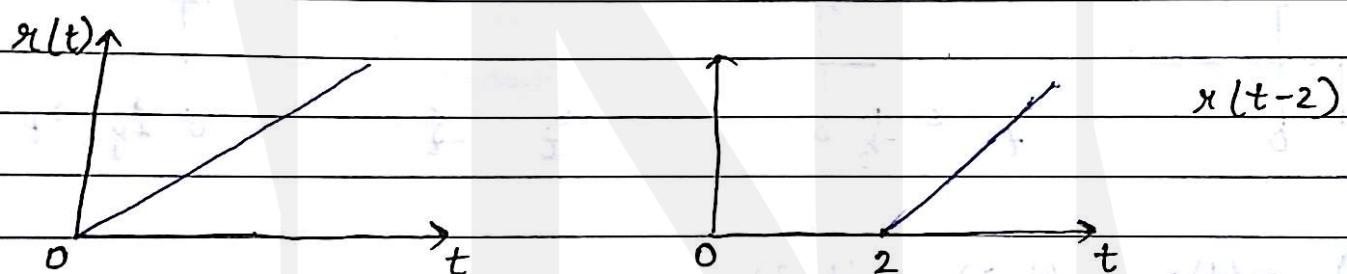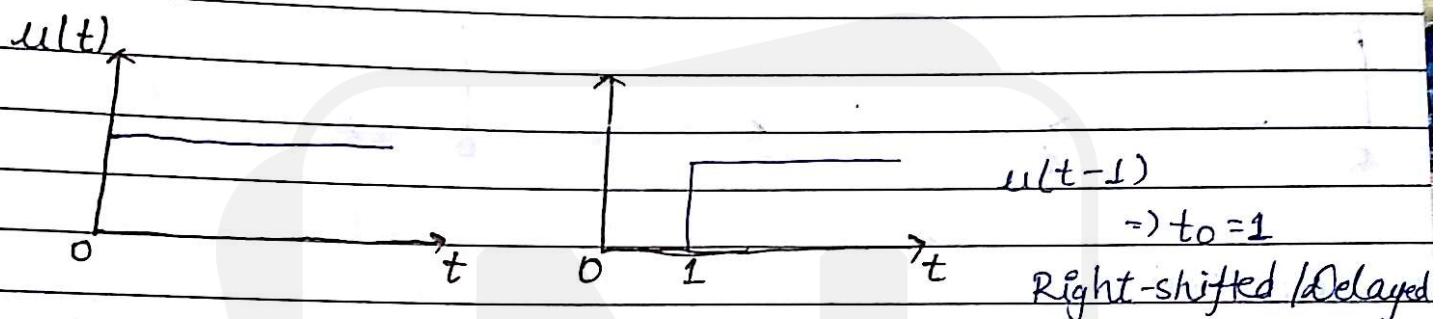
If $t_0 < 0$, signal is left-shifted and this operation results in advancement of the signal by t_0 .




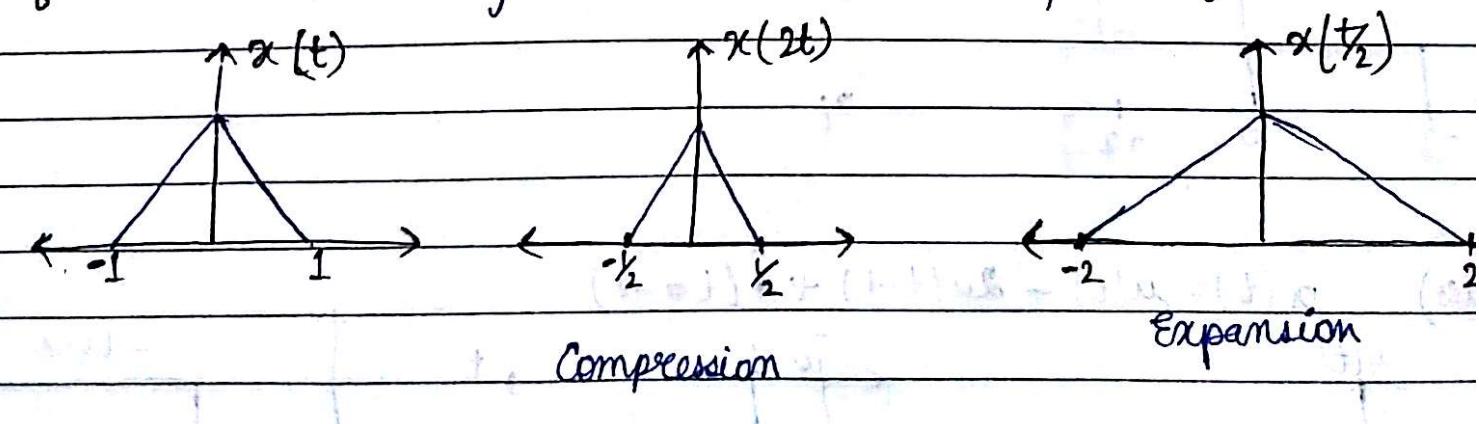
2) Time Scaling - Replace t by at , where a is scaling factor
a cannot be zero

If $a > 1$, scaling results in compression of the signal


If $0 < a < 1$, scaling results in expansion of the signal




#SSR - Shift shifting, Scaling, Reversal

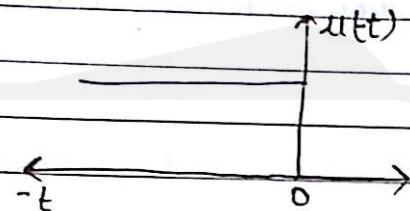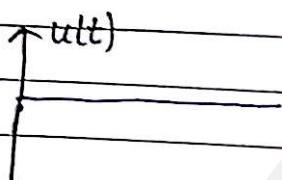Page _____
Date _____3) Time Reversal - Replace t by $-t$ Result of this operation is known as Folding / Reflection / Time reversal about the time origin $t=0$.# Mirror image about y -axis


Ques) $u(-2t+1)$

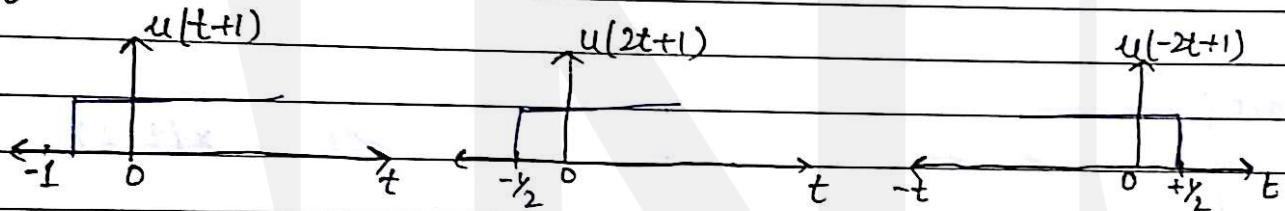


Ques) $x(t) = u(t-2) + u(t+3)$

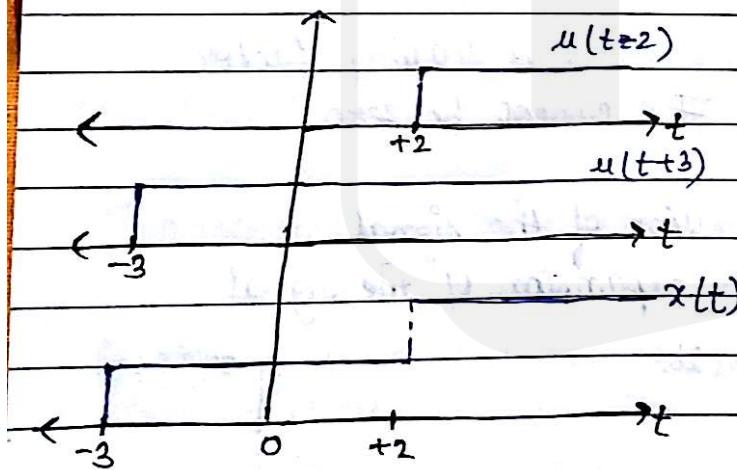



Ques) $x(t) = u(t) - 2u(t-1) + u(t-2)$

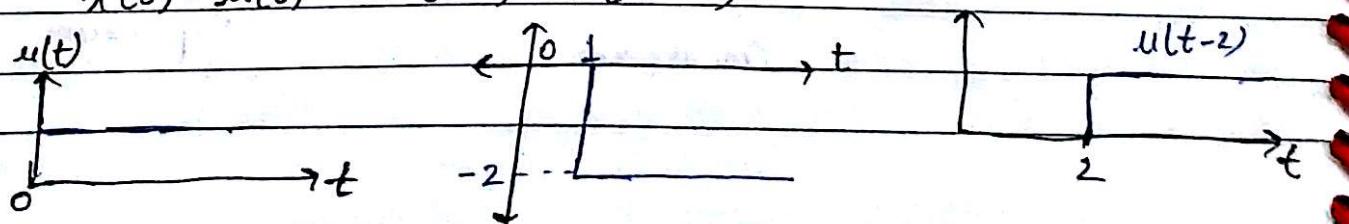

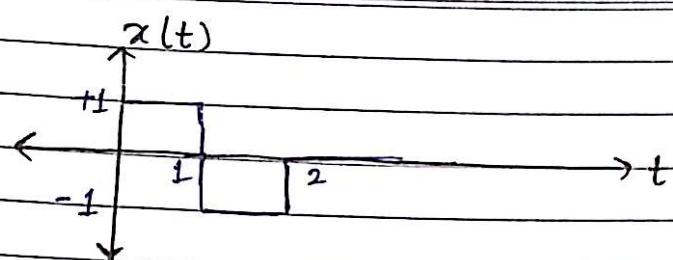

Ques) Draw the given signal -


$$x(t) - x(t-1) = x(t)$$

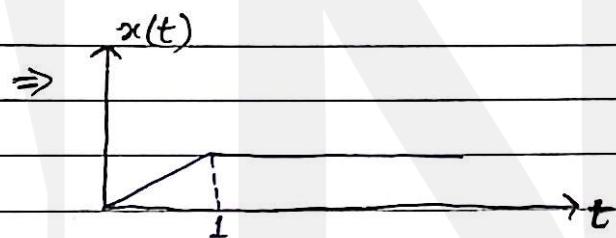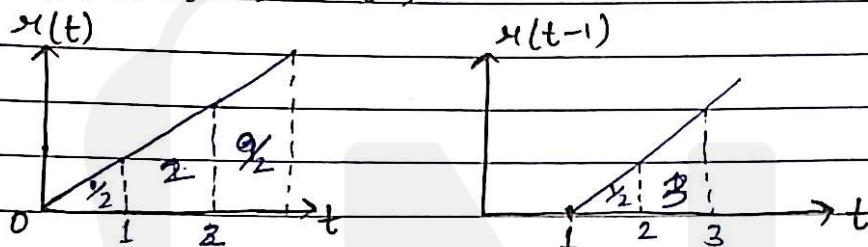


Ques) $x(t) = x(t) - x(t-1) - u(t-1)$



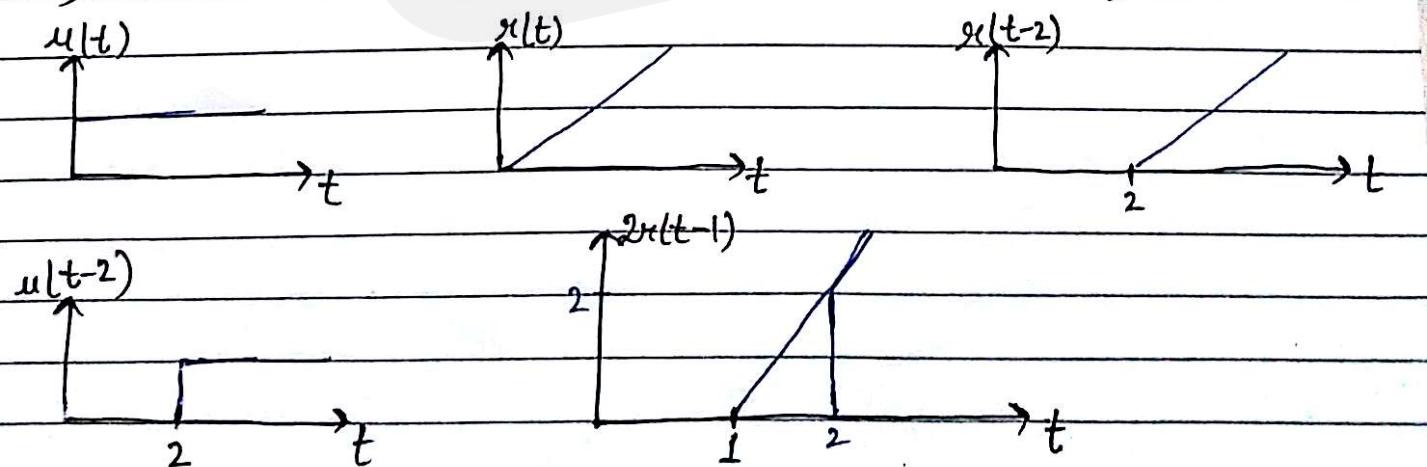Ques) $x(t) = u(t) + x(t) - 2x(t-1) + x(t-2) - u(t-2)$



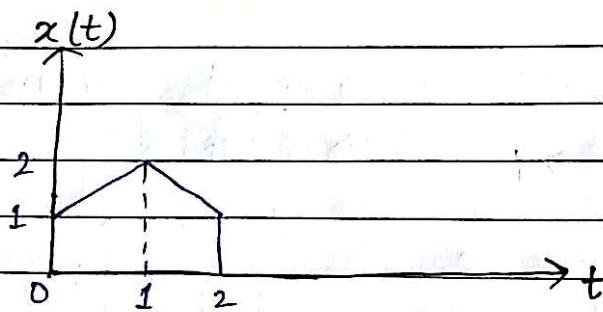

→ Causal, Anti-causal & Non-causal Signals

A signal is said to be a "Causal signal" if it has values for $t \geq 0$


Anti-causal signals that have values only for negative values of time variable 't' or 'n':

OR

For discrete signals, anti-causal signals are those signals that have values ranging from $-\infty$ to -1 .

e.g. $u(t+1)$


eg.

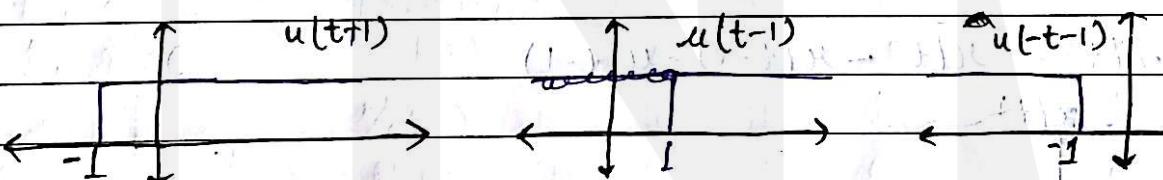


Non-causal signals - Can have values for all possible values for time variable 't' i.e. $(-\infty, \infty)$

Ques) Check for the causality of given signals-

(i) $u(n+3) - u(n-2)$

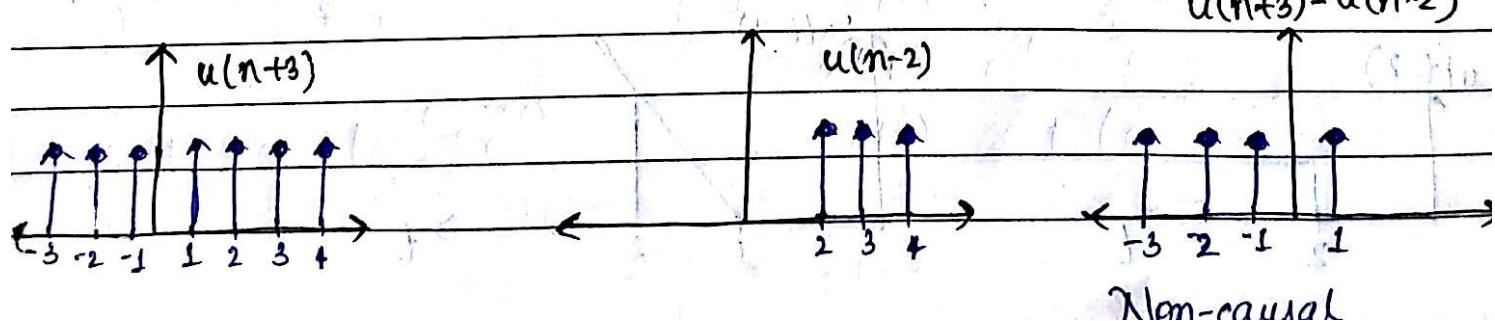

Ques) $u(2t+1)$

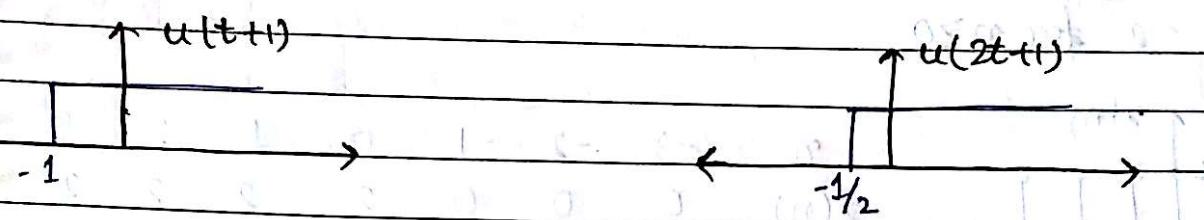

→ Even & Odd signals-

Even signals - symmetrical about vertical axis

$$\text{i.e. } x(t) = x(-t) \quad \text{eg. cost}$$

Odd signals - not symmetrical about vertical axis

$$\begin{cases} x(t) \neq x(-t) \\ x(-t) = -x(t) \end{cases} \quad \text{eg. sint}$$

e^n of even fn, n is even
odd fn, n is odd

1) Even + Even = Even

2) Odd + Odd = Odd

3) Even * Even = Even

4) Odd * Odd = Even

5) Even + Odd = Neither even nor odd

→ calculation of even & odd part of a signal-


$$x_e(t) = \frac{x(t) + x(-t)}{2}$$

$$x_o(t) = \frac{x(t) - x(-t)}{2}$$

For discrete signals, replace 't' with 'n'.

Date: 11/11/11

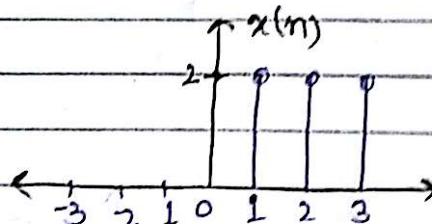e.g. $x(n) = 0 \text{ for } n < 0$
 $= 2 \text{ for } n \geq 0$



n	-3	-2	-1	0	1	2	3
$x(n)$	0	0	0	2	2	2	2
$\sqrt{x(-n)}$	2	2	2	2	0	0	0
$x(-n)$	0	0	0	2	2	2	2
$x_e(n)$	0	1	1	1	2	1	1
$x_o(n)$	-1	-1	-1	0	1	1	1

$$x_e(n) = \begin{cases} 0^{\frac{1}{2}}, & n < 0 \text{ & } n \geq 0 \\ 2^{\frac{1}{2}}, & n = 0 \end{cases}$$

$$x_o(n) = 0, \text{ for all } n = 0$$

$$= -1, \quad n < 0$$

$$= 1, \quad n > 0$$

Ques) Obtain the odd & even part of signal $u(n)$.

n	-3	-2	-1	0	1	2	3
$u(n)$	0	0	0	1	1	1	1
$u(n) = \begin{cases} 0, & n < 0 \\ 1, & n \geq 0 \end{cases}$	0	0	0	1	1	1	1
$u(-n)$	0	0	0	1	1	1	1
$u_e(n)$	0	0	0	1	1	1	1
$u_o(n)$	0	0	0	0	0	0	0

$$u_n(e) = \begin{cases} 0^{\frac{1}{2}}, & n < 0 \\ \frac{1}{2}, & n \geq 0 \\ 1^{\frac{1}{2}}, & n = 0 \end{cases}$$

$$u_o(n) = 0 \quad \forall n$$

$$\frac{1}{2}, \quad n < 0$$

$$0, \quad n = 0$$

$$\frac{1}{2}, \quad n \geq 0$$

Ques) Calculate even & odd part for $x(t) = e^{-2t} \cos t$

$$x(-t) = e^{2t} \cos t$$

$$x_e(t) = \cos t (e^{-2t} + e^{2t})$$

$$x_e(t) = \cos t (e^{-2t} + e^{2t})$$

2.

Ques) Obtain even & odd part for $y(n)$

$$y(n) = -1, n < 0$$


$$1, n=0$$

$$2, n > 0$$

n	-3	-2	-1	0	1	2	3
$y(n)$	-1	-1	-1	1	2	2	2
$y(-n)$	2	2	2	1	-1	-1	-1

$y_e(n)$	$\frac{1}{2}$	$\frac{1}{2}$	$\frac{1}{2}$	1	$\frac{1}{2}$	$\frac{1}{2}$	$\frac{1}{2}$
$y_o(n)$	$-\frac{3}{2}$	$-\frac{3}{2}$	$-\frac{3}{2}$	0	$\frac{3}{2}$	$\frac{3}{2}$	$\frac{3}{2}$


→ Waveform Synthesis

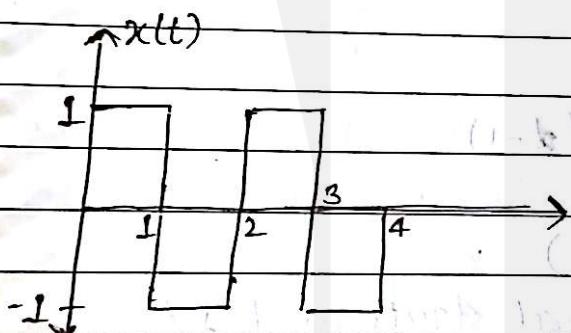

$$x(t) = 1[u(t-0) - u(t-1)] + (-1)[u(t-1) - u(t-2)] + 1[u(t-2) + u(t-3)] \\ + (-1)[u(t-3) - u(t-4)]$$

$$= u(t) - u(t-1) - u(t-1) + u(t-2) + u(t-3) - u(t-3) + u(t-4)$$
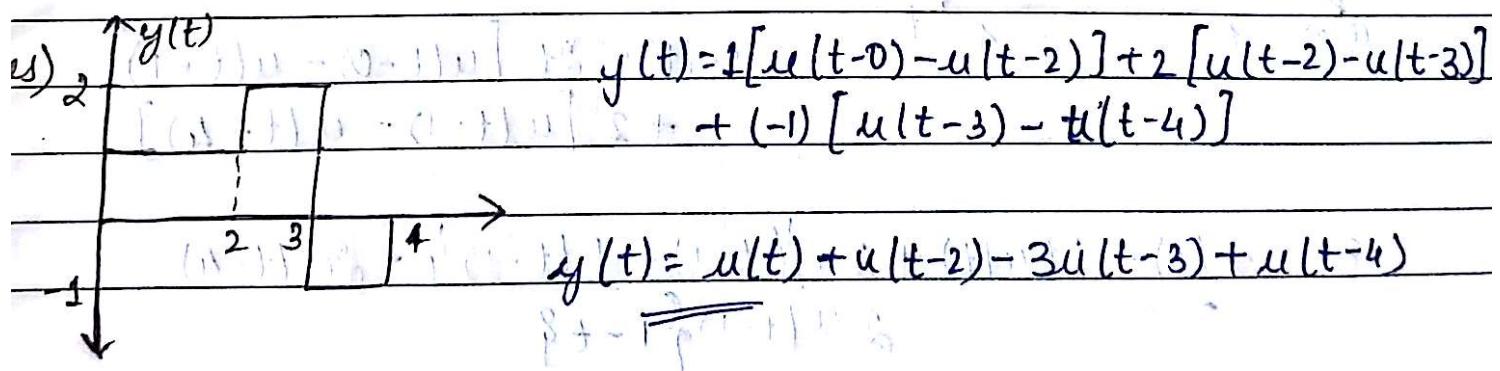
$$\underline{x(t) = u(t) - 2u(t-1) + 2u(t-2) + u(t-4)}$$



$$x(t) = u(t-1) + u(t-2) - u(t-3) - u(t-4)$$

$$x(t) = u(t-1) - u(t-2) + 2[u(t-3) - u(t-4)]$$


$$x(t) = u(t-1) - u(t-2) - u(t-3) + 2[u(t-4) - u(t-5)]$$

$$\Rightarrow x(t) = k(t-1) [u(t-1) - u(t-2)]$$

And the gate signal starts at $t=1$ & ends at $t=4$

$$x(t) = k(t-1)$$

$$x(t) = k - o(t-1)$$

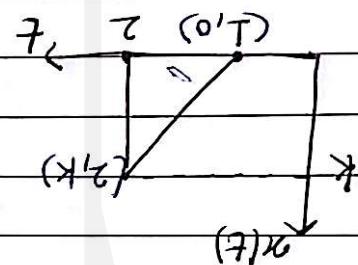


(Ques) Differentiate the given waveform

$$x(t) = kt$$

$$(o-t) = o - k(t-0) \quad \text{or} \quad x(t) = o - k(t-0)$$

$$y - o = k - o(x - 0)$$


$$y - y_1 = f_2 - f_1(x - x_1)$$

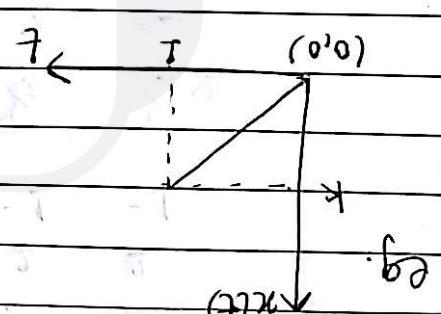


$$x(t) = u(t-1) + u(t-2) - u(t-3) - u(t-4)$$

$$u(t-3) + 1[u(t-3) - u(t-4)]$$
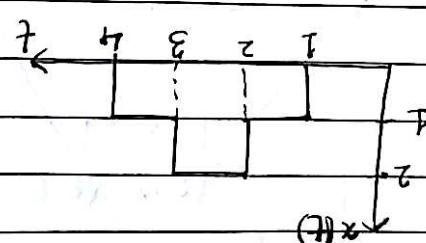
$$x(t) = 1[u(t-0) - u(t-1)] + 2[u(t-2) -$$



Ques) 2

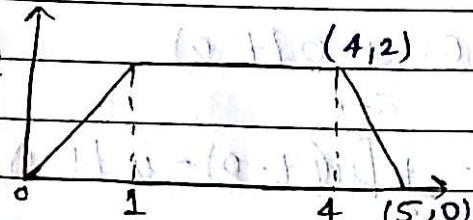


$$x(t) - 0 = 2 - 0 \quad (t - 4)$$

$$4 - 5$$

$$x(t) = -2(t-4) [u(t-4) - u(t-5)] + 2tu(t) + 2u(t-1) \{1-t\}$$

$$\oplus -\underline{2u(t-4)}$$

Ques) 2

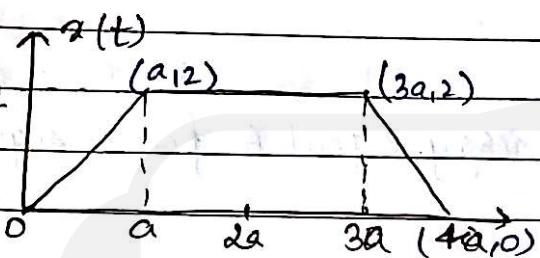

$$x(t) - 0 = 2 - 0 \quad (x - 4a)$$

$$3a - 4a$$

$$x(t) = \frac{2}{a} (4a - x)$$

$$x(t) = \frac{2}{a} (t) [u(t) - u(t-a)] + 2 [u(t-a) - u(t-3a)] - \underline{\frac{2}{a} (t-4a) [u(t-3a) - u(t-4a)]}$$


We know that, $r(t) = \begin{cases} t u(t), & t \geq 0 \\ 0, & t < 0 \end{cases}$

$$x(t) = \frac{1}{a} t u(t) - \frac{1}{a} t u(t-a) + u(t-a) - u(t-3a) - \frac{1}{a} t u(t-3a) + 4u(t-3a) + \frac{1}{a} t u(t-4a) - 4u(t-4a)$$

$$\# t u(t-a) = (t-a+a) u(t-a)$$

$$= (t-a) u(t-a) + a u(t-a)$$

$$= \underline{x(t-a)} +$$

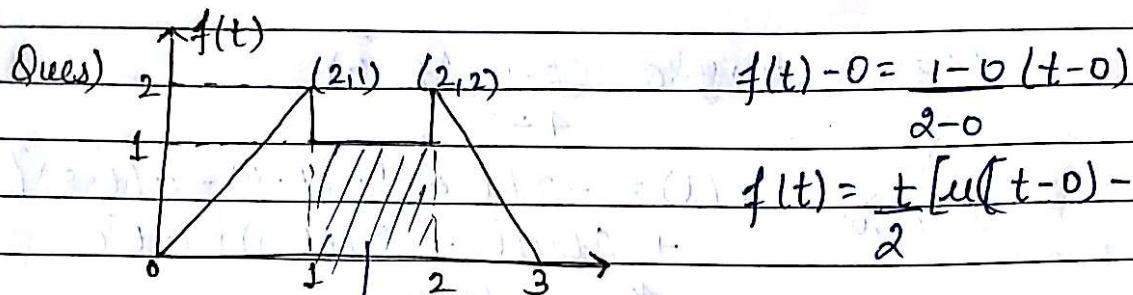

$$2[u(t-1) - u(t-2)]$$

Ques) Check whether the given signal is energy signal or power signal.

$$x(n) = \left(\frac{1}{2}\right)^n u(n)$$

Energy,

$$E_x = \sum_{n=-\infty}^{\infty} |x(n)|^2$$

$$= \sum_{n=0}^{\infty} \left(\frac{1}{4}\right)^n \cdot 1$$

$$= 1 + \left(\frac{1}{4}\right)^1 + \left(\frac{1}{4}\right)^2 + \left(\frac{1}{4}\right)^3 + \dots \quad (\text{Infinite G.P.})$$

$$= \frac{1}{1-\frac{1}{4}} = \frac{1}{1-\left(\frac{1}{4}\right)} = \frac{4}{3}$$

Power,

$$P_x = \lim_{N \rightarrow \infty} \frac{1}{2N+1} \sum_{n=0}^N \left(\frac{1}{4}\right)^n$$

$$\text{Sum of a finite G.P.} = \frac{a(1-r^n)}{(1-r)}$$

$$= \lim_{N \rightarrow \infty} \frac{1}{2N+1} \left[\frac{\left(\frac{1}{4}\right)^{1-(2N+1)} - \left(\frac{1}{4}\right)^{2N+1}}{1 - \frac{1}{4}} \right]$$

$$= \frac{1}{\infty} = 0$$

$$\lim_{t \rightarrow \infty} \frac{\sin at}{at} = 0$$

$$\lim_{t \rightarrow 0} \frac{\sin at}{at} = 1$$

Page _____ Date _____

Page _____ Date _____

Ques) Check whether the given signal is energy or power signal:-
 $x(t) = A \cos t$

$$\begin{aligned} E_x &= \int_{-\infty}^{\infty} A^2 \cos^2 t dt = 2 \int_0^{\infty} A^2 \cos^2 t dt \\ &= 2A^2 \int_0^{\infty} (1 + \cos 2t)^2 dt \\ &= \frac{A^2}{2} \int_0^{\infty} (1 + \cos^2 2t + 2\cos^2 t) dt \\ &= \frac{A^2}{2} \left[t \right]_0^{\infty} + x \\ &= \infty \end{aligned}$$

\Rightarrow Energy signal

$$\begin{aligned} \text{Ques) } x(t) &= e^{j(t+\gamma_0)} = e^{j\theta} = \cos \theta + j \sin \theta \\ &\Rightarrow |e^{j\theta}| = |\cos \theta + j \sin \theta| = 1 \end{aligned}$$

$$E_x = \int_{-\infty}^{\infty} 1^2 dt = \left[t \right]_{-\infty}^{\infty} = \infty \quad \text{Energy signal}$$

$$\begin{aligned} \text{Now, } P_x &= \lim_{T \rightarrow \infty} \frac{1}{2T} \int_{-T}^T |x(t)|^2 dt = \lim_{T \rightarrow \infty} \frac{1}{2T} \left[t \right]_{-T}^T \\ &= \lim_{T \rightarrow \infty} \frac{1}{2T} \cdot 2T \\ &= \lim_{T \rightarrow \infty} 1 \end{aligned}$$

$$= 1$$

Power signal

→ Periodic and Aperiodic Signals

A signal is said to be periodic if it repeats itself after a regular period of time

$$\text{i.e. } x(t) = x(t + T), \quad x(n) = x(n + N)$$

Fundamental time period (t_0) - The smallest value of time period T after which the signal starts repeating itself

e.g. for $x(t) = \sin t$

$$[t_0 = 2\pi]$$

$$\text{e.g. } x(n) = e^{j\omega_0 n} \\ x(n+N) = e^{j\omega_0(n+N)} = e^{j\omega_0 n} + e^{j\omega_0 N}$$

$$\text{also, } \omega_0 = 2\pi f$$

$$\Rightarrow N = \frac{2\pi}{\omega_0}$$

$$\Rightarrow x(n+N) = e^{j\omega_0 n} + e^{j\frac{2\pi}{\omega_0} N} \quad [e^{j2\pi} = 1]$$

$$N = \frac{2\pi}{\omega_0} (m)$$

to make time integer as discrete values can only have integer values

fundamental time period

$$\text{e.g. } \sin \sqrt{2} n$$

to cannot be irrational, in terms of π and also not in terms of j (complex no.).

Ques) Check for the periodicity of $x(n) = \sin \omega n \cdot u(n)$

exist only for $n \geq 0$.

whereas periodic fns exist from $(-\infty, \infty)$.

$\Rightarrow \sin \omega n \cdot u(n)$ is aperiodic

Ques) $y(n) = y_1(n) + y_2(n) + y_3(n) + y_4(n)$

$$\begin{array}{c} N_1 \\ \text{---} \\ N_2 = 40 \end{array} \quad \begin{array}{c} \downarrow \\ N_2 = 64 \end{array} \quad \begin{array}{c} \downarrow \\ N_3 \\ N_2 \end{array} = 50 \quad \begin{array}{c} \downarrow \\ N_4 = 100 \end{array}$$

$$\frac{N_1}{N_2} = \frac{40}{64} = \frac{5}{8}$$

$$\frac{N_1}{N_3} = \frac{40}{50} = \frac{4}{5}$$

$$\frac{N_1}{N_4} = \frac{40}{100} = \frac{2}{5}$$

ratios should be RATIONAL

A no. is said to be a rational no. if it can be written in the form p/q where p and q are integers, $p \neq 0, q \neq 0$.

To calculate T_o of composite fn $= \text{LCM of denominator } x \text{ to of first sig}$

$$= \text{LCM}(8, 5, 5) \times 40$$

$$= 1600$$

Ques) $x(n) = x_1(n) + x_2(n) + x_3(n)$

$$\begin{array}{c} \downarrow \\ N_1 = 4 \\ N_2 = 1.25 \\ N_3 = \sqrt{2} \end{array}$$

$$\frac{N_1}{N_2} = \frac{4}{1.25}$$

$$\frac{N_1}{N_3} = \frac{4}{\sqrt{2}}$$

irrational

Ques) Check for the periodicity $e^{j(t+\pi/4)-\underline{c(n)}}$
 cannot be periodic

⇒ Signal is not periodic

$$\begin{aligned} \text{Ques)} \quad & e^{(-1+j)\pi n} \\ &= e^{j(1+j)\pi n} = e^{j(\frac{1}{j}+1)n} \\ &= e^{j(-\frac{j}{j^2}+1)n} = e^{j(1-n)} \\ &= e^{j(j+1)n} \\ \Rightarrow & \boxed{\omega_0 = j+1} \end{aligned}$$

→ Linear & Non-Linear Systems -

- 1)
- 2) Stable & Unstable
- 3) Static & Dynamic

A system is said to be linear if it follows the 'superposition Theorem'.

Superposition Theorem implies that response resulting from several input signals can be computed as sum of responses resulting from each input signal alone.

If $x_n(t)$ is input, output should be $y_n(t)$.


i.e. $\left. \begin{array}{l} x_1(t) \rightarrow y_1(t) \\ x_2(t) \rightarrow y_2(t) \\ x_3(t) \rightarrow y_3(t) \end{array} \right\} \text{if } \beta$

A system is linear if it follows the following steps -

1) $x_1(t) + x_2(t) \rightarrow y_1(t) + y_2(t)$ [Additive]

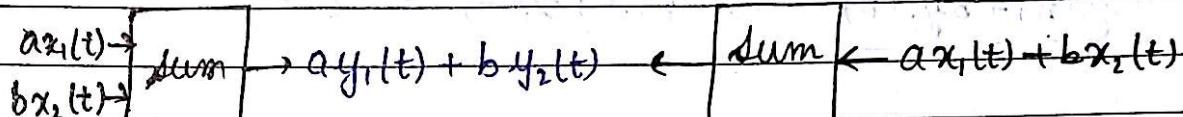2) $\alpha x_1(t) \rightarrow \alpha y_1(t)$ [Scaling property]

Superposition Principle states that response to weighted sum of input signals must be equal to weighted sum of outputs corresponding to each of these individual input signals.



e.g. Check if $y(t) = t \cdot x(t)$ is a linear signal

$$\text{Step 1: } ay_1(t) = atx_1(t) \quad \text{--- (I)}$$

$$by_2(t) = bt \cdot x_2(t) \quad \text{--- (II)}$$

Adding (I) & (II),

$$ay_1(t) + by_2(t) = t [ax_1(t) + bx_2(t)] \quad \text{--- (III)}$$

$$\text{Step 2: } y_3(t) = tx_3(t)$$

$$\text{where } x_3(t) = ax_1(t) + bx_2(t)$$

$$\Rightarrow ay_1(t) + by_2(t) = t [ax_1(t) + bx_2(t)] \quad \text{--- (IV)}$$

eqn's (III) & (IV) are same, hence $y(t) = t \cdot x(t)$ is a linear signal

Ques) Check for linearity : $y(n) = 2x(n) - 3$

$$\text{Step 1: } ay_1(n) = 2x_1(n) - 3$$

$$by_2(n) = b2x_2(n) - 3$$

$$\text{Add } ay_1(n) + by_2(n) = 2 [ax_1(n) + bx_2(n) - 3] \quad \text{--- (I)}$$

$$\text{Step 2: } y_3(n) = 2x_3(n) - 3$$

$$ay_1(n) + by_2(n) = 2 [ax_1(n) + bx_2(n)] - 3 \quad \text{--- (II)}$$

eqn's (I) & (II) are ^{not} same,

$\Rightarrow y_1(t) = t \cdot x(t)$ is a non-linear system.

Ques) $y(n) = x^2(n)$

Step 1: $ay_1(n) = ax_1^2(n)$

$by_2(n) = bx_2^2(n)$

$ay_1(n) + by_2(n) = ax_1^2(n) + bx_2^2(n) \quad \text{--- (1)}$

Step 2: $y_3(n) = x_3^2(n)$

$ay_1(n) + by_2(n) = [ax_1^2(n) + bx_2^2(n)]^2 \quad \text{--- (II)}$

$\textcircled{1} \neq \textcircled{II} \Rightarrow \text{non-linear}$

Ques) $y(n) = x(n+1) - x(n-1)$

Step 1: $ay_1(n) = a[x_1(n+1) - x_1(n-1)]$

$by_2(n) = b[x_2(n+1) - x_2(n-1)]$

$ay_1(n) + by_2(n) = a[x_1(n+1) - x_1(n-1)] + b[x_2(n+1) - x_2(n-1)] \quad \text{--- (1)}$

Step 2: $y_3(n) = x_3(n+1) - x_3(n-1)$

$ay_1(n) + by_2(n) = \{ax_1(n+1) + bx_2(n+1)\}$

$+ \{ax_1(n-1) + bx_2(n-1)\} \quad \text{--- (II)}$

$\textcircled{1} = \textcircled{II} \Rightarrow \text{linear}$

Ques) $\frac{dy(t)}{dt} + 3ty(t) = t^2x(t)$

$a\frac{dy_1}{dt} + 3aty_1(t) = at^2x_1(t)$

$b\frac{dy_2}{dt} + 3bt y_2(t) = bt^2x_2(t)$

$a\frac{dy_1}{dt} + b\frac{dy_2}{dt} + 3aty_1(t) + 3bt y_2(t) = at^2x_1(t) + bt^2x_2(t)$

Time variant & Time in-variant system

A system is said to be time invariant if the behaviour and characteristics of system are fixed over time.

OR

A system is said to be time invariant if time-shifting input signal results in an identical time shift in the output.

How to check for time variance -

1) Delay (only in input)

2) Replace t by $(t-t_0)$ in both input and output

$$\text{eg. } y(t) = t \cdot x(t)$$

i) Delay: $y(t, t_0) = t \cdot x(t-t_0)$ — (1)

ii) Replace: $y(t-t_0) = (t-t_0) \cdot x(t-t_0)$ — (II)

$$(1) \neq (II) \Rightarrow \text{Time variant}$$

Ques) $y(t) = x(t) \sin t$

$$y(t, t_0) = x(t-t_0) \sin t \quad (1)$$

$$y(t-t_0) = x(t-t_0) \sin(t-t_0) \quad (II)$$

$$(1) \neq (II) \Rightarrow \text{Time variant}$$

Ques) $y(t) = x(t^2)$

$$y(t, t_0) = x(t^2 - t_0) \quad (1)$$

$$y(t-t_0) = x(t-t_0)^2 \quad (II)$$

$$(1) \neq (II) \Rightarrow \text{Time variant}$$

→ Invertible & Non-Invertible System -

In case multiple inputs give a single output, then it is not possible to predict the responding input by looking at output. Such systems are non-invertible systems.

→ Laplace Transform -

It is a powerful tool in solving circuit problems.

It is generally used in solving differential of circuit.

It transforms time signal into s domain where s is a Laplace operator having operator ($s = \pm\sigma + j\omega$).

OR we can say that it transforms time domain signal to frequency domain.

Formulae -

$$L[f(t)] = F(s) = \int_0^{\infty} f(t) \cdot e^{-st} dt$$

$$1) L[1] = \frac{1}{s}$$

$$7) L[e^{at}] = \frac{1}{s-a}$$

$$2) L[K] = \frac{K}{s}$$

$$8) L[\sin \omega t] = \frac{\omega}{s^2 + \omega^2}$$

$$3) L[u(t)] = \frac{1}{s}$$

$$9) L[\cos \omega t] = \frac{s}{s^2 + \omega^2}$$

$$4) L[s(t)] = \frac{t}{s}$$

$$10) L[e^{at} \sin \omega t] = \frac{\omega}{(s-a)^2 + \omega^2}$$

$$5) L[t] = \frac{1}{s^2}$$

$$11) L[e^{at} \cos \omega t] = \frac{s-a}{(s-a)^2 + \omega^2}$$

$$6) L[x(t)] = \frac{1}{s^2}$$

$$12) L[e^{at} f(t)] = F(s-a)$$

Date _____

 $u(t)$

Ques) $L[u(t-t_0)] = ? = \int_0^\infty u(t-t_0) e^{-st} dt$



$$= \int_{t_0}^\infty u(t-t_0) e^{-st} dt$$

$$= \int_{t_0}^\infty 1 \cdot e^{-st} dt = \frac{e^{-t_0 s}}{s}$$

Ques) $L[u(t+t_0)] = ? = \int_0^\infty u(t+t_0) e^{-st} dt$



$$= \int_{-t_0}^\infty u(t+t_0) e^{-st} dt$$

$$= \frac{e^{t_0 s}}{s}$$

Time-shifting property - In case any funcⁿ is delayed/advanced by a time factor say t_0 , then the LT of this fn will be $e^{\pm t_0 s}$ times LT of normal function.

i.e. $L[f(t \pm t_0)] = e^{\pm t_0 s} F(s)$

Properties of Laplace Transform-

1) Multiplication by a constant : $L[Kf(t)] = K \cdot F(s)$

2) Sum and difference : $L[f_1(t) \pm f_2(t)] = F_1(s) \pm F_2(s)$

3) Frequency shifting :

4) $L\left[\frac{df(t)}{dt}\right] = sF(s) - f(0^+)$

$$5) L\left[\frac{d^2 f(t)}{dt^2}\right] = s^2 F(s) - s \cdot f(0^+) - f'(0)$$

$$6) L\left[\int_0^t f(t) dt\right] = \frac{f(0^+)}{s} + \frac{1}{s} F(s)$$

$$7) \frac{dF(s)}{ds} = -L[t \cdot f(t)] \quad [\text{Diff. in } s \text{ domain}]$$

The differentiation in s domain corresponds to multiplication by t in the time domain.

$$8) \int_s^\infty F(s) ds = L\left[\frac{1}{t}\right] \quad [\text{Diff. Integration in } s \text{ domain}]$$

The integration of $F(s)$ in s domain corresponds to division by t in time domain.

Initial Value Theorem -

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s)$$

Final Value Theorem -

$$f(\infty) = \lim_{s \rightarrow 0} sF(s)$$

$$f(t) = 9 - 2e^{-5t}$$

$$F(s) = \frac{9}{s} - \frac{2}{s+5} = \frac{9s+45-2s}{s^2+5s} = \frac{7s+45}{s(s+5)}$$

$$\text{Now, } f(0^+) = \lim_{s \rightarrow \infty} s \cdot \frac{7s+45}{s(s+5)} = \lim_{s \rightarrow \infty} \frac{s(7+\frac{45}{s})}{s(1+\frac{5}{s})}$$

= 7

Date _____

Ques) $\lim_{s \rightarrow 0} sF(s) = (2s+1)s$

$$\lim_{s \rightarrow 0} \frac{s^2(2+\frac{1}{s})}{s^2(1+\frac{2}{s}+\frac{5}{s^2})} = \boxed{2}$$

Ques) Obtain initial and final value and $f(t)$.

$$F(s) = \frac{5s+3}{s(s+1)}$$

$$\lim_{s \rightarrow 0} sF(s) = \lim_{s \rightarrow 0} \frac{5s+3}{s+1} = 3$$

$$\lim_{s \rightarrow \infty} sF(s) = \lim_{s \rightarrow \infty} \frac{5s+3}{s+1} = 5$$


Now, $F(s) = \frac{5s+3}{s(s+1)} = \frac{A}{s} + \frac{B}{s+1}$

$$\Rightarrow F(s) = \frac{3}{s} + \frac{2}{s+1}$$

Applying Inverse Laplace, we get

$$f(t) = 3 + 2e^{-t}$$

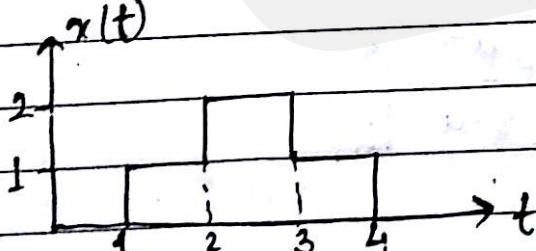Ques) Obtain Laplace Transform of given waveform -




$$x(t) = 1[u(t-1)-u(t-2)] + 2[u(t-2)-u(t-3)] + 1[u(t-3)-u(t-4)]$$

$$x(t) = u(t-1) + u(t-2) - u(t-3) - u(t-4)$$

Date _____

$$X(s) = \frac{1}{s} e^{-1s} + \frac{e^{-2s}}{s} - \frac{e^{-3s}}{s} - \frac{e^{-4s}}{s}$$

Ques) Obtain the Laplace Transform.

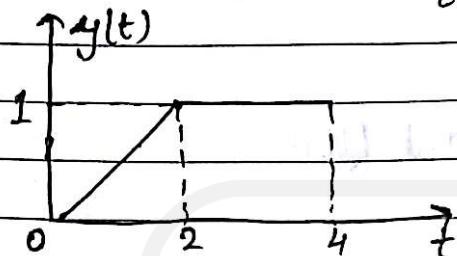

$$y(t) = \frac{1}{2} [u(t) - u(t-2)] + [u(t-2) - u(t-4)]$$

$$= \frac{1}{2} [u(t) - (t-2+2)u(t-2)]$$

$$\Rightarrow y(s) = \frac{1}{2} \left[\frac{1}{s^2} - \frac{e^{-2s}}{s^2} - \frac{2e^{-2s}}{s} + \frac{e^{-2s}}{s} - \frac{e^{-4s}}{s} \right]$$

Ques) Find out the LT of $x(t) = 4(t-3a) + 8(t+3a) + u(t-4a)$

$$x(s) = \frac{1}{s} e^{-3as} + e^{3as} + \frac{1}{s} e^{-4as}$$

$$\text{Ques) } F(s) = \int_s^\infty e^{-at} u(t-b) e^{-st} dt$$


$$= \int_b^\infty e^{-at} e^{-st} dt = \int_s^\infty e^{-t(s+a)} dt$$

$$= \left[\frac{e^{-(s+a)t}}{-s-a} \right]_b^\infty$$

(Ques) $i(t) = 1.5 (1 - e^{-4t}) u(t) - 1.5 [1 - e^{-4(t-0.1)}] u(t-0.1)$

$$I(s) = \frac{1.5}{s} - \frac{1.5}{s+4} - 1.5e^{-0.1s} + \frac{1.5}{s+4} e^{-0.1s}$$

Ques) Obtain the LT of given waveform

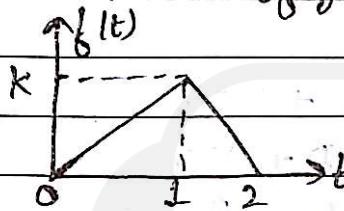

$$f(t) = k u(t) - 2k(t-1)u(t-1)$$

$$+ k(t-2)u(t-2)$$

since $u(t) = x(t)$

$$\Rightarrow f(t) = k u(t) - 2kx(t-1) + k^2(t-2)$$

$$F(s) = \frac{k}{s^2} - \frac{2k}{s} e^s + \frac{k e^{-2s}}{s^2}$$

$$F(s) = \frac{k}{s^2} \left[1 - \frac{2e^{-s}}{s^2} - \frac{e^{-2s}}{s^2} \right]$$

Unit-II

Page No. 10/20

Date _____

25/Aug/17

→ Solⁿ of Differential Eqⁿs -I) First order & second order homogeneous eqⁿ-

$$\frac{dy(x)}{dt} + y(t) = 0$$

↓ ↓

$$\text{replace } D + 1 = 0$$

$$P_1 = -1$$

$$\begin{aligned} C.F. &= k e^{P_1 t} \\ C.F. &= k e^{-t} \end{aligned}$$

$$\frac{d^2 y(x)}{dt^2} + 3 \frac{dy(x)}{dt} + 2y(t) = 0$$

$$D^2 + 3D + 2 = 0$$

$$(D+1)(D+2) = 0$$

$$P_1 = -1, P_2 = -2$$

$$\begin{aligned} C.F. &= k_1 e^{P_1 t} + k_2 e^{P_2 t} \\ &= k_1 e^{-t} + k_2 e^{-2t} \end{aligned}$$

II) First/second order Non-homogeneous eqⁿ containing constant or exponential fn on right hand side-

Exponential fn

Case I: Constant on right side

Make put RHS = 0

Find P₁ and C.F.

$$\text{Sol}^n = P_1 + C.F.$$

$$\text{eg. } \frac{dy(t)}{dt} + y = 5e^{2t} / e^{at}$$

$$A.E. \quad D + 1 = 0$$

$$D = -1$$

$$1) C.F. = k e^{-t}$$

$$2) P.I. = \frac{5e^{2t}}{D+1}$$

Replace D by 2 (i.e. replace D by a for e^{at})

Date: _____

$$\Rightarrow P.I. = \frac{5e^{2t}}{D+1} = \frac{5e^{2t}}{3}$$

$$\text{Now, } y = CF + PI = ke^{-t} + \frac{5e^{2t}}{3}$$

$$\text{eg. } \frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = e^{2t}$$

$$A.E \Rightarrow D^2 + 3D + 2 = 0$$

$$(D+1)(D+2) = 0$$

$$D = -1, -2$$

$$\text{Now, } P.I. = \frac{e^{2t}}{D^2 + 3D + 2}$$

$$\text{Put } D =$$

II] Constant on RHS -

$$\text{eg. } \frac{dy}{dt} + y = 5$$

$$A.E] D+1=0$$

$$D = -1$$

$$C.F = ke^{-t}$$

$$P.I. = \frac{5}{D+1} e^{ot}$$

$$\text{eg.) } \frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = 5$$

$$A.E: D^2 + 3D + 2 = 0$$

$$D = -1, -2$$

$$P.I. = \frac{5}{D^2 + 3D + 2} e^{ot}$$

$$\text{Put } D = 0$$

$$\Rightarrow P.I. =$$

Type 3: First & second order Non-homogeneous eqⁿ with:
RHS as a sine or cosine fn.

$$\text{eg. } \frac{dy}{dt} + yt = \sin 5t$$

$$A-E \Rightarrow D+1=0$$

$$D = -1$$

$$C.F. = K e^{-t}$$

$$P.I. = \sin 5t$$

$$D+1$$

Replace D^2 by $-a^2$,

To do so, we need to make $D \rightarrow D^2$,

\therefore Rationalizing the fraction,

$$= \frac{\sin 5t}{(D+1)(D-1)}$$

$$= \frac{(D-1) \sin 5t}{D^2 - 1}$$

$$\text{Put } D^2 = -a^2 = -(5)^2$$

$$= (D-1) \sin 5t$$

$$-25-1$$

$$= (D-1) \sin 5t$$

$$-26$$

Equating $D = \frac{d}{dt}$,

$$P.I. = \frac{d}{dt} \left(\frac{\sin 5t}{-26} \right) - \frac{\sin 5t}{(-26)}$$

$$= -\frac{1}{26} 5 \cos 5t + \frac{\sin 5t}{26}$$

$$P.I. = \frac{\sin 5t}{26} - \frac{5 \cos 5t}{26}$$

and, $\{y = C.F. + P.I.\}$

2nd Order - non-homogeneous differential equation of second order

$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y = \sin 5t$$

$$D^2 + 3D + 2 = 0$$

$$P.I. = \underline{\sin 5t}$$

$$D^2 + 3D + 2$$

$$\text{Put } D^2 = -(5)^2$$

$$= \underline{\sin 5t}$$

$$-25 + 3D + 2$$

$$= \underline{\sin 5t}$$

$$3D - 23$$

$$= \underline{\sin 5t} \cdot \underline{(3D+23)}$$

$$(3D-23) \quad (3D+23)$$

$$= \underline{(3D+23) \sin 5t} \quad (1-\epsilon) \quad (1+\epsilon)$$

$$9D^2 - 529$$

$$= \underline{(3D+23) \sin 5t} \quad (1-\epsilon)$$

$$-225 - 529 = \underline{(3D+23) \sin 5t} \quad (1+\epsilon)$$

Again equate $D = \frac{d}{dt}$ & solve $(1-\epsilon)$

→ Circuit Analysis by Classical Method-

Transient Response - Whenever a circuit is switched from one condition to another, then there is a transition period during which the current & voltage change from former values to new one. This period is known as 'Transition time' & the value of current & voltage are known as 'Transient Response'.

Steady State Response - When the transient period is over OR the transition has died out, the circuit is said to be in steady state.

Zero Input response

Zero Input Response - The value of current & voltage which results from initial condition when applied input is zero.

Zero State Response - The values of current & voltage for an input which is applied when all the initial conditions are zero. Such networks/circuits are said to be at rest.

→ Order of Differential Eqⁿ-

If a circuit contains only one storage element (L or C) \Rightarrow 1st order
 " two " \Rightarrow 2nd order

- The circuit changes are assumed to occur at time $t=0$ & represented by a switch.
- Switching ON/OFF at $t=0$ does not disturb the storage elements so that $I(0^-) = I(0^+)$.

In case of capacitor $V_C(0^-) = V_C(0^+)$

→ Voltage-current relationship for storage elements -

$$1) V = IR, I = \frac{V}{R}$$

$$2) V_L(t) = L \frac{dI_L(t)}{dt} ; I(t) = \frac{1}{L} \int_{-\infty}^t V_L(t) dt$$




$$\text{or } I(t) = \frac{1}{L} \int_0^t V_L(t) dt + I_L(0)$$

$$3) V_C(t) = \frac{1}{C} \int_{-\infty}^t I_C(t) dt ; I_C(t) = C \cdot \frac{dV_C(t)}{dt}$$

$$= \frac{1}{C} \int_0^t I_C(t) dt + V_C(t)$$


→ Initial / Boundary conditions in a circuit -

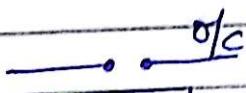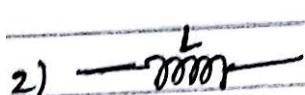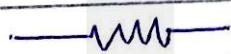Circuit Element Eq. ckt at $t=0^+$ Eq. ckt. at $t=\infty$




$$V_L = \infty$$


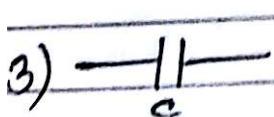
$$I = I_{\max}, \text{ Voltage drop} = 0$$



$$I_C = C \frac{dV_C(t)}{dt} \Big|_{t=0}$$

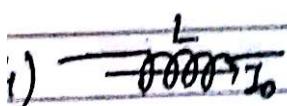

$$I_0$$

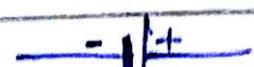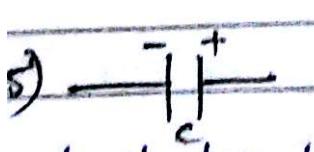


$$I_0^+$$

Circuit Analysis

Now calculate $i(0^+)$, $\frac{di}{dt}(0^+)$, $\frac{d^2i}{dt^2}(0^+)$, $i(t)$

transient response

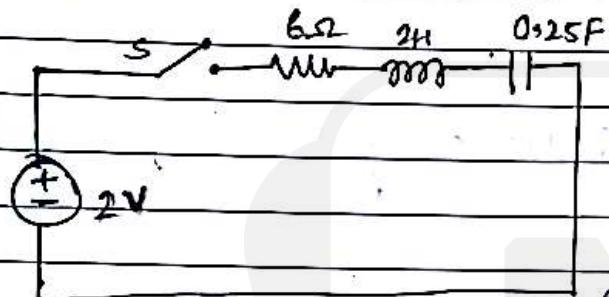of a given circuit where source is of 2V and resistance is of 6Ω.
Inductor = 2H, capacitor = 0.25F when the switch S is closed at time $t=0$.



Applying KVL,

$$V_s = 6i(t) + 2\frac{di}{dt} + \frac{1}{C} \int i(t) dt + V_c(0^-)$$

$$2 = 6i(t) + 2\frac{di}{dt} + \frac{1}{C} \int i(t) dt + V_c(0^-)$$

— ① (no initial charge)

$$2 = v(t)16 + \int v(t) dt + \frac{4}{C} \frac{dv(t)}{dt}$$

$$2 = \frac{4}{C} \frac{dv(t)}{dt} \Rightarrow \frac{dv(t)}{dt} = \frac{1}{2}$$

Double diff.,

$$0 = 16 \frac{dv(t)}{dt} + \frac{1}{2} v(t) + \frac{1}{C} \frac{d^2v(t)}{dt^2}$$

$$0 = -\frac{1}{2} \left(\frac{1}{2}\right) + 0 + \frac{1}{4} \frac{d^2v(t)}{dt^2}$$

$$\frac{d^2v(t)}{dt^2} = -2$$

~~Applying KVL,~~

~~$$V = R^o(t) + L \frac{di^o(t)}{dt}$$~~

~~$$V = R^o + L D i$$~~

~~$$LD + R = 0$$~~

~~$$D = -\frac{R}{L} - \frac{i}{L}$$~~

~~$$\Rightarrow i(t) = K e^{-\frac{Rt}{L}} + \frac{V}{R}$$~~

~~$$C.F. = K e^{\frac{Rt}{L}}$$~~

~~$$-Rt$$~~

~~$$K e$$~~

~~$$P.I. =$$~~

~~$$LD + R$$~~

~~$$\text{Put } D = 0$$~~

~~$$= \frac{V}{R + L} = \frac{V}{R}$$~~

~~X~~~~Applying $i(0^+) = 0$~~ ~~Because at $t=0^+$, L behaves as open ckt. (Initial cond'n)~~~~Putting $t = 0^+$,~~~~i.e. at $i(0^+)$~~

~~$$\text{eqn ① becomes, } 2 = 6i^o(0^+) + 4 \int_0^t i^o(t) dt + 2 \frac{di^o(t)}{dt}$$~~

~~$$2 = 2 \frac{di^o(t)}{dt}$$~~

~~$$\text{or } \boxed{\frac{di^o(t)}{dt} = 1} \quad \text{--- ②}$$~~

~~Double diff. of eqn ①,~~

~~$$0 = 6 \frac{d^2 i^o(t)}{dt^2} + 2 \frac{d^3 i^o(t)}{dt^3} + 4i^o(t) \quad \text{--- ③}$$~~

~~Put $d = D$,~~

~~$$\text{Q3} \quad 6D^2 i^o + 2D^3 i^o + 4i^o = 0$$~~

~~$$\text{or} \quad 3D + 2D^2 + 2 = 0$$~~

$$D^2 + 3D + 2 = 0$$

$$(D+1)(D+2) = 0$$

$$D = -1, D = -2$$

Now, C.F. = $k_1 e^{-D_1 t} + k_2 e^{-D_2 t}$
 $i(t) = k_1 e^{-t} + k_2 e^{-2t} \quad \text{--- (IV)}$

Apply initial condition in eqⁿ (IV), [To determine values of k_1 & k_2]

i.e. $t=0$

$$i(0^+) = k_1 + k_2 \quad \text{--- (V)}$$

Diffr. eqⁿ (IV) w.r.t. t,

$$\frac{di(t)}{dt} = -k_1 e^{-t} - 2k_2 e^{-2t}$$

Put $t=0$,

$$\frac{di(0^+)}{dt} = -k_1 - 2k_2$$

$\rightarrow 1$ (from (V))

$$1 = -k_1 - 2k_2$$


$$\text{and, } \frac{0 = k_1 + k_2}{1 = -k_2}$$

$$\Rightarrow k_1 = 1, k_2 = -1$$

Putting these values in eqⁿ. (IV),

$$i(t) = e^{-t} - e^{-2t}$$

Date: _____

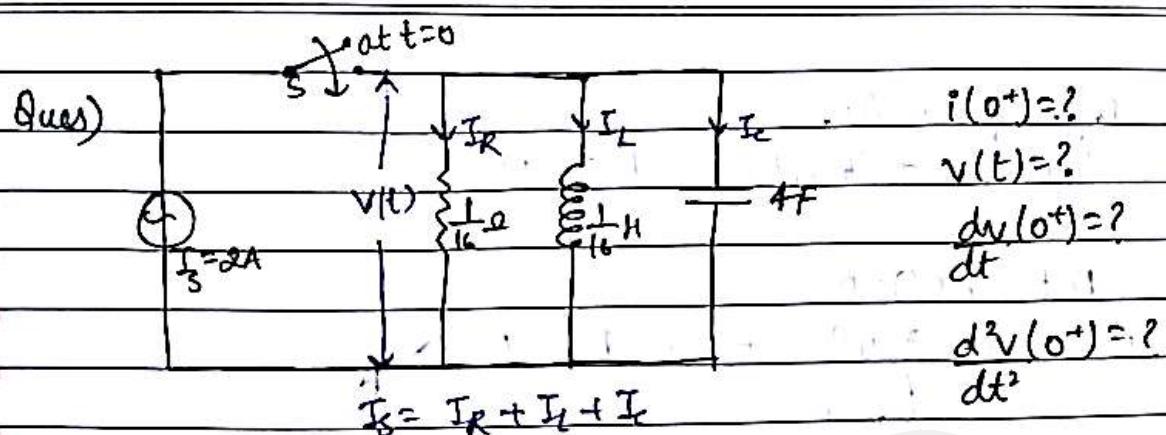

Applying KCL,

$$I_S = \frac{V(t)}{R} + \frac{1}{L} \int_0^t V(t) dt + I_C(0^+) + C \cdot \frac{dv(t)}{dt}$$

Since all three elements are connected in parallel, voltage across each is same.

$$\Rightarrow I_S = 16V(t) + 16 \int_0^t V(t) dt + 4 \frac{dv(t)}{dt} \quad \text{--- (1)}$$

At initial condⁿ, C acts as short circuited element.

$$\Rightarrow R_C = 0$$

 \Rightarrow entire current flows through this branch \Rightarrow Voltage across $s/C = 0$.

$$\Rightarrow v(0^+) = 0$$

Putting $v(0^+) = 0$ in eqⁿ (1),

$$I_S = 0 + 0 + 4 \frac{dv(0^+)}{dt}$$

or
$$\frac{dv(0^+)}{dt} = \frac{1}{2} \quad \text{--- (11)}$$

Date _____

Double diff. of eqⁿ ①,

$$0 = 16 \frac{dv(t)}{dt} + 16v(t) + \frac{4d^2v(t)}{dt^2}$$

$$\text{Put } v(0^+) = 0$$

$$0 = 16 \cdot \frac{dv(0^+)}{dt} + 0 + \frac{4d^2v(0^+)}{dt^2}$$

$$\frac{dv(0^+)}{dt} = \frac{1}{2}$$

$$0 = 8 + \frac{4d^2v(0^+)}{dt^2}$$

$$\Rightarrow \left[\frac{d^2v(0^+)}{dt^2} = -2 \right]$$

~~0 = 16~~ Diff. eqⁿ ①,

$$0 = 16 \frac{dv(t)}{dt} + 16v(t) + \frac{4d^2v(t)}{dt^2}$$

$$0 = 16D + 4D^2 + 16$$

$$\text{or } D^2 + 4D + 4 = 0$$

$$(D+2)^2 = 0$$

$$\text{or } D = -2$$

$$CF = k_1 e^{-Dt} + k_2 t e^{-Dt}$$

$$v(t) = k_1 e^{-Dt} + t k_2 e^{-Dt} \quad \text{--- (ii)}$$

Applying initial condⁿ, $t=0^+$ $v(0^+) = 0$

$$v(0^+) = k_1 + 0k_2$$

$$\boxed{k_1 = 0}$$

Solv. eqⁿ (ii)
w.r.t. t,

$$\frac{dv(t)}{dt} = -2k_1 e^{-2t} t (k_2 e^{-2t} + -2k_2 t e^{-2t})$$

Date _____

Again, put $t=0^+$,


$$\frac{dv(0^+)}{dt} = -\alpha k_1 + k_2$$

$$\text{or } \left| \frac{1}{2} = k_2 \right.$$

from (1)

$$\Rightarrow v(t) = \frac{1}{2} e^{-\alpha t}$$

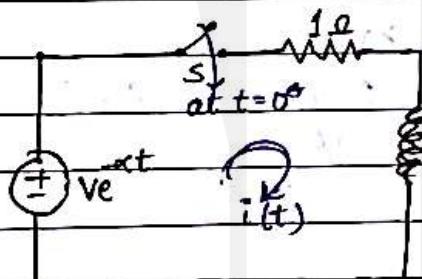Ques) For a given ckt., voltage source is an exponential fn $v(t) = ve^{-\alpha t}$
 where α is constant, the switch S is closed at $t=0$, $R=1\Omega$,
 $L=1H$. The ckt. is shown below. Calculate $i(t)$.



Applying KVL,

$$ve^{-\alpha t} = i(t)R + L \frac{di(t)}{dt}$$

$$\Rightarrow ve^{-\alpha t} = i(t) + \frac{di(t)}{dt} \quad \text{--- (1)}$$

$$\text{or } 0 = D + 1$$

$$D = -1$$

$$\therefore CF = ke^{-t}$$

$$\text{P.I.} = ve^{-\alpha t}$$

$$-\alpha + 1$$

$$\text{or } i(t) = ke^{-t} + \frac{ve^{-\alpha t}}{1-\alpha} \quad \text{--- (II)}$$


Put $t=0$,

$$0 = K + V$$

$$\text{or } K = \frac{V}{\alpha - 1}$$

$$\Rightarrow i(t) = \frac{ve^{-t}}{\alpha - 1} + \frac{ve^{-\alpha t}}{1-\alpha}$$

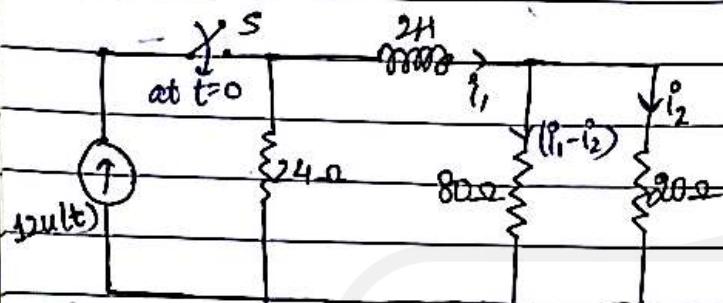- Ques) Calculate the current i_1, i_2 and voltage v_i of the given network.
- at $t=0^+$
 - at $t=0^-$
 - at $t=\infty$
 - at $t=50\text{ms}$




Since input voltage signal is an unit signal (which exists only for $t \geq 0$),

$$\Rightarrow i_1(0^-) = 0, i_2(0^-) = 0 \\ v_i(0^-) = 0$$

Applying KVL, Also at $t=0^+$, L behaves as open ckt.

$$i_1(0^+) = 0; i_2(0^+) = 0$$

Simplified ckt:

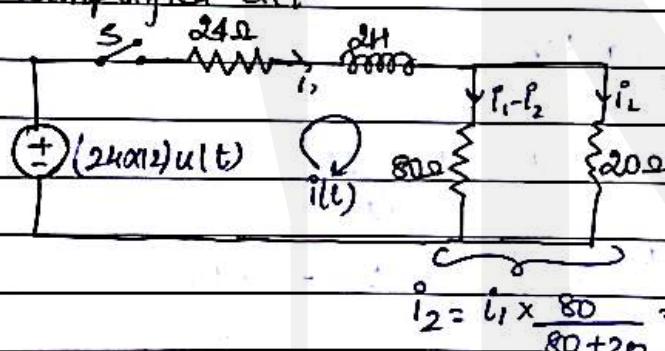

Applying KVL,

$$288 = 24i_1 + 2 \frac{di_1}{dt} + 80(i_1 - i_2) \quad \text{①}$$

$$i_2 = i_1 \times \frac{80}{80+20} = 0.8i_1$$

$$\Rightarrow \text{eqn ① becomes, } 288 = 24i_1 + 2 \frac{di_1}{dt} + 80(i_1 - 0.8i_1)$$

$$288 = 24i_1 + 2 \frac{di_1}{dt} + 16i_1$$

$$144 = 20i_1 + \frac{di_1}{dt}$$

$$\text{Now, } D + 20 = 0$$

$$D = -20$$

$$\text{Now, } \underline{i_1} = k e^{-20t}$$

$$\text{P.I.} = \frac{144}{20} = 7.2$$

$$i(t) =$$

$$\text{Now, } i_1(t) = ke^{-20t} + 7.2$$

$$\text{at } t=0^+, i_1(0^+) = 0$$

$$0 = k + 7.2$$

$$\Rightarrow k = -7.2$$

$$i_1(t) = -7.2e^{-20t} + 7.2$$

$$\text{Now, at } t=\infty, i_1(\infty) = -7.2e^{-\infty} + 7.2 = 7.2$$


$$i_1(\infty) = 7.2 \text{ mA}$$

$$\text{and, } i_2(t) = \frac{4}{5} i_1$$

$$\therefore i_2(\infty) = \frac{4}{5} \times 7.2 = 5.76$$

Ques) Consider a series RL ckt. excited by sinusoidal voltage

$$v(t) = V_m \sin(\omega t + \phi)$$

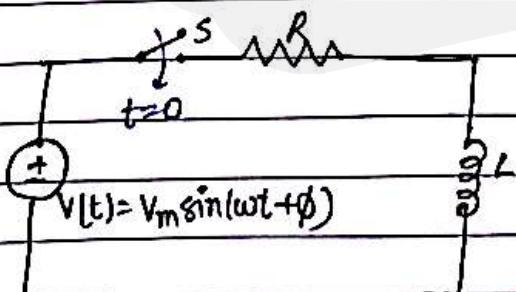

Applying KVL,

$$v(t) = iR + L \frac{di}{dt}$$

$$V_m \sin(\omega t + \phi) = R i + \frac{L}{L} \frac{di}{dt}$$

$$\text{At } t=0, \quad D + R = 0$$

$$\Rightarrow D = -R_L$$

Date: 11/11/11

$$C.F. = k e^{-\frac{R}{L}t}$$


$$P.I. = \frac{V(t)}{(D - R_L)} \times \frac{(D - R_L)}{(D + R_L)}$$

$$= \frac{(D - R_L) V(t)}{D^2 - (R_L)^2}$$

Replace D^2 with $-w^2$,

$$i(t) = k e^{-\frac{R}{L}t} - \frac{V_m}{R^2 + w^2 L^2} [wL \cos(wt + \phi) - R \sin(wt + \phi)]$$

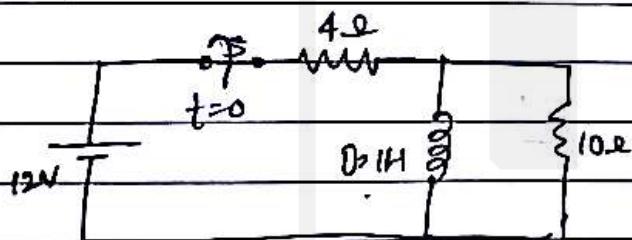Ques) A 12V battery is suddenly disconnected at $t=0$. Find the inductor current at $t=0$ and $V_L(t)$.



at $t=\infty$, L behaves as short circuit
 \Rightarrow no current flows through 10Ω

$$\Rightarrow P = \frac{12}{4} = 3A$$

Applying KVL at $t=0^-$,

Ques)

→ Solutions of Circuits Using Laplace Transform

$$\frac{d^2y}{dt^2} + 3\frac{dy}{dt} + 2y(t) = 5u(t) \quad \text{--- (1)}$$

Taking Laplace transform on both sides,

$$L\left(\frac{d^2y}{dt^2}\right) = s^2 Y(s) - sy(0^+) - y'(0^+)$$

$$L\left(\frac{dy}{dt}\right) = sY(s) - y(0^+)$$

$$Ly(t) = Y(s)$$

$$L\{5u(t)\} = \frac{5}{s}$$

∴ Eqⁿ (1) becomes,

$$s^2 Y(s) - sy(0^+) - y'(0^+) + 3sY(s) - 3y(0^+) + 2Y(s) = \frac{5}{s}$$

--- (11)


Given that: Value of $y(0^+) = -1$

$$y'(0^+) = 2$$

∴ Eqⁿ (11) becomes,

$$s^2 Y(s) - s(-1) - (2) + 3sY(s) + 2Y(s) = \frac{5}{s}$$

$$\text{or } Y(s) [s^2 + 3s + 2]$$

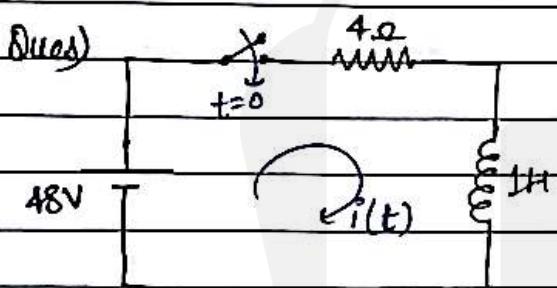

Assume initial current through inductor
= 3A

Applying KVL,

$$48 = 4i(t) + \frac{di(t)}{dt} \quad \text{--- (1)}$$

Taking Laplace on both sides,

$$\frac{48}{s} = 4 I(s) + S I(s) - i(0^+)$$

$$\frac{48}{s} = (s+4) I(s) - 3$$


$$I(s) = \frac{3s + 48}{s(s+4)}$$

$$= \frac{A}{s} + \frac{B}{s+4}$$

$$= \frac{12}{s} - \frac{9}{s+4}$$

$$I(t) = 12 - 9e^{-4t} \rightarrow \text{Applying Inverse LT,}$$

Ques)

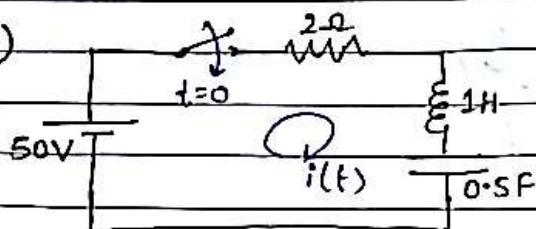

$$50 = 2i(t) + \frac{di(t)}{dt} + 2 \int_0^t i(t) dt$$

Applying Laplace,

$$2I(s) + [sI(s) - i(0^+)] + 2 \frac{I(s)}{s} = 50$$

$$I(s) [2 + s + \frac{2}{s}] = \frac{50}{s}$$

$$I(s) [s^2 + 2s + 2] = 50$$


$$\text{or } I(s) = \frac{50}{s^2 + 2s + 2}$$

$$= \frac{50}{(s+1)^2 + 1}$$

Applying Inverse LT,

$$= 50(\sin t)e^{-t}$$

Ques)

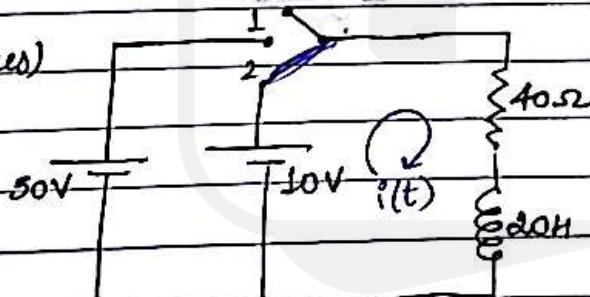

Switch is held in pos. 1 for a long time, then it is moved to pos. 2.

$$i(0^+) = i(0^-) = \frac{50}{40} = \frac{5}{4}$$

Applying KVL,

$$10 = 40i(t) + 20 \frac{di(t)}{dt}$$

Applying LT,

$$10 = 4I(s) + 20[sI(s) - i(0^+)]$$

Date: _____

$$\frac{10}{s} = 40I(s) + 20sI(s) - 20\left(\frac{5}{4}\right)$$

$$\frac{10}{s} + 25 = I(s)[40 + 20s]$$

$$\frac{25s + 10}{20s^2 + 40s} = -I(s)$$

$$I(s) = \frac{5s + 2}{4s(s+2)}$$

Applying partial fraction,

$$I(s) = \frac{1}{4s} + \frac{1}{s+2}$$

Applying ILT,

$$i(t) = \frac{1}{4} + e^{-2t}$$

Ques) Find the current $i(t)$ if the voltage source is $v(t) = 2e^{-t/2}$

$$v_c(0^-) = 0, R = 1, C = \frac{1}{2} F$$

$$v(t) = 2e^{-t/2}$$

$$v(t) = 1i(t) + 2 \int_0^t i(t) dt$$

$$i(t)$$

Unit - III
Graph Theory

Page 1 of 1
 Date 28/09/17

A graph is a geometrical representation of any network / circuit which consists of branches and nodes.



Branch: Circuit elements like R, C, L are replaced by straight lines known as branch which does not give any idea about the type of element. Representation - 'b'.

Node: The end points of a branch or common point of intersection of two or more branches.


Nodes are represented by 'n'.

→ How to draw a graph?

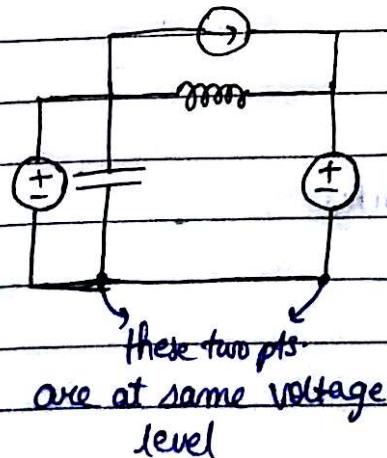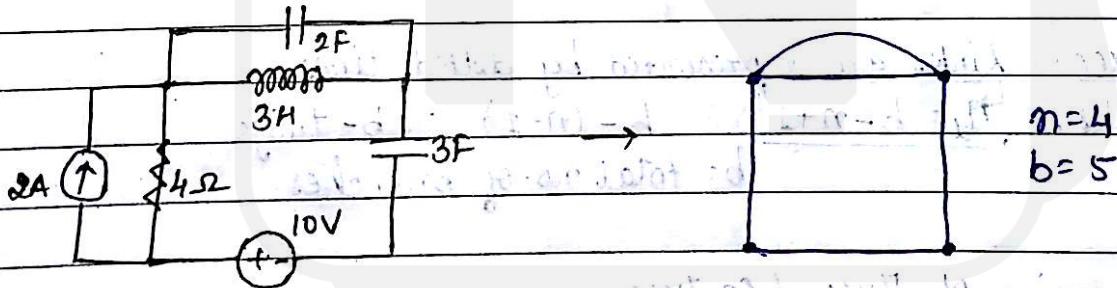- Step - 1) Replace all the ckt. elements by st. lines.
- 2) Replace ideal voltage source by short ckt.
- 3) Replace ideal current source by open ckt.
- 4) If two elements are in series, then these elements can be replaced by either one branch or by two branches.



Always try to minimize the no. of nodes

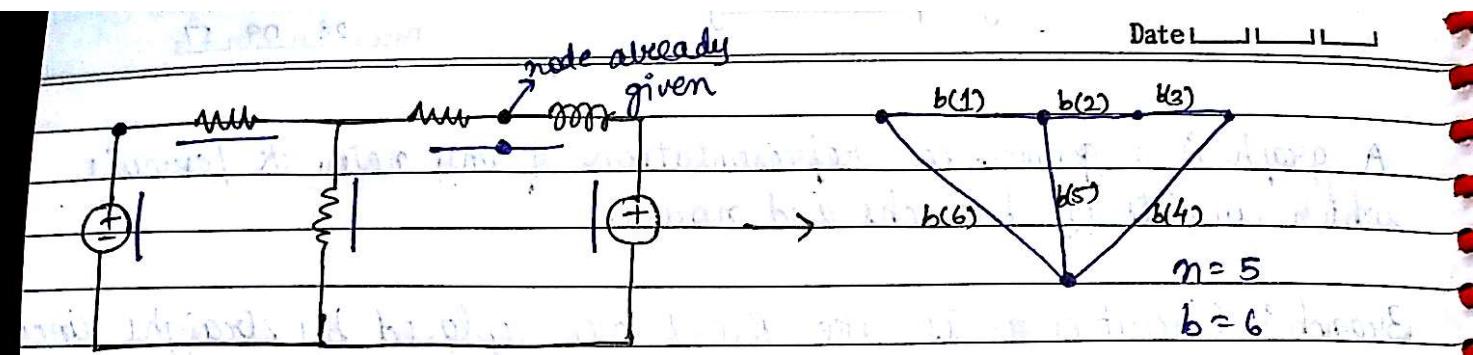

→ Planar Graph - A graph is said to be planar if there are no cross lines when drawn on paper.

→ Non-planar graph - A graph which cannot be drawn on a paper without cross lines.

→ Tree -

- A tree is open set of interconnected branches without any closed loop
- In tree, there exists only one path b/w any two nodes.
- The tree branch is represented by solid lines & is known as Twig.
- No. of twigs, $n_t = n - 1$

$$n = \text{no. of nodes}$$

- Link or Co-tree - Links are represented by dotted lines


- No. of links, $n_l = b - n + 1 = b - (n - 1) = b - \text{twigs}$

$$b = \text{total no. of branches}$$

Graph is union of Tree & Co-tree.


e.g. To draw a tree -

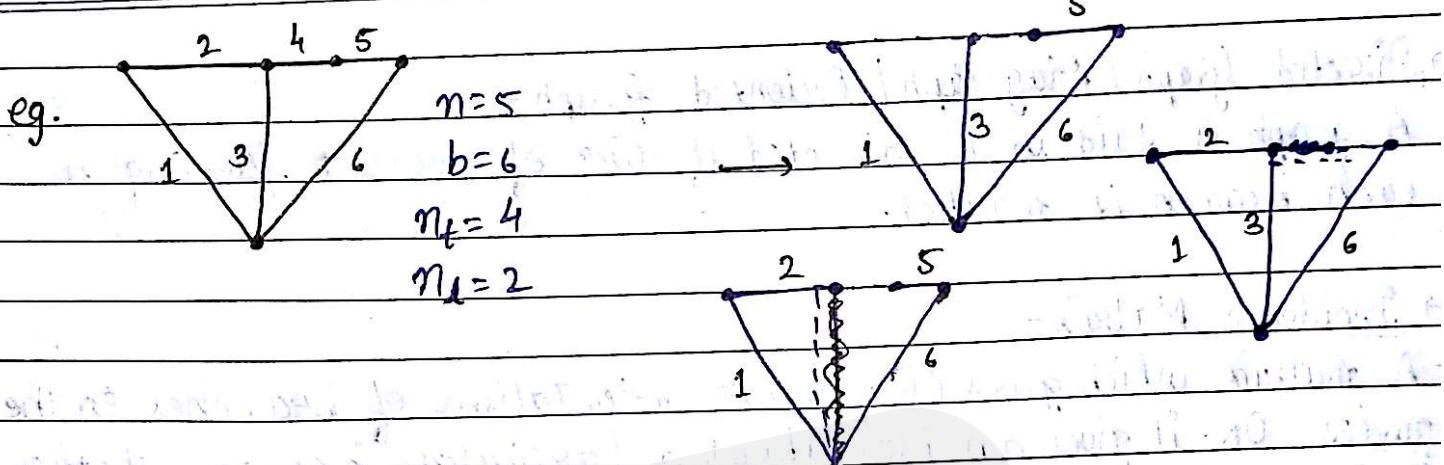- i) Draw the graph of given circuit
- ii) Count the no. of nodes, branches, twigs, links
- iii) Draw as many solid lines as n_t .
- iv) " dotted lines as n_l .




A single graph can have multiple no. of trees

Ques)

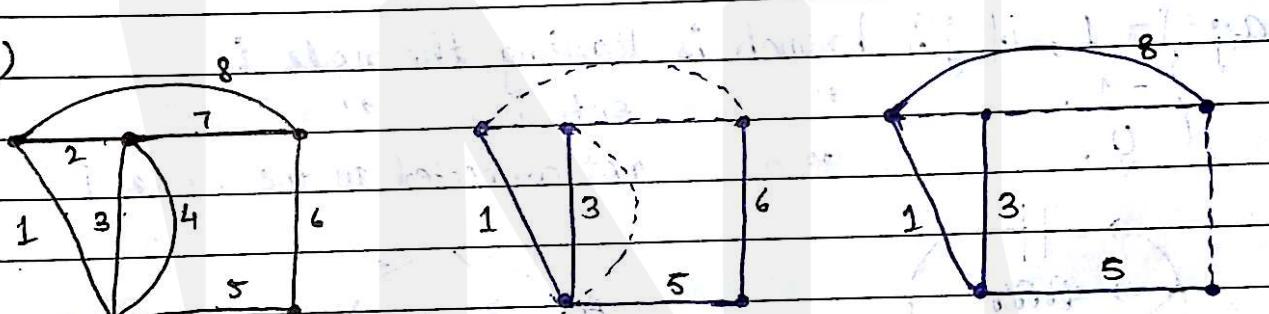

$$n=5, b=8$$

$$n_f=2, n_L=4$$

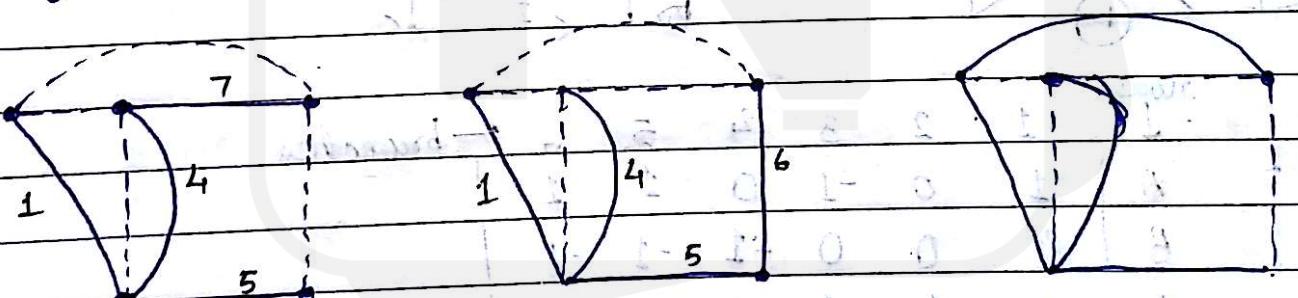



→ Directed Graph / Diagraph / Oriented graph -

A graph is said to be directed if direction of current flowing in each branch is marked.

→ Incidence Matrix -

- A matrix which gives idea about orientation of branches to the nodes OR it gives an idea about a particular branch whether it is leaving or entering a particular node.
- Represented by $[A_c]$

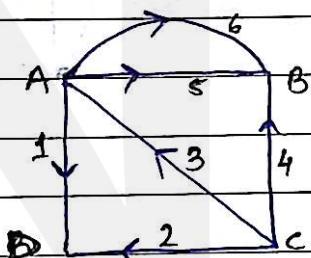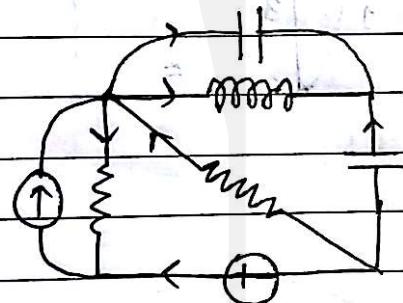$a_{ij} = \begin{cases} +1, & \text{if } j\text{th branch is leaving the node } i \\ -1, & \text{entering " } \\ 0, & \text{not connected to the node } i \end{cases}$




nodes ↓ 1 2 3 4 5 6 ← branches

$$[A_c] = \begin{bmatrix} A & 1 & 0 & -1 & 0 & 1 & 1 \\ B & 0 & 0 & 0 & -1 & -1 & -1 \\ C & 0 & 1 & 1 & 1 & 0 & 0 \\ D & -1 & -1 & 0 & 0 & 0 & 0 \end{bmatrix}$$

If direction of branches is not specified in the graph, we can assume any direction.

→ Properties of complete incidence matrix $[A_{C}]$

- 1) Sum of each column of $[A_{C}]$ is zero.
- 2) Determinant of $[A_{C}]$, ie. $|A_C| = 0$ always.

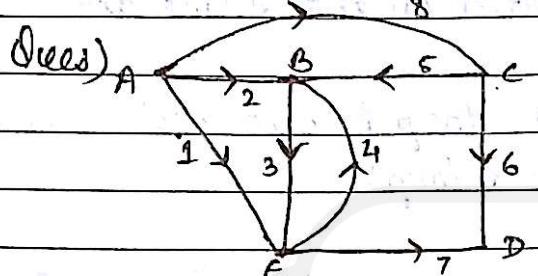

	1	2	3	4	5	6	7	8
A	1	1	0	0	0	0	-1	1
B	0	-1	1	-1	-1	0	0	0
C	0	0	0	0	1	1	0	-1
D	0	0	0	0	0	-1	-1	0
E	-1	0	-1	1	0	0	1	0

→ Reduced Incidence Matrix $[A]$

- If a node in a graph is taken as reference node or datum node, then the incidence matrix obtained will be reduced IM.
- Any node of given graph can be taken as reference node if this does not change the behaviour of the circuit.

No. of Trees of a graph = $\text{Det } [A_A]$

- Reduced IM can also be written as $[A] = [A_t \ A_l]$

→ Fundamental loop Matrix / Tie-set Matrix -

- It is a matrix used to find branch current in terms of link current for a given tree of a graph.


- It is formed by only one link associated with other tungs.

- No. of tie-sets or fundamental loops = no. of links

- KVLI is applicable in each loop

Procedure for obtaining tie-sets -

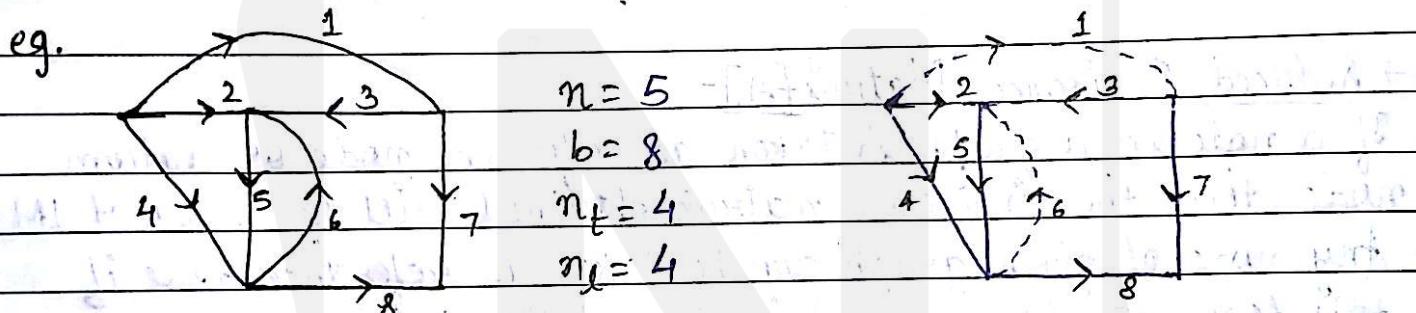- i) draw the graph
- ii) form the tie-sets with each link in the graph for the entire tree.
- iii) Assume the direction of tie-sets oriented in the same dirⁿ as that of link.
- iv) $b_{ij} = \begin{cases} -1, & \text{if the } j\text{th branch is in the loop } i, \text{ but dir}^n \\ & \text{are different (for branch \& loop)} \\ +1, & \text{dir}^n \text{ is same} \\ 0, & \text{if the } j\text{th branch is not associated with loop } i. \end{cases}$




Tie-set matrix is represented by $[B_f]$

tie-sets

	1	2	3	4	5	6	7	8
(2,4,5)	0	+1	0	-1	+1	0	0	0
(5,6)	0	0	0	0	1	1	0	0
(5,6,3,8)	0	0	+1	0	+1	0	-1	+1
(1,4,7,8)	1	0	0	-1	0	0	1	-1

Each tie-set loop chosen should have only one dotted line.

Ques)

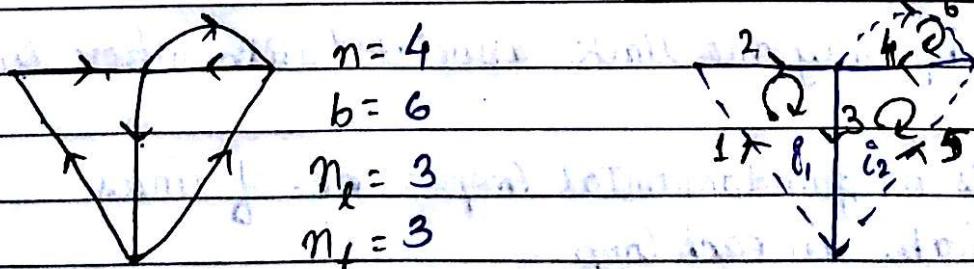

v_1	v_2	v_3	v_4	v_5	v_6	Date: 11/11/11
J_1	J_2	J_3	J_4	J_5	J_6	
i_1	2	3	4	5	6	
$[B_f] =$	$i_1 \begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 0 \\ i_2 & 0 & 0 & +1 & +1 & +1 \\ i_3 & 0 & 0 & 0 & 1 & 0 \end{bmatrix}$					

- NOTE: 1) Dirⁿ of link determines the dirⁿ of loop.
 2) No. of loops = no. of links

3) $B_f = [B_{f1} : B_{f2} : B_{f3}] = [B_{f1} : v]$

\downarrow \downarrow
links links

- 4) Tie-set gives branch current in terms of links current.
 5) If j_1, j_2, \dots, j_6 are the corresponding branch currents,
 then (for B_f matrix shown above),

$$J_1 = i_1$$

$$J_3 = i_1 + i_2$$

$$J_5 = i_2$$

$$J_2 = i_1$$

$$J_4 = i_2 + i_3$$

$$J_6 = i_3$$

- 6) Tie-set matrix gives loop eqⁿ by adding voltage of each branch in a particular tie set.


Let v_1, v_2, \dots, v_6 be the branch voltages.

Then

$$v_1 + v_2 + v_3 = 0, \text{ for } i_1$$



~~$v_2 + v_3 + v_4 + v_5 = 0, \text{ for } i_2$~~

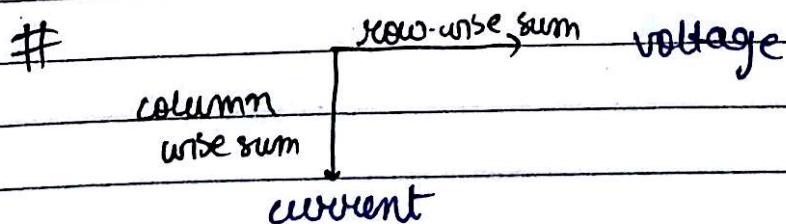~~$v_4 + v_5 + v_6 = 0, \text{ for } i_3$~~



→ Procedure for obtaining a Cut-set matrix -

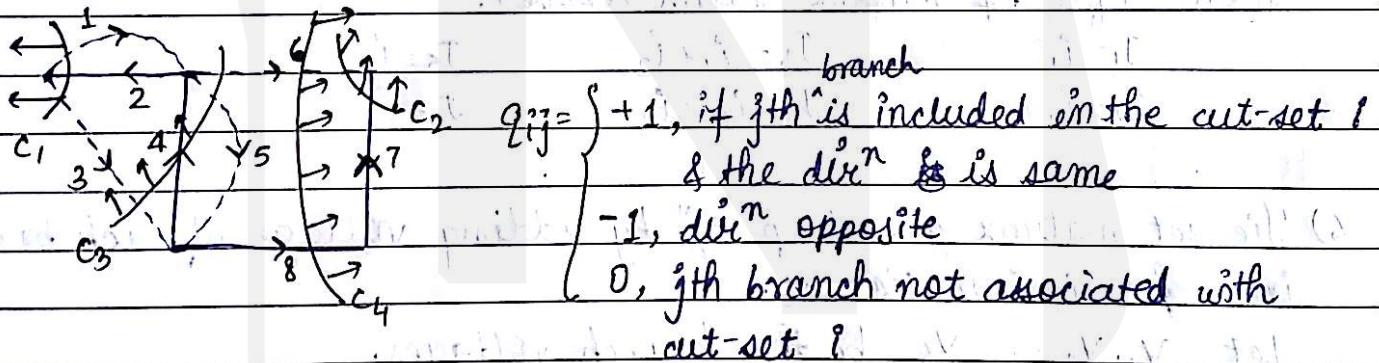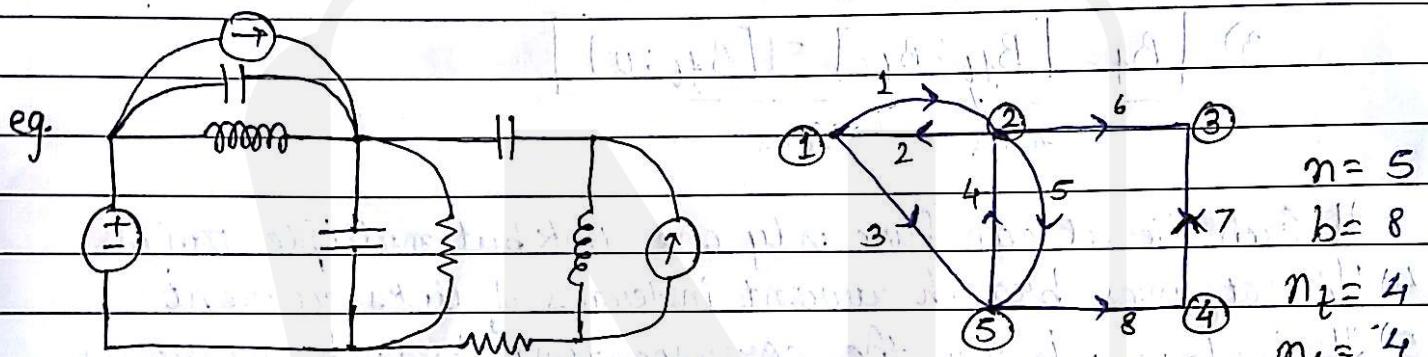- 1) Draw the graph of the given circuit.
- 2) Select a tree.
- 3) Count the no. of twigs; and the no. of cut-sets are equal to the no. of trees twigs.
- 4) dirⁿ of cut-set depends upon the dirⁿ of twig.
- 5) One cut-set must have a twig but not more than one.



Cut-set matrix,

	1	2	3	4	5	6	7	8
$Q_f = C_1$	-1	+1	-1	0	0	0	0	0
C_2	0	0	0	0	0	+1	+1	0
C_3	0	0	-1	+1	-1	-1	0	0
C_4	0	0	0	0	0	+1	0	1

Cut-set matrix can also be written as:

$$[Q_f] = [Q_{ft} : Q_{f,t}] = [U : Q_{f,t}]$$

$$[Q_f] = \begin{vmatrix} 2 & 7 & 4 & 8 & : & 1 & 3 & 5 & 6 \\ -1 & 0 & 0 & 0 & : & -1 & -1 & 0 & 0 \\ 0 & +1 & 0 & 0 & : & 0 & 0 & 0 & +1 \\ 0 & 0 & +1 & 0 & : & 0 & -1 & -1 & -1 \\ 0 & 0 & 0 & 1 & : & 0 & 0 & 0 & +1 \end{vmatrix}$$

To check whether our $[Q_f]$ is correct, verify the presence of atleast one diagonal matrix in the matrix $[Q_{ft}]$.


NOTES:

i) KCL eqⁿ can be obtained from $[Q_f]$.

If I_1, I_2, \dots, I_8 be branch currents, then for each row

$$\left. \begin{array}{l} -I_1 + I_2 - I_3 = 0 \\ I_6 + I_7 = 0 \\ -I_3 + I_4 - I_5 - I_6 = 0 \\ I_6 + I_8 = 0 \end{array} \right\} [Q_f] I_b = 0$$

Ques)

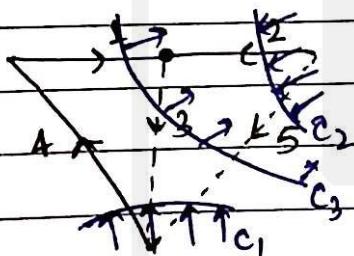

$$Q_f = \begin{matrix} C_1 & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ C_2 & \begin{matrix} 0 & 0 & -1 & 1 & -1 \\ 0 & 1 & 0 & 0 & 1 \end{matrix} \\ C_3 & \begin{matrix} 1 & 0 & -1 & 0 & -1 \end{matrix} \end{matrix}$$

$$Q_f = \begin{vmatrix} 4 & 2 & 1 & : & 3 & 5 \\ 1 & 0 & 0 & : & -1 & -1 \\ 0 & 1 & 0 & : & 0 & 1 \\ 0 & 0 & 1 & : & -1 & -1 \end{vmatrix}$$

→ Interrelation b/w various matrices & various parameters -

$$1) [A] = [A_t : A_L]$$


$$2) [B_f] = [B_{ft} : B_{fl}] = [B_{ft} : V]$$

$$3) [Q_f] = [Q_{ft} : Q_{fl}] = [V : Q_{fl}]$$

$$4) \text{KVL eqn: } B_f V_b = 0$$

$$5) \text{KCL eqn: } Q_f I_b = 0$$

$$A I_b = 0$$

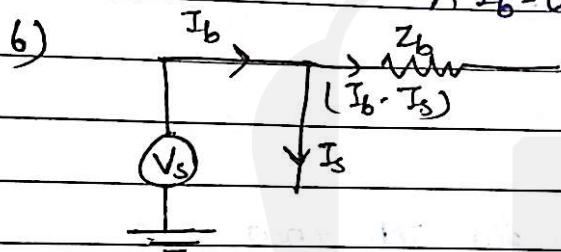

$$V_b = \frac{V_s}{Z_b} + Z_b (I_b - I_s)$$

$$I_b = I_s + Y_b (V_b - V_s)$$

$$7) A \text{ and } B_f \text{ are orthogonal i.e. } [A(B_f)^T = 0]$$

$$8) B_f \text{ and } Q_f \text{ are orthogonal}$$

$$\text{i.e. } [B_f (Q_f)^T = 0]$$

→ Relation b/w matrices :-

$$1) A(B_f)^T = 0$$

$$[A_t : A_L] \begin{bmatrix} B_{ft}^T \\ U \end{bmatrix} = 0 \quad [U^T = U]$$

$$A_t B_f^T + A_L = 0$$

$$(2) B_f \cdot (Q_f)^T = 0$$

$$[B_{ft} : V] \begin{bmatrix} V \\ Q_{fl}^T \end{bmatrix} = 0$$

$$B_{ft} + Q_{fl}^T = 0$$

$$\text{or } \boxed{B_{ft}^T = -A_L(A_t^{-1})} \quad \text{--- (1)}$$

$$\boxed{Q_{fl}^T = -B_{ft}} \quad \text{--- (ii)}$$

$$3) A \text{ and } Q_f$$

$$\text{from (1) \& (ii), } \boxed{Q_{fl} = A_L(A_t^{-1})}$$

Relation among parameters

① Relation b/w link voltages & twig voltages.

v_L & v_t

$$\beta_{fl} v_b = 0$$

$$[\beta_{fl} : v] \begin{bmatrix} v_t \\ v_L \end{bmatrix} = 0$$

$$\beta_{fl} v_t + v_L = 0$$

$$\Rightarrow v_L = -\beta_{fl} v_t$$

Also,

$$\Rightarrow v_L = \alpha_{fl}^T v_t$$

$$\therefore \beta_{fl} = -\alpha_{fl}^T$$

②

Relation b/w

v_b & v_t

$\frac{v_b}{\text{link}}$ $\frac{v_t}{\text{twig}}$

$$\begin{bmatrix} v_b \\ v_t \end{bmatrix} = \begin{bmatrix} v_t \\ \dots \\ v_L \end{bmatrix}$$

$$\begin{bmatrix} v_b \\ v_t \end{bmatrix} = \begin{bmatrix} v_t \\ \dots \\ \alpha_{fl}^T v_t \end{bmatrix} = v_t \begin{bmatrix} 1 \\ \alpha_{fl}^T \end{bmatrix}$$

$$v_b = v_t \alpha_{fl}^T$$

③

v_b & v_L

$$\begin{bmatrix} v_b \\ v_t \end{bmatrix} = \begin{bmatrix} v_t \\ \dots \\ v_L \end{bmatrix} = \begin{bmatrix} -\beta_{fl}^{-1} v_L \\ v_t \\ v_L \end{bmatrix} = v_L \begin{bmatrix} -\beta_{fl}^{-1} \\ 1 \\ 1 \end{bmatrix}$$

$$v_b = -\beta_{fl}^{-1} v_L$$

(4)

If A T₂

$$\delta_f I_b \Rightarrow$$

$$[V : \delta_{f\ell}] \left[\begin{array}{c} I_t \\ I_e \end{array} \right] = 0$$

$$I_t + \delta_{f\ell} I_e = 0$$

$$I_t = -\delta_{f\ell} I_e$$

(5)

A E D

$$A I_b \Rightarrow$$

$$[A_t : A_e] \left[\begin{array}{c} I_t \\ I_e \end{array} \right] = 0$$

$$A_t I_t + A_e I_e = 0$$

$$I_t = -A_e^{-1} A_t I_e$$

$$I_t = -A_e^{-1} A_t I_e$$

$$\therefore I_t = -\delta_{f\ell} I_e \Rightarrow A_e A_t^{-1} I_e = B_{ft}^T I_e$$

(6)

I_b & I_e

$$[I_b] = \left[\begin{array}{c} I_t \\ I_e \end{array} \right] = \left[\begin{array}{c} B_{ft}^T I_e \\ I_e \end{array} \right] = B_{fe}^T I_e$$

$$I_b = B_{fe}^T I_e$$

(7)

$$V_b = A^T V_n$$

V_b & V_n

Network Analysis using Graph Theory

$$V_b = V_s + Z_b (I_b - I_s) \quad \text{---(1)}$$

$$I_b = I_s + Y_b (V_b - V_s) \quad \text{---(2)}$$

where, V_b is the branch voltage matrix, of size 6×1 $\left\{ \begin{matrix} = \\ \vdots \\ = \end{matrix} \right\} = 7$

I_b : Branch current matrix, of size 6×1 $\left\{ \begin{matrix} = \\ \vdots \\ = \end{matrix} \right\} = 7$

V_s : voltage source matrix, of size 6×1

I_s : current source matrix, of size 6×1

Z_b → branch impedance matrix - of 6×6

Y_b → branch Admittance matrix, of 6×6

* Loop Analysis

$$V_b = V_s + Z_b (I_b - I_s)$$

Premultiply by fundamental cut set matrix:-

$$B_f V_b = B_f V_s + B_f Z_b (I_b - I_s)$$



$$B_f V_b = B_f V_s + B_f Z_b (I_s^T I_L - I_s)$$

$$0 = B_f V_s + B_f^T Z_b I_L - B_f Z_b I_s$$

$$\underbrace{B_f Z_b I_s}_V - \underbrace{B_f V_s}_V = \underbrace{B_f Z_b B_f^T}_{Z_L} I_L$$

CLASSTIME / Page No.
Date / /

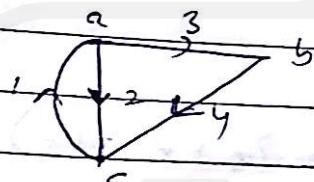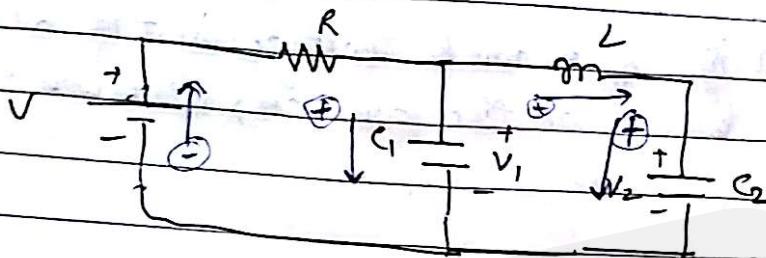Q Obtain the matrix loop eqn of the given network :-



$$\text{Impedance of } C_1 \Rightarrow \frac{1}{C_1 s}$$


$$n = 3$$

$$b = 4$$

$$t = 2$$

$$l = 2$$
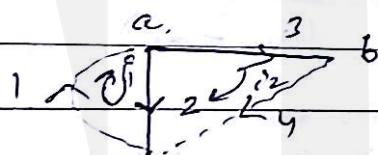
$$\text{Impedance of Inductor} \Rightarrow Ls$$



$$V_S = \begin{bmatrix} -V_3 \\ V_1 \\ 0 \\ V_2 \end{bmatrix}$$

$$B_f = \begin{bmatrix} S_1 & 1 & 1 & 0 & 0 \\ S_2 & 0 & -1 & 1 & 1 \end{bmatrix}$$

$$Z_b = \begin{bmatrix} 1 & 2 & 3 & 4 \\ 1 & R & 0 & 0 \\ 2 & 0 & \frac{1}{C_1 s} & 0 & 0 \\ 3 & 0 & 0 & Ls & 0 \\ 4 & 0 & 0 & 0 & \frac{1}{C_2 s} \end{bmatrix}$$

$$I_S = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$V_L = -B_f V_S$$

$$Z_L = B_f Z_b B_f^T \quad I_L = \begin{bmatrix} i_1 \\ i_2 \end{bmatrix}$$

$$V_L = \begin{bmatrix} V - V_1 \\ V_1 - V_2 \end{bmatrix}$$

$$Z_L = \begin{bmatrix} R + \frac{1}{C_1 s} & -\frac{1}{C_1 s} \\ -\frac{1}{C_1 s} & Ls + \frac{1}{C_1 s} + \frac{1}{C_2 s} \end{bmatrix}$$

CLASSTIME	Page No.
Date	/ /

sign convention for voltage source metric

The polarity of branch voltage is +ve at the tail end of the arrow on the branch, otherwise -ve.

* Nodal Analysis

$$I_b = I_s + Y_b (V_b - V_s) \quad \text{--- (1)}$$

Premultiply by the reduced incidence matrix.

$$A I_b = A I_s + A Y_b (V_b - V_s)$$

$$0 = A I_s + A Y_b V_b - A Y_b V_s$$

$$\{ V_b = A^T V_n \}$$

$$0 = A I_s + A Y_b A^T V_n - A Y_b V_s$$

$$A Y_b V_s - A I_s = A Y_b A^T V_n$$

$\curvearrowleft I_n$

$\curvearrowright Y_n$


matrix

Node

eqn

$$I_n = Y_n V_n$$

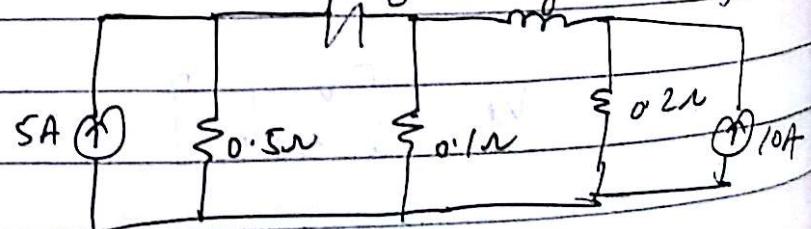Q) Write matrix node eqn for a given network:-



CLASSTIME	PAGE NO.
Date	/ /

SOM



$$n=4$$

$$b=5$$

Taking 'd' node as datum/reference node:-

$$[A] = \begin{matrix} a & \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ -1 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & -1 & 0 & 1 \end{bmatrix} \\ b & \\ c & \end{matrix}$$

$$[Y_b] = \begin{matrix} 1 & \begin{bmatrix} 1 & 2 & 3 & 4 & 5 \\ 2 & 0 & 0 & 0 & 0 \\ 0 & 10 & 0 & 0 & 0 \\ 0 & 0 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0.25 & 0 \\ 0 & 0 & 0 & 0 & -0.5 \end{bmatrix} \\ 2 & \\ 3 & \\ 4 & \\ 5 & \end{matrix}$$

$$V_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad I_s = \begin{bmatrix} 5 \\ 0 \\ 10 \\ 0 \\ 0 \end{bmatrix}$$

* Cut Set Analysis $\rightarrow I_n = \{ - \}$
 $I_b = I_s + Y_b (V_b - V_s) \quad Y_n = \{ - \}$

Premultiplying ~~both~~ by Φ_f :-

$$\Phi_f I_b = \Phi_f I_s + \Phi_f Y_b V_b \quad \boxed{\Phi_f Y_b V_b}$$

$$\boxed{V_b = \Phi_f^T V_t}$$

$$0 = \Phi_f^T I_s + \Phi_f^T Y_b \Phi_f^T V_t - \Phi_f^T V_b V_b$$

$$\Phi_f^T V_b V_b - \Phi_f^T I_s = \underbrace{\Phi_f^T Y_b \Phi_f^T V_t}_{\text{matrix}} \quad \text{matrix}$$

$$\boxed{I_t = Y_t \cdot V_t} \quad \text{cut set matrix}$$

Lecture 1

CLASSTIME / Page No.

Date / /

Two networks are said to be dual of each other, if incidence matrix of one network is same as that of other.

Procedure to obtain the dual of a network :

Step

1. Mark (•) in the ^{center of} each loop.
2. Mark an extra dot (•) outside the ckt, which is known as reference/datum node.
3. Draw the dotted line such that each ~~to~~ ckt element is cut by only one line
4. Draw the dual network by connecting all the nodes to the dual of ckt element.

series \longleftrightarrow parallel

$V \longleftrightarrow I$

$R \longleftrightarrow G$


$L \longleftrightarrow C$

node \longleftrightarrow loop

$RCL \longleftrightarrow RVL G$

tree \longleftrightarrow cotree

twig \longleftrightarrow link

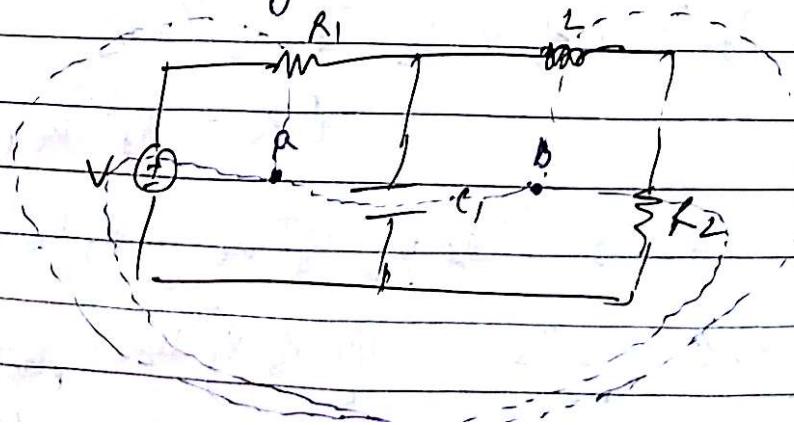

$$\begin{aligned}
 P(s) &= s^2 + 2s^2 + 2s + 1 \\
 &\quad \text{H(3)} \\
 &= (s^2 + 2s + 2)(s^2 + 2s + 2) \\
 &\quad \downarrow \qquad \downarrow \\
 &\quad \text{non-Hurwitz} \qquad \text{Hurwitz}
 \end{aligned}$$

$\therefore P(s)$ is non-Hurwitz

$\therefore P(s)$ is also non-Hurwitz.

Positive Real function

A function $T(s)$ is said to be positive real if ~~satisfies~~ the following conditions:-

* If $T(s)$ is real for ' s ' is real.

* $T(s)$ polynomial is always Hurwitz polynomial DC (check only denominator)

* $T(s)$ may have poles on jw axis.

* These poles are simple poles & their residues are real & +ve.

* The real part of $T(j\omega)$ is > 0

Necessary & sufficient conditions for a function to be positive real are as follows:-

Condition 1 $T(s)$ must not have any poles in the right half of the 's' plane i.e. ~~poles~~ denominator $D(s)$ must be Hurwitz polynomial

2 Only simple poles can exist on the imaginary axis.

3 The poles and zeros of a PRF are real or occur in conjugate pairs.

4 The difference in highest powers of $N(s)$ & $D(s)$ may differ at most by unity.

5 The difference in lowest powers of $N(s)$ & $D(s)$ may differ at most by unity.

Ques Check whether the given $f(s)$ is a PRF:-

$$(1) \quad f(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

$$(1) \quad D(s) = s^2 + 4s + 3$$

! !
Yes, it is Hurwitz.

C2 x

$$(2) \quad M_1(s) = s^2 + 8$$

$$N_1(s) = 6s$$

$$M_2(s) = s^2 + 3$$

$$N_2(s) = 4s$$

$$M_1 M_2 - N_1 N_2 = (s^2 + 8)(s^2 + 3) - 24s^2 \geq 0$$

$$= s^4 + 11s^2 + 24 - 24s^2 \geq 0$$

$$= s^4 - 13s^2 + 24 \geq 0$$

put $s = j\omega$

$$\Rightarrow \omega^4 + 13\omega^2 + 24 \geq 0 \text{ for all } \omega$$

∴ it is a PRF

LAST TIME Page No.
Date / /

2 Only simple poles can exist on the imaginary axis.

3 The poles and zeros of a PRF are real or occur in conjugate pairs.

4 The difference in highest powers of $N(s)$ & $D(s)$ may differ at most by unity.

5 The difference in lowest powers of $N(s)$ & $D(s)$ may differ at most by unity.

Ques Check whether the given $f(s)$ is a PRF:-

$$(2) \quad f(s) = \frac{s^2 + 6s + 8}{s^2 + 4s + 3}$$

$$(1) \quad D(s) = s^2 + 4s + 3$$

Yes, it is Nyquist.

$$(2) \quad \infty$$

$$(3) \quad M_1(s) = s^2 + 8$$

$$N_1(s) = 6s$$

$$M_2(s) = s^2 + 3$$

$$N_2(s) = 4s$$

$$M_1 M_2 - N_1 N_2 = (s^2 + 8)(s^2 + 3) - 8s^2 - 24s^2 \geq 0$$

$$= s^4 + 11s^2 + 24 - 24s^2 \geq 0$$

$$= s^4 - 13s^2 + 24 \geq 0$$

$$\text{put } s = j\omega$$

$$\Rightarrow \omega^4 + 13\omega^2 + 24 \geq 0 \text{ for all } \omega$$

\therefore it is a PRF

CLASSTIME / PAGE NO.
Date / /

$$(11) \quad Z(s) = \frac{s^3 + 5s^2 + 9s + 3}{s^3 + 4s^2 + 7s + 9}$$

SLNL

~~Ans~~ ~~Ans~~
 $N(s) = 4s^2 + 9$
 $D(s) = s^3 + 7s$

$$4s^2 + 9 \quad \int s^3 + 7s \quad \left(\begin{array}{l} s/4 \\ s^3 + \frac{9}{4}s \end{array} \right)$$

$$\overline{26s} \quad \overline{4s^2 + 9}$$

{ }
{ }

yes it is P.R.F

$$(3) \quad m(s) = 5s^2 + 3$$

$$n_1(s) = s^3 + 9s$$

$$m_2(s) = 4s^2 + 9$$

$$n_2(s) = s^3 + 7s$$

$$\Rightarrow (5s^2 + 3)(4s^2 + 9) - (s^3 + 9s)(s^3 + 7s)$$

$$\Rightarrow 20s^4 + 57s^2 + 27 - s^6 - 16s^4 - 63s^2$$

$$\Rightarrow -s^6 + 20s^4 - 6s^2 + 27$$

$$\star s = j\omega$$

$$-j^6\omega^6 + 20\omega^4 + 6\omega^2 + 27$$

$$\omega^6 + 20\omega^4 + 6\omega^2 + 27 \geq 0 \text{ for all } \omega$$

yes it is P.R.F

$$(14) P(s) = \frac{2s^2 + s}{s(s^2 + 1)}$$

CLASS/NAME	PAGE NO.
	1

D(s) = $s^3 + s$

yes Hurwitz

C₂
roots = $\pm j$

Solving by partial

$$= \frac{A}{s} + \frac{Bs + C}{s^2 + 1}$$

$$= \frac{5}{s} + \frac{-3}{s^2 + 1}$$

~~Note!~~
Check only ~~for poles only~~
at ~~for poles only~~
i.e. for $s < 0$
-A doesn't matter.

As the residue of complex poles are -ve, \therefore not a PRP

C₁ Check for two real nos:—

C₂ $f(s) = \frac{s+2}{s+1}$

C₁ $s=1$ ~~2~~ \therefore lying in left side
 \therefore Hurwitz

C₃ ? put $s=j\omega$
 $\Re\{f(j\omega)\} > 0$

$$\Rightarrow \frac{j\omega + 2}{j\omega + 1} (j\omega - 1)$$

$$= s \frac{-\omega^2 + j\omega - 2}{(-2)} \Rightarrow \frac{-\omega^2 - 2}{-2} \Rightarrow \frac{\omega^2 + 2}{2} > 0$$

\therefore yes L.H.

CLASS DATE	Page No.
Date	/ /

~~Q~~ $y(s) = \frac{s^2 + 2s + 10}{s+10}$

~~C1~~ $s = -10$ Minus π

~~C2~~ $M_1(s) = s^2 + 20$

$N_1(s) = 2s$

$M_2(s) = 10$

$N_2(s) = s$

$(s^2 + 20)(10) - (2s)(s)$

$10s^2 + 200 - 2s^2$

$8s^2 + 200$

put $s = j\omega$

$-8\omega^2 + 200 \neq 0$ not always

~~Q~~ $f(s) = \frac{s^2 + s + 6}{s^2 + s + 1}$

~~C1~~ Minus π

~~C2~~ λ

~~C3~~ $M_1(s) = s^2 + 6$

$N_1(s) = s$

$M_2(s) = s^2 + 1$

$N_2(s) = s$

$(s^2 + 6)(s^2 + 1) - s^2$

$s^4 + 2s^2 + 6 - s^2$

$s^4 + 6s^2 + 6$

$\omega^4 - 6\omega^2 + 6 \neq 0$

CLASSTIME	Page No.
Date	/ /

As we can't conclude whether the real part of $f(jw)$ is > 0 or not.

In that case, Sturm's test is done to check the true realness.

$$w^4 - 6w^2 + 6$$

$$\text{put } w^2 = x$$

$$A_0(n) = x^2 - 6x + 6$$

$$\frac{dA_0}{dx} = A_1(n) = 2x - 6$$

$$\left[\frac{A_0(n)}{A_1(n)} = (K_1 x - K_0) - \frac{A_3(x)}{A_0(x)} \right]$$

$$\begin{array}{r} \frac{A_0(n)}{A_1(n)} \\ 2x-6 \end{array} \overline{) x^2 - 6x + 6} \begin{array}{l} \frac{x-3}{x^2-3x} \\ \hline -3x+6 \\ \hline -3x+9 \\ \hline -3 \end{array}$$

$$\frac{A_0(n)}{A_1(n)} = (2x-6) + \overline{-3} \quad x^2 - 6x + 6$$

$$\begin{array}{c} A_3(n) = 3 \\ \begin{array}{c|ccccc|c} & A_0 & A_1 & A_2 & A_3 & & \text{sign changes} \\ \hline x=0 & + & - & + & + & 2 & \leftarrow \\ x=0 & + & + & + & + & 0 & \leftarrow \end{array} \end{array}$$

if some ; then
PRF
otherwise it can't
be PRF.

Unit-IV

DETA
Page No.
Date / /

11 Oct/17

Network Functions -


$$H(s) = \frac{N(s)}{D(s)}$$

Laplace operator

$$= \frac{a_0 s^n + a_1 s^{n-1} + a_2 s^{n-2} + \dots + a_n}{b_0 s^n + b_1 s^{n-1} + b_2 s^{n-2} + \dots + b_m}$$

$$= \frac{a_0 (s-z_1)(s-z_2) \dots (s-z_n)}{b_0 (s-p_1)(s-p_2) \dots (s-p_m)}$$
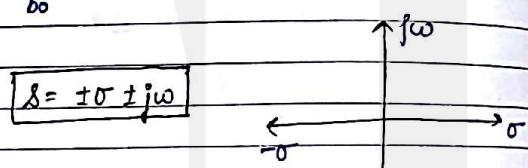
$$= \frac{a_0}{b_0} = K \text{ (scale factor)}$$



zeroes represented by o
poles " x

$$\text{eg. } N(s) = \frac{2s(s+1)}{(s+2)(s^2+2s+2)}$$

Roots of numerator gives zeroes
Roots of denominator give poles


$\therefore z_1 \text{ at } s=0 \quad ; \quad z_2 \text{ at } s=-1$

for poles,

$$p_1 = -2$$


$$p_2 = (-1+j), (-1-j)$$

Plotting these on s-plane,

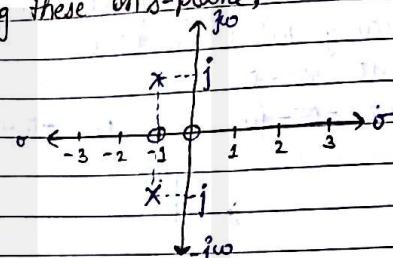

$$N(s) = \frac{\text{scale factor}}{(s^2+16)} = \frac{2s}{(s+j4)(s-j4)}$$

scale factor: Ratio of co-efficient of highest power terms of N^n & D^n .

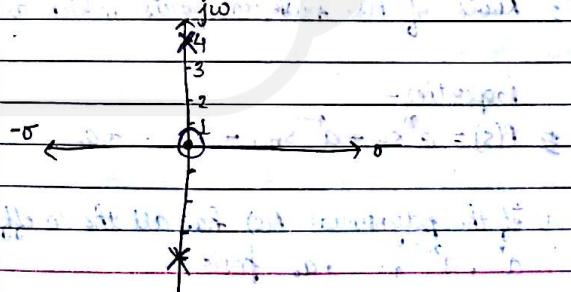Zero is at $s=0$.Poles: $p_1 = -j4, p_2 = +j4$ 

(Ans) $f(t) = e^{-\sigma t} \cos \omega t$


$$\begin{aligned} L[f(t)] &= \frac{s+\sigma}{(s+\sigma)^2 + \omega^2} \\ &= s+\sigma \end{aligned}$$

$$(s+\sigma + j\omega)(s+\sigma - j\omega)$$

Putting $N^r = 0$ & $D^r = 0$

At $\sigma = -\sigma$
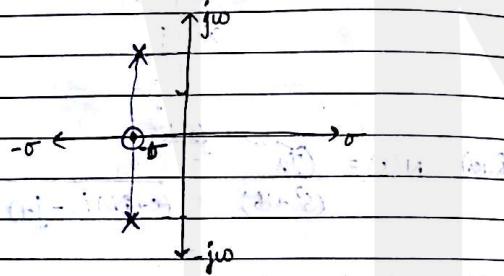
$$P_1 = -\sigma - j\omega \quad P_2 = -\sigma + j\omega$$



Properties of Hermitz Polynomial

It is a polynomial satisfying the following conditions -

- 1) $P(s)$ is real when s is real
- 2) Roots of $P(s)$ have real parts which are 0 or -ve.

Properties -

$$\therefore P(s) = a_n s^n + a_{n-1} s^{n-1} + \dots + a_0$$

- 3) If the polynomial $P(s)$ has all the co-efficients a_n, a_{n-1}, \dots, a_0 positive.

2) There should not be any missing terms unless the polynomial is even or odd.

3) Both even & odd parts of Hermitz polynomial have roots only on $j\omega$ axis.

4) The continued fraction expansion of the ratio of odd to even parts or even to odd parts of a Hermitz polynomial must give all the positive quotient terms.

5) If $P(s)$ is Hermitz poly and $W(s)$ is a multiplicative factor, then
 $P(s) W(s)$ is also a Hermitz poly. if
 $W(s)$ is also a Hermitz poly.

6) In case of either only even or only odd poly., it is not possible to obtain continued fraction expansion.

In such cases, a poly. $P(s)$ is Hermitz if the ratio of $P(s)$ and its derivative gives a continued fraction expansion with all positive quotient terms.

e.g. Check whether the given poly. is Hermitz or not

$$P(s) = s^4 + s^3 + 5s^2 + 3s + 4$$

- Step 1) All the co-efficients are +ve
- Step 2) Not applicable

3) even part: $s^4 + 5s^2 + 4 \rightarrow M(s)$
 odd part: $s^3 + 3s \rightarrow N(s)$

Now finding $M(s) \rightarrow$ because $M(s)$ has higher degree
 $N(s)$

Otherwise find $N(s)$ from $M(s)$

$$\begin{array}{r} s^3 + 3s \\ \times s^4 + 5s^2 + 4 \\ \hline -s^4 + 3s^2 \\ \hline 2s^2 + 4 \\ \hline s^3 + 3s \\ \hline s^2 + 2s \\ \hline s^2 + 4 \\ \hline \end{array}$$

$$\begin{array}{r} 2s^2 + 4s \\ \times 4 - 4s \\ \hline \end{array}$$

till remainder becomes equal to zero

If no -ve co-efficient occurs in the successive quotients, then it's a Hurwitz poly.

(Ques) Find the value of a so that the given polynomial is Hurwitz.

$$P(s) = s^4 + s^3 + as^2 + 2s + 3$$

$$M(n) = s^4 + as^2 + 3$$

$$N(n) = s^3 + 2s$$

$$(s^3 + 2s) \mid s^4 + as^2 + 3 \quad (s)$$

$$s^4 + 2s^2$$

$$(a-2)s^2 + 3 \quad \frac{s^3 + 2s}{s/a-2} \Rightarrow a-2 > 0$$

$$\frac{(a-2)^3 + 3a}{(a-2)} \quad a > 2$$

$$\left(\frac{2-3}{a-2} \right) s \quad (a-2)s^2 + 3 \quad ($$

$$> 0$$

$$\left\{ \begin{array}{l} 2 - \frac{3}{a-2} > 0 \\ a-2 - 3 > 0 \end{array} \right.$$

$$2a-4-3 > 0$$

$$\boxed{a > \frac{7}{2}}$$

(Ques) Find the range of values of m so that the given poly. is Hurwitz.

$$P(s) = 2s^4 + s^3 + ms^2 + s + 2$$

$$M(s) = 2s^4 + ms^2 + 2$$

$$N(s) = s^3 + s$$

$$(s^3 + s) \mid 2s^4 + ms^2 + 2 \quad (2s^4 + 2s^2)$$

$$(m-2)s^2 + 2 \quad s^3 + s \quad \frac{1}{(m-2)} \Rightarrow m > 2$$

$$s^3 + 2s$$

$$\frac{(1-2)}{m-2} s \quad ($$

$$1 - 2 > 0$$

$$m-2$$

$$m-2-2 > 0$$

$$m > 4 \Rightarrow [m \in (4, \infty)]$$

$$P(s) = 4s^6 + 2s^5 + 17s^4 + 8s^3 + 16s^2 + 6s + 3$$

$$M(s) = 4s^6 + 17s^4 + 16s^2 + 3$$

$$N(s) = 2s^5 + 8s^3 + 6s$$

$$2s^5 + 8s^3 + 6s \quad 4s^6 + 17s^4 + 16s^2 + 3 \quad (2s^5 + 8s^3 + 6s)$$

$$4s^6 + 16s^4 + 12s^2$$

$$s^4 + 4s^2 + 3 \quad 2s^5 + 8s^3 + 6s \quad (2s^5 + 8s^3 + 6s)$$

$$2s^5 + 8s^3 + 6s$$

NOTE: If the continued fraction expansion suddenly terminates, then the last divisor is the common factor. We have to then

determine the other factor by dividing $P(s)$ by this divisor.

These factors are then checked individually whether they are Hurwitz or not.

If both factors are Hurwitz, then given polynomial is Hurwitz; otherwise not.

$$4s^4 + 2s^3 +$$

$$\begin{array}{r} s^4 + 4s^2 + 3 \\ \times s^6 + 2s^5 + 17s^4 + 8s^3 + (6s^2 + 6)s + 3 \\ \hline - 4s^6 + - 16s^4 + + 12s^2 \\ \hline - 2s^5 + s^4 + 8s^3 + 4s^2 + 6s + 3 \\ \hline 2s^5 + - 8s^3 + + 6s \\ \hline s^4 + 4s^2 + 3 \\ \hline s^4 + 4s^2 + 3 \\ \hline \end{array}$$

$$\therefore \text{Factors are: } (s^4 + 4s^2 + 3)(4s^2 + 2s + 1)$$

Check individually

Ques) $P(s) = s^5 + 2s^2 + 3s + 6$

$M(s) = 2s^2 + 6$

$N(s) = s^3 + 3s$

$2s^2 + 6 \quad s^3 + 3s \left(\frac{\Delta}{2} \right)$

$s^3 + 3s \quad \text{roots in 2nd quadrant}$

$\therefore \text{It lies in -ve } x\text{-axis}$

$\therefore \text{It is not a Hurwitz poly.}$

Update 1
 $(s^2 + 6) \quad s^3 + 2s^2 + 3s + 6$

$$\begin{array}{r} s^6 + 6 \\ \hline - 2s^6 + - 2s^5 + - 2s^4 + - 2s^3 + - 2s^2 + - 2s \\ \hline 2s^5 + 6 \\ \hline 2s^2 + 6 \\ \hline \end{array}$$

Factors are: $(2s^2 + 6) \left(\frac{s^2 + 1}{2} \right)$

$4s \quad 2s^2 + 6 \left(\frac{s^2 + 1}{2} \right)$

$6) \quad 4s \left(\frac{4s}{6} \right)$

$\frac{4s}{X}$

$\frac{s+2}{2}$

$\leftarrow \times \rightarrow$

Lies in -ve x -axis

\therefore It is a Hurwitz poly.

Ques) $P(s) = s^5 + 9s^4 + 7s^3 + s^2 + 4s$

Constant term is missing.

\therefore It is not a Hurwitz poly.

NOTE:

1) Quadratic eqn is always a Hurwitz poly.

$$\text{Ques.) } P(s) = s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4$$

$$M(s) : 2s^6 + s^4 + 8s^2 + 4$$

$$N(s) : s^7 + 2s^5 + 4s^3 + 8s$$

$$\begin{aligned} & (2s^6 + s^4 + 8s^2 + 4) \left(s^7 + 2s^5 + 4s^3 + 8s \right) \left(\frac{s}{2} \right) \\ & \quad s^7 + \frac{s^5}{2} + 4s^3 + 2s \\ & \left(\frac{3s^5 + 6s}{2} \right) 2s^6 + s^4 + 8s^2 + 4 \left(\frac{4s}{3} \right) \\ & \quad s^6 + \frac{+24s^2}{3} \\ & \quad + s^4 + 4 \left(\frac{3s^5 + 6s}{2} \right) \left(\frac{ns}{2} \right) \\ & \quad \frac{3s^5 + 6s}{2} \end{aligned}$$

$$\begin{aligned} \text{Now, } & s^7 + 2s^6 + 2s^5 + 2s^4 + 2s^3 + 2s^2 + 2s + 1 \\ & s^4 + 4 \left(s^7 + 2s^6 + 2s^5 + s^4 + 4s^3 + 8s^2 + 8s + 4 \right) \\ & \quad + 4s^3 \\ & 2s^6 + 2s^5 + s^4 + 8s^2 + 8s + 4 \\ & 2s^6 + 2s^5 + s^4 + 8s^2 + 8s + 4 \\ & 2s^5 + s^4 + 8s + 4 \\ & 2s^5 + s^4 + 8s + 4 \\ & s^4 + 4 \\ & s^4 + 4 \\ & 4 \end{aligned}$$

Network synthesis -

Can be synthesised in 4 basic funcⁿ-

- 1) Foster - I / Foster series $\rightarrow Z(s)$
- 2) Foster - II / " parallel $\rightarrow Y(s)$
- 3) Cauer - I / $\left\{ \begin{array}{l} \text{Immittance} \\ \text{Admittance} \end{array} \right.$
- 4) Cauer - II / $\left\{ \begin{array}{l} \text{Impedance} \\ \text{Admittance} \end{array} \right.$

In case of Foster - I, starting fn must be impedance or $Z(s)$

Foster - II, starting fn must be admittance fn $Y(s)$

Ques.) An impedance fn has a pole-zero diagram as shown and $Z(-2) = -130$

Synthesise foster - I diagram.

$$\begin{aligned} & \text{scale factor} \\ & \Rightarrow Z(s) = K \frac{(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)} \\ & -130 = K \frac{[(-2)^2 + 1][(-2)^2 + 9]}{16 (-2)[(-2)^2 + 4]} \\ & \Rightarrow K = 2 \end{aligned}$$

$$\therefore Z(s) = 2 \frac{(s^2 + 1)(s^2 + 9)}{s(s^2 + 4)}$$

Two-port Networks

12/10/17



DELLA
Page No. / /
Date / /

Z Parameter -

$$(V_1, V_2) = f(I_1, I_2)$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\Rightarrow V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (1)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (11)}$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

There are two types of fn-


i) Driving point fn-ratio of quantity of same port
eg. Z_{11}, Z_{22}

ii) Transfer fn-ratio of quantities of diff. ports
eg. Z_{12}, Z_{21}

Transfer fn's are further classified into -

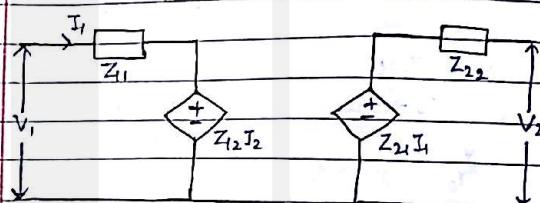
- i) Forward- ratio of o/p by i/p
- ii) Reverse- ratio of i/p by o/p

$Z_{11} \rightarrow$ Driving pt. if impedance when o/p is OP
 $Z_{22} \rightarrow$ Driving pt. o/p impedance when i/p is OP
 $Z_{12} \rightarrow$ Reverse Transfer Impedance, i/p is o/c
 $Z_{21} \rightarrow$ Forward Transfer Impedance, o/p is o/c



Eq. ckt. of Z-parameter

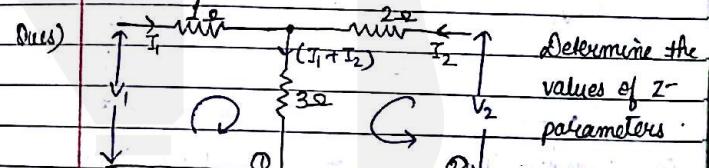$Z_{12} I_2$ & $Z_{21} I_1$ current dependent voltage sources



Applying KVL in

$$\text{Loop 1: } V_1 = I_1(1) + 3(I_1 + I_2) \quad \text{--- (1)}$$

$$V_1 = \frac{4}{Z_{11}} I_1 + \frac{3}{Z_{12}} I_2 \quad \text{--- (1)}$$

$$\text{Loop 2: } V_2 = 3I_1 + 5I_2 \quad \text{--- (11)}$$

$$\therefore Z = \begin{bmatrix} 4 & 3 \\ 3 & 5 \end{bmatrix}$$

OR

case I: when $I_2 = 0$

$$V_1 = 4I_1$$

$$V_2 = 3I_1$$

$$\frac{V_1}{I_1} = 4$$

$$\frac{V_2}{I_1} = 3$$

$$Z_{11} = 4$$

$$Z_{21} = 3$$

case II: when $I_1 = 0$

$$V_2 = 2I_2 + 3I_2$$


$$V_1 = 3I_2$$

$$\frac{V_2}{I_2} = 5$$

$$\frac{V_1}{I_2} = 3$$

$$Z_{12} = 5$$

$$Z_{22} = 3$$

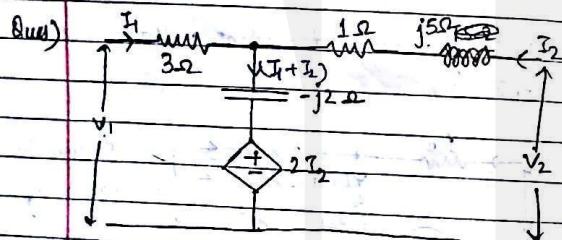

case I: when $I_2 = 0$

$$V_1 = 3I_1 - j2(I_1)$$

$$\frac{V_1}{I_1} = (3 - j2)$$

$$Z_{11} = (3 - j2)\Omega$$

$$V_2 = (-j2)I_1$$

$$\frac{V_2}{I_1} = -j2$$

$$Z_{21} = (-j2)\Omega$$

when $I_1 = 0$

$$V_1 = 2I_2 - j2I_2$$

$$\frac{V_1}{I_2} = (2 - j2)$$


$$Z_{12} = (2 - j2)\Omega$$

$$V_2 = (j5 + 1 - j2 + 2)I_2$$

$$\frac{V_2}{I_2} = 3 + 3j$$

$$Z_{22} = (3 + 3j)\Omega$$

Ques) Obtain the Z-parameters

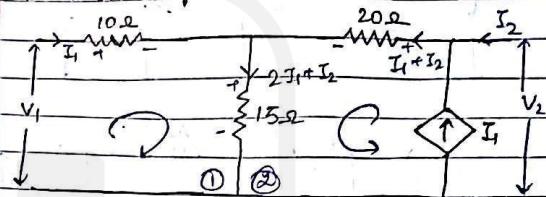

In case there is a current source in the ckt, look for a resistance connected in parallel to the current source and then convert them into voltage source.

Applying KVL in loop ①,

$$V_1 - 10I_1 - 15(2I_1 + I_2) = 0$$

$$V_1 = 40I_1 + 15I_2$$

$$Z_{11} = 40\Omega, Z_{12} = 15\Omega$$

Applying KVL in loop ②,


$$V_2 - 20(I_1 + I_2) - 15(2I_1 + I_2) = 0$$

$$V_2 - 20I_1 - 20I_2 - 30I_1 - 15I_2 = 0$$

$$V_2 = 50I_1 + 35I_2$$

$$Z_{21} = 50\Omega, Z_{22} = 35\Omega$$

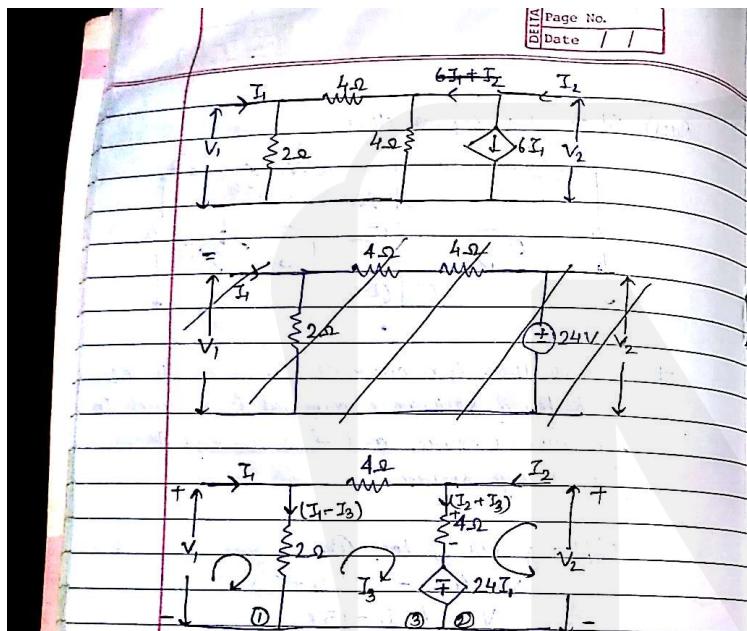Ques) Obtain the Z parameters of the given network.



Applying KVL in loop

$$\textcircled{1}: V_1 = 2(I_1 - I_3) \quad \text{--- (1)}$$

$$\textcircled{2}: V_2 = 4(I_2 + I_3) - 24I_1 \quad \text{--- (II)}$$

$$\textcircled{3}: -2(I_3 - I_1) - 4I_3 - 4(I_2 + I_3) + 24I_1 = 0 \\ -2I_3 + 2I_1 - 4I_3 - 4I_2 - 4I_3 + 24I_1 = 0 \\ 10I_3 = 26I_1 - 4I_2$$

$$I_3 = 2.6I_1 - 0.4I_2$$

Putting this value of I_3 in eqn $\textcircled{1}$,

$$V_1 = 2I_1 - 2(2.6I_1 - 0.4I_2)$$


$$V_1 = -3.2I_1 + 0.8I_2$$

DETA	Page No.
	1 / 1


$$Z_{11} = -3.2\Omega, Z_{12} = 0.8\Omega$$

$$\text{eqn } \textcircled{1}, V_2 = 4I_2 + 4I_3 - 24I_1 \\ V_2 = 4I_2 + 4(2.6I_1 - 0.4I_2) - 24I_1 \\ V_2 = -14.4I_1 + 2.4I_2$$

$$Z_{21} = -14.4\Omega, Z_{22} = 2.4\Omega$$

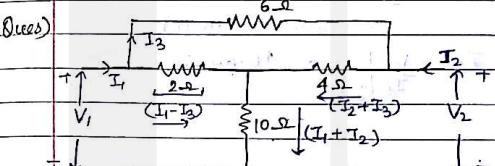

Case I: when $I_2 = 0$

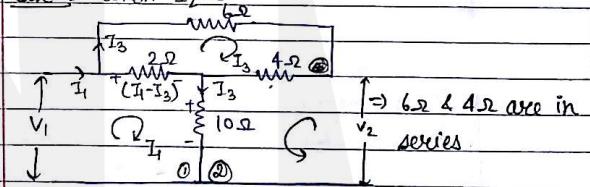

Applying KVL in loop $\textcircled{1}$,

$$V_1 - 2(I_1 - I_3) - 10I_1 = 0 \quad \text{--- (1)}$$

$$\text{loop } \textcircled{2}, V_2 - 4I_3 - 10I_1 = 0 \quad \text{--- (II)}$$

Applying current distribution (for parallel resistances)

$$I_3 = I_1 \times \frac{2}{10+2} \Rightarrow I_3 = 0.16I_1$$

Putting this value in eqⁿ ①,

$$V_1 - 12I_1 + 2I_3 = 0$$

$$V_1 - 12I_1 + 2(0.16I_1) = 0$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} = 11.68 \Omega$$

$$\text{eq}^n \text{ ②, } V_2 = 10I_1 + 4I_3 \\ = 10I_1 + 4(0.16I_1)$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} = 10.64 \Omega$$

→ Admittance Parameters / Impedance Parameters -
short circuit parameters

$$(I_1, I_2) = f(V_1, V_2)$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{--- ①}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{--- ②}$$


$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

Ques)

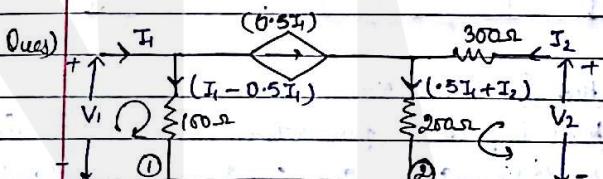

KVL in loop ①, $V_1 - 150(I_1 - 0.5I_2) = 0$

$$V_1 = 50I_1$$


$$Y_{11} = 50 \Omega, Y_{12} = 0 \Omega$$

loop ②, $V_2 - 200I_2 - 200(0.5I_1 + I_2) = 0$


$$V_2 = 100I_1 + 500I_2$$

$$Y_{21} = 100 \Omega, Y_{22} = 50 \Omega$$

Ques) Obtain the Y-parameters.

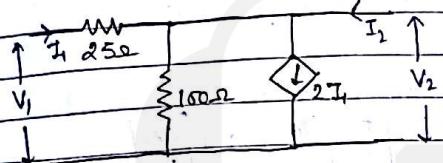

Equivalent ckt. of Y parameters-

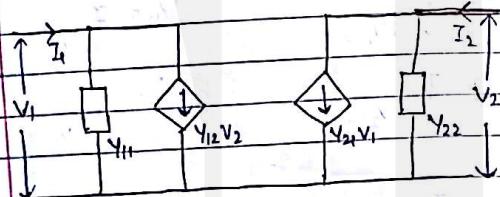

→ Hybrid Parameters-


Most important parameters used in transistor modelling as they are combination of Y and Z parameters.

$$(V_1, I_2) = f(I_1, V_2)$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

$$\Rightarrow V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- (1)}$$
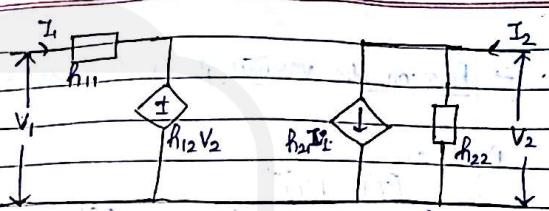
$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- (11)}$$



$$h_{11} = V_1 \Big| \frac{(V_2=0)}{I_1}$$

$$h_{12} = V_1 \Big| \frac{(I_1=0)}{V_2}$$

$$h_{21} = \frac{I_2}{I_1} \Big| \frac{(V_2=0)}{V_1}$$

$$h_{22} = \frac{I_2}{V_2} \Big| \frac{(I_1=0)}{V_1}$$

→ Transmission (Chain / ABCD) / T Parameters-

Aux current used in power transmission lines

$$(V_1, I_2) = f(V_2, -I_1)$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_1 \end{bmatrix}$$

$$V_1 = AV_2 - BI_1 \quad \text{--- (1)}$$

$$I_2 = CV_2 - DI_1 \quad \text{--- (11)}$$

→ Inverse Hybrid parameters-

$$(I_1, V_2) = f(V_1, I_2)$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}$$

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

DETA Page No. / / Date / /

→ Relation b/w various parameters set -

1) Z and Y
 $[Z] = [Y]^{-1}$
 $\begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix}^{-1}$

2) Z in terms of $A B C D$ -
 $V_1 = AV_2 - BI_2 \quad \text{--- (1)}$
 $I_1 = CV_2 - DI_2 \quad \text{--- (2)}$
 $\text{or } CV_2 = I_1 + DI_2$
 $V_2 = \frac{I_1}{C} + \frac{D}{C} I_2 \quad \text{--- (3)}$

$Z_{21} = \frac{1}{C}$, $Z_{22} = \frac{D}{C}$
------------------------	--------------------------

Put value of V_2 in eqⁿ (1),
 $V_1 = \frac{A}{C} I_1 + \frac{AD}{C} I_2 - BI_2$
 $= A I_1 + \left(\frac{AD - BC}{C} \right) I_2$