

Graph Theory

class notes 11th 11th

11


Graph :- Graph is defined as a collection of nodes (points) and branches, which shows the geometrical interconnection of the elements of a network.

Branch :- A line segment.

In graph, components are replaced by a line segments, these line segments are known as branches.

Node :-

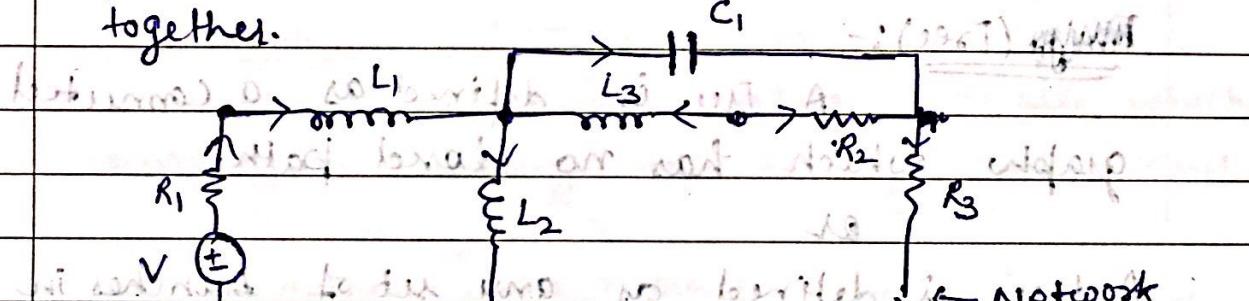The end points of a branch or a common point at which two or more branches meet together.



At the different parts of the network, there are different types of nodes.

• If the network has no cut-off, then it is called a connected network.


• If the network has a cut-off, then it is called a disconnected network.

• If the network has no orientation, then it is called an undirected graph.

• If the network has orientation, then it is called a directed graph.

Directed Graph :-

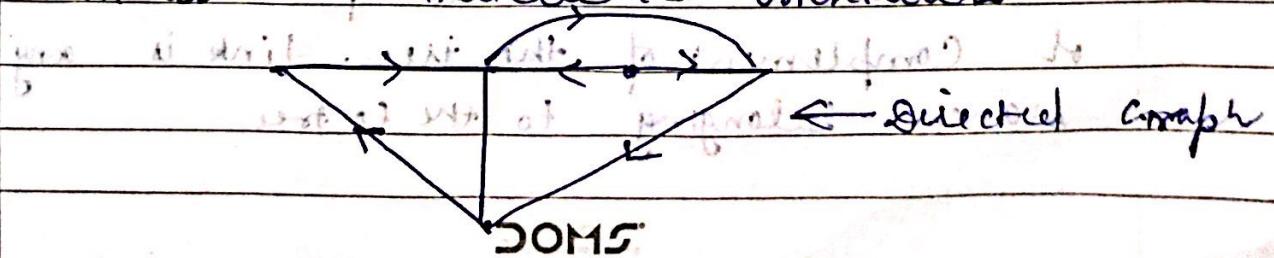
A graph whose branches are oriented is known as directed or oriented graph or we can say each branch of graph carries an arrow to indicate its orientation.



- How to draw a Graph:-
- ① Replace All the elements by branches
 - ② Short ckt the Voltage source.
 - ③ open ckt the current Source.

Planar Graph :-

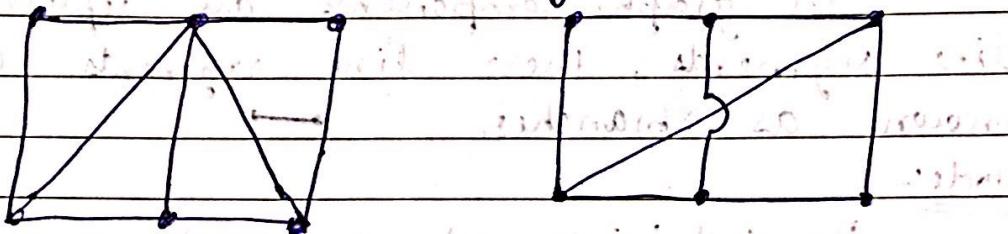A graph is said to planar graph if that can be drawn on a sheet of paper without crossing lines.



Planar Graph

Non-Planar Graph

Trees (Tree) :-

A tree is defined as a connected graph which has no closed path.

or

A tree is defined as any set of branches in the original graph that is just sufficient to connect all the nodes. This number is $n-1$.

The tree branches are known as Twigs.

no. of Twigs

$$nt = n-1 \quad \{ \text{minimum} \}$$

no. of Nodes

Links or chords or Co-Tree :-

The branches of graph which are not in the tree form the Co-tree or Complement of the tree. Link is any branch belonging to the Co-tree.

Ques

* Graph = Tree \cup Co-Tree (or twigs)

* Graph = Twigs \cup Links.

No. of Links	8	2	1	
No. of Twigs	0	0	1	
Total no. of Branches	0	1 + 0	1	
Branches in a graph	0	0	0	0
$n_b = b - (n-1)$	0	0	0	0
$n_l = b - n + 1$	0	1 + 0	0	1

Ans

Incidence matrix:-


This matrix indicates which branch is entering and leaving which node.

for a graph with n nodes and b branches, the complete incidence matrix A_C is an $n \times b$ matrix whose elements are defined as:-

$a_{nb} = +1$ if branch b leaves node n

-1 if branch b enters node n .

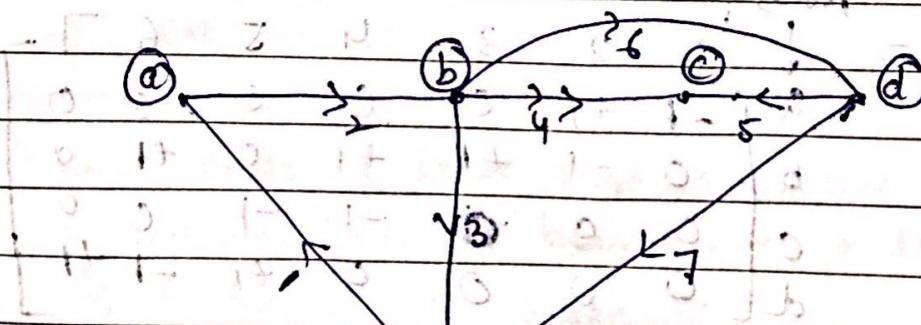0 if branch b is not incident with node n .



Twigs in a graph with 5 nodes :-

the number of twigs in the graph is 1. The first twig is the tree formed by the nodes a, b, c, and d. The second twig is the node e.

Complete Incidence matrix of this graph
is :-

Nodes Branches →	1	2	3	4	5	6	7
a	-1	+1	0	0	0	0	0
b	0	-1	+1	+1	0	+1	0
c	0	0	0	-1	+1	0	0
d	0	0	0	0	+1	-1	+1
e	+1	0	-1	0	+1	0	-1

Since each branch b enters a single node and leaves a single other node, each column contains a single -1 and a single +1 with all elements equal to zero.

Reduced Incidence Matrix:-
By eliminating any one row, we get reduced incidence matrix A or incidence matrix A'. The dimension of this matrix is $(n-1) \times b$. i.e $n \times b$.

Nodes | Branches →

A =	1	2	3	4	5	6	7
a	-1	+1	0	0	0	0	0
b	0	-1	+1	+1	0	+1	0
c	0	0	0	-1	-1	0	0
d	0	0	0	0	+1	-1	+1

If we rearrange the columns of incident matrix A so that first nt columns corresponds to twigs and next n-s columns to the sinks.
DOMS

Nodes / Branches \rightarrow At : A_L

$$\begin{array}{c} \text{Nodes} \\ \downarrow \\ \text{Branches} \end{array} \xrightarrow{\quad} \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 \end{matrix} \quad \begin{matrix} -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & +1 & +1 & 0 & -1 & 0 \\ 0 & 0 & -1 & 0 & 0 & -1 \\ 0 & 0 & 0 & +1 & 0 & +1 \end{matrix}$$
$$[A] = [A_L : A_E]$$

Properties of Complete Incidence Matrix:-

- 1.) The sum of entries in any column is zero.
- 2.) The rank of complete incidence matrix of a oriented graph is $n-1$.
- 3.) The determinant of complete incidence matrix is always zero.

* fundamental loop matrix of Tiesets :-

If a link is added to a tree, the resulting graph contains one closed path, called a loop (or a circuit).

Properties of Loop of a Graph:-

- i) There are exactly two paths between any pair of nodes in the circuit.
- ii) There exist at least two branches in a Loop.
- iii) Maximum possible branches in a loop are equal to no. of nodes in the graph.

DOMS


The loops which contains only one link are independent and are called as basic or fundamental loops (f-loops) or tie sets.

The no. of f-loops = no. of links

Orientation of f-loops is chosen to be same as that of its link.

Procedure for obtaining Tie-set matrix:-

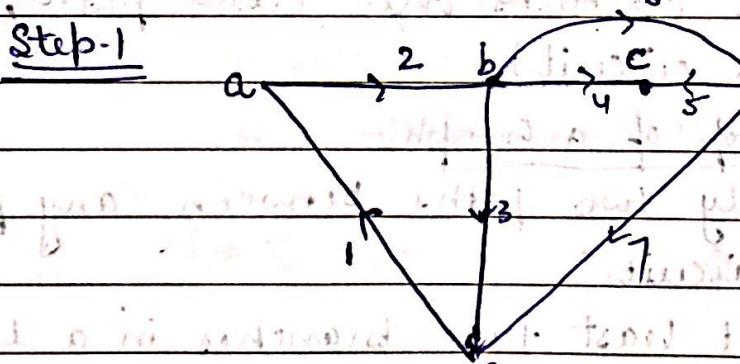- 1.) Draw the Graph of given network.
- 2.) Select a Tree.
- 3.) No. of Tie-sets = No. of links.
- 4.) Each Tie-set contains one and only one link.
- 5.) The orientation of loop is defined by the orientation of the corresponding link.




Draw the Graph.

DOMS

Step-2

Select a tree

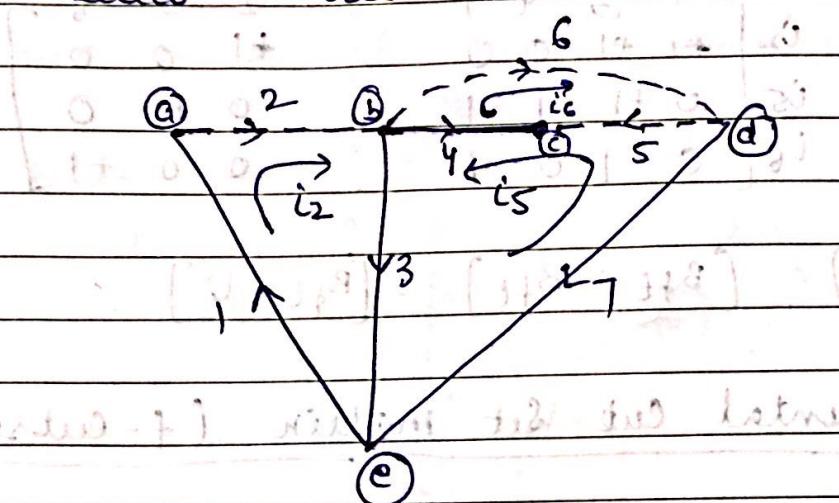

Step-3 No. of Tie-sets = 3 (As there are 3 links)

Step-4 for a graph with n links and b branches
the tie-set matrix is $n \times b$ matrix, where
elements are defined as:-

$b_{ab} = +1$, if branch b is in the tie-set and orientation
of tie-set & branch coincides
 -1 , if branch b is in the tie-set and orientation
of tie-set & branch do not coincide
 0 , if branch b is not in the tie-set.

$$[B_f] = \begin{matrix} & \downarrow & \text{Branches} \rightarrow \\ \text{Tie-sets} & & \end{matrix}$$

	1	2	3	4	5	6	7
i ₂	+1	+1	+1	0	0	0	0
i ₅	0	0	+1	-1	+1	0	-1
i ₆	0	0	-1	0	0	+1	+1

DOMS

Tiesets branches

$$\begin{matrix} \downarrow \\ [B_f] = \end{matrix} \begin{matrix} 1 & 3 & 4 & 7 & 2 & 5 & 6 \\ i_1 & +1 & +1 & 0 & 0 & +1 & 0 & 0 \\ i_2 & 0 & +1 & -1 & -1 & 0 & +1 & 0 \\ i_3 & 0 & -1 & 0 & 1 & 0 & 0 & +1 \end{matrix}$$

$$[B_f] = [B_{fT} : B_{fL}] = [B_{fT} : U]$$

* Fundamental Cut-Set matrix (f-cutsets)

Cut-set is a minimal set of branches that if removed, divides a connected graph into two connected sub-graphs i.e. it separates the nodes of the graph into two groups.


Cut-sets containing only one twig are independent and are known as basic or fundamental cut-sets (f-cut-sets).

The no. of f-cut sets = No. of twigs
Orientation of f-cut-set is shown to be same as that of its twig.

Procedure for obtaining f-cut-set matrix:-

- ① Draw the graph of given network.
- ② Select a tree.
- ③ No. of Cut-sets = No. of twigs.
- ④ Each cut-set contains one and only one twig.

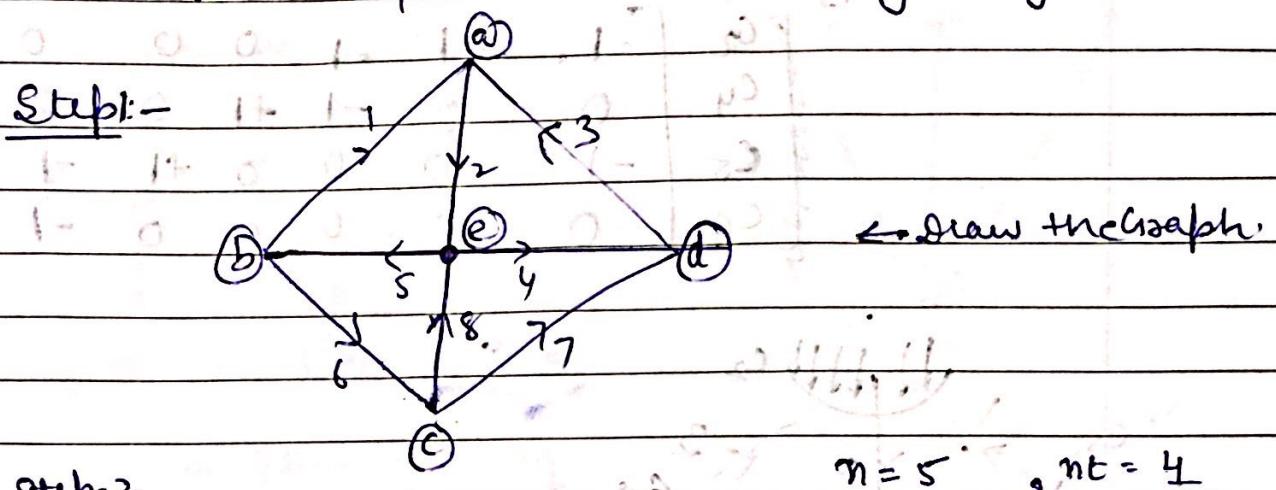⑤ The orientation of cut-set is defined by the orientation of the corresponding twigs.




Step-2

Select a Tree

$$n = 5, n_t = 4$$
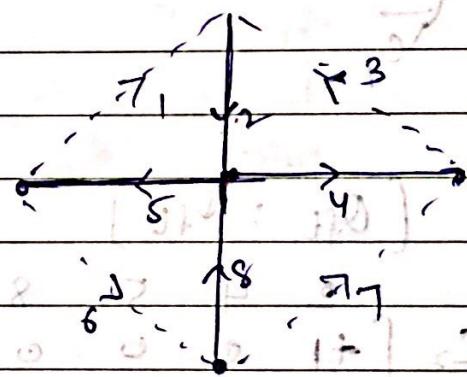
$$b=7, \text{ No. of cut-set} = \underline{4}$$



Step 3:- No. of cut sets = No. of Twigs (4)

c_2, c_4, c_5, c_8

Step 4 :-

$q_{cb} = +1$ if branch b is in the cut-set and its orientation coincides with cut-set.

-1 If branch b is in the Cut-set and their deviations do not coincide.


only branch b is not in the cut set.

DOMS

Cut-sets
↓
→ branches.

$$[Q_f] = [u : Q_{fe}] \quad 1 \ 2 \ 3 \ 4 \ 5 \ 6 \ 7 \ 8$$
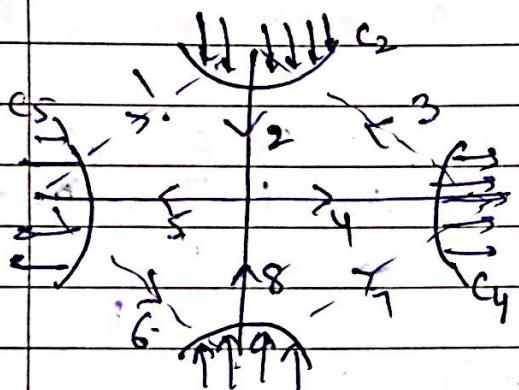
$$\begin{cases} C_2 \\ C_4 \\ C_5 \\ C_8 \end{cases} \begin{bmatrix} -1 & +1 & -1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & +1 & 0 & 0 & +1 & 0 \\ -1 & 0 & 0 & 0 & +1 & -1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & -1 & +1 & +1 \end{bmatrix}$$




$$[Q_f] = [u : Q_{fe}]$$

$$= C_2 \begin{bmatrix} 2 & 4 & 5 & 8 & 1 & 3 & 6 & 7 \\ +1 & 0 & 0 & 0 & -1 & -1 & 0 & 0 \end{bmatrix} \\ C_4 \begin{bmatrix} 2 & 4 & 5 & 8 & 1 & 3 & 6 & 7 \\ 0 & +1 & 0 & 0 & 0 & -1 & 0 & +1 \end{bmatrix} \\ C_5 \begin{bmatrix} 2 & 4 & 5 & 8 & 1 & 3 & 6 & 7 \\ 0 & 0 & +1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix} \\ C_8 \begin{bmatrix} 2 & 4 & 5 & 8 & 1 & 3 & 6 & 7 \\ 0 & 0 & 0 & +1 & 0 & 0 & -1 & +1 \end{bmatrix}$$


$$[Q_f] = [u : Q_{fe}]$$

Q.1


Draw the graphs of given networks:-

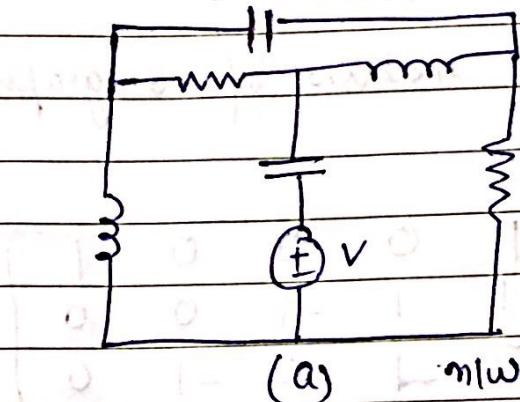

(a) η/ω

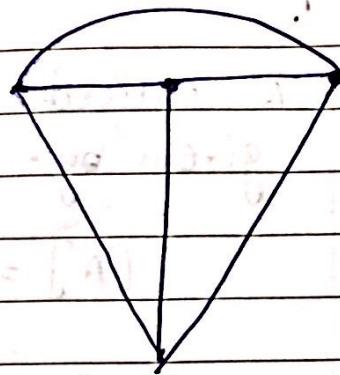


Graph

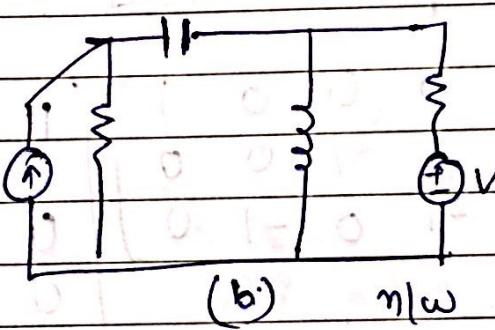


(b) η/ω




Graph

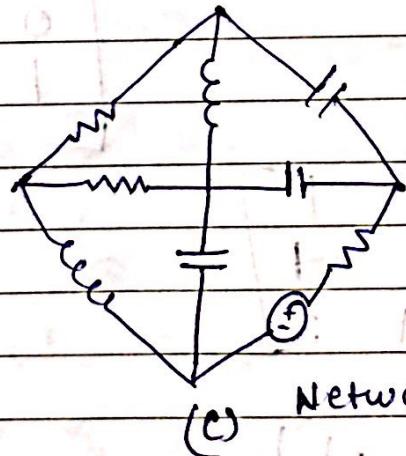


(c) Network

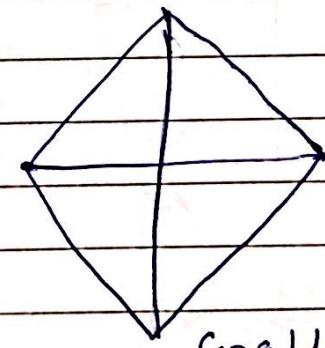

Graph

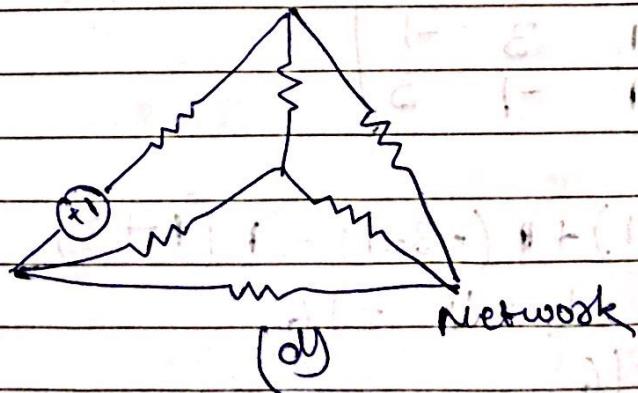

DOMS

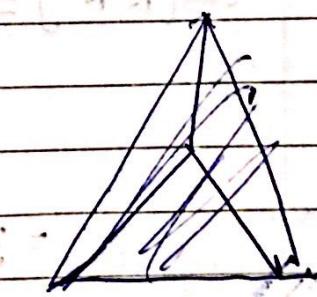

Graph

$$\boxed{\text{No. of Trees} = \det [A \cdot A^T]}$$

Q. 1. A reduced incidence matrix of a graph is given by :-

$$[A] = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

Obtain the no. of possible trees

Soln

$$A \cdot A^T = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & -1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & -1 & 0 \\ 0 & 0 & -1 \\ 1 & 0 & 0 \end{bmatrix}$$

$$= \begin{bmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$\det[A \cdot A^T] = \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}$$

$$= 3(9-1) + 1(-3-1) - 1(1+3)$$


$$= 24 - 4 - 4 = 16$$

So No. of Trees = 16 } Ans.

DOMS

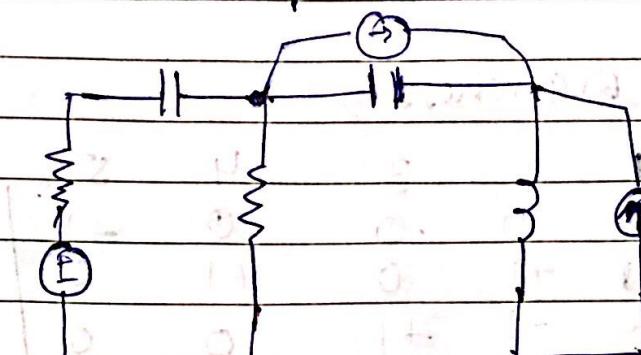Q.2

Draw the possible trees of given network and also obtain (1) Incidence matrix






(2) Tie-Set matrix

(3) Cut-Set matrix

Solⁿ

Graph of the network

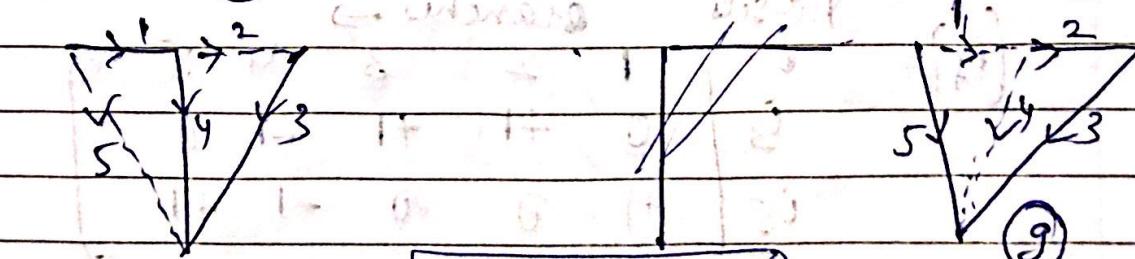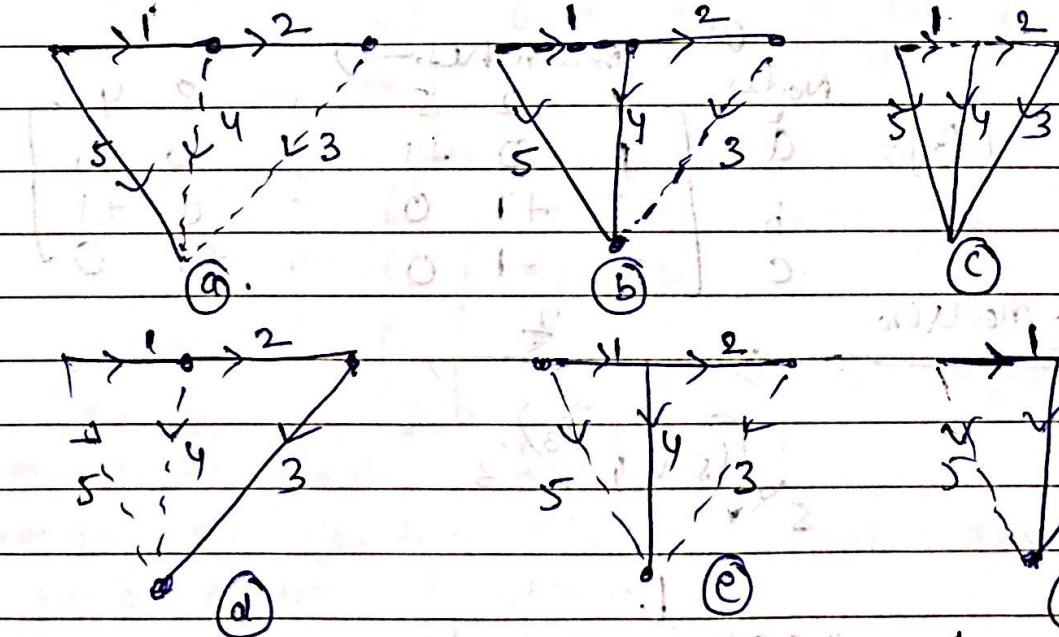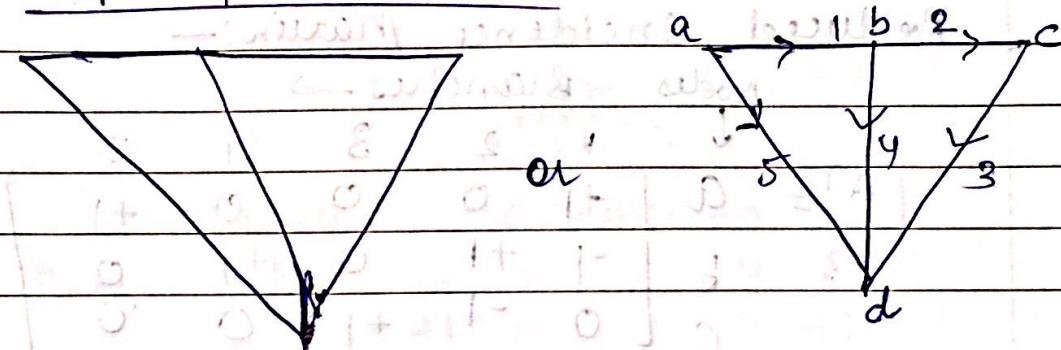

No. of trees = 8

DOMS

The complete incidence matrix

$$\text{Nodes} \quad \text{Branches} \rightarrow$$

$$\downarrow$$

$$[A_G] = \begin{matrix} & 1 & 2 & 3 & 4 & 5 \\ a & +1 & 0 & 0 & 0 & +1 \\ b & -1 & +1 & 0 & +1 & 0 \\ c & 0 & -1 & +1 & 0 & 0 \\ d & 0 & 0 & -1 & -1 & -1 \end{matrix}$$

Reduced Incidence Matrix:-

$$\text{Nodes} \quad \text{Branches} \rightarrow$$

$$\downarrow \quad 1, 2, 3, 4, 5$$


$$[A] = \begin{matrix} & 1 & 2 & 3 & 4 & 5 \\ a & +1 & 0 & 0 & 0 & +1 \\ b & -1 & +1 & 0 & +1 & 0 \\ c & 0 & -1 & +1 & 0 & 0 \end{matrix}$$

$$\text{Nodes} \quad \text{Branches} \rightarrow$$

$$\downarrow \quad 1, 2, 5 \quad 3, 4$$

$$[A] = \begin{matrix} & 1 & 2 & 5 & 3 & 4 \\ a & 1 & 0 & +1 & 0 & 0 \\ b & -1 & +1 & 0 & 0 & +1 \\ c & 0 & -1 & 0 & +1 & 0 \end{matrix}$$

Tie-Set Matrix

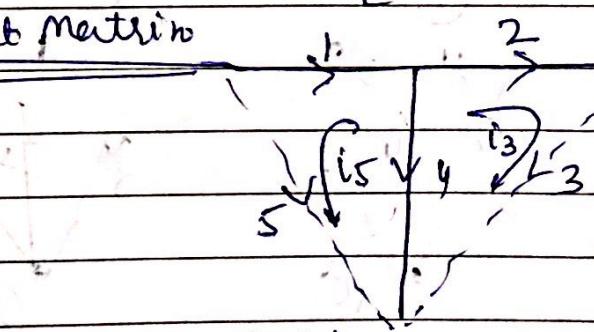

$$\text{Tie-sets} \quad \text{Branches} \rightarrow$$

$$\downarrow \quad 1, 2, 3, 4, 5$$


$$[B_T] = \begin{matrix} & 1 & 2 & 3 & 4 & 5 \\ t_3 & 0 & +1 & +1 & -1 & 0 \\ t_5 & +1 & 0 & 0 & -1 & +1 \end{matrix}$$

DOMS

11

Tie-sets	Branches →
$[B_f] =$	\downarrow
	1 2 4 3 5
c_3	$\begin{bmatrix} 0 & +1 & -1 & +1 & 0 \end{bmatrix}$
c_5	$\begin{bmatrix} +1 & 0 & -1 & 0 & +1 \end{bmatrix}$

Cut-Set matrix

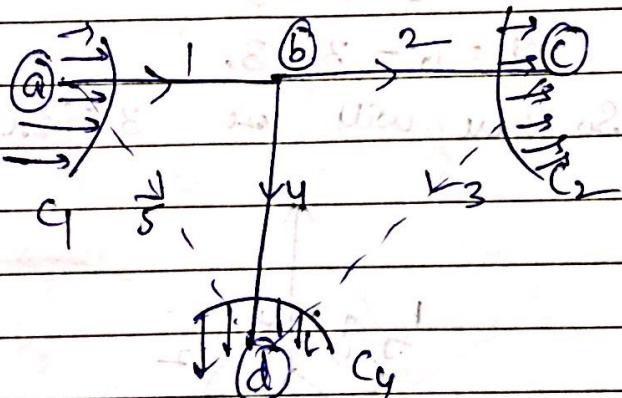


Cut-sets	Branches →
$[Q_f] =$	\downarrow
	1 2 3 4 5
c_1	$\begin{bmatrix} +1 & 0 & 0 & 0 & +1 \end{bmatrix}$
c_2	$\begin{bmatrix} 0 & +1 & -1 & 0 & 0 \end{bmatrix}$
c_4	$\begin{bmatrix} 0 & 0 & +1 & +1 & +1 \end{bmatrix}$

Cut-sets	Branches →
$[Q_f] =$	\downarrow
	1 2 4 3 5
c_1	$\begin{bmatrix} +1 & 0 & 0 & 0 & +1 \end{bmatrix}$
c_2	$\begin{bmatrix} 0 & +1 & 0 & -1 & 0 \end{bmatrix}$
c_4	$\begin{bmatrix} 0 & 0 & +1 & +1 & +1 \end{bmatrix}$

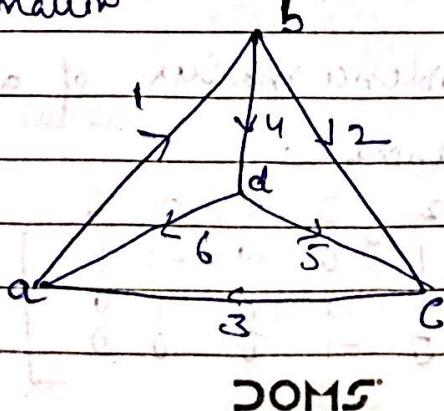Q.3

Consider the graph shown in figure. Select a tree with twigs (4, 5, 6) for this tree and write down the tie-set matrix.



Tier-set

Solⁿ
=

$$n = 4$$


$$b = 6$$

$$nt = n - 1 = 3$$

$$nl = b - (n - 1)$$

$$nl = 6 - 3 = 3.$$

So there will be 3 Tiers:-

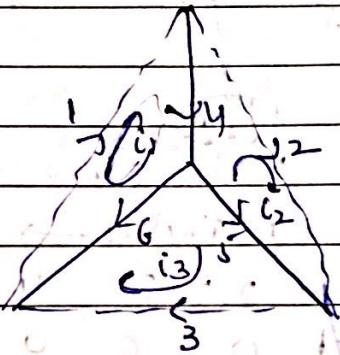

Tie-sets Branches →

1 4 5 2 3 6

$$\begin{bmatrix} B_f \end{bmatrix} = \begin{bmatrix} i_1 & +1, 0 & 0 & +1, 0 & +1 \\ i_2 & 0 & +1 & 0 & -1 & -1 & 0 \\ i_3 & 0 & 0 & +1 & 0 & +1 & -1 \end{bmatrix}$$

or

Tie-sets

Branches →

4 5 6 1 2 3

$$\begin{bmatrix} B_f \end{bmatrix} = \begin{bmatrix} i_1 & +1, 0 & 0 & 1 & +1, 0 & 0 \\ i_2 & -1 & -1 & 0 & 0 & +1 & 0 \\ i_3 & 0 & +1 & -1 & 0 & 0 & +1 \end{bmatrix}$$

Q.4

The reduced incidence matrix of a graph is given by

newly

Branches →

$$\begin{bmatrix} A \end{bmatrix} = \begin{bmatrix} a & 1 & 2 & 3 & 4 & 5 & 6 \\ b & 0 & -1 & 1 & 0 & 1 & 0 \\ c & 1 & 0 & -1 & 0 & 0 & 0 \end{bmatrix}$$


DOMS

Draw the oriented graph. Select a tree and find f-cutset matrix.

Soln

Complete Incidence Matrix:-


	Nodes	Branches \rightarrow
$A_C =$	1	2
a	0	1 0 -1 1
b	0	-1 1 0 1 0
c	1	0 -1 0 0 0
d	-1	0 0 1 0 0 -1

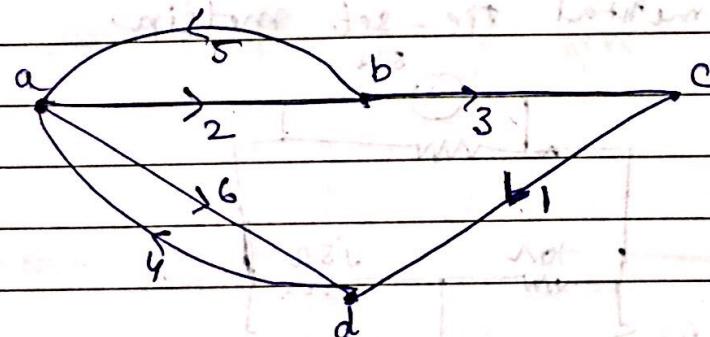

$$n = 4$$

$$nt = n-1 = 3.$$

$$nl = b-n+1 = 6-3=3$$

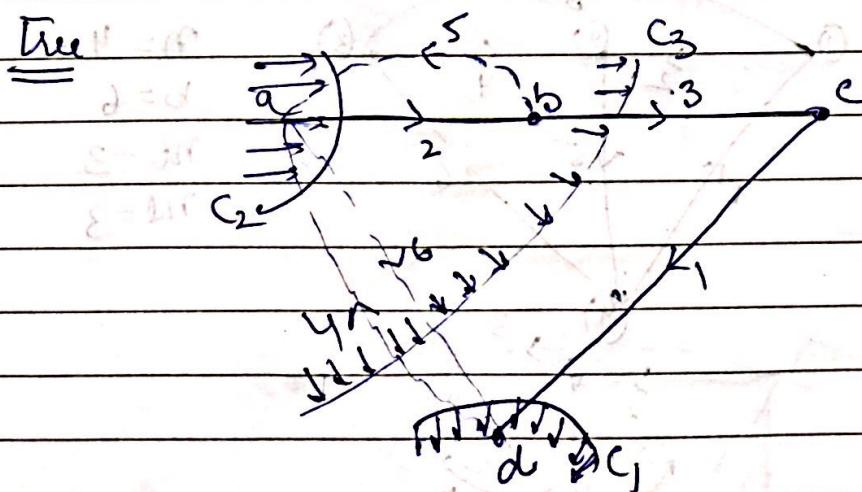

Cut-sets Branches \rightarrow

	1	2	3	4	5	6
G_1	+1	0	0	-1	0	+1
G_2	0	+1	0	-1	-1	+1
G_3	0	0	+1	-1	0	+1

DOMS


Cut-Sets branches →

	1	2	3	4	5	6
c_1	1	0	0	-1	0	1
c_2	0	1	0	-1	-1	1
c_3	0	0	1	-1	0	1


$$\Omega_f = [W : \Omega_{f\ell}]$$

Q-5

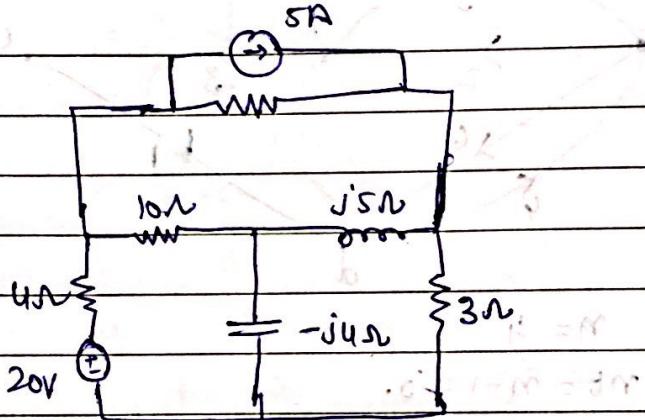for a given network draw the graph.
 Select 2,4,5 as tree branches and obtain fundamental tie-set matrix.



Solⁿ

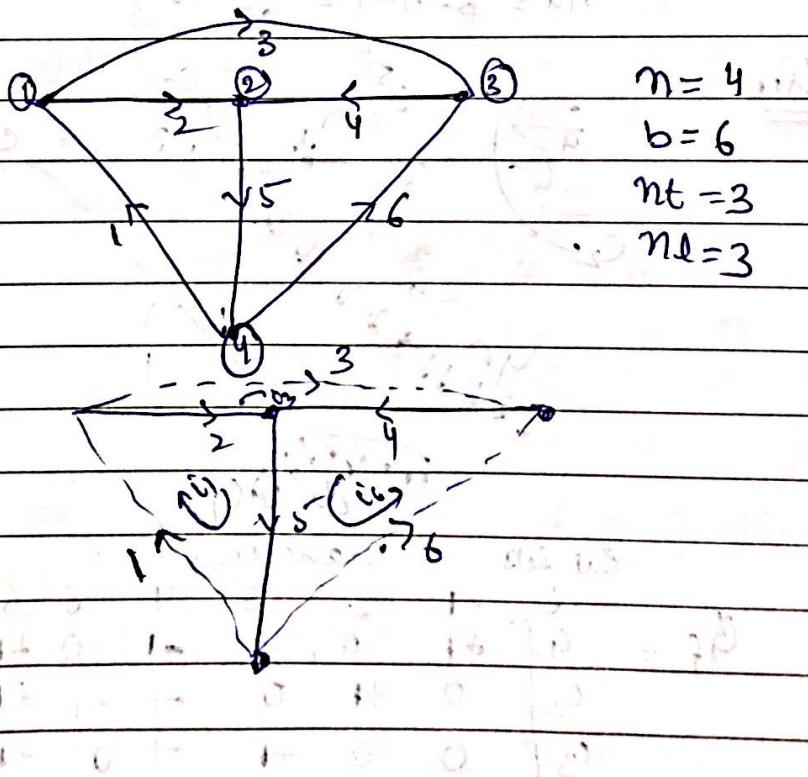


Tierets Branches →

$$B_f = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$



$$\begin{bmatrix} 0 & 1 & 1 & 1 & 1 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & -1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

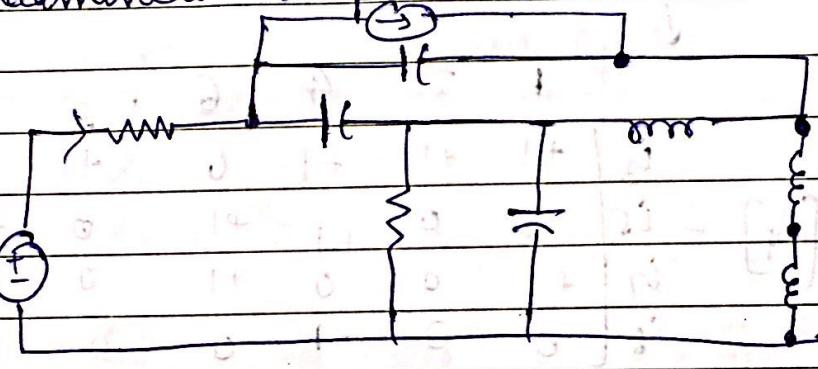Q.6 Draw the Graph of given circuit and obtain fundamental loop matrix and cut-set matrix.



Soln

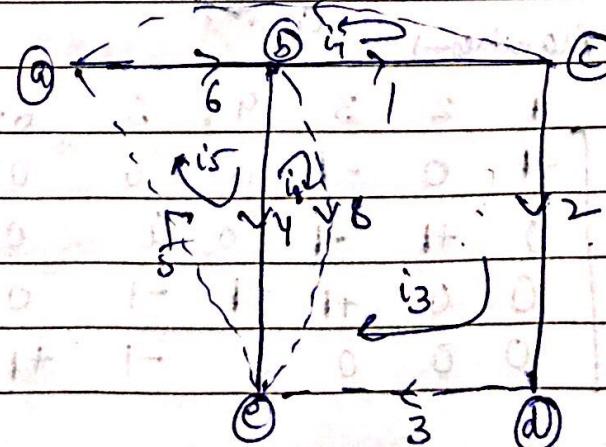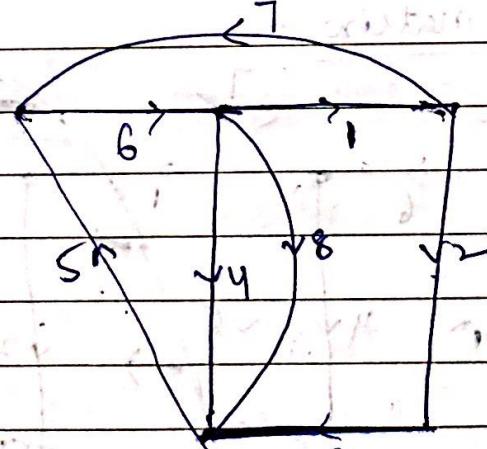

DOMS


Tie-Sets Branches →

	↓	1	2	3	4	5	6	7	8
i_3		+1	+1	+1	-1	0	0	0	0
i_5		0	0	0	1	1	1	0	0
i_7		1	0	0	0	0	0	1	0
i_8		0	0	0	-1	0	0	0	+1

Tie-Sets Branches →

	↓	1	2	4	6	13	5	7	8
i_3		+1	+1	-1	0	+1	0	0	0
i_5		0	0	+1	+1	0	+1	0	0
i_7		+1	0	0	+1	0	0	+1	0
i_8		0	0	-1	0	0	0	0	+1

for Cut-set matrix:-

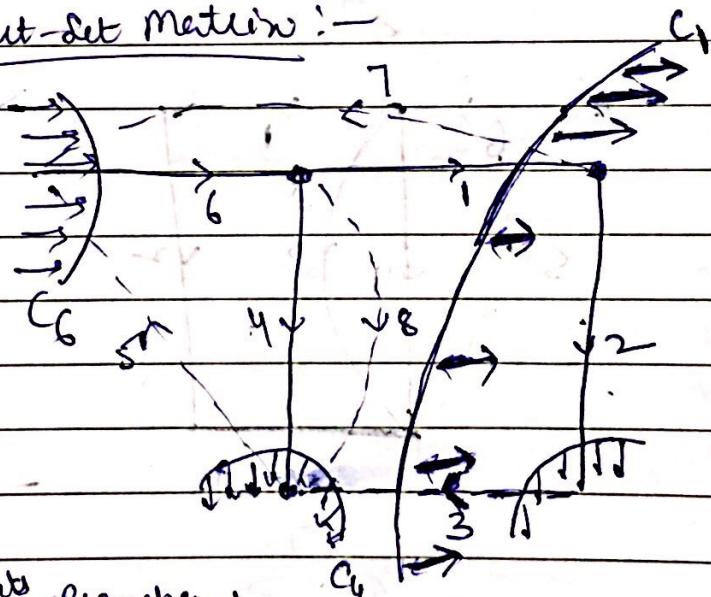

Cut-sets Branches →

	↓	1	2	3	4	5	6	7	8
c_1		+1	0	-1	0	0	0	-1	0
c_2		0	+1	-1	0	0	0	0	0
c_3		0	0	+1	+1	-1	0	0	+1
c_4		0	0	0	0	-1	+1	-1	0

Cut-sets Branches →

$$\downarrow$$

$$C_1 \begin{bmatrix} 1 & 2 & 4 & 6 & 3 & 5 & 7 & 8 \\ +1 & 0 & 0 & 0 & -1 & 0 & -1 & 0 \end{bmatrix}$$

$$C_2 \begin{bmatrix} 0 & +1 & 0 & 0 & -1 & 0 & 0 & 0 \end{bmatrix}$$

$$C_4 \begin{bmatrix} 0 & 0 & +1 & 0 & 1 & -1 & 0 & +1 \end{bmatrix}$$

$$C_6 \begin{bmatrix} 0 & 0 & 0 & +1 & 0 & -1 & -1 & 0 \end{bmatrix}$$

* Sub-matrices of A , B_f and Φ_f :-

$$A = [A_L : A_U]$$

$$B_f = [B_{fL} : B_{fU}] = [B_{fL} : U]$$

$$\Phi_f = [\Phi_{fL} : \Phi_{fU}] = [U : \Phi_{fU}]$$

Inter-Relations among various Matrices.

① Relation Between A & B_f :-

$$A \cdot B_f^T = 0$$

$$[A_L : A_U] \begin{bmatrix} B_{fL}^T \\ U \end{bmatrix} = 0$$

$$A_L B_{fL}^T + A_U = 0$$

$$B_{fL}^T = -A_L^{-1} A_U$$

So $B_{fL}^T = [-A_L^{-1} A_U]^T$ — (A)

② Relation Between A & Φ_f :-

KCL Equations

$$A \mathbf{I}_b = 0$$

$$\Phi_f \mathbf{I}_b = 0$$

where $\mathbf{I}_b = \begin{bmatrix} I_t \\ I_e \end{bmatrix}$

So

$$[A_t : A_L] \begin{bmatrix} I_t \\ I_e \end{bmatrix} = 0$$

$$A_t I_t + A_L I_e = 0$$

$$I_t = -A_L^{-1} A_t I_e \quad \text{--- (1)}$$

and

$$[\Phi_{ft} : \Phi_{fe}] \cdot \begin{bmatrix} I_t \\ I_e \end{bmatrix} = 0$$

$$[U : \Phi_{fe}] \cdot \begin{bmatrix} I_t \\ I_e \end{bmatrix} = 0$$

$$I_t + \Phi_{fe} I_e = 0$$

$$I_t = -\Phi_{fe} I_e \quad \text{--- (2)}$$

from eqn ① & ② :-

$$+ A_t^{-1} A_L I_e = -\Phi_{fe} I_e$$

$$\boxed{\Phi_{fe} = A_t^{-1} A_L} \quad \text{--- (3)}$$

③ Relation Between B_f and Φ_f :-

from Eqⁿ (A) & (B) :-

$$\Phi_{fl} = -B_{ft}^T$$

$$B_{ft} = -\Phi_{fl}^T$$

* Relationships Among Parameters:-

$$\text{KVL: } B_f V_b = 0$$

$$\text{KCL: } A I_b = 0$$

$$\Phi_f I_b = 0$$

$$V_b = \begin{bmatrix} V_t \\ \vdots \\ V_e \end{bmatrix} \quad \text{and} \quad I_b = \begin{bmatrix} I_t \\ \vdots \\ I_e \end{bmatrix}$$

① Relation Between Link Voltages and Twig Voltages:-

$$[B_{ft} : U] \begin{bmatrix} V_t \\ \vdots \\ V_e \end{bmatrix} = 0$$

$$B_{ft} V_t + V_L = 0$$

$$V_L = -B_{ft} V_t$$

or

$$V_L = \Phi_f^T V_t$$

② Relation Between Branch Voltages & Twig Voltages:-

$$V_b = \begin{bmatrix} V_b \\ \vdots \\ V_e \end{bmatrix} = \begin{bmatrix} U V_L \\ \vdots \\ \Phi_f^T V_t \end{bmatrix}$$

$$V_b = (\Phi_f^T V_t)$$

(4) Relation between Branch Voltages and Node Voltages:-

$$V_b = A^T V_n$$

Voltages of Various Nodes

(5) Relation Between Twig Currents & Link Currents:-

$$I_t = -A_t^{-1} A_l I_e = -Q_{pe} I_e = B_{ft}^T E_e$$

(6) Relation Between Branch Currents & Link Currents:-

$$I_b = \begin{bmatrix} I_t \\ I_u \end{bmatrix} = \begin{bmatrix} B_{ft}^T & I_e \\ I_e & U_e \end{bmatrix} = \begin{bmatrix} B_{ft}^T \\ U_e \end{bmatrix} I_e$$

$$I_b = B_f^T I_e$$

* Network Analysis:-

for a general network with many branches, branch voltages and branch currents can be written as:-

$$V_b = V_s + Z_b (I_b - I_s) \quad \text{--- (1)}$$

$$I_b = I_s + Y_b (V_b - V_s) \quad \text{--- (2)}$$

where V_b : Branch Voltage Matrix of $b \times 1$


I_b : Branch Current " of $b \times 1$

V_s : Voltage Source Matrix of $b \times 1$

I_s : Current Source Matrix of $b \times 1$

Z_b : Branch Impedance Matrix of $b \times b$

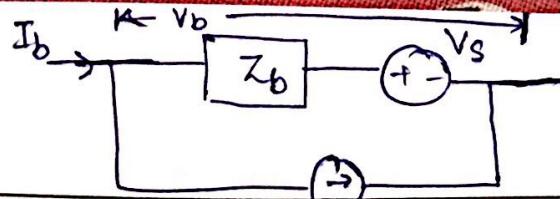Y_b : Branch Admittance Matrix of $b \times b$.



① Loop Analysis:-

The branch voltages are given by eqn ①:-

$$V_b = V_s + Z_b (I_b - I_s)$$

Premultiplication by B_f gives:-

$$B_f V_b = B_f V_s + B_f Z_b (I_b - I_s)$$

$$0 = -B_f V_s + B_f Z_b (B_f^T I_L - I_s)$$

$$\left[\text{Since } B_f V_b = 0 \right]$$

and $B_f^T I_L = I_b$

$$B_f Z_b I_s - B_f V_s = B_f Z_b B_f^T I_L$$

Let

$$B_f Z_b I_s - B_f V_s = V_L$$

$$B_f Z_b B_f^T = Z_L$$

$$V_L = Z_L I_L$$

This is called as Matrix Loop equation
where

$Z_L \rightarrow$ Loop Impedance Matrix

$I_L \rightarrow$ Loop Current Matrix

$$I_L = Z_L^{-1} V_L$$

② Nodal Analysis:-

The branch currents are given by eqn ② :-

$$I_b = I_s + Y_b (V_b - V_s)$$

Premultiplication by A, gives:-

$$A I_b = A I_s + A Y_b (V_b - V_s)$$

$$0 = A I_s + A Y_b (V_b - V_s)$$

since $\begin{bmatrix} A I_b = 0 \\ V_b = A^T V_n \end{bmatrix}$

or

$$A Y_b V_s - A I_s = A Y_b A^T V_n$$

Let

$$A Y_b V_s - A I_s = I_n$$

$$A Y_b A^T = Y_n$$

$$I_n = Y_n V_n$$

This is called as Matrix Node equation

where Y_n : Node Admittance matrix

Y_n : Node Voltage matrix

The node voltages are obtained by the relation :-

$$V_n = Y_n^{-1} I_n$$

③ Cut-Set Analysis:-

The Branch currents are given by eqⁿ ②:-

$$I_b = I_s + Y_b (V_b - V_s)$$

Now

$$\Omega_f I_b = \Omega_f I_s + \Omega_f Y_b (V_b - V_s) = 0$$

Since $\Omega_f I_s = 0$

$$\Omega_f I_s + \Omega_f Y_b (V_b - V_s) = 0$$

Since $V_b = \Omega_f^T V_t$

$$\Omega_f [I_s + Y_b (\Omega_f^T V_t - V_s)] = 0$$

$$\Omega_f Y_b V_s - \Omega_f I_s = \Omega_f Y_b \Omega_f^T V_t$$

let $\Omega_f Y_b V_s - \Omega_f I_s = I$

$$\Omega_f Y_b \Omega_f^T = Y_t$$

then

$$I = Y_t V_t$$

This is called as matrix cut-set equation

or Node pair equation.

where

Y_t : Node pair Admittance matrix


V_t : Toe branch voltage matrix.

$$\begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \end{bmatrix}$$

DOMS


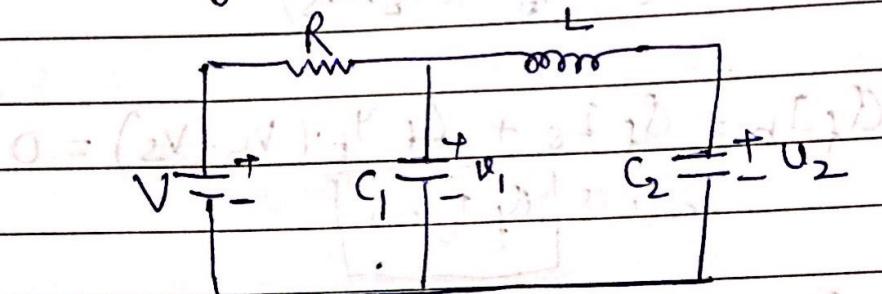
Q.7

Write the matrix loop equation for the n/w given, using the loop analysis.



Solⁿ

Graph of Network:-

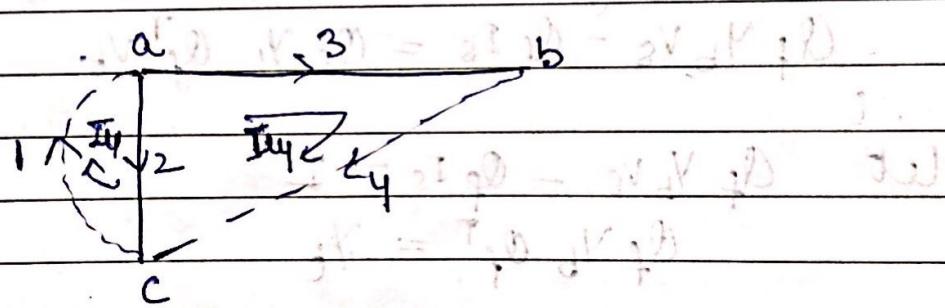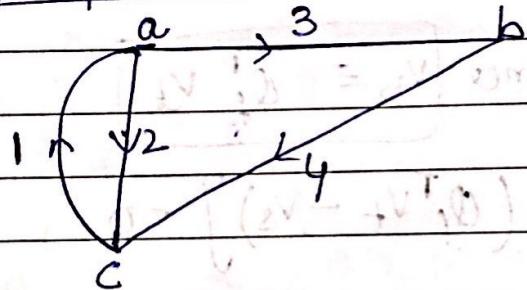

Tie-Set matrix

Tiesets

Branches \rightarrow

$$\begin{aligned} T_{11} & \left[\begin{matrix} 1 & 2 & 3 & 4 \\ +1 & +1 & 0 & 0 \end{matrix} \right] \\ T_{22} & \left[\begin{matrix} 0 & -1 & +1 & +1 \end{matrix} \right] \end{aligned}$$

Branch Admittance Matrix

$$Z_b = \begin{bmatrix} R & 1 & 0 & 0 \\ 0 & \frac{1}{C_{1S}} & L_S & 0 \\ 0 & 0 & 0 & \frac{1}{C_{2S}} \end{bmatrix}$$

DOMS

The loop impedance matrix :-

$$Z_L = B_f Z_b B_f^T = 0$$

$$= \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} R & 0 & 0 & 0 \\ 0 & \frac{1}{C_1 s} & 0 & 0 \\ 0 & 0 & Ls & 0 \\ 0 & 0 & 0 & \frac{1}{C_2 s} \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} R & 0 & 0 & 0 \\ \frac{1}{C_1 s} & -\frac{1}{C_1 s} & 0 & 0 \\ 0 & 0 & Ls & 0 \\ 0 & 0 & 0 & \frac{1}{C_2 s} \end{bmatrix}$$

$$Z_L = \begin{bmatrix} R + \frac{1}{C_1 s} & -\frac{1}{C_1 s} \\ -\frac{1}{C_1 s} & Ls + \frac{1}{C_1 s} + \frac{1}{C_2 s} \end{bmatrix}$$

Voltage Source Matrix :-

$$V_s = \begin{bmatrix} -V \\ i_1 \\ 0 \\ U_2 \end{bmatrix}$$

Current Source Matrix :-

$$I_s = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

DOMS

Hence

$$V_d = B_f Z_b I_s - B_f V_s \quad [\text{As } I_s = 0]$$


$$\begin{bmatrix} 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix} = - \begin{bmatrix} 1 & 4 & 0 \\ 0 & 1 & 1 \\ 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} -V \\ 0 \\ 0 \end{bmatrix}$$

$$V_1 = \begin{bmatrix} V - V_1 \\ V_1 - V_2 \end{bmatrix}$$

So, the matrix loop equation can be written as :-


$$\begin{bmatrix} V - V_1 \\ V_1 - V_2 \end{bmatrix} = \begin{bmatrix} R + \frac{1}{C_{1S}} & -\frac{1}{C_{1S}} \\ -\frac{1}{C_{1S}} & L_S + \frac{1}{C_{1S}} + \frac{1}{C_{2S}} \end{bmatrix} \begin{bmatrix} I_{L1} \\ I_{L2} \end{bmatrix}$$

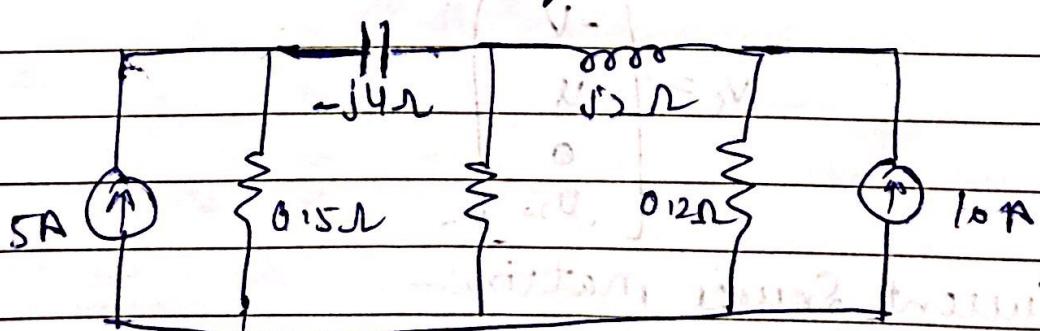Q.8 for a given network, obtain the incidence matrix, the node admittance matrix and matrix node equation.



Sol

Graph of Network:-

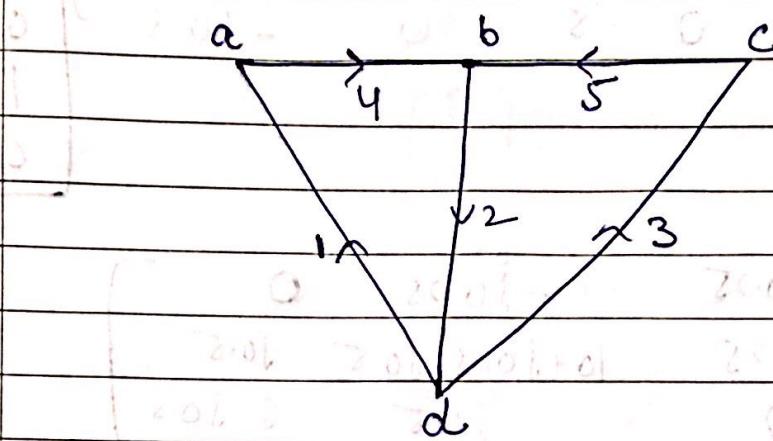

If Node 'd' is taken as the reference.

Then Incidence Matrix is.

Nodes
↓
branches →

$$[A] = \begin{matrix} & \begin{matrix} 1 & 2 & 3 & 4 & 5 \end{matrix} \\ \begin{matrix} a \\ b \\ c \end{matrix} & \begin{bmatrix} 1 & 0 & 0 & 1 & 0 \\ -1 & 0 & 0 & -1 & -1 \\ 0 & 1 & 0 & -1 & 1 \end{bmatrix} \end{matrix}$$

The Branch Admittance matrix:-

$$Y_b = \begin{bmatrix} 2 & 0 & 0 & 0 & 0 \\ 0 & 10 & 0 & 0 & 0 \\ 0 & 0 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & j0.25 \\ 0 & 0 & 0 & 0 & -j0.5 \end{bmatrix}$$

Node Admittance matrix:-

$$Y_n = A Y_b A^T$$

$$AY_b = \begin{bmatrix} -1 & 0 & 0 & 1 & 0 \\ 0 & 1 & 0 & -1 & -1 \\ 0 & 0 & 1 & -1 & 0 \\ 0 & 0 & -1 & 0 & 1 \\ 0 & 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 2 & 0 & 0 & 0 & 0 \\ 0 & 10 & 0 & 0 & 0 \\ 0 & 0 & 5 & 0 & 0 \\ 0 & 0 & 0 & 0 & j0.25 \\ 0 & 0 & 0 & 0 & -j0.5 \end{bmatrix}$$

DOMS

Then

$$AY_b R^T = \begin{bmatrix} -2 & 0 & 0 & j0.25 & 0 & 0 \\ 0 & 10 & 0 & -j0.25 & j0.5 & 0 \\ 0 & 0 & -5 & 0 & 0 & -j0.5 \end{bmatrix} \begin{bmatrix} -1 & 0 & 0 \\ 0 & 10 & 0 \\ 0 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$

So

$$Y_n = \begin{bmatrix} 2+j0.25 & -j0.25 & 0 \\ -j0.25 & 10+j0.25-j0.5 & j0.5 \\ 0 & j0.5 & 5-j0.5 \end{bmatrix}$$

Voltage Source Matrix:

$$[V_s] = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Current Source Matrix:

$$[I_s] = \begin{bmatrix} 5 \\ 0 \\ 0 \\ 10 \\ 0 \\ 0 \end{bmatrix}$$

$$\text{Then } I_n = AY_b V_s - A[I_s]$$

DOMS

$$I_n = - \begin{bmatrix} -5 \\ 0 \\ -10 \end{bmatrix}$$

$$I_n = \begin{bmatrix} 5 \\ 0 \\ 10 \end{bmatrix}$$

So the matrix node equation :-

$$I_n = Y_n V_n$$

$$\begin{bmatrix} 5 \\ 0 \\ 10 \end{bmatrix} = \begin{bmatrix} 2+j0.25 & -j0.25 & 0 \\ -j0.25 & 10-j0.25 & j0.5 \\ 0 & j0.5 & 5-j0.5 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \\ V_c \end{bmatrix}$$

Q.9 The reduced incidence matrix of a graph is given, draw the graph and obtain the f-loop and f-cut set matrices. Also verify the results.


Solⁿ

$$A = a \begin{bmatrix} 0 & 0 & 1 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ -1 & 0 & -1 & 0 & 0 & -1 & 0 \end{bmatrix} \leftarrow \text{Given}$$


The complete incidence matrix.

$$A_c = a \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \\ 0 & 0 & 1 & 1 & 1 & 0 & -1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 1 \\ -1 & 0 & -1 & 0 & 0 & -1 & 0 \\ 1 & -1 & 0 & -1 & 0 & 0 & 0 \end{bmatrix}$$

The oriented Graph:-

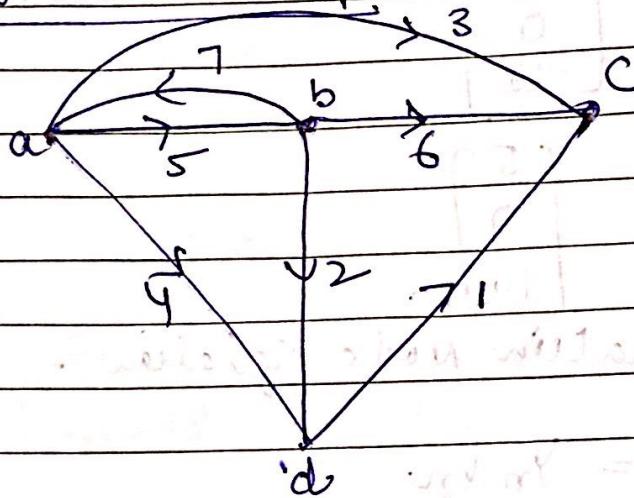


Tree

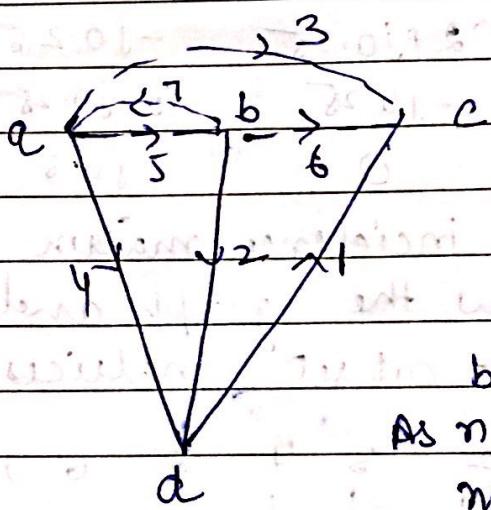

$$\text{As } n = 4 \quad nt = 3$$

$$nt = 3$$

$nl = 4$. \therefore no. of f-loops

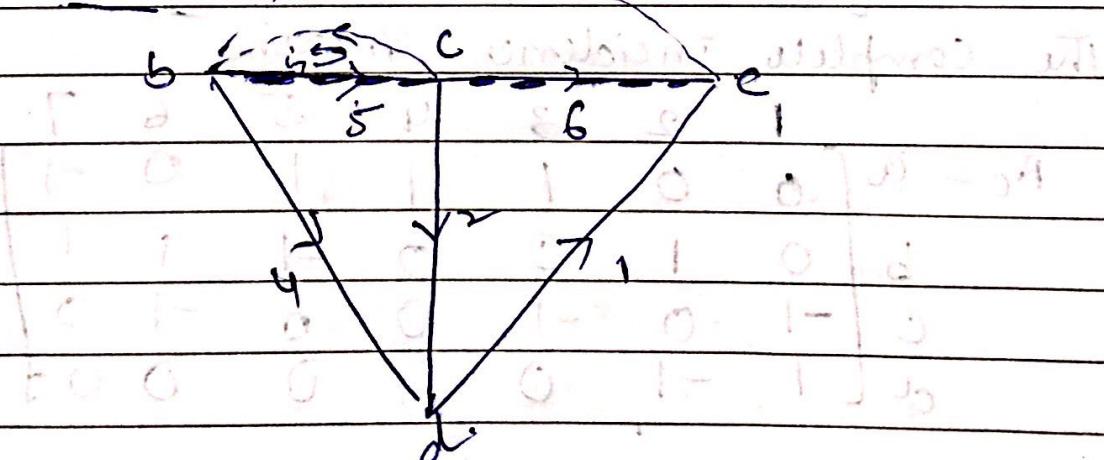

f-loop Matrix -

f-loops Branches →

$$\downarrow \quad \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 \end{matrix}$$


$$[B_f] = \begin{bmatrix} i_3 & -1 & 0 & 1 & -1 & 0 & 0 & 0 \\ i_5 & 0 & 1 & 0 & -1 & 1 & 0 & 0 \\ i_6 & -1 & -1 & 0 & 0 & 0 & 1 & 0 \\ i_7 & 0 & -1 & 0 & 1 & 0 & 0 & 1 \end{bmatrix}$$

$$\text{or} \quad \begin{matrix} 1 & 2 & 4 & 3 & 5 & 6 & 7 \end{matrix}$$

$$[B_f] = \begin{bmatrix} i_3 & -1 & 0 & -1 & 1 & 0 & 0 & 0 \\ i_5 & 0 & 1 & -1 & 0 & 1 & 0 & 0 \\ i_6 & -1 & -1 & 0 & 0 & 0 & 1 & 0 \\ i_7 & 0 & -1 & 1 & 0 & 0 & 0 & 1 \end{bmatrix}$$

f-Cut Set Matrix

No. of f-Cutsets = No. of Twigs = 3.

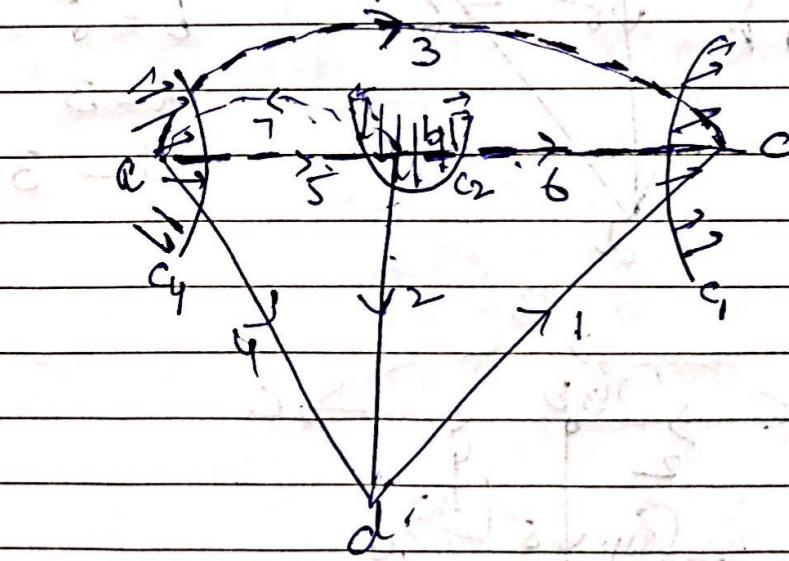


Cuts → Branches →

$$Q_f = \begin{bmatrix} c_1 & 1 & 2 & 4 & 3 & 5 & 6 & 7 \\ c_2 & 0 & +1 & 0 & 0 & -1 & 1 & 1 \\ c_3 & 0 & 0 & +1 & +1 & +1 & 0 & -1 \end{bmatrix}$$

DOMS

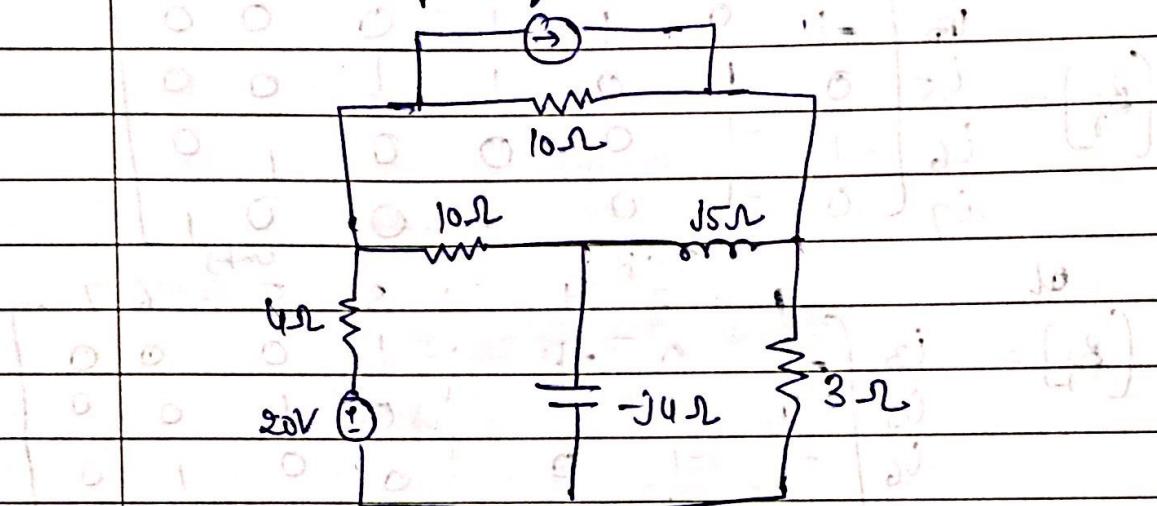
Q.10

for the network as shown in figure, draw the network graph. Select 2, 4, 5 as the branches. obtain the loop incidence matrix and loop equations.



Soln:

Graph

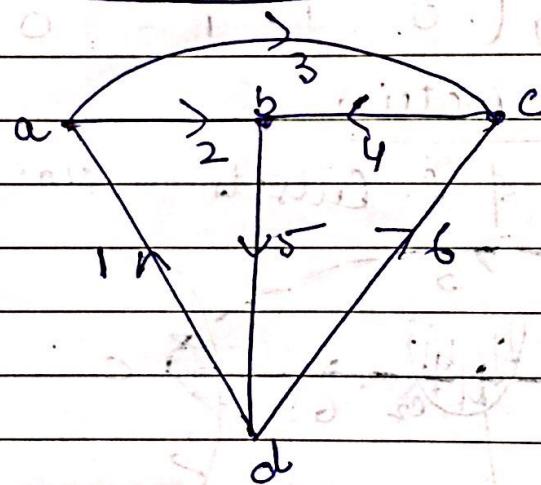


$$n = 4$$

$$b = 6$$

$$n_L = 3$$

$$n_L = 3$$

Tree

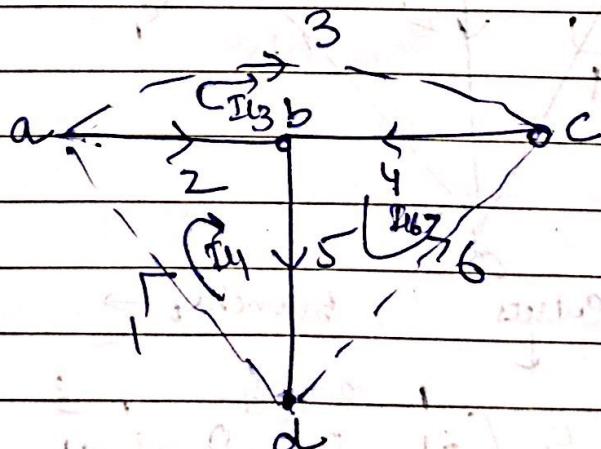

20MC

f-loop matrix

$$\begin{array}{c} \text{Tiesets} \\ \downarrow \\ \text{Branches} \rightarrow \end{array}$$

$$[B_f] = \begin{matrix} i_1 & \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & 0 \\ 0 & -1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 1 \end{bmatrix} \\ i_2 & \\ i_3 & \\ i_4 & \end{matrix}$$

The Branch Impedance Matrix —

$$[Z_b] = \begin{bmatrix} 4 & 0 & 0 & 0 & 0 & 0 \\ 0 & 10 & 0 & 0 & 0 & 0 \\ 0 & 0 & 10 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & -j4 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

Now, The Loop Impedance Matrix :-

$$Z_L = B_f Z_b B_f^T$$

$$= \begin{bmatrix} 4 & 10 & 0 & 0 & -j4 & 0 \\ 0 & -10 & 10 & j5 & 0 & 0 \\ 0 & 0 & 0 & j5 & -j4 & 3 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 1 & -1 & 0 \\ 0 & 1 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 0 & 0 & 1 \end{bmatrix}$$

$$Z_L = \begin{bmatrix} 14-j4 & -10 & -j4 \\ -10 & 20+j5 & j5 \\ -j4 & j5 & 3+j \end{bmatrix}$$

DOMS

The voltage and current source matrices are

$$V_S = \begin{bmatrix} -20 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad \text{and} \quad I_S = \begin{bmatrix} 0 \\ 0 \\ 5 \\ 0 \\ 0 \end{bmatrix}$$

So

$$V_L = B_f Z_b I_S - B_f V_S$$

$$B_f = \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 \\ 4 & 0 & 0 & 0 & 0 & -j4 \\ 0 & -10 & 0 & j5 & 0 & 0 \\ 0 & 0 & 20 & 0 & j5 & -j4 \\ 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix} \quad Z_b = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 & 0 \\ 0 & 1 & 1 & 1 & 0 \\ 0 & 0 & 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} -20 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} -20 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 0 \\ 5 \\ 0 \end{bmatrix} - \begin{bmatrix} -20 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 20 \\ 5 \\ 0 \end{bmatrix}$$


$$\begin{bmatrix} 20 \\ 5 \\ 0 \end{bmatrix} = \begin{bmatrix} V_L \\ V_B \\ I_B \end{bmatrix}$$

DONE

So, the matrix loop equation is: -


$$\begin{bmatrix} 20 \\ 50 \\ 0 \end{bmatrix} = \begin{bmatrix} 14-j4 & -10 & -j4 \\ -10 & 20+j5 & j5 \\ -j4 & j5 & 3+j \end{bmatrix} \begin{bmatrix} I_{11} \\ I_{12} \\ I_{13} \end{bmatrix}$$

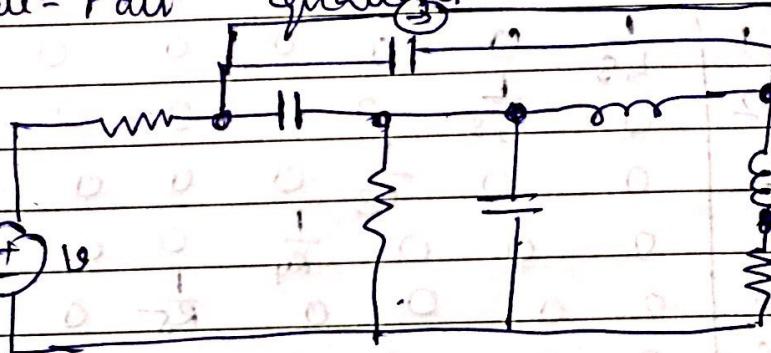- Q.11 Draw the Directed Graph of the network Ans. as shown, choose a tree, write the cut-set matrix, branch admittance matrix and node-pair equations.



Sel M

Graph: -

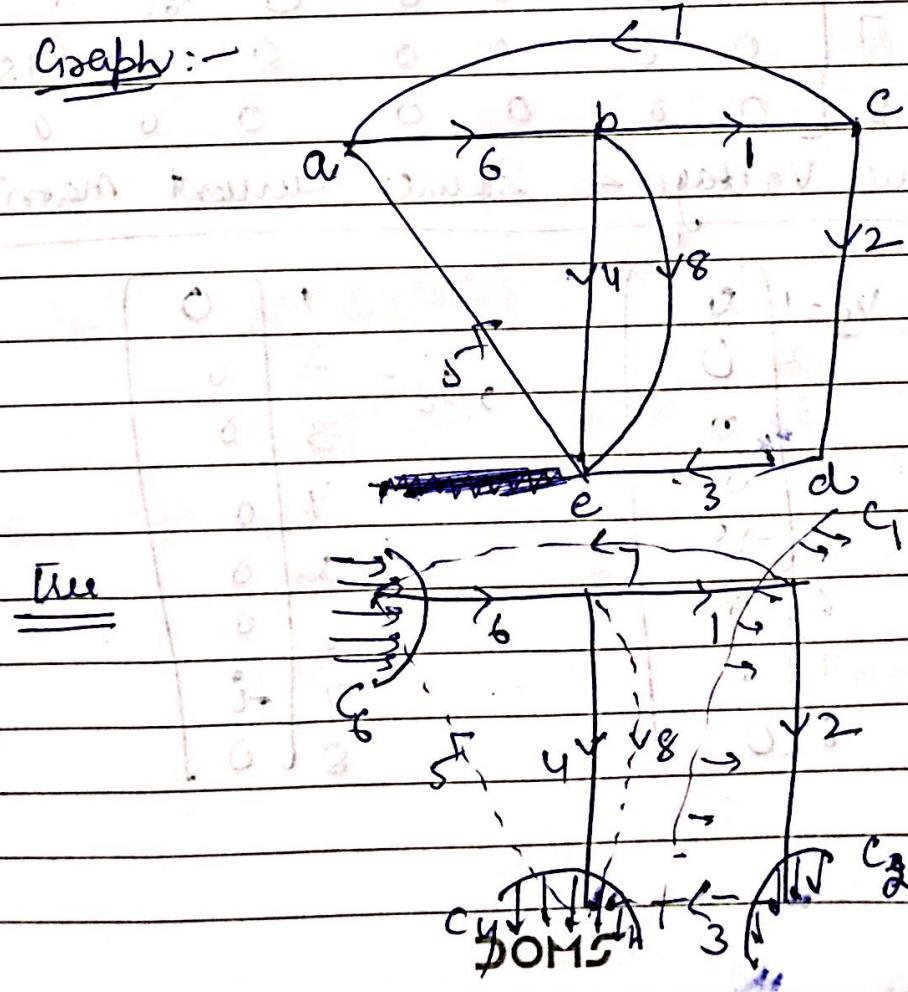

$$n = 5$$

$$b = 7$$

$$n_t = 4 =$$

$$n_l = 3$$

4 nos. of cut-sets

Tree

Cut-set matrix:-

Cut sets Branches →

	1	2	3	4	5	6	7	8
C_1	1	0	-1	0	0	0	-1	0
C_2	0	1	-1	0	0	0	0	0
C_3	0	0	1	1	-1	0	0	1
C_4	0	0	0	0	-1	1	-1	0

Branch Admittance Matrix:-

	1	2	3	4	5	6	7	8	9
1	$\frac{1}{4s}$	0	0	0	0	0	0	0	0
2	0	$\frac{1}{2s}$	0	0	0	0	0	0	0
3	0	0	$\frac{1}{R_3}$	0	0	0	0	0	0
4	0	0	0	$\frac{1}{R_4}$	0	0	0	0	0
5	0	0	0	0	$\frac{1}{R_5}$	0	0	0	0
6	0	0	0	0	0	G_6s	0	0	0
7	0	0	0	0	0	0	G_7s	0	0
8	0	0	0	0	0	0	0	G_8s	0

The Source Voltage & Source Current matrices are:-

$$V_S = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ -V \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$I_S = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ -i \\ 0 \end{bmatrix}$$

The Node-Pair Admittance matrix

$$Y_t = \alpha_p Y_b \alpha_f^T$$

$$Y_t = \begin{bmatrix} \frac{1}{L_1 s} & 0 & -\frac{1}{R_3} & 0 & 0 & 0 & -C_7 s & 0 \\ 0 & \frac{1}{L_2 s} & -\frac{1}{R_3} & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & \frac{1}{R_3} & \frac{1}{R_4} & -\frac{1}{R_5} & 0 & 0 & C_8 s \\ 0 & 0 & 0 & 0 & -\frac{1}{R_5} & C_6 s & -C_7 s & 0 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ -1 & -1 & 1 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & -1 & -1 \\ 0 & 0 & 0 & 1 \\ -1 & 0 & 0 & -1 \\ 0 & 0 & 1 & 0 \end{bmatrix}$$

$$Y_t = \begin{bmatrix} \frac{1}{L_1 s} + \frac{1}{R_3 s} + C_8 s & \frac{1}{R_8} & -\frac{1}{R_3} & C_8 s \\ \frac{1}{R_3} & \frac{1}{L_2 s} + \frac{1}{R_3} & -\frac{1}{R_3} & 0 \\ -\frac{1}{R_3} & -\frac{1}{R_8} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + C_8 s & \frac{1}{R_5} \\ C_8 s & 0 & \frac{1}{R_5} & \frac{1}{R_5} + C_6 s + C_7 s \end{bmatrix}$$

The current matrix :-

$$I = (G_f \gamma_b V_s - G_f I_s)$$

$$\begin{bmatrix} 0 \\ 0 \\ \frac{V}{R_S} \\ \frac{V}{R_S} - i \end{bmatrix} = \begin{bmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 \\ \frac{V}{R_S} & 0 & 0 & 0 \\ \frac{V}{R_S} - i & 0 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} -i \\ 0 \\ \frac{V}{R_S} \\ \frac{V}{R_S} - i \end{bmatrix}$$


So, the matrix Node Eqⁿ is :-

$$I = \gamma_b V_t$$

$$\begin{bmatrix} 0 \\ 0 \\ \frac{V}{R_S} \\ \frac{V}{R_S} - i \end{bmatrix} = \begin{bmatrix} 1 + \frac{1}{L_1 S} + C_{1S} & \frac{1}{R_3} & -\frac{1}{R_3} & G_S \\ \frac{1}{L_1 S \cdot R_3 S} & \frac{1}{R_3} & \frac{1}{L_2 S} + \frac{1}{R_3} & -\frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_3} & \frac{1}{R_3} + \frac{1}{R_4} + \frac{1}{R_5} + G_S & \frac{1}{R_5} \\ G_S & 0 & 0 & \frac{1}{R_5} + G_S + C_S \end{bmatrix}$$

Ans.

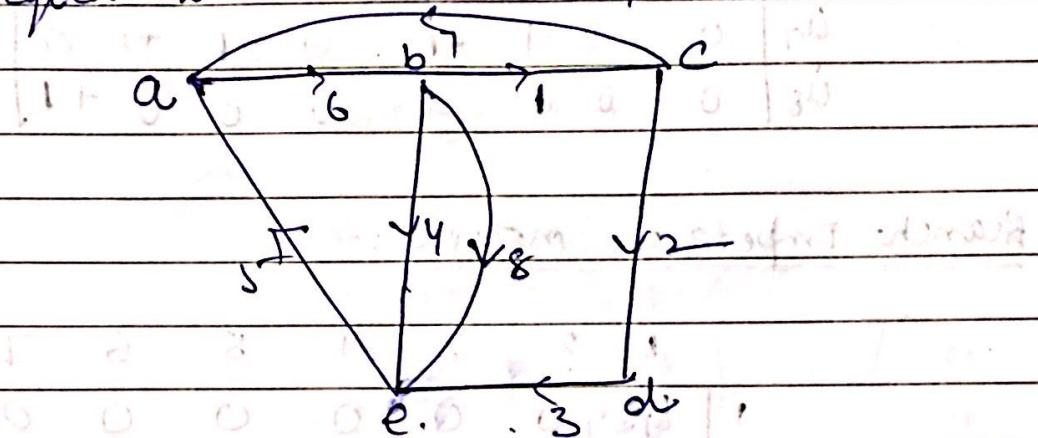Q.12 for a given graph, write the incidence matrix A, loop matrix B and branch impedance matrix. Then determine the loop impedance matrix and write the loop equation in matrix form.




Soln Let Node e is taken as reference node. So the incidence matrix is:-

Nodes \rightarrow Branches

$$[A] = \begin{matrix} & \text{Nodes} \\ \text{Branches} & \downarrow \end{matrix} \begin{bmatrix} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

Tree

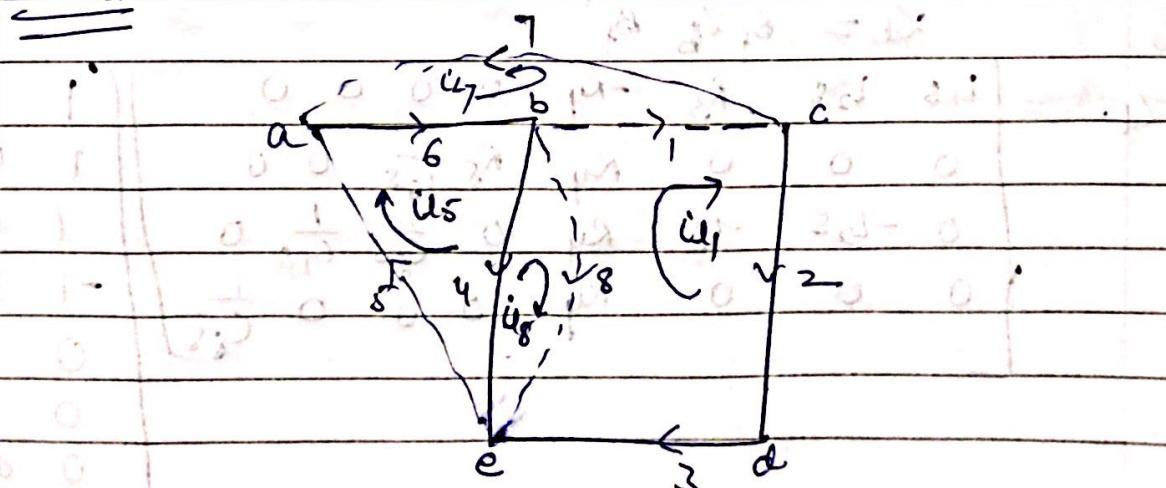

DOMS

Tie-set matrix.

Tie-sets
↓ Branches →

$$[B_f] = \begin{bmatrix} u_1 & +1 & +1 & +1 & -1 & 0 & 0 & 0 \\ u_5 & 0 & 0 & 0 & +1 & +1 & 0 & 0 \\ u_7 & 0 & -1 & -1 & +1 & 0 & +1 & 0 \\ u_8 & 0 & 0 & 0 & -1 & 0 & 0 & +1 \end{bmatrix}$$

Branch Impedance matrix :-

$$[Z_b] = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \\ L_1s & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & L_2s & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & R_3 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & R_4 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & R_5 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{C_6s} & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{C_7s} \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & \frac{1}{C_8s} \end{bmatrix}$$

Now, the loop Impedance matrix is:-

$$Z_L = B_f Z_b B_f^T$$

$$Z_L = \begin{bmatrix} L_1s & L_2s & R_3 & -R_4 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & R_4 & R_5 & \frac{1}{C_6s} & 0 & 0 \\ 0 & -L_2s & -R_3 & R_4 & 0 & \frac{1}{C_6s} & \frac{1}{C_7s} & 0 \\ 0 & 0 & 0 & R_4 & 0 & 0 & 0 & \frac{1}{C_8s} \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 1 & 0 & -1 & 0 \\ 1 & 0 & -1 & 0 \\ -1 & 1 & 1 & -1 \\ 0 & 1 & 0 & 0 \\ 0 & 1 & 1 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 1 \end{bmatrix}$$

DOMS

$$[Z_b] = \begin{bmatrix} L_1 s + L_2 s + R_3 + R_4 & -R_4 & -L_2 s - R_3 - R_4 & R_4 \\ -R_4 & R_4 + R_5 + \frac{1}{C_6 s} & R_4 + \frac{1}{C_6 s} & -R_4 \\ -L_2 s - R_3 - R_4 & R_4 + \frac{1}{C_6 s} & L_2 s + R_5 + R_4 + \frac{1}{C_6 s} + \frac{1}{C_7 s} & -R_4 \\ R_4 & -R_4 & -R_4 & R_4 + \frac{1}{C_8 s} \end{bmatrix}$$

The Loop voltage matrix

$$V_L = B_f Z_b I_S - B_f V_S$$

$$= \begin{bmatrix} 0 & 0 \\ 0 & -U \\ -\frac{i}{G_S} & 0 \\ 0 & 0 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -\frac{i}{G_S} \\ 0 \end{bmatrix}$$

Hence, The matrix loop equation is:-

$$V_L = Z_b I_L$$


$$\begin{bmatrix} 0 \\ 0 \\ \frac{-i}{G_S} \\ 0 \end{bmatrix} = \begin{bmatrix} L_1 s + L_2 s + R_3 + R_4 & -R_4 & -L_2 s - R_3 - R_4 & R_4 \\ -R_4 & R_4 + R_5 + \frac{1}{C_6 s} & R_4 + \frac{1}{C_6 s} & -R_4 \\ -L_2 s - R_3 - R_4 & R_4 + \frac{1}{C_6 s} & L_2 s + R_5 + R_4 + \frac{1}{C_6 s} + \frac{1}{C_7 s} & -R_4 \\ R_4 & -R_4 & -R_4 & R_4 + \frac{1}{C_8 s} \end{bmatrix}$$

$$\begin{bmatrix} I_{L1} \\ I_{L2} \\ I_{L3} \\ I_{L4} \end{bmatrix}$$

Ans.

DOMS

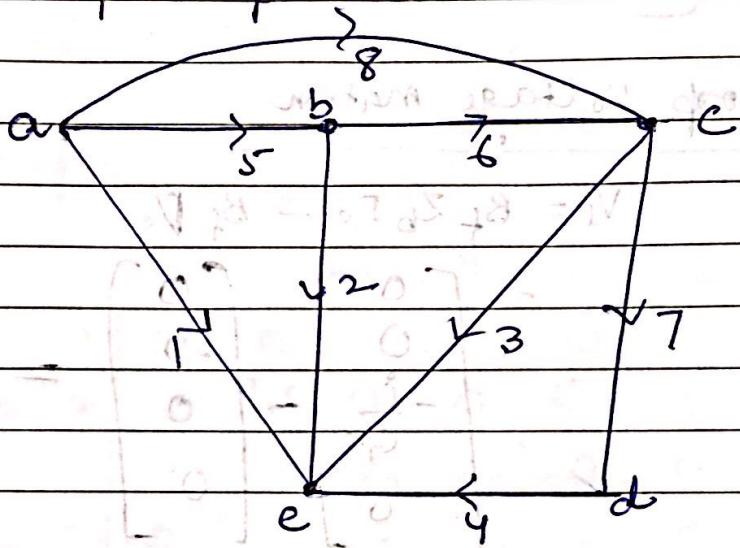Q.13 Write the Incidence Matrix of the graph
 & given and then express branch voltages
 in terms of node voltages. Write the loop
 matrix B and express branch currents
 in terms of loop currents.



Solⁿ

Taking e_5 as reference node:

Nodey branches \rightarrow

$$[A] = \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \\ 0 & 1 & 0 & 0 & -1 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 0 & 0 & 1 & 0 & 0 & -1 & 0 \end{bmatrix}$$


As, we know that:-

$$V_b = A^T V_n$$

DOMS

v_1	1	0	0	0	v_a
v_2	0	1	0	0	v_b
v_3	0	0	1	0	v_c
v_4	0	0	0	1	v_d
v_5	1	-1	0	0	
v_6	0	1	-1	0	
v_7	0	0	1	-1	
v_8	1	0	-1	0	

tree

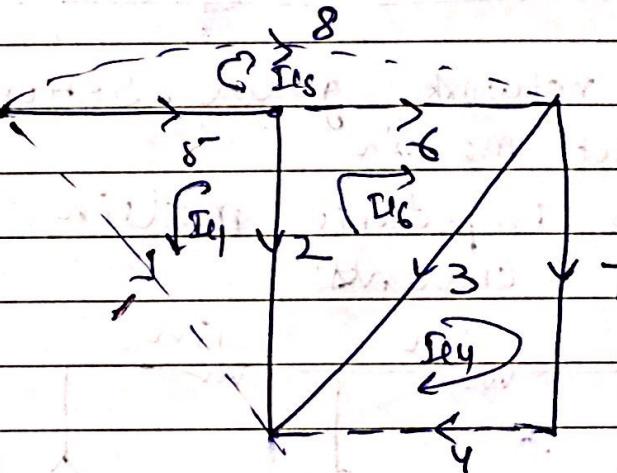

Now, As we know


$$I_b = B_f^T \bar{I}_L$$

I_1	1	0	0	0	I_{L1}
I_2	-1	0	-1	-1	I_{L2}
I_3	0	-1	1	1	I_{L3}
I_4	0	1	0	0	I_{L4}
I_5	-1	0	0	-1	
I_6	0	0	1	0	
I_7	0	1	0	0	
I_8	0	0	0	1	

Ans

DOMS


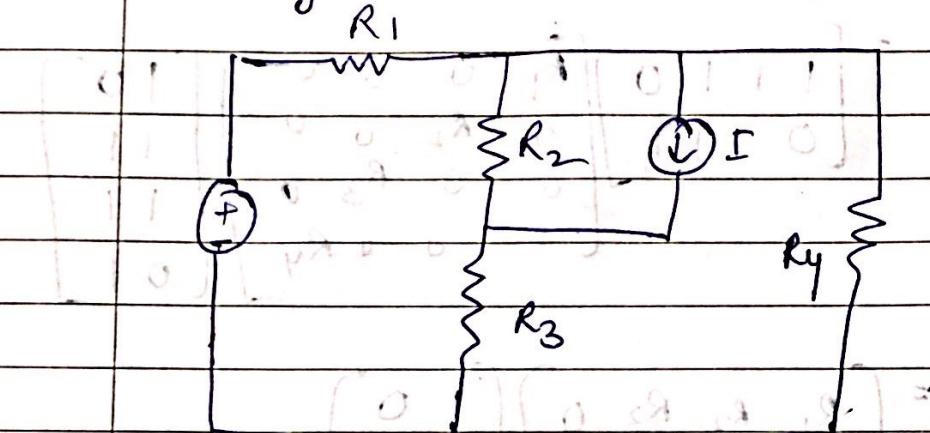
Q.14 Write the loop equations in matrix form for the given circuit.



Soln

Graph

Tree

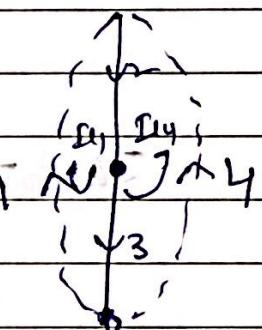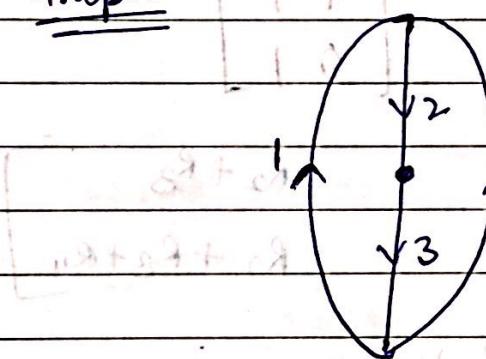

Tie-Set Matrix

$$[B_f] = \frac{\partial I_1}{\partial V_2} \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 \\ 0 & 0 & 1 & 1 \end{bmatrix}$$

$$[Z_b] = \begin{bmatrix} R_1 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 \\ 0 & 0 & R_3 & 0 \\ 0 & 0 & 0 & R_4 \end{bmatrix}$$

$$V_s = \begin{bmatrix} -V \\ 0 \\ 0 \\ 0 \end{bmatrix}, I_s = \begin{bmatrix} 0 \\ I \\ 0 \\ 0 \end{bmatrix}$$

DOMS

So, The loop impedance matrix :-

$$Z_L = B_f Z_b B_f^T$$

$$= \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} R_1 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 \\ 0 & 0 & R_3 & 0 \\ 0 & 0 & 0 & R_4 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ 1 & 1 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} R_1 & R_2 & R_3 & 0 \\ 0 & R_2 & R_3 & R_4 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & 1 \\ 1 & 1 \\ 0 & 1 \end{bmatrix}$$

$$\therefore Z_L = \begin{bmatrix} R_1 + R_2 + R_3 & -R_2 - R_3 \\ R_2 + R_3 & R_2 + R_3 + R_4 \end{bmatrix}$$

$$V_L = B_f Z_b I_S - B_f V_S$$

$$= \begin{bmatrix} R_1 & R_2 & R_3 & 0 \\ 0 & R_2 & R_3 & R_4 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix} - \begin{bmatrix} 1 & 1 & 1 & 0 \\ 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -V \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\therefore = \begin{bmatrix} IR_2 \\ IR_2 \end{bmatrix} - \begin{bmatrix} -V \\ 0 \end{bmatrix} = \begin{bmatrix} IR_2 + V \\ IR_2 \end{bmatrix}$$


So, The loop eqn in matrix form:-

$$\begin{bmatrix} 2R_2 + V \\ IR_2 \end{bmatrix} = \begin{bmatrix} R_1 + R_2 + R_3 & -R_2 - R_3 \\ R_2 + R_3 & R_2 + R_3 + R_4 \end{bmatrix} \begin{bmatrix} I_{L1} \\ I_{L4} \end{bmatrix}$$

DOMS


Ans

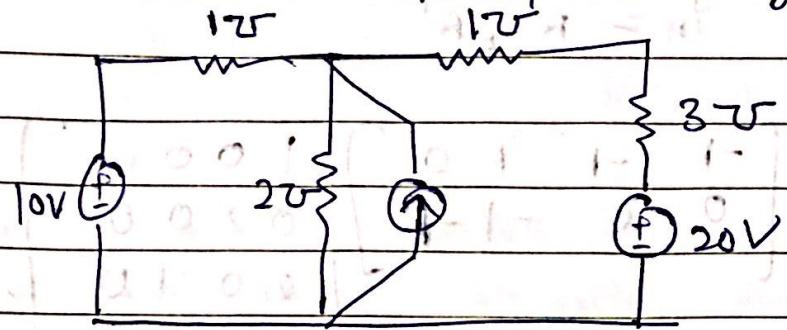Q.15 write the node eqn for the given network.



Sgn

Graph

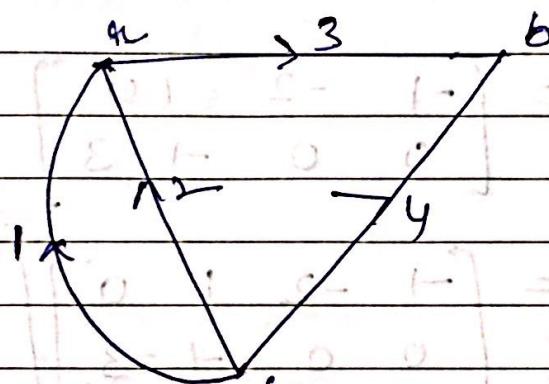

Taking C as reference node

Nodey Branches →

$$[A] = \begin{bmatrix} & 1 & 2 & 3 & 4 \\ a & -1 & -1 & 1 & 0 \\ b & 0 & 0 & -1 & -1 \end{bmatrix}$$

$$[Y_b] = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 2 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 3 \end{bmatrix}$$

$$V_s = \begin{bmatrix} -10 \\ 0 \\ 0 \\ -20 \end{bmatrix}, \quad \text{and } I_s = \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$

DOMS

$$Y_n = A Y_b A^T$$

$$AY_b = \begin{bmatrix} -1 & -1 & 1 & 0 \\ 0 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & 2 & 0 & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 3 \end{bmatrix}$$

$$= \begin{bmatrix} -1 & -2 & 1 & 0 \\ 0 & 0 & -1 & -3 \end{bmatrix}$$

$$\therefore Y_n = \begin{bmatrix} -1 & -2 & 1 & 0 \\ 0 & 0 & -1 & -3 \end{bmatrix} \begin{bmatrix} -1 & 0 \\ -1 & 0 \\ 1 & -1 \\ 0 & -1 \end{bmatrix}$$

$$Y_n = \begin{bmatrix} -4 & -1 \\ -1 & 4 \end{bmatrix}$$

And

$$I_n = A Y_b V_s - A I_s$$

$$= \begin{bmatrix} -1 & -2 & 1 & 0 \\ 0 & 0 & -1 & -3 \end{bmatrix} \begin{bmatrix} -10 \\ 0 \\ 0 \\ -20 \end{bmatrix} - \begin{bmatrix} -1 & -1 & 1 & 0 \\ 0 & 0 & -1 & -1 \end{bmatrix} \begin{bmatrix} 0 \\ 1 \\ 0 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} 10 \\ 60 \end{bmatrix} - \begin{bmatrix} -1 \\ 0 \end{bmatrix} = \begin{bmatrix} 11 \\ 60 \end{bmatrix}$$


Hence, the node equations are:-

DOMS

$$I_n = Y_m V_m \text{ shorted branch}$$


$$\begin{bmatrix} 11 \\ 60 \end{bmatrix} = \begin{bmatrix} 4 & -1 \\ -1 & 4 \end{bmatrix} \begin{bmatrix} V_a \\ V_b \end{bmatrix} \quad \underline{\text{Ans.}}$$

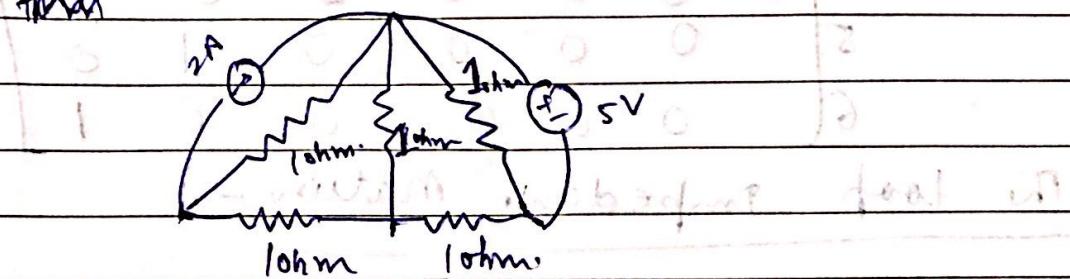Q.16 for a given network, draw the graph, write the tie-set schedule, and obtain then



Soln

Graph.

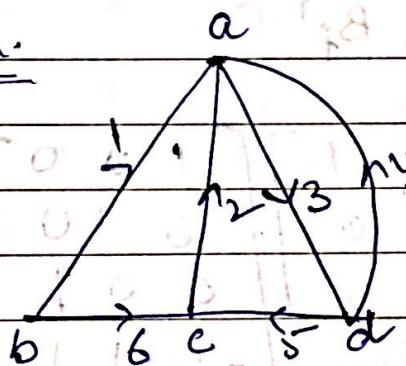


$$n = 4$$

$$b = 6$$

$$nt = 4 - 1 = 3$$

$$nl = 3.$$

Tree

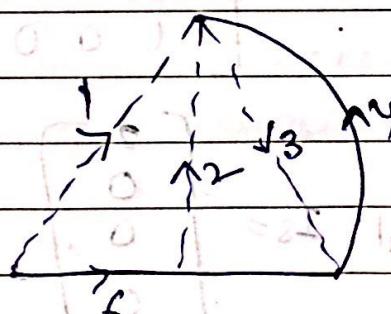

Tie-set matrix

$$[B_f] = \begin{bmatrix} 1 & 1 & 0 & 0 & -1 & 1 & -1 \\ 2 & 0 & 1 & 0 & -1 & 1 & 0 \\ 3 & 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix}$$

DOMS

The Branch Impedance Matrix:-

	1	2	3	4	5	6
1	1	0	0	0	0	0
2	0	1	0	0	0	0
3	0	0	1	0	0	0
4	0	0	0	1	0	0
5	0	0	0	0	1	0
6	0	0	0	0	0	1

The Loop Impedance Matrix:-

$$Z_L = B_f Z_b B_f^T$$

$$Z_L = \begin{bmatrix} 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 \\ 0 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 1 \end{bmatrix} = \begin{bmatrix} 3 & 1 & 0 \\ 1 & 2 & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$V_S = \begin{bmatrix} 0 \\ 0 \\ 0 \\ -5 \\ 0 \\ 0 \end{bmatrix} \quad \text{and} \quad I_S = \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 & 0 \\ 1 & 0 & 0 & 1 & 0 & 0 \end{bmatrix}$$

So

$$V_L = B_f Z_b \Sigma s - B_f V_s$$

$$= \begin{bmatrix} 1 & 0 & 0 & 0 & 1 & -1 \\ 0 & 1 & 0 & 0 & 1 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \end{bmatrix} \begin{bmatrix} 2 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} - \begin{bmatrix} 1 & 0 & 0 & -1 & 1 & -1 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 1 & 0 & 0 \end{bmatrix} \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$


$$= \begin{bmatrix} 2 \\ 0 \\ 0 \end{bmatrix} - \begin{bmatrix} s \\ s \\ s \end{bmatrix}$$

$$V_L = \begin{bmatrix} -3 \\ -5 \\ +5 \end{bmatrix}$$

Ans'

* Network with Mutual Inductance:-

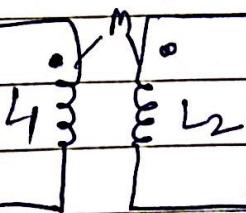As we have seen earlier, if there is no mutual coupling b/w the branches, the branch impedance or admittance matrix is a diagonal matrix otherwise it may have non-zero elements in the off-diagonal locations also.




(with positive coupling)

Branch Inductance

$$L_b = \begin{bmatrix} L_1 & M \\ M & L_2 \end{bmatrix}$$

DOMS

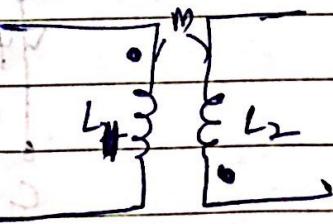


(with opposing coupling)

Branch Inductance


$$L_b = \begin{bmatrix} L_1 & -M \\ M & L_2 \end{bmatrix}$$

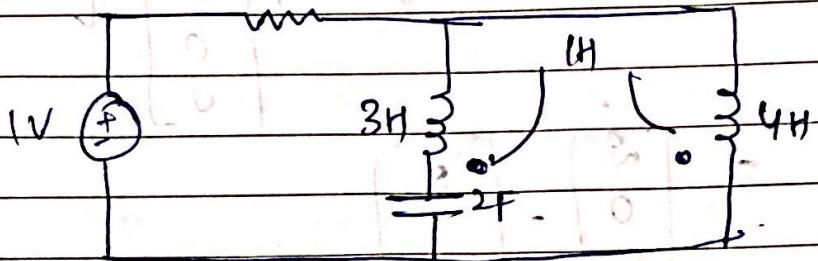Q.17 for the given network, write down the f-cut set matrix for the tree having 3H inductor and 2F capacitor as twigs and write the matrix cut-set equations.




Soln since the dots are on the same side, the mutual inductance would be positive.

graph:

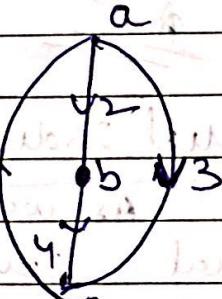

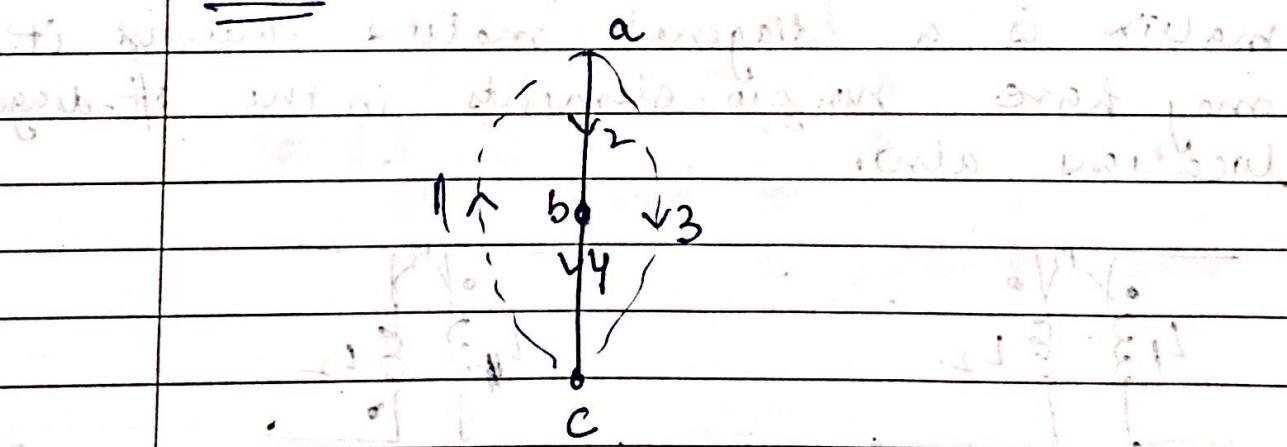Tree with 3H inductor & 2F capacitor as twigs.



f-cut matrix

$$\{Q_f\} = \begin{matrix} \text{Cut sets} \\ \downarrow \\ C_1 \\ C_2 \\ C_3 \end{matrix} \begin{bmatrix} 1 & 2 & 3 & 4 \\ -1 & 1 & 1 & 0 \\ -1 & 0 & 1 & 1 \end{bmatrix}$$

DOMS

$$Y_b = [Z_b]^{-1} = \begin{bmatrix} [1]^{-1} & 0 & 0 & 0 \\ 0 & \begin{bmatrix} 3s & s \\ s & -4s \end{bmatrix}^{-1} & 0 \\ 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & \left[\frac{1}{2s}\right]^{-1} \end{bmatrix}$$

$$\text{Invertible matrix } \Rightarrow \text{ Inverse matrix with } 0 \text{ and } 1 \\ \text{Matrix inverse} = \begin{bmatrix} 1 & 0 & 0 & 0 \\ 0 & \frac{4}{11}s & -\frac{1}{11}s & 0 \\ 0 & -\frac{1}{11}s & \frac{3}{11}s & 0 \\ 0 & 0 & 0 & 2s \end{bmatrix}$$

$$\Omega_f Y_b = \begin{bmatrix} -1 & \frac{3}{11}s & \frac{2}{11}s & 0 \\ -1 & -\frac{1}{11}s & \frac{3}{11}s & 2s \end{bmatrix}$$

$$Y_T = \Omega_f Y_b \Omega_f^T = \begin{bmatrix} -1 & \frac{3}{11}s & \frac{2}{11}s & 0 \\ -1 & -\frac{1}{11}s & \frac{3}{11}s & 2s \end{bmatrix} \begin{bmatrix} -1 & -1 \\ 1 & 0 \\ 1 & 1 \\ 0 & 1 \end{bmatrix}$$

$$\text{Invertible matrix} = \begin{bmatrix} 1 + \frac{5}{11}s & 1 + \frac{2}{11}s & 0 \\ 1 + \frac{2}{11}s & 1 + \frac{3}{11}s + 2s & 0 \\ 0 & 0 & 1 \end{bmatrix}$$

$$I = \Omega_f Y_b V_s - \Omega_f E_S = \Omega_f Y_b V_s \quad [\text{since } E_S = 0]$$


$$= \begin{bmatrix} -1 & \frac{3}{11}s & \frac{2}{11}s & 0 \\ -1 & -\frac{1}{11}s & \frac{3}{11}s & 2s \end{bmatrix} \begin{bmatrix} -1 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 1 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Hence, The matrix cut-set \mathbf{g}_n^n is:-

$$\Sigma = Y_T V_\Theta$$


$$\begin{bmatrix} 1 \\ 1 \end{bmatrix} = \begin{bmatrix} 1 + \frac{5}{11s} & 1 + \frac{2}{11s} \\ 1 + \frac{2}{11s} & 1 + \frac{3}{11s} + 2s \end{bmatrix} \begin{bmatrix} V_2 \\ V_4 \end{bmatrix}$$

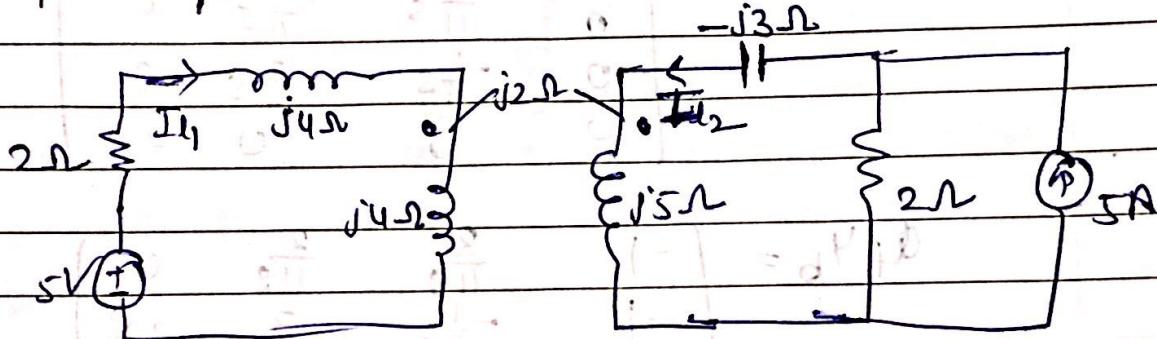Q.18 for a given network (a) determine the f-loop matrix and f-loop equations.



Soln

Graph:-

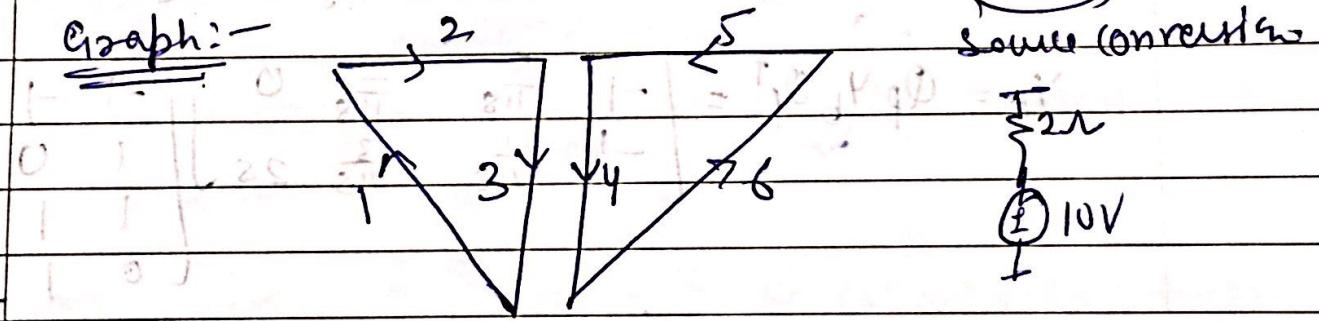


The Branch Impedance Matrix:-

$$Z_b = \begin{matrix} & 1 & 2 & 3 & 4 & 5 & 6 \end{matrix}$$

$$\begin{matrix} 1 & \left| \begin{matrix} 2 & 0 & 0 & 0 & 0 & 0 \end{matrix} \right. \\ 2 & \left| \begin{matrix} 0 & -j4 & 0 & 0 & 0 & 0 \end{matrix} \right. \\ 3 & \left| \begin{matrix} 0 & 0 & j4 & j2 & 0 & 0 \end{matrix} \right. \\ 4 & \left| \begin{matrix} 0 & 0 & j2 & j5 & 0 & 0 \end{matrix} \right. \\ 5 & \left| \begin{matrix} 0 & 0 & 0 & 0 & 1 & -j3 \end{matrix} \right. \\ 6 & \left| \begin{matrix} 0 & 0 & 0 & 0 & 0 & 2 \end{matrix} \right. \end{matrix}$$

DOMS

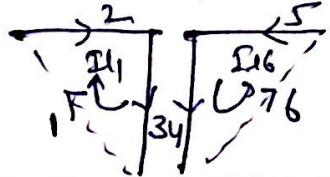

The f-Loop Matrix:-

f-Loop Branches \Rightarrow

$$\text{Forward } B_f = \begin{bmatrix} 1 & 2 & 3 & 4 & 5 & 6 \\ 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix}$$

$$\text{Result } B_f Z_b = \begin{bmatrix} 2+j4 & j4 & j2 & 0 & 0 \\ 0 & 0 & j2 & j5 & -j3 \\ 0 & 0 & 0 & 0 & 0 \end{bmatrix}$$

So, the Loop Impedance Matrix:-

$$Z_L = B_f Z_b B_f^T$$

$$Z_L = \begin{bmatrix} 2 & j4 & j4 & j2 & 0 & 0 \\ 0 & 0 & j2 & j5 & -j3 & 2 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 \end{bmatrix}$$

$$Z_L = \begin{bmatrix} 2+j8 & 2 \\ j2 & 2+j2 \end{bmatrix}$$

The Loop Voltage Matrix:-

$$V_L = B_f Z_b I_s - B_f V_s$$

$$= 0 - \begin{bmatrix} 1 & 1 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 1 & 1 \end{bmatrix} \begin{bmatrix} -5 \\ 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix} = \begin{bmatrix} 5 \\ 10 \end{bmatrix}$$

Hence, loop eqn are:-


$$V_L = Z_L I_L$$

$$\begin{bmatrix} 5 \\ 10 \end{bmatrix} = \begin{bmatrix} 2+j8 & j2 \\ j2 & 2+j2 \end{bmatrix} \begin{bmatrix} I_{11} \\ I_{12} \end{bmatrix}$$


Ans,

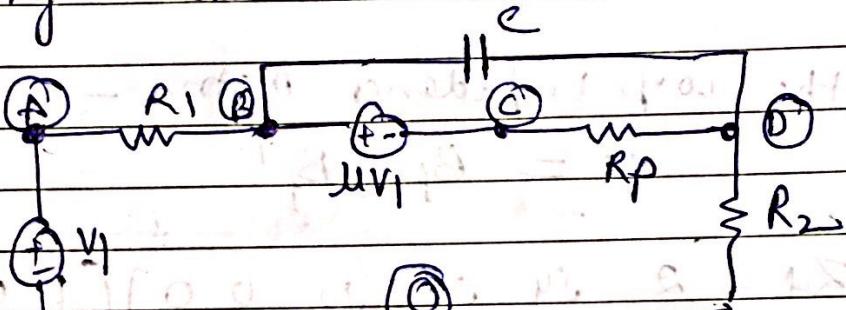Q. 19

Draw the graph of given network and find a tree of network; Considering '0' as a datum node and assuming elements BD and BC as links, determine the tie-set schedule, branch impedance matrix and source voltage matrix, obtain loop equations using above said matrices.



Soln

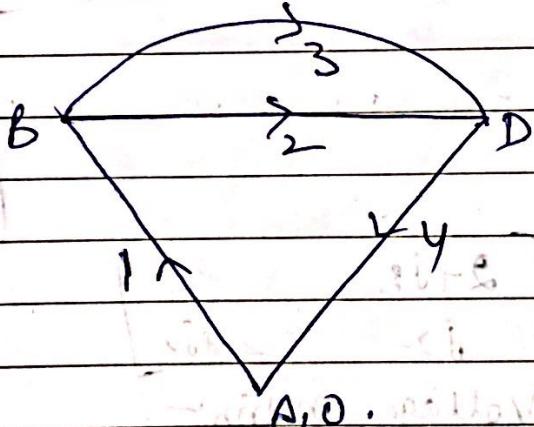


Branch 1 w.r.t to R_1

" 2 " R_p


" 3 " C

" 4 " R_2

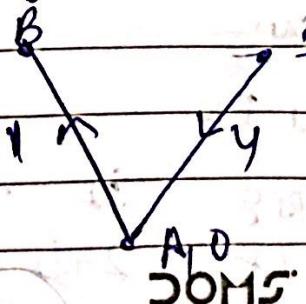Tree with given condition i.e. BD & BC as links



As 2 Link \rightarrow 2 No. of Tie-sets.

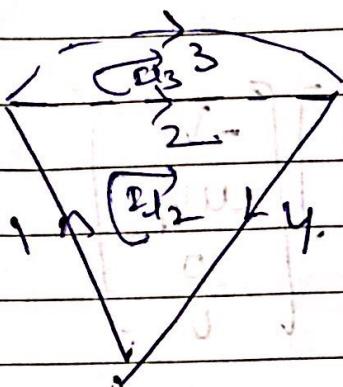

Tie-set schedule:-

$$[B_f] = \begin{matrix} \text{Tie-sets} & \text{Branches} \rightarrow \\ \downarrow & \\ I_{L1} & [1 \ 2 \ 3 \ 4] \\ I_{L2} & [1 \ 0 \ 1 \ 1] \\ I_{L3} & [1 \ 0 \ 0 \ 1] \end{matrix}$$

1) The Branch Impedance Matrix:-

$$Z_b = \begin{bmatrix} R_1 & 0 & 0 & 0 \\ 0 & R_2 & 0 & 0 \\ 0 & 0 & \frac{1}{C_s} & 0 \\ 0 & 0 & 0 & R_2 \end{bmatrix}$$

Source voltage matrix:-

$$V_s = \begin{bmatrix} -V_1 \\ \mu V_1 \\ 0 \\ 0 \end{bmatrix}$$

DOMS

So, The Loop Voltage matrix -

$$V_L = B_f Z_b I_s - B_f V_s$$

$$= 0 - \begin{bmatrix} 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} -V_1 \\ V_2 \\ 0 \\ 0 \end{bmatrix}$$

$$V_L = \begin{bmatrix} V_1 - V_2 \\ V_1 \end{bmatrix}$$

Loop Impedance matrix -

$$Z_L = B_f Z_b B_f^T$$

$$\begin{bmatrix} 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} R_1 & 0 & 0 & 0 \\ 0 & R_p & 0 & 0 \\ 0 & 0 & \frac{1}{C_s} & 0 \\ 0 & 0 & 0 & R_2 \end{bmatrix} \begin{bmatrix} 1 & 1 \\ 1 & 0 \\ 0 & 1 \\ 0 & 1 \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 1 & 0 & 1 \\ 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} R_1 & R_1 \\ R_p & 0 \\ 0 & \frac{1}{C_s} \\ R_2 & R_2 \end{bmatrix}$$

$$Z_L = \begin{bmatrix} R_1 + R_p + R_2 & 0 & R_1 + R_2 \\ 0 & R_1 + R_2 & R_1 + \frac{1}{C_s} + R_2 \end{bmatrix}$$

Hence, matrix loop equations are:-

$$\begin{bmatrix} V_1 - iV_1 \\ V_1 \end{bmatrix} = \begin{bmatrix} R_1 + R_p + R_2 & R_1 + R_2 \\ R_1 + R_2 & R_1 + \frac{1}{C_S} + R_2 \end{bmatrix} \begin{bmatrix} I_{L_2} \\ I_{L_3} \end{bmatrix}$$

Duals and Duality:-

According to ohm's law

$$V = IR \quad \text{---(1)}$$


$$I = G V \quad \text{---(2)}$$

from eqn ① & ②, it is to be noted that either eqn may be found from the other by interchanging each symbol by its pair opposite. i.e. I and V , G and R .


(1) in open ckt $I=0, V \neq 0$

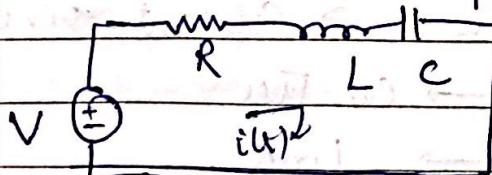(2) in short ckt $V=0, I \neq 0$

So, we can say that there is a systematic symmetry of opposites, or duality between resistance and conductance, voltage and current, open circuit and short-circuit i.e. R is the dual of G , G is dual of R , V is dual of I , I is dual of V , short circuit is dual of open-circuit, open circuit is dual of short circuit.


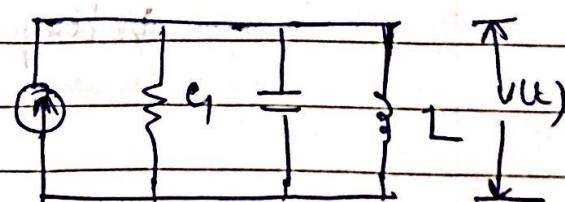
$$V = Ri(t) + \frac{1}{L} \int i(t) dt + \frac{1}{C} \int i(t) dt$$



$$I = G V(t) + \frac{1}{L} \int V(t) dt + \frac{1}{C} \int V(t) dt$$

DOMS

These two networks are called as dual of each other.

So, we can say, two networks are said to be dual of each other, if the mesh equations of one are the same as the node equations of the other.

→ In terms of graphs, we can say that two graphs G_1 and G_2 are said to be dual of each other, if the incidence matrix of any of them is a loop matrix of the other.

Some of Dual Relations are as follows:-

Voltage (V) \leftrightarrow Current (I)

Resistance (R) \leftrightarrow Conductance (G)

Inductance (L) \leftrightarrow Capacitance (C)

Impedance (Z) \leftrightarrow Admittance (Y)

Voltage Source (V_s) \leftrightarrow Current Source (I_s)

KVL \leftrightarrow KCL

Mesh \leftrightarrow Node

Mesh Current \leftrightarrow Node Voltage

Mesh Equations \leftrightarrow Nodal Equations


Thevenin's Theorem \leftrightarrow Norton's Theorem

Voltage Division \leftrightarrow Current Division

Tree \leftrightarrow Co-Tree

Twig \leftrightarrow Link

Cut-Set \leftrightarrow Tiset (Loop)

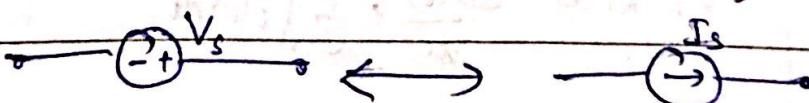

DOMS


$$\begin{array}{ccc}
 \text{Diagram 1: } & & \text{Diagram 2: } \\
 \text{Left: } +V(t) - \xrightarrow{i(t)} & \longleftrightarrow & \text{Right: } +V(t) - \xrightarrow{i(t)} \\
 & & \\
 \text{Left: } +V(t) - \xrightarrow{\frac{dV(t)}{dt}} & \longleftrightarrow & \text{Right: } +V(t) - \xrightarrow{i(t)} \\
 \text{Left: } V(t) = R i(t) & & \text{Left: } i(t) = G V(t) \\
 & & \\
 \text{Left: } +V(t) - \xrightarrow{\frac{dV(t)}{dt}} & \longleftrightarrow & \text{Left: } +V(t) - \xrightarrow{i(t)} \\
 \text{Left: } V(t) = L \frac{di(t)}{dt} & & \text{Left: } i(t) = C \frac{dV(t)}{dt} \\
 & & \\
 \text{Left: } +V(t) - \xrightarrow{i(t)} & \longleftrightarrow & \text{Left: } +V(t) - \xrightarrow{i(t)} \\
 & & \\
 \text{Left: } V(t) = \frac{1}{C} \int_0^t i(t) dt + V_0 & \longleftrightarrow & \text{Left: } i(t) = \frac{1}{L} \int_0^t V(t) dt + i_0
 \end{array}$$

Procedure for Constructing Dual of a Network:-


- i) A dot is placed in the centre of each mesh. Label each node with a number or alphabet.
- ii) Place an extra dot outside the network. This will be the reference or datum node.
- iii) Draw dashed line between the nodes in such a way that each line crosses only one ~~one~~ ~~line~~ network element and a dashed line has been drawn through every element in the original network.
- iv) The dashed lines, along with the dual elements, constitute the dual of original network.

Q.20


Draw the dual of network given:-

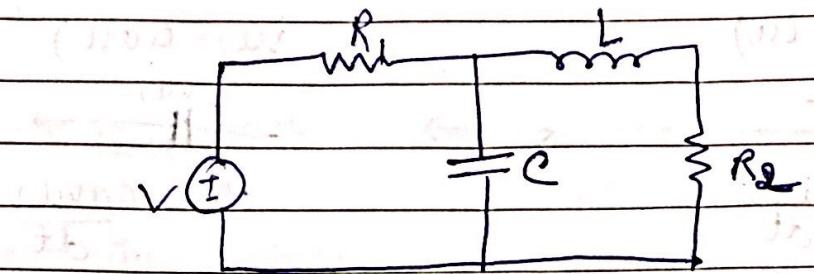

Soln

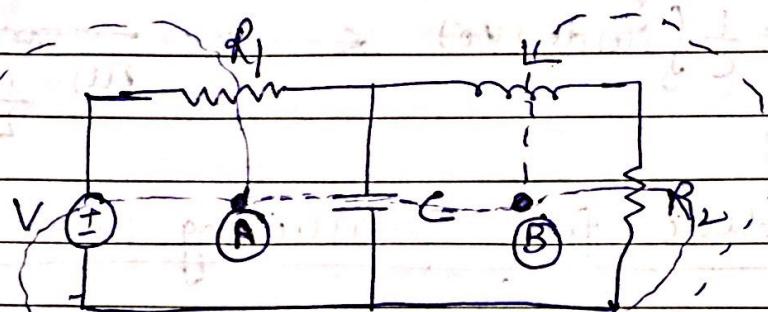



Dual Network:-

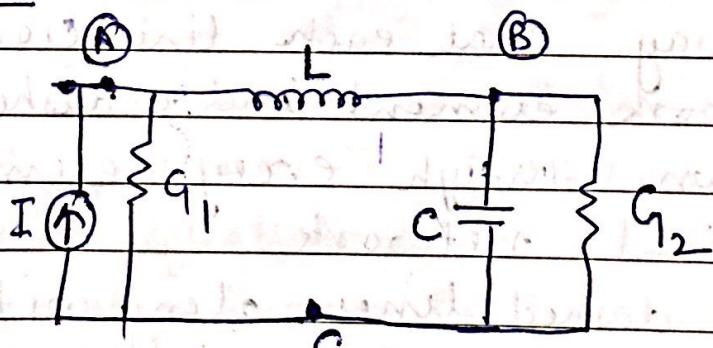




Q.21

Draw the dual of Given network:-

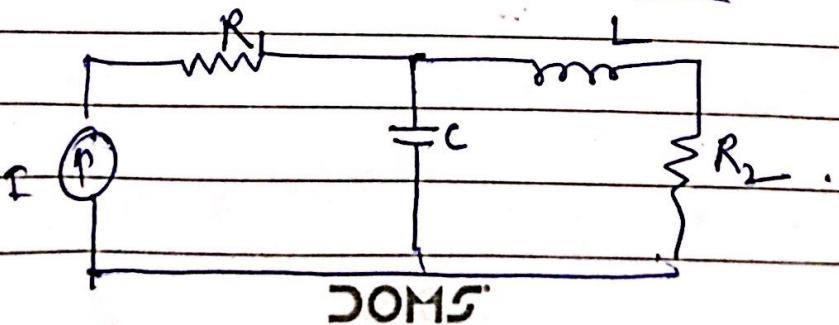

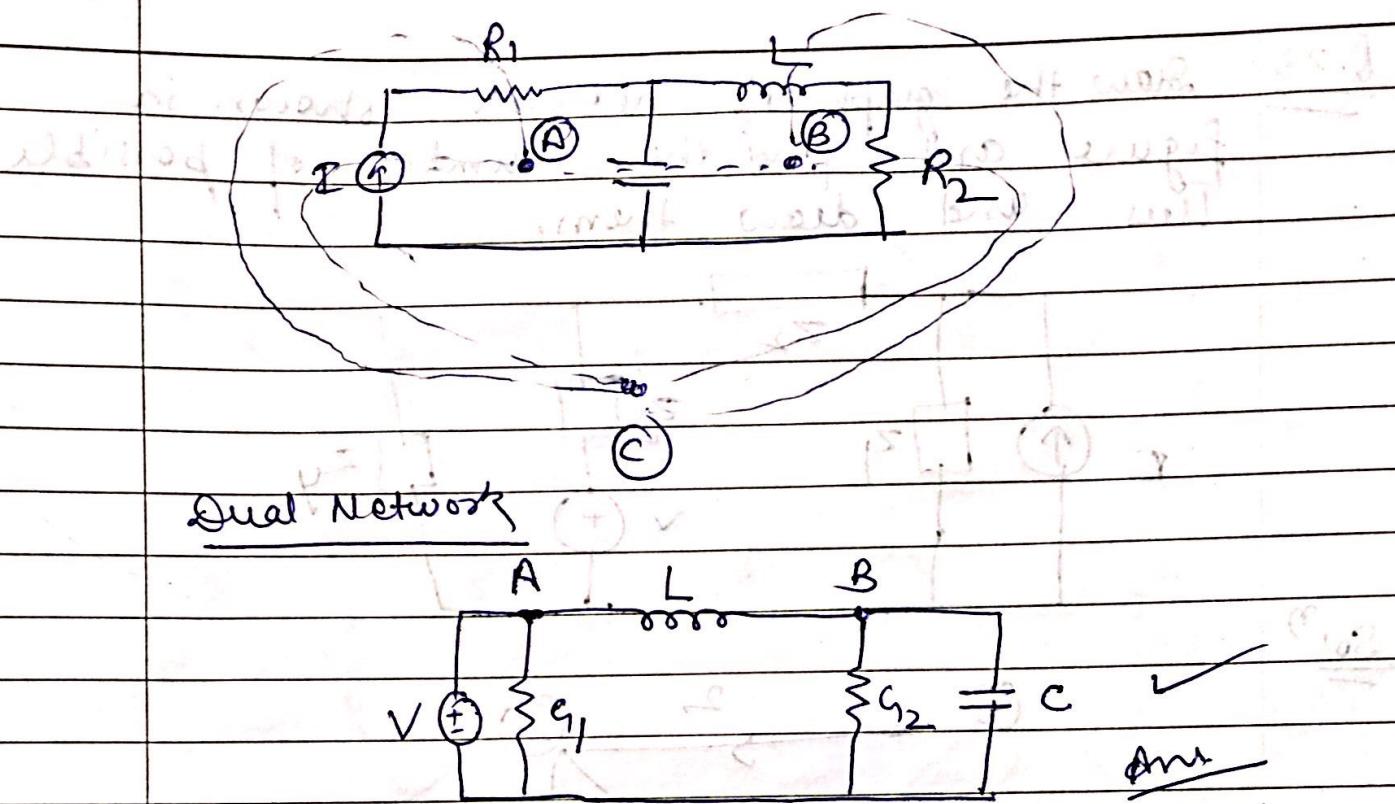


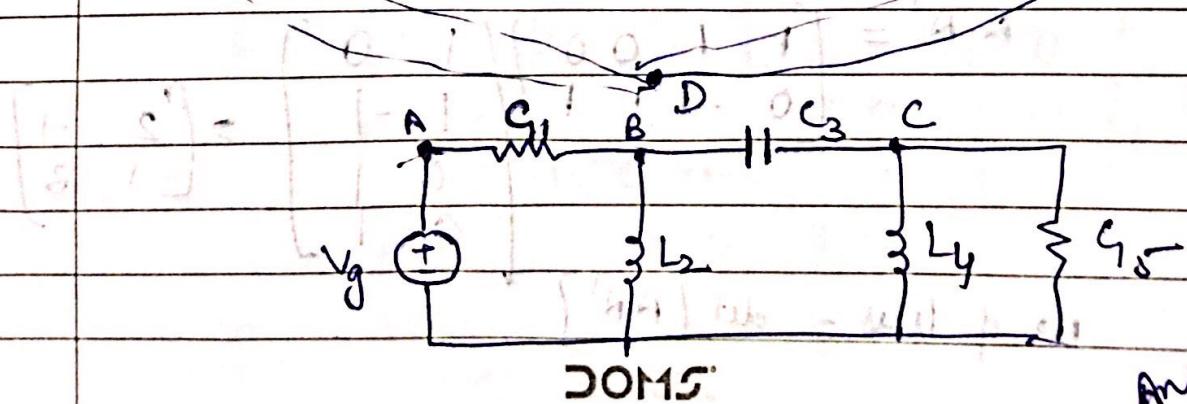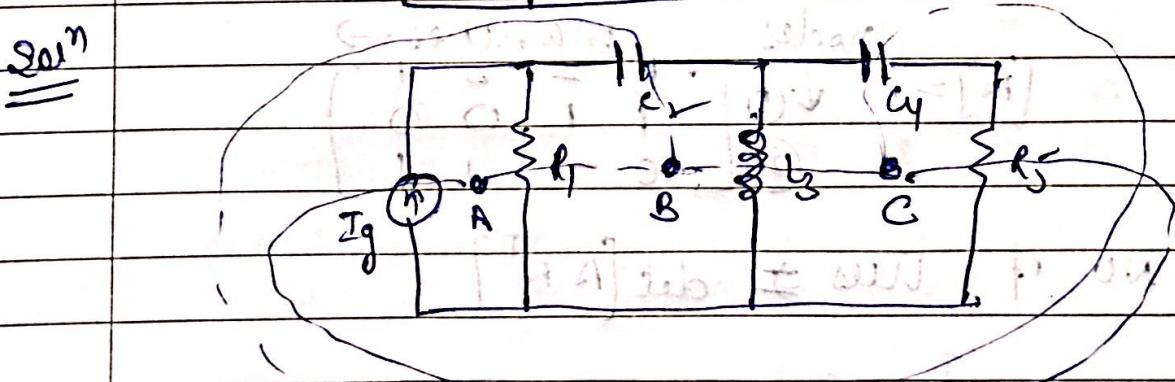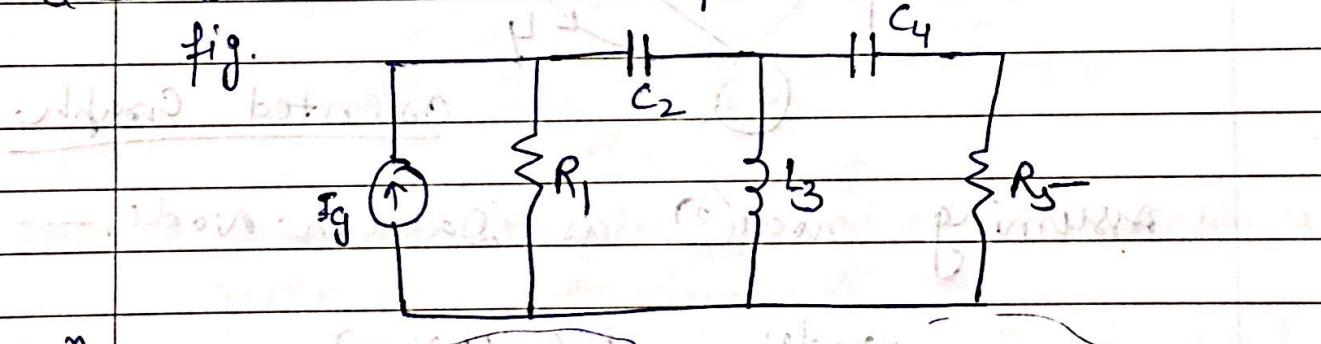Q.22 Draw the dual of the network shown in fig.




Ans /

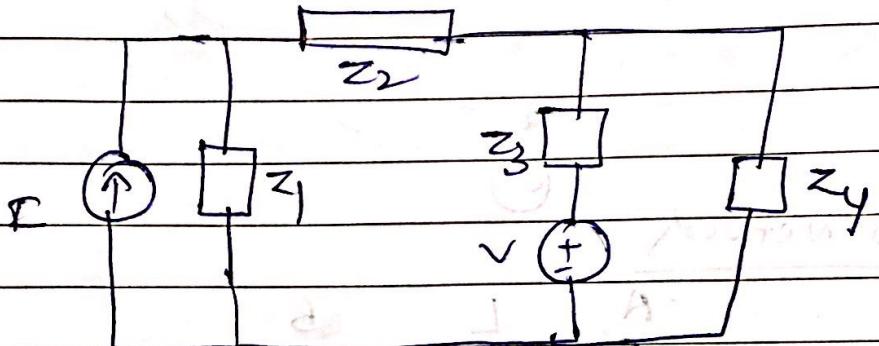Q. 23 Draw the graph of network shown in figure and find the number of possible trees and draw them.



Solⁿ

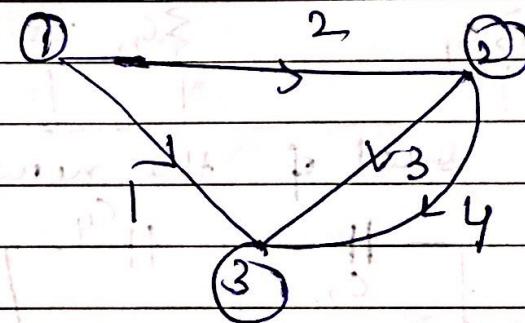

Oriented Graph

Assuming node (3) as datum node. →

$$[A] = \begin{matrix} \text{nodes} \\ \downarrow \end{matrix} \begin{matrix} 1 & 2 & 3 & 4 \\ 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{matrix}$$

$$\text{No. of trees} \propto \det[A \ A^T]$$


$$A \cdot A^T = \begin{bmatrix} 1 & 1 & 0 & 0 \\ 0 & -1 & 1 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 2 & -1 \\ -1 & 3 \end{bmatrix}$$

$$\text{No. of trees} = \det[A \ A^T]$$

DOMS

$$= \begin{vmatrix} 2 & -1 \\ -1 & 3 \end{vmatrix} = 6 - 1 = 5.$$

So, No. of trees = 5

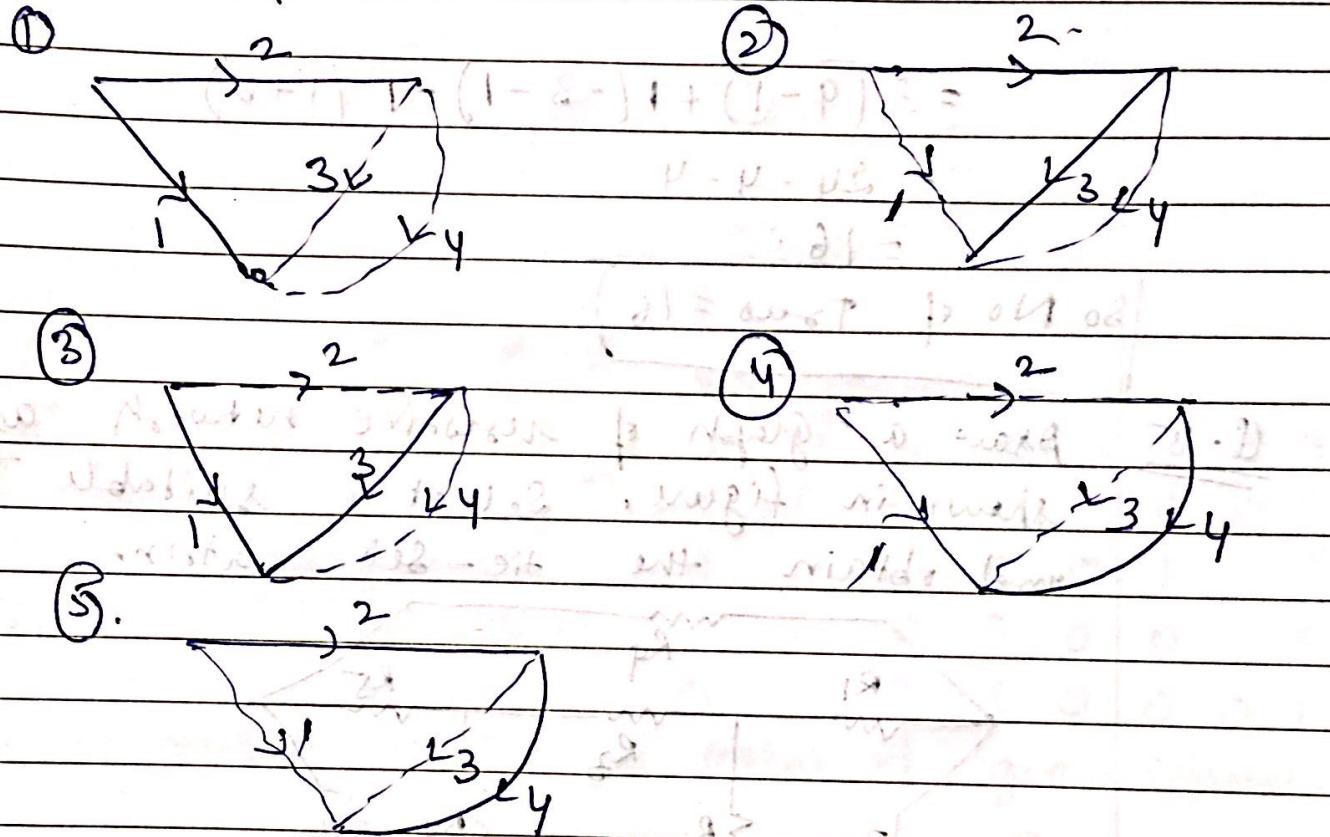

Q.24 A reduced Incidence matrix of a graph is given by:-

$$[A] = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & 1 & 0 \end{bmatrix}$$

obtain the no. of possible trees.

$$\text{No. of trees} = \det[A \cdot A^T]$$

$$A \cdot A^T = \begin{bmatrix} 1 & 1 & 0 & 0 & 0 & 1 \\ 0 & -1 & 1 & -1 & 0 & 0 \\ -1 & 0 & -1 & 0 & 1 & 0 \end{bmatrix} \begin{bmatrix} 1 & 0 & -1 \\ 1 & -1 & 0 \\ 0 & 1 & -1 \\ 0 & -1 & 0 \\ 0 & 0 & 1 \end{bmatrix} = \begin{bmatrix} 8 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{bmatrix}$$

$$\det [A \cdot A^T] = 2 \begin{vmatrix} 3 & -1 & -1 \\ -1 & 3 & -1 \\ -1 & -1 & 3 \end{vmatrix}$$


$$= 3(9-1) + 1(-3-1) - 1(1+3)$$

$$= 24 - 4 - 4$$

$$= 16$$

So, No. of Trees = 16.

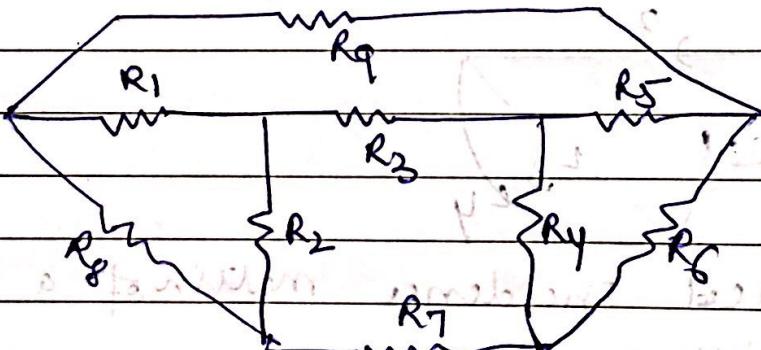Q. 25 Draw a graph of resistive network as shown in figure. Select a suitable tree and obtain the tie-set matrix.



Soln

$$\begin{matrix} 1 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{matrix}$$

$$\begin{matrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{matrix}$$

Graph: $\begin{pmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 1 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 1 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 1 \end{pmatrix}$

$$n = 6$$


$$b = 9$$

$$nt = 5$$

$$nl = 4$$

DOMS


As $n_l = 4$, so No of Tie-sets = 4.

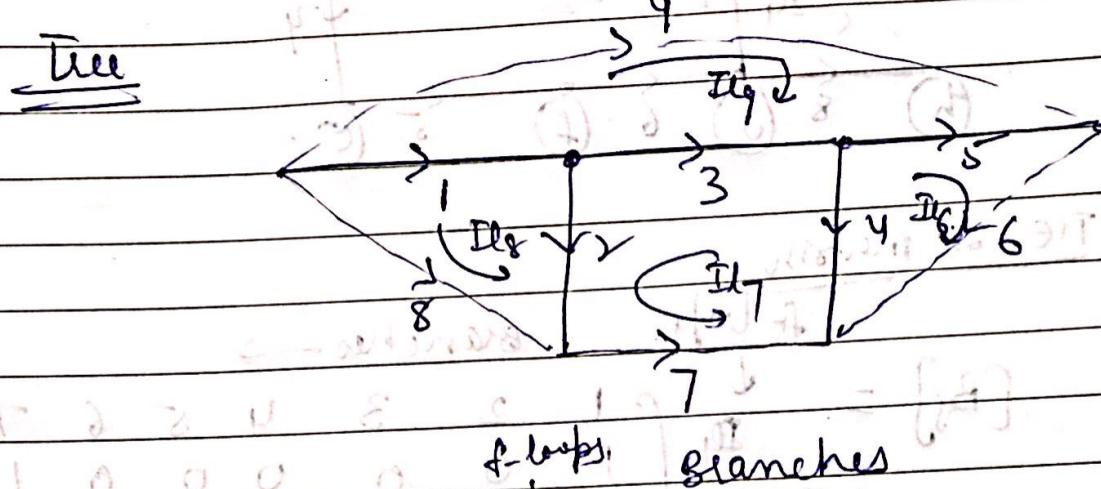


Tie-set Matrix $[B_f] =$

$$\begin{matrix}
 & 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 & 9 \\
 I_{1,6} & 0 & 0 & 0 & -1 & 1 & 1 & 0 & 0 & 0 \\
 I_{1,7} & 0 & 1 & -1 & -1 & 0 & 0 & 1 & 0 & 0 \\
 I_{1,8} & -1 & -1 & 0 & 0 & 0 & 0 & 0 & 1 & 0 \\
 I_{1,9} & -1 & 0 & -1 & 0 & -1 & 0 & 0 & 0 & 1
 \end{matrix}$$

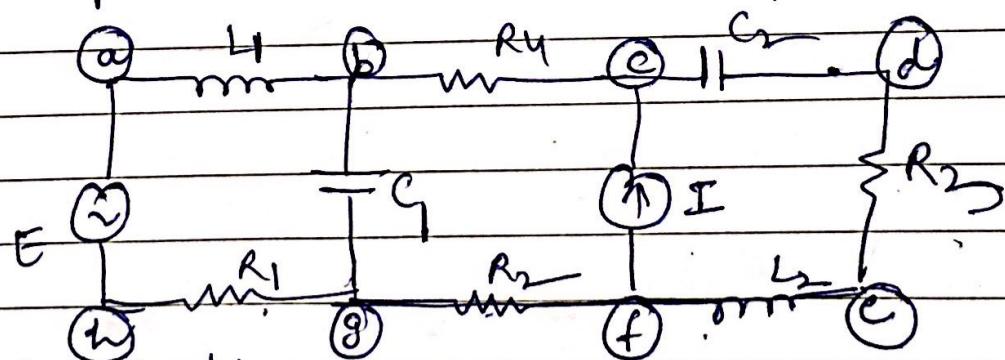Q.26 Develop the Tie-set matrix of given circuit.



Soln oriented graph:-

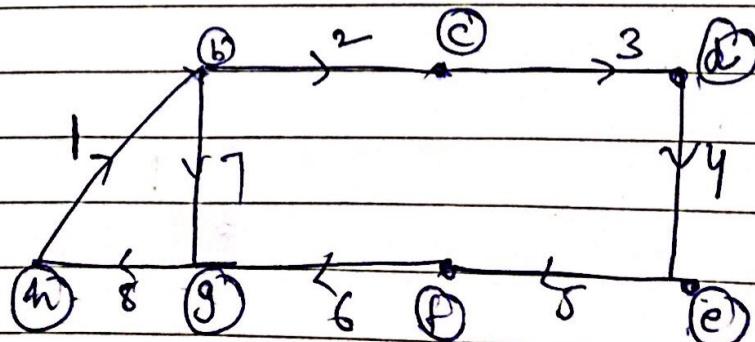


$$n = 7$$

$$b = 8$$

DOMS

$$n_t = n - 1 = 6$$

$$n_l = 8 - 6 = 2.$$

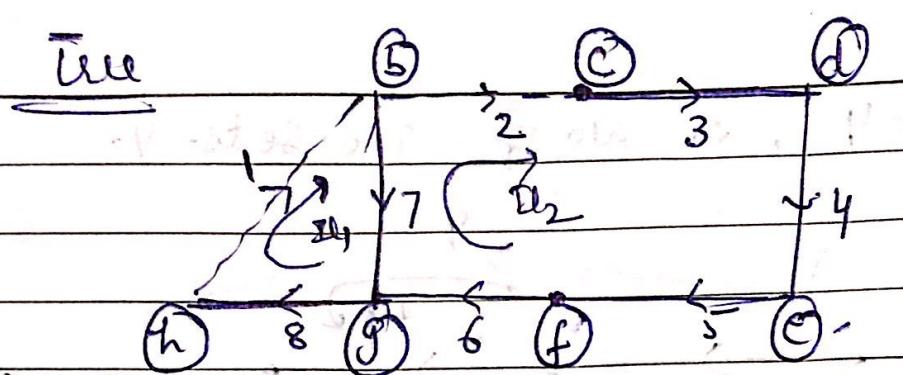

Tie-set matrix

f loops Branches →

$$[B_f] = \begin{matrix} & \downarrow \\ \text{f loops} & \end{matrix} \quad \begin{matrix} 1 & 2 & 3 & 4 & 5 & 6 & 7 & 8 \end{matrix}$$

$$= \begin{matrix} \text{Branches} \\ \downarrow \\ \text{f loops} \end{matrix} \quad \begin{bmatrix} 1 & 0 & 0 & 0 & 0 & 0 & 1 & 1 \\ 0 & 1 & 0 & 0 & 0 & 0 & -1 & 0 \end{bmatrix}$$

Ans