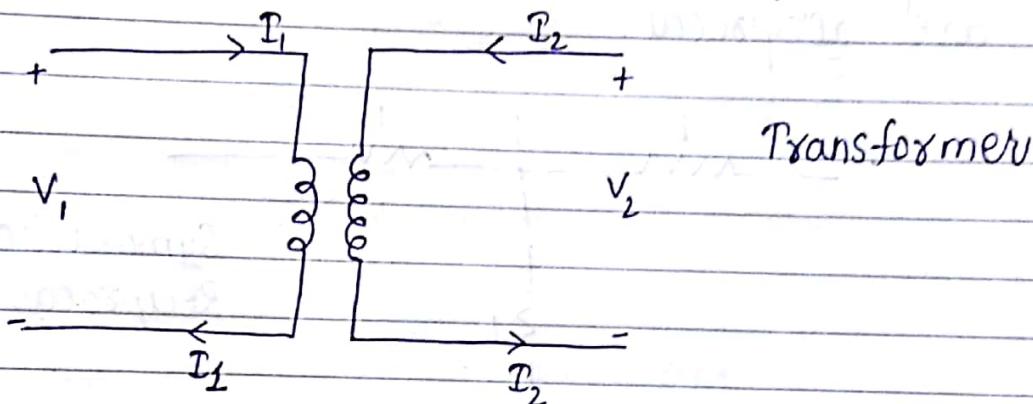


25/09/17


# Two Port Network

- ① Port - Pair of terminal from which current can enter or leave the n/w.



Any system can be modeled using 2-port n/w.

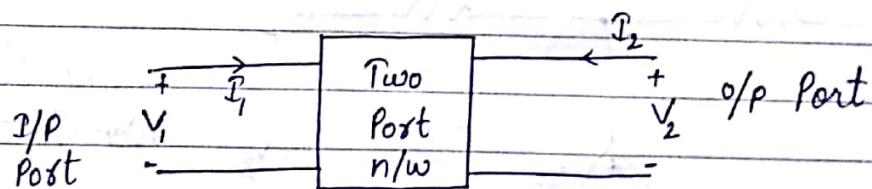I/p Port -  $V_1, I_1$   
 o/p Port -  $V_2, I_2$



$V_1, I_1, V_2, I_2$  - 6 Combinations

6 parameters - Z parameter

Y parameter

H parameter

G parameter

T (ABCD) parameter

T' parameter


→ Symmetrical N/w

A n/w is said to be symmetrical if we divide the n/w in two ports then the one should be


mirror image of other.

→ Reciprocal N/w

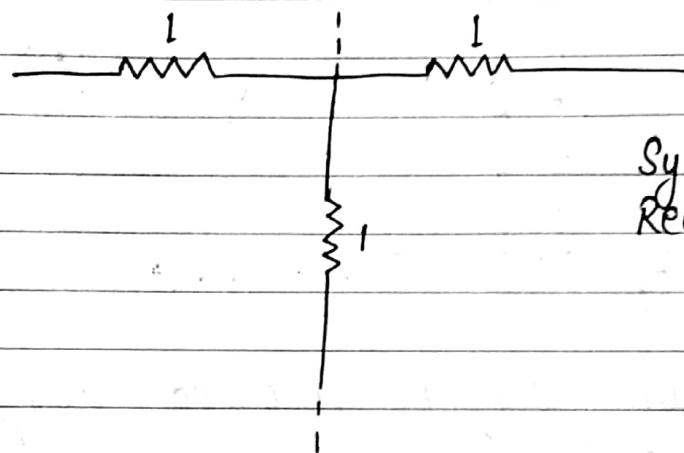A n/w is said to be reciprocal which obeys reciprocity theorem. All basic n/w's passive n/w are reciprocal.



Symmetrical  
Reciprocal

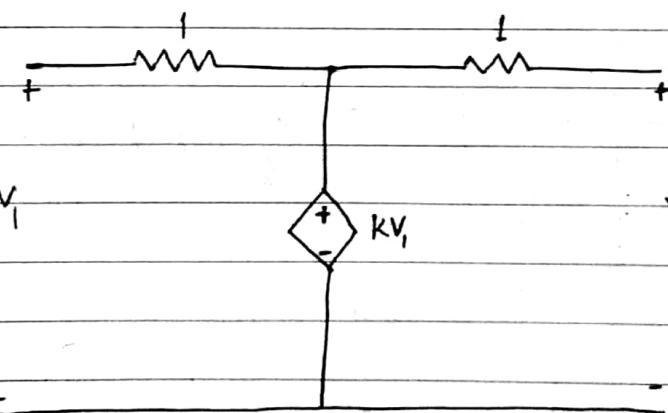

Symmetrical  
Non-Reciprocal

Z Parameter (Open ckt. parameter)

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$


$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

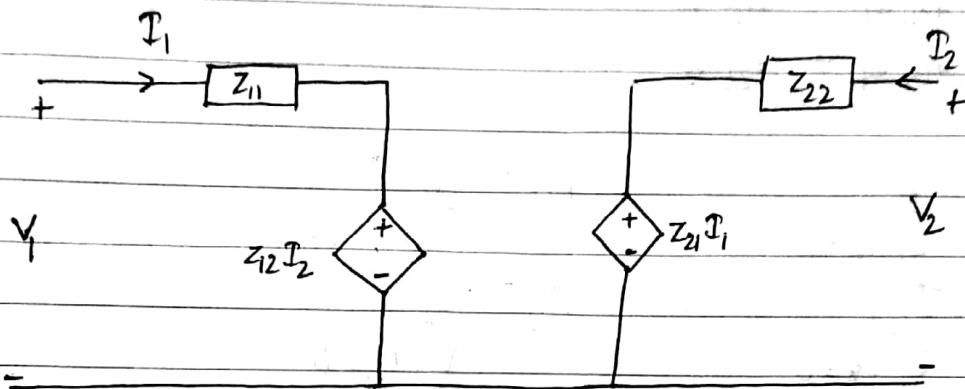Dependent  $\rightarrow V_1, V_2$   
 Independent  $\rightarrow I_1, I_2$



### Y Parameter (Short ckt parameter)

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$


$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

Dependent  $\rightarrow I_1, I_2$

Independent  $\rightarrow V_1, V_2$

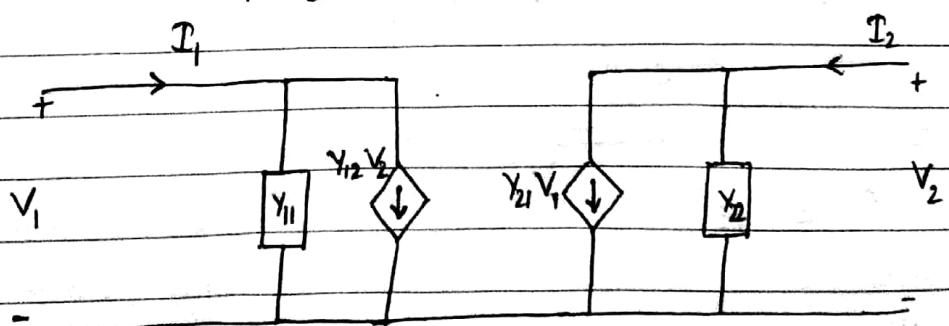

$Y_{11}, Y_{22} \rightarrow$  Admittance

## H parameter (Hybrid Parameter)

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

O/P Post - short circuit

I/P Post - open circuit

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}$$


$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

$\frac{V_1}{I_1}$  - Impedance  
 $\frac{I_2}{V_2}$  - Admittance

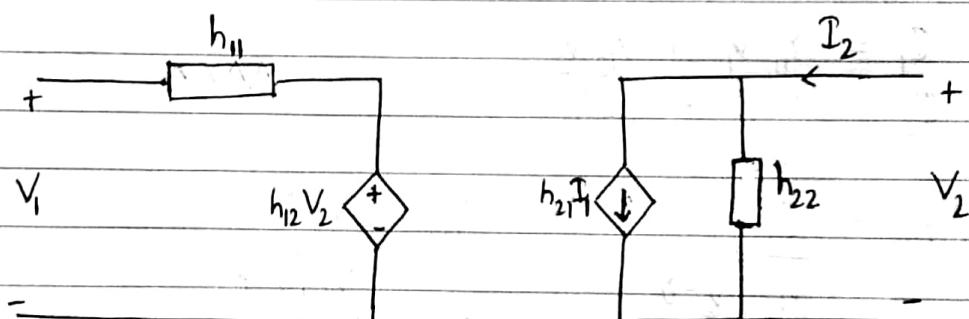$h_{21}$  - Forward current gain  
 $h_{12}$  - Reverse voltage gain



H-parameter is used to model the BJT

Dependent  $\rightarrow V_1, I_2$

Independent  $\rightarrow V_2, I_1$

## G parameter


$$G = H^{-1}$$

O/P Post  $\rightarrow$  Open circuit

I/P Post  $\rightarrow$  short circuit

$$I_1 = g_{11} V_1 + g_{12} I_2$$


$$V_2 = g_{21} V_1 + g_{22} I_2$$

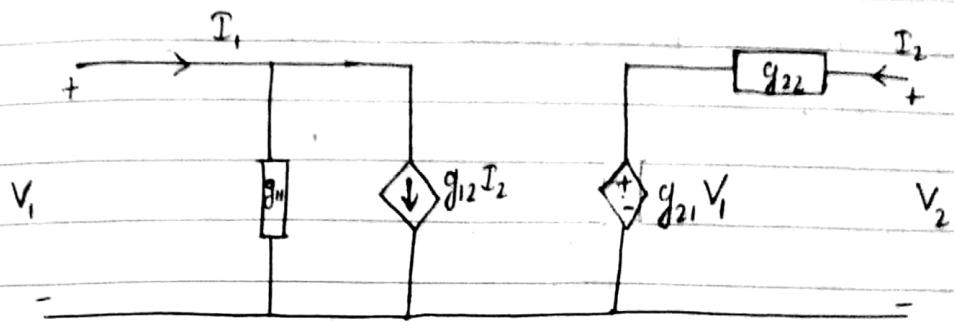

### T Parameter (ABCD)

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

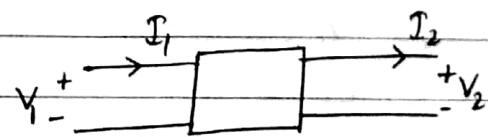


### T' Parameter

$$T' = [T]^{-1}$$

$$V_2 = A'V_1 - B'I_1$$

$$I_2 = C'V_1 - D'I_1$$

Q: Find the Z parameter

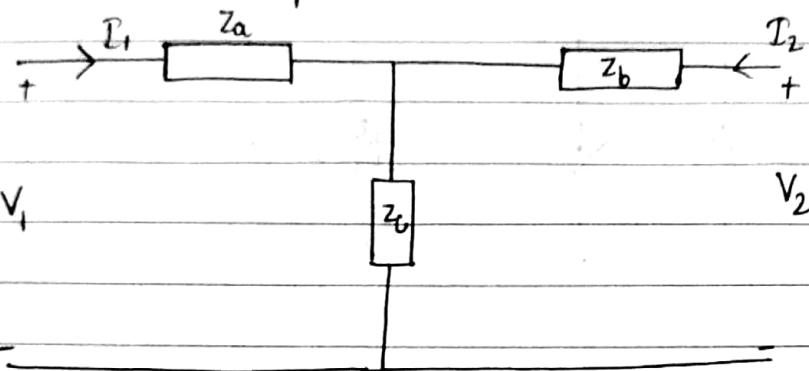

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

Apply KVL to top loop

$$V_1 = Z_a I_1 + Z_c I_1$$

$$\frac{V_1}{I_1} = Z_a + Z_c$$

$$\Rightarrow Z_{11} = Z_a + Z_c$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = Z_c$$

Similarly

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

Apply KVL

$$V_2 = Z_b I_2 + Z_c I_2$$

$$\frac{V_2}{I_2} = Z_b + Z_c$$

$$\Rightarrow Z_{22} = Z_b + Z_c$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = Z_c$$

Method 2:

Apply KVL

$$\begin{aligned} V_1 &= Z_a I_1 + Z_c (I_1 + I_2) \\ &= (Z_a + Z_c) I_1 + Z_c I_2 \end{aligned}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$\text{Compare: } Z_{11} = Z_a + Z_c$$

$$Z_{12} = Z_c$$

Similarly


$$\Rightarrow V_2 = Z_b I_2 + Z_c (I_1 + I_2) \quad V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$= Z_c I_1 + (Z_b + Z_c) I_2$$

Compare :  $Z_{21} = Z_c$


$$Z_{22} = Z_b + Z_c$$

26/09/17

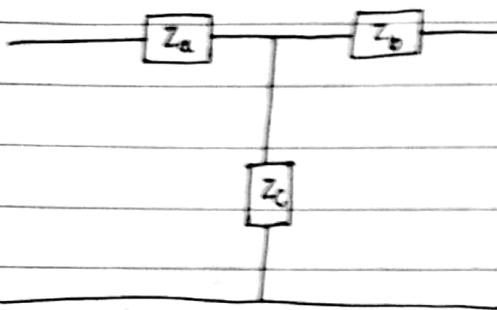

$$[Z] = \begin{bmatrix} Z_a + Z_c & Z_c \\ Z_c & Z_b + Z_c \end{bmatrix}$$

Very Important

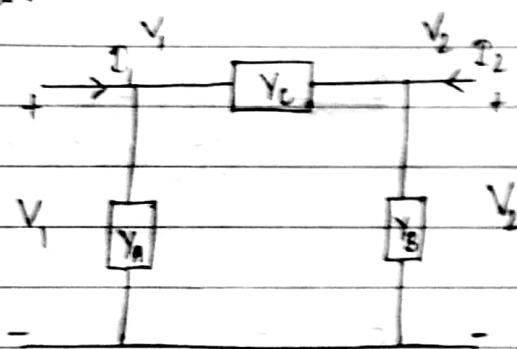

$$V_1 Y_c + Y_c (V_1 - V_2) = I_1 I_1$$

$$(Y_b + Y_c) V_1 - Y_c V_2 = I_1 - ①$$

At  $V_2$

$$V_2 Y_b + Y_c (V_2 - V_1) = I_2$$

$$(Y_b + Y_c) V_2 - Y_c V_1 = I_2 - ②$$

Compare


$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

$$\Rightarrow Y_{11} = Y_b + Y_c \quad Y_{21} = -Y_c$$

$$Y_{12} = -Y_c \quad Y_{22} = Y_b + Y_c$$

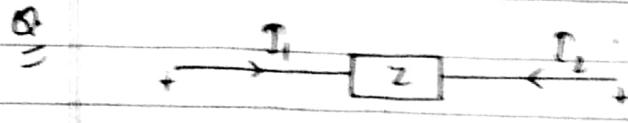
$$[Y] = \begin{bmatrix} Y_b + Y_c & -Y_c \\ -Y_c & Y_b + Y_c \end{bmatrix}$$



$$Y = \frac{1}{Z}$$

$V_1$        $V_2$

Find Y parameter

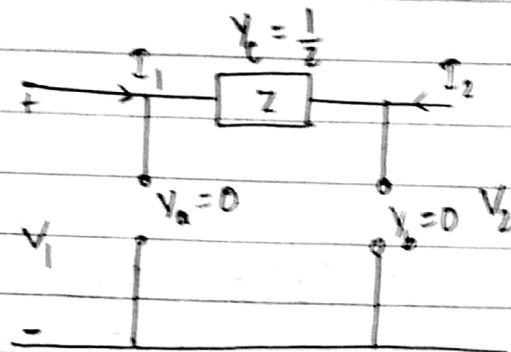

$$Y_{11} = \frac{1}{Z}$$

$$Y_{12} = -\frac{1}{Z}$$

$$Y_{21} = -\frac{1}{Z}$$

$$Y_{22} = \frac{1}{Z}$$


$$[Y] = \begin{bmatrix} k_z & -k_z \\ -k_z & k_z \end{bmatrix}$$

~~Determinate~~  $|Y| = 0$

$$[Z] = [Y]^{-1}$$

[Z] doesn't exist
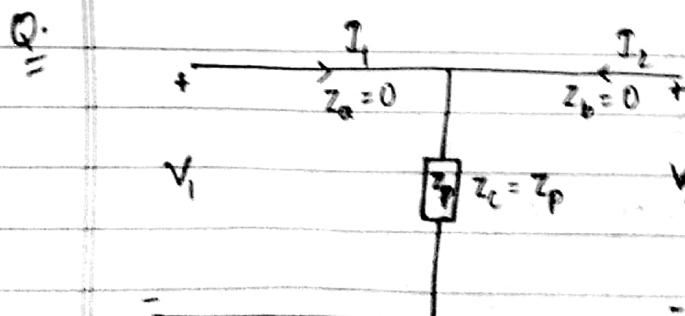
$$\begin{bmatrix} a & b \\ c & d \end{bmatrix}^{-1} = \frac{1}{ad - bc} \begin{bmatrix} d & -b \\ -c & a \end{bmatrix}$$





Find Z and Y parameter

$$Z_{11} = Z_p \quad Z_{12} = Z_p \quad Z_{21} = Z_p \quad Z_{22} = Z_p$$

$$[Z] = \begin{bmatrix} Z_p & Z_p \\ Z_p & Z_p \end{bmatrix}$$

$|Z| = 0 \Rightarrow$  Y parameter of this ckt does not exist

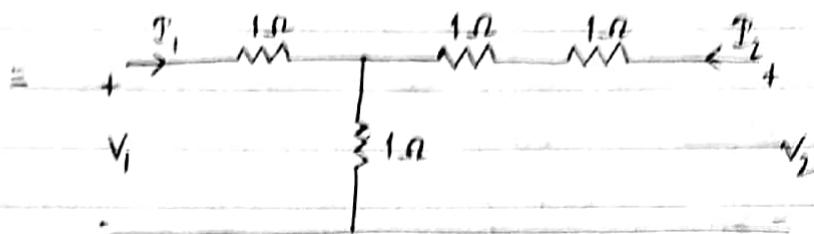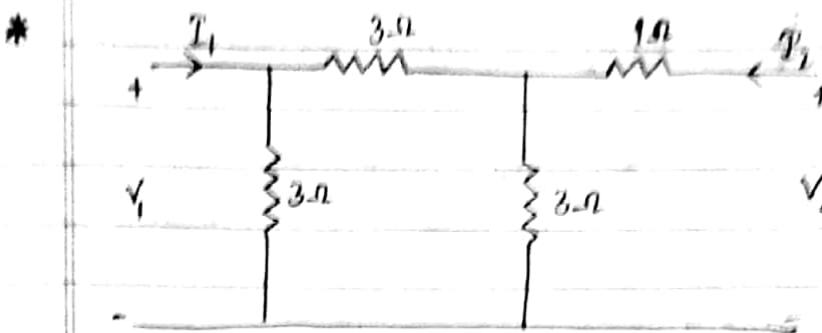


$$Z_a = 1 \quad Z_b = 2 \quad Z_c = 1$$

$$Z_{11} = 2 \quad Z_{12} = 1 \quad Z_{21} = 1 \quad Z_{22} = 3$$

$$[Z] = \begin{bmatrix} 2 & 1 \\ 1 & 3 \end{bmatrix} \quad |Z| = 5$$

$$[Y] = \frac{1}{5} \begin{bmatrix} 3 & -1 \\ -1 & 2 \end{bmatrix}$$
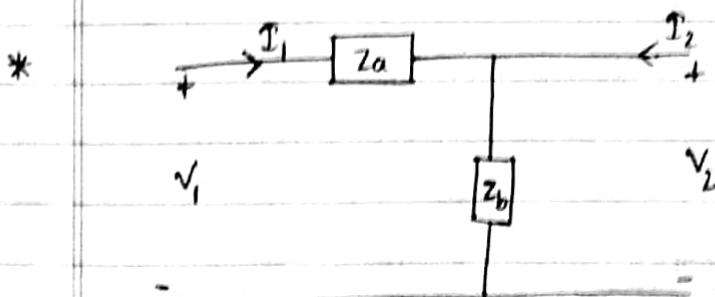
$$Y_{11} = \frac{3}{5} \quad Y_{12} = -\frac{1}{5} \quad Y_{21} = \frac{1}{5} \quad Y_{22} = \frac{2}{5}$$



Find ABCD parameters

$$V_1 = AV_2 + BI_2$$

$$VI_1 = CV_2 + DI_2$$

$$\begin{aligned} V_1 &= Z_a I_1 + Z_b (I_1 + I_2) \\ &= (Z_a + Z_b) I_1 + Z_b I_2 \end{aligned}$$

$$V_2 = (I_1 + I_2) Z_b$$

$$V_2 = I_1 Z_b + I_2 Z_b$$

$$I_1 = V_2 - I_2 \quad \text{---(1)}$$

$$V_1 = (Z_a + Z_b)(V_2 - I_2) + Z_b I_2$$

$$= \frac{Z_a V_2}{Z_b} - Z_a I_2 + V_2 - Z_b I_2 + Z_b I_2$$

$$V_1 = \left( \frac{Z_a + Z_b}{Z_b} \right) V_2 - Z_a I_2 \quad \text{--- (1)}$$

$$\Rightarrow A = \frac{Z_a + Z_b}{Z_b} \quad B = Z_a$$

From (2)

$$C = \frac{1}{Z_b} \quad D = 1$$

$$T = \begin{bmatrix} \frac{Z_a + Z_b}{Z_b} & Z_a \\ \frac{1}{Z_b} & 1 \end{bmatrix}$$

### Condition for Symmetry

A two port n/w is said to be symmetrical if the ports can be interchanged w/o changing the port voltage and current.

$$\rightarrow Z_{11} = Z_{22}$$

$$\rightarrow Y_{11} = Y_{22}$$

$$\rightarrow A = D \quad \rightarrow A' = D'$$

$$\rightarrow h_{11} h_{22} - h_{12} h_{21} = 1$$

$$\rightarrow g_{11} g_{22} - g_{12} g_{21} = 1$$

### Condition for reciprocal

A two port n/w is said to be reciprocal if the ratio of excitation to the response is invariant and to <sup>an</sup> <sub>inter</sub> change of position of excitation and response in the n/w.

N/w's containing passive elements are generally reciprocal.

$$Z_{12} = Z_{21}$$

$$Y_{12} = Y_{21}$$

$$AD - BC = 1$$


$$A'D' - B'C' = 1$$

$$h_{12} = -h_{21}$$

$$h_{12} = -g_{21}$$

## Interconnection of two port n/w

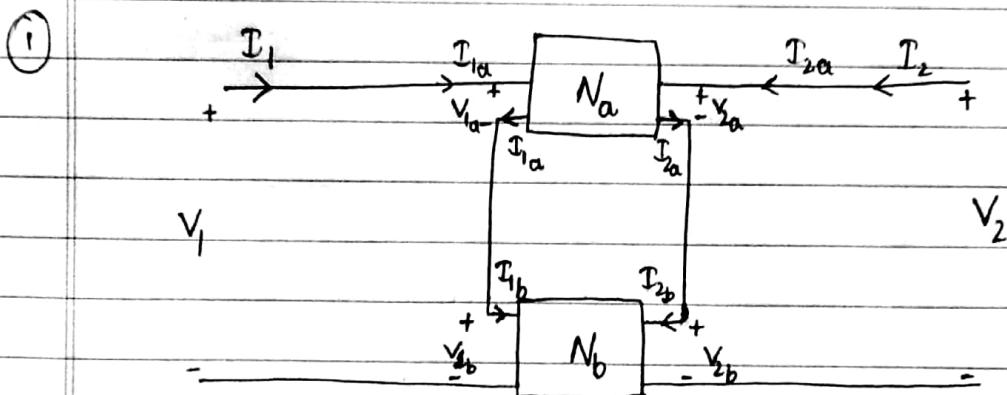- (1) Series Connection
- (2) Parallel Connection
- (3) Cascade Connection
- (4) Series - Parallel connection



$$I_1 = I_{1a} = I_{1b}$$

$$I_2 = I_{2a} = I_{2b}$$

$$V_1 = V_{1a} + V_{1b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$\begin{cases} V_{1a} = Z_{11a} I_{1a} + Z_{12a} I_{2a} \\ V_{2a} = Z_{21a} I_{1a} + Z_{22a} I_{2a} \end{cases}$$

$$\begin{cases} V_{1b} = Z_{11b} I_{1b} + Z_{12b} I_{2b} \\ V_{2b} = Z_{21b} I_{1b} + Z_{22b} I_{2b} \end{cases}$$

$$\begin{aligned} V_1 &= V_{1a} + V_{1b} \\ &= Z_{11a} I_{1a} + Z_{12a} I_{2a} + Z_{11b} I_{1b} + Z_{12b} I_{2b} \end{aligned}$$

$$= (Z_{11a} + Z_{11b}) I_1 + (Z_{12a} + Z_{12b}) I_2 - \textcircled{A}$$

$$\begin{aligned} V_2 &= V_{2a} + V_{2b} \\ &= (Z_{21a} + Z_{21b}) I_1 + (Z_{22a} + Z_{22b}) I_2 - \textcircled{B} \end{aligned}$$

$$Z_{11} = Z_{11a} + Z_{11b}$$

$$Z_{21} = Z_{21a} + Z_{21b}$$

$$Z_{12} = Z_{12a} + Z_{12b}$$

$$Z_{22} = Z_{22a} + Z_{22b}$$

$$[Z] = [Z_a] + [Z_b]$$

12/10/17

## Network Analysis Synthesis

- Synthesise a n/w from a given n/w fn.
- To realize the n/w as a physical passive n/w two important considerations are:
  - i) Possibility
  - ii) Stability
- ii) By possibility means the response of the n/w is zero for  $t < 0$ .
- ii) For a stability three cond's must be satisfied:
  - a)  $T(s)$  cannot have poles in right half of s plane.
  - b)  $T(s)$  cannot have multiple poles in imaginary axis.
  - c) The degree of numerator of  $T(s)$  cannot exceed by more than unity  
denominator

## Hurwitz Polynomial

Hurwitz polynomial is a denominator polynomial of n/w fn satisfying certain cond's. A polynomial  $P(s)$  is said to be Hurwitz if:

- i)  $P(s)$  is real when  $s$  is real
- ii) The roots of  $P(s)$  have real parts which are 0 or -ve.

## Properties of Hurwitz

As a result of above two cond's  $P(s)$  have

following properties

- i) All coefficients must be +ve & b/w highest order term in as and lowest order term, none of the coefficient may be 0 unless the polynomial is even or odd.
- ii) Both odd & even part of  $p(s)$  have roots on  $\Im(\omega)$  axis only.
- iii) Even part of  $p(s)$  as  $M(s)$  and odd part of  $p(s)$  as  $N(s)$   

$$P(s) = M(s) + N(s)$$
- iv) If  $p(s)$  is either even or odd, all of its roots are on  $\Im(\omega)$  axis expansion
- v) The continued fraction of the — ratio  

$$\psi(s) = \frac{M(s)}{N(s)} \text{ or } \frac{N(s)}{M(s)}$$
 deals all +ve coefficient terms
- vi) If  $P(s)$  is Hurwitz polynomial and  $w(s)$  is multiplicative factor the  $P_1(s) = P(s) w(s)$  is also Hurwitz polynomial if  $w(s)$  is also Hurwitz.
- vii) In the case of the polynomial is either only even or only odd it is not possible to obtain continued fraction expansion then the polynomial  $P(s)$  is Hurwitz if the ratio of  $P(s)$  and its derivative gives continued fraction expression.

Q:

$$P(s) = s^4 + s^3 + 5s^2 + 3s + 4$$

$$M(s) = s^4 + 5s^2 + 4$$

$$N(s) = s^3 + 3s$$

$$\psi(s) = \frac{M(s)}{N(s)} = \frac{s^4 + 5s^2 + 4}{s^3 + 3s}$$

$$\begin{array}{r} s^3 + 3s \\ \times s^4 + 5s^2 + 4 \\ \hline s^4 + 3s^2 \end{array}$$

$$\begin{array}{r} 2s^2 + 4 \\ \times s^3 + 3s \\ \hline s^3 + 2s \end{array}$$

$$\begin{array}{r} s \\ \times 2s^2 + 4 \\ \hline -2s^2 \end{array}$$

$$\begin{array}{r} 4 \\ \times s \\ \hline -s \end{array}$$

0

It is Hurwitz since all the coefficients are +ve.

Q.  
 Sol:-

$$\begin{aligned} P(s) &= s^4 + s^3 + 2s^2 + 4s + 1 \\ M(s) &= s^4 + 2s^2 + 1 \\ N(s) &= s^3 + 4s \\ \psi(s) &= \frac{M(s)}{N(s)} \end{aligned}$$

$$\begin{array}{r} s^3 + 4s \\ \times s^4 + 2s^2 + 1 \\ \hline s^4 + 4s^2 \end{array}$$

$$\begin{array}{r} -2s^2 + 1 \\ \times s^3 + 4s \\ \hline s^3 - \frac{1}{2}s \end{array}$$

$$\frac{5}{2}s$$

Since the quotient is -ve it is not Hurwitz

Q.  $P(s) = s^3 + 2s^2 + 3s + 6$

$$M(s) = 2s^2 + 6$$

$$N(s) = s^3 + 3s$$

$$\psi(s) = \frac{N(s)}{M(s)}$$

$$\begin{array}{r} 2s^2 + 6 \\ \hline s^3 + 3s \end{array}$$

X

Hurwitz

$$w(s) = s^3 + 3s$$

$$w'(s) = 3s^2 + 3$$

$$\begin{array}{r} 3s^2 + 3 \\ \hline s^3 + s \end{array}$$

$$\begin{array}{r} 3s^2 + 3 \\ \hline 2s \end{array}$$

$\frac{3s}{2}$

$$\begin{array}{r} 2s \\ \hline 2s \end{array}$$

$\frac{2}{3}s$

X

Hurwitz ✓

## Positive real Functions

These fns are imp. b'coz they represent physically reliable passive driving pt. immitance. A fn  $T(s) = \frac{N(s)}{D(s)}$  is  $\neq$  +ve real if the

following cond's are satisfied :

- i)  $T(s)$  is real for  $s$  real
- ii)  $D(s)$  is Hurwitz polynomial.


The necessary & sufficient cond<sup>n</sup> for fn  $T(s)$  to be +ve, real if following are satisfied:

- Denominator of  $T(s)$  should be Hurwitz polynomial. This cond<sup>n</sup> is checked only when the poles of  $T(s)$  are on  $J(w)$  axis otherwise not.
- $T(s)$  may only have simple poles on  $J(w)$  axis with real & +ve residue.
- Real part of  $T(jw) \geq 0$  for all  $w$


### Synthesis

- Synthesizing the one port n/w with two kind of elements LC, RC, RL
- There are various method for synthesizing one port n/w. We will focus on four basic form

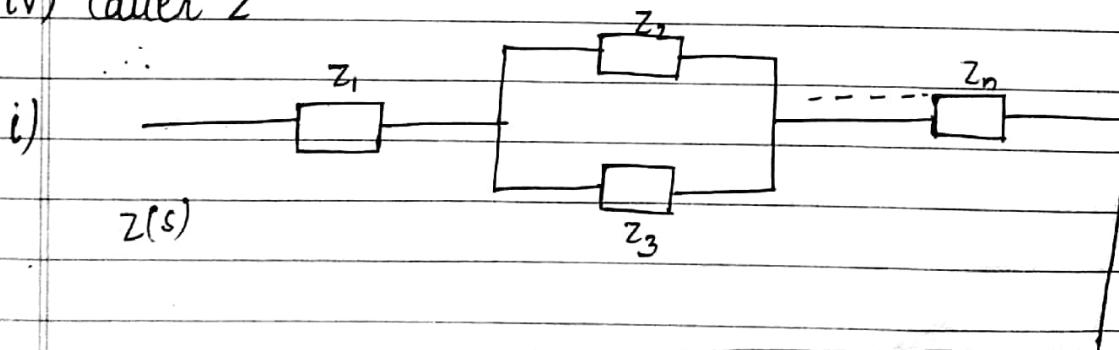
- i) Foster 1 ~~work~~ (Foster series form)
- ii) Foster 2 (Foster parallel form)
- iii) Cauer 1
- iv) Cauer 2




2.)

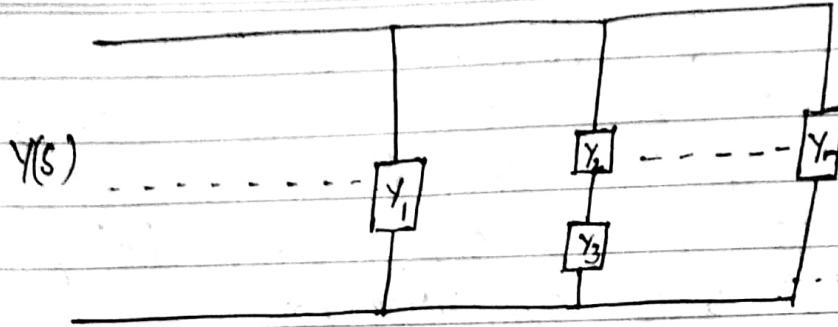

3.)

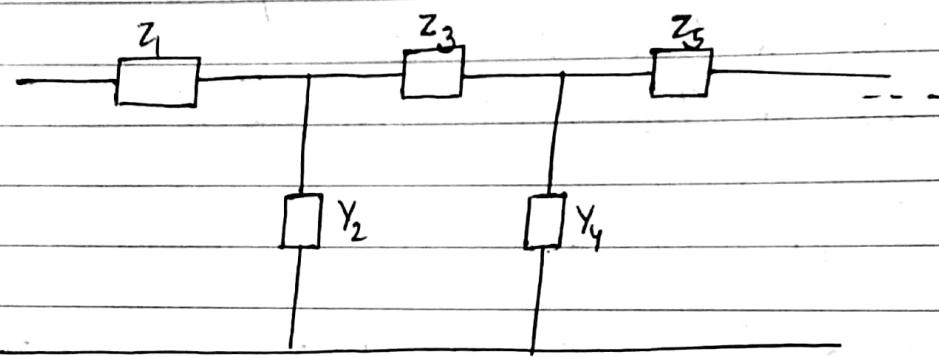

4.)

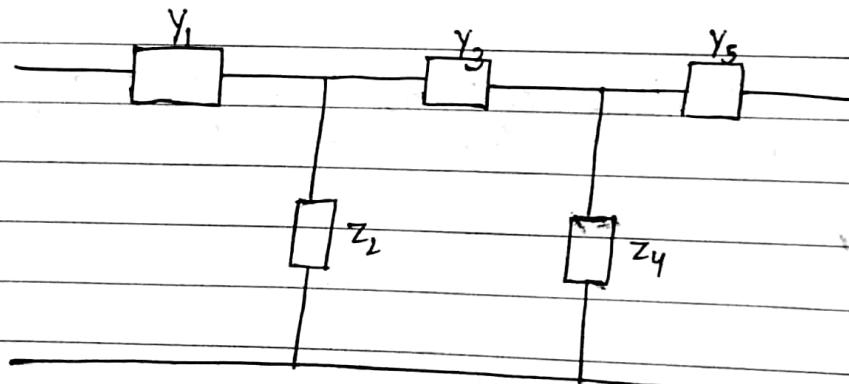

24/10/17

Page No.  
Date

### Cauer 1

$$Z(s) = \frac{2(s^2+1)(s^2+9)}{s(s^2+4)} = \frac{2s^4 + 20s^2 + 18}{s^3 + 4s}$$


$$s^3 + 4s \Big) 2s^4 + 20s^2 + 18 \quad \begin{matrix} L=2 \\ 2s \leftarrow z_1 \end{matrix}$$

$$\frac{2s^4 + 8s^2}{12s^2 + 18} \Big) s^3 + 4s \quad \begin{matrix} 12s \leftarrow z_2 \\ 3s^3 + \frac{3}{2}s \end{matrix}$$

$$\frac{5s}{2} \Big) 12s^2 + 18 \quad \begin{matrix} 24s \leftarrow z_3 \\ 12s^2 \end{matrix}$$

$$18 \Big) \frac{5s}{2} \quad \begin{matrix} \frac{5s}{36} \leftarrow z_4 \end{matrix}$$
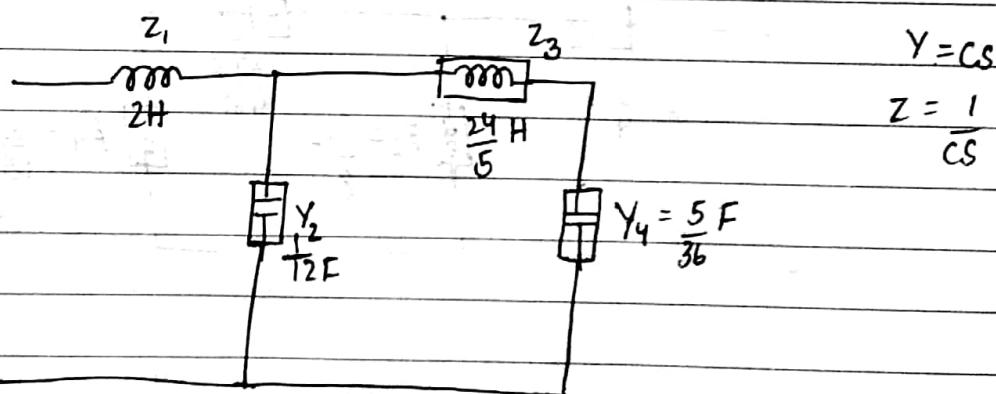
$$\frac{5s}{2}$$
  
$$\underline{\times}$$



### Cauer 2

$$Z(s) = \frac{18 + 20s^2 + 2s^4}{4s + s^3}$$

$$4s + s^3) \quad 18 + 20s^2 + 2s^4 \left( \frac{9}{2s} \right)^{-2}$$

$$18 + \frac{9}{2}s^2$$

$$\frac{31s^2 + 2s^4}{2} \quad 4s + s^3 \left( \frac{8}{31s} \right)^{-2}$$

$$4s + \frac{16}{31}s^3$$


$$\frac{15s^3}{31} \quad \frac{31s^2 + 2s^4}{2} \left( \frac{961}{30s} \right)^{-2}$$

$$\frac{31s^2}{2}$$

$$2s^4) \quad \frac{15s^3}{31} \left( \frac{15}{62s} \right)^{-2}$$

$$\frac{15s^3}{31}$$

X

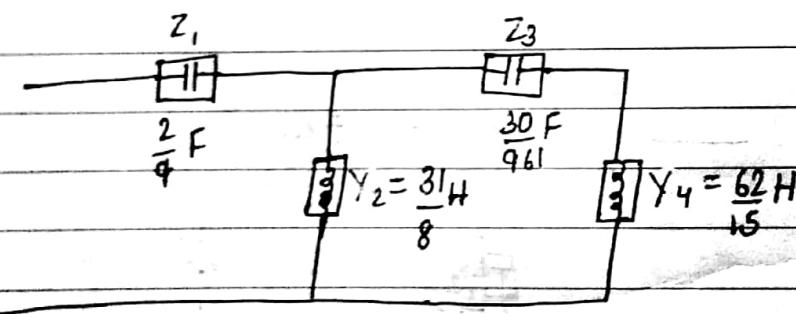

RC Impedance or RL admittance fn  
poles

The false & zeroes lie on -ve <sup>real</sup> zero axis including origin. of complex s plane.

The false & zeroes alternate along the <sup>-ve</sup> real axis

The residue of false of  $Z_{RC}$  or  $Y_{RL}$  must be real & +ve

The singularity nearest to  $-\infty$  must be zero,  
i.e. fn of  $z_{RC}$  or  $y_{RL}$  tends to 0 with  $s$  tends to  $\infty$ .

The singularity nearest to origin must be a pole

RL impedance or RC admittance fn

The poles & zeroes lie on -ve real axis including origin of complex s plane.

The poles & zeroes alternate along the -ve real axis.

The  $\infty$  residue of the pole of  $\neq z_{RC}$  or  $z_{RL}$  must be real & +ve.

The singularity nearest to origin must be zero  
i.e. the fn  $z_{RL}$  or  $y_{RC}$  tends to 0 when  $s \rightarrow 0$ .

The singularity nearest to  $-\infty$  must be a pole  
i.e. fn  $z_{RL}$  or  $y_{RC}$  tends to  $\infty$  when  $s \rightarrow -\infty$

$$\begin{array}{c|c} z_{RL} & j\omega \\ \hline y_{RC} & \\ \hline \times \times 0 & s \end{array} \quad \begin{array}{c|c} z_{RC} & \\ \hline y_{RL} & \\ \hline -0 \times 0 \times & \end{array}$$

$$Z(s) = (s+1)(s+4)$$

$$s(s+2)(s+5)$$

Poles - 0, -2, -5

Origin zeroes -1, -4

$$\begin{array}{l} z_{RC} \\ y_{RL} \end{array}$$

HAPPY HALLOWEEN!



Page No.  
Date

$$(1) \quad Z(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$$

$Z_{RC}$   
 $Y_{RC}$

~~30/10/17~~

$$(1) \quad Z(s) = \frac{s(s+2)(s+5)}{(s+1)(s+4)}$$

Solve

Foster 1


Foster 2

Sol<sup>1</sup>-

$$P \Rightarrow -1, -4$$

$$\text{zeroes} \Rightarrow 0, -2, -5$$

jw

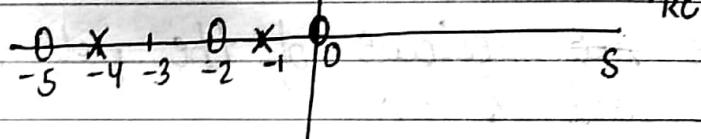

$$\begin{aligned} Z(s) &= \frac{(s+2)(s+1)(s+4) - 4(s+2)}{(s+1)(s+4)} \\ &= s+2 - \frac{4}{(s+1)(s+4)} \\ &= s+2 - \frac{4}{3(s+1)} - \frac{8}{3(s+4)} \end{aligned}$$


$$\frac{Z(s)}{s} = 1 + \frac{4}{s(s+1)} + \frac{8}{3(s+4)}$$

$$\frac{Z(s)}{s} = 1 + \frac{\frac{4}{3}}{s+1} + \frac{\frac{8}{3}}{s+4}$$

$$Z(s) = s + \frac{\frac{4}{3}s}{s+1} + \frac{\frac{8}{3}s}{s+4}$$

$$\frac{R \times Ls}{R+Ls} = \frac{RLs}{Ls+R} = \frac{RLs}{L(s+R)} = \frac{RLs}{s+\frac{R}{L}}$$

Date:

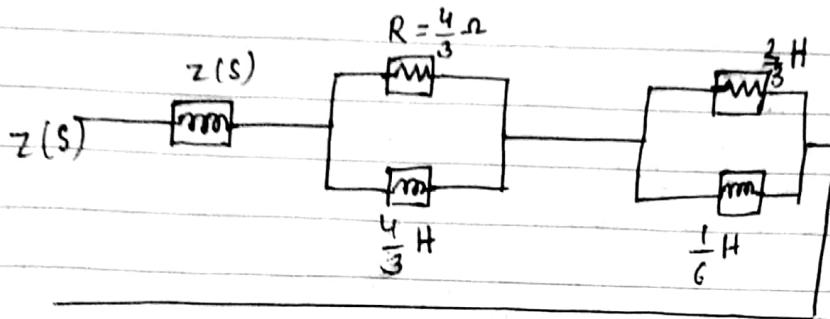

~~31/10/17~~

$$Z(s) = \frac{(s+1)(s+4)}{s(s+2)(s+5)}$$

Poles = 0, -2, -5

Zeros = -1, -4


$Z_{RC}$

$Y_{RL}$

Foster 1

$$Z(s) = \frac{2/5}{s} + \frac{1/3}{s+2} + \frac{4/15}{s+5}$$

$$\frac{\frac{1}{CS} \times R}{\frac{1}{CS} + R}$$

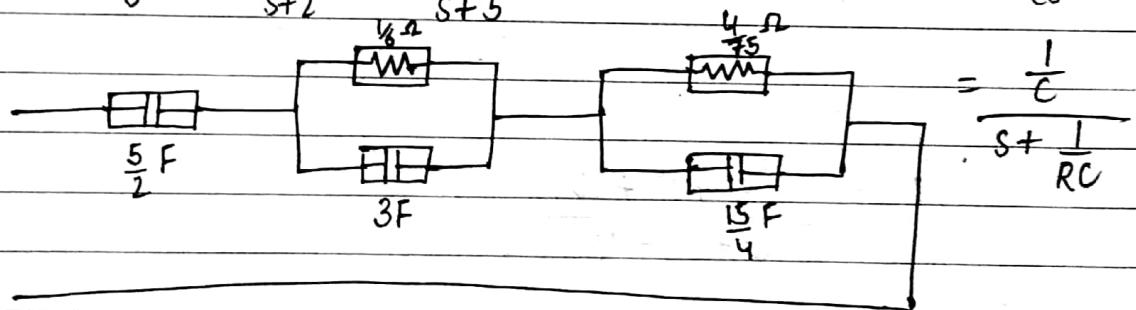

Foster 2

$$Y(s) = \frac{1}{Z(s)} = \frac{s(s+2)(s+5)}{(s+4)(s+1)}$$

Poles = -4, -1

Zeros = 0, -2, -5


$$= \frac{s(s+2)(s+5)}{(s+1)(s+4)}$$

$Z_{RL}$

$Y_{RC}$

$$Y(s) = s + \frac{4/3 s}{s+1} + \frac{2/3 s}{s+4}$$
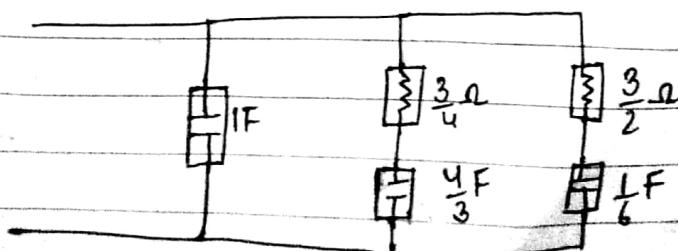
$$\frac{Rs}{s+R} \times \frac{\frac{1}{s}}{s+\frac{1}{RC}}$$



$$\frac{CS}{RCST+1} \quad RF \frac{fS}{(S+k_C)} \quad \frac{\frac{1}{R}G}{S+\frac{1}{RC}}$$

Page No. \_\_\_\_\_  
Date \_\_\_\_\_


Cauer 1

$$Z(s) = \frac{s^2 + 5s + 4}{s^3 + 7s^2 + 10s}$$

$$\begin{array}{r}
 \cancel{s^3 + 7s^2 + 10s}) \ s^2 + 5s + 4 \ (\cancel{1})^{z_1} \\
 \cancel{s^2 + 7s + 10} \\
 \hline
 -2s - 6 \ ) \ s^3 + 7s^2 + 10s \ (-\cancel{s^2})^{z_2} \\
 \cancel{s^3 + 3s^2} \\
 \hline
 4s^2 + 10s \ ) -2s - 6 \ (\frac{1}{2s})^{z_3} \\
 \hline
 -2s - 5 \\
 \hline
 -1 \ ) 4s^2 + 10s \ (-4s^2)^{z_4} \\
 4s^2 \\
 \hline
 10s \ ) -1 \ (\frac{-1}{10s})^{z_5} \\
 \hline
 X
 \end{array}$$

$$Y(s) = \frac{s^3 + 7s^2 + 10s}{s^2 + 5s + 4}$$

$$\begin{array}{r}
 s^2 + 5s + 4 \ ) \ s^3 + 7s^2 + 10s \ (\cancel{s})^{z_1} \\
 \cancel{s^3 + 5s^2 + 4s} \\
 \hline
 2s^2 + 6s \ ) \ s^2 + 5s + 4 \ (\cancel{s})^{z_2} \\
 \cancel{s^2 + 3s} \\
 \hline
 2s + 4 \ ) 2s^2 + 6s \ (\cancel{s})^{z_3} \\
 \cancel{2s^2 + 4s} \\
 \hline
 2s \ ) 2s + 4 \ (\frac{1}{2s})^{z_4} \\
 \hline
 4 \ ) 2s \ (\frac{1}{2})^{z_5} \\
 2s \\
 \hline
 X
 \end{array}$$

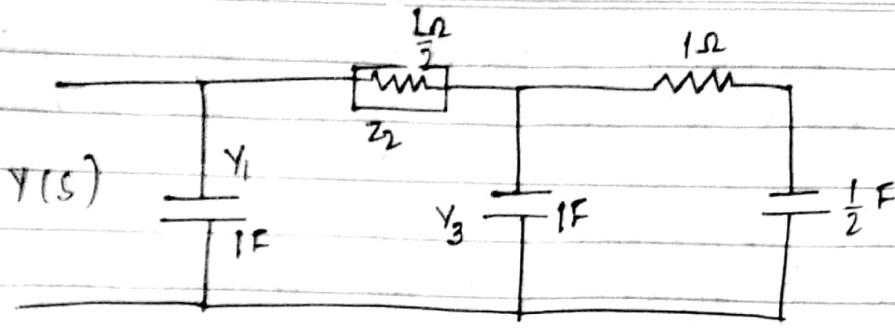

Cauer 2

$$\cancel{Z(s)} = \cancel{Y(s)} = \frac{10s + 7s^2 + s^3}{4 + 5s + s^2}$$

$$Z(s) = \frac{4 + 5s + s^2}{10s + 7s^2 + s^3}$$

$$\cancel{(4 + 5s + s^2)} \cancel{10s + 7s^2 + s^3} \cancel{\left(\frac{5s}{2}\right)}$$

$$\frac{10s + 7s^2 + s^3}{4 + 5s + s^2} \left( \frac{4}{10s} \right)^{z_1}$$

$$4 + \frac{14s}{5} + \frac{2s^2}{5}$$


$$\frac{\frac{11s}{5} + \frac{3s^2}{5}}{10s + 7s^2 + s^3} \left( \frac{50}{11} \right)^{z_2}$$

$$10s + \frac{30s^2}{11}$$

$$\frac{47s^2 + s^3}{11} \left( \frac{121}{235s} \right)^{z_3}$$

$$\frac{11s}{5} + \frac{121s^2}{235}$$
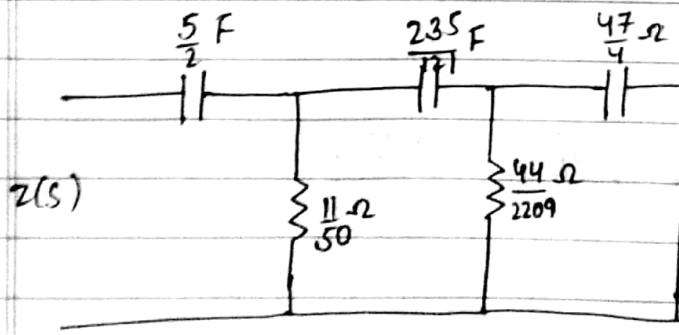
$$\frac{4s^2}{47} \left( \frac{47s^2 + s^3}{11} \right) \left( \frac{2209}{44} \right)^{z_4}$$



$$\frac{47s^2}{11} \left( \frac{4s^2}{47} \right) \left( \frac{4}{47s} \right)^{z_5}$$

$$\frac{4s^2}{47} X$$


Filter is frequency selective ckt which passes desired band of freq. & rejects the others.




Parameters of filter:

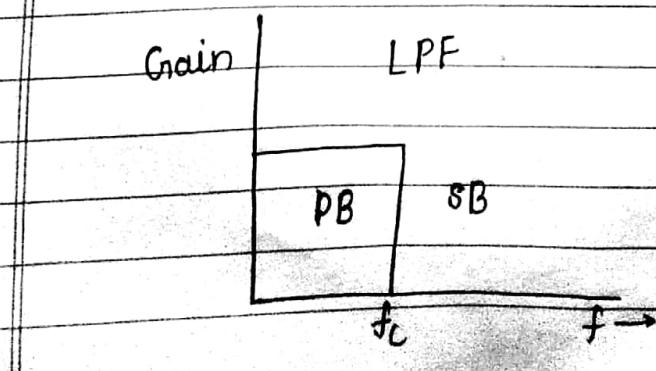- 1.) Characteristic impedance - The charac. impedance  $z_0$  or  $\omega_0$  of a filter must be chosen such that the filter may fit into a given line or with  $\omega$  between two type of equipments.
- 2.) Pass band: Band in which ideal filter have to pass all frequencies w/o reduction in magnitude are k/a pass band.
- 3.) Stop band: Band in which ideal filter have to attenuate all frequencies are k/a stop band.
- 4.) Cut off frequency  $f_c$ : The freq. which separates pass band & stop band is defined as cut off freq. of the filter.

Classification of filter


- Low pass filter
- High pass filter
- Band pass filter
- Band stop or band reject filter



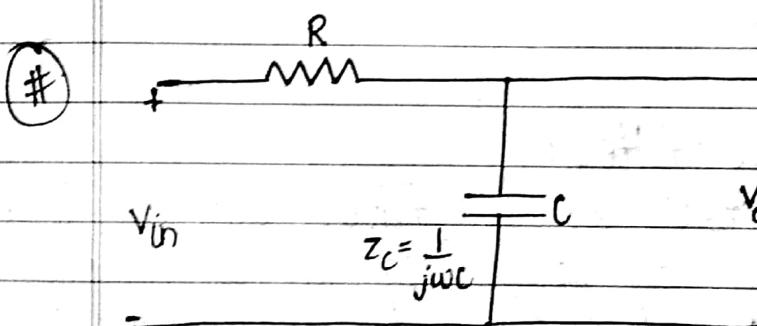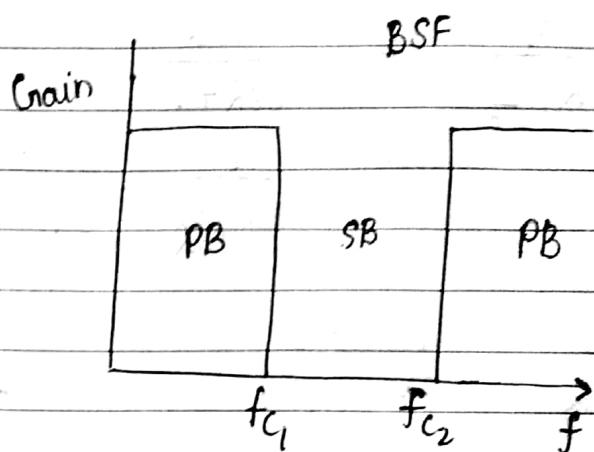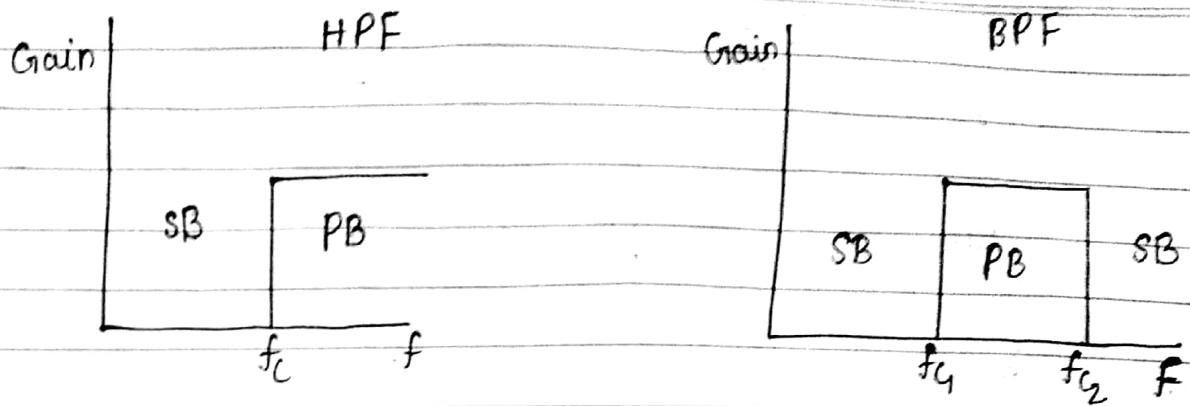

$$f = 0 \quad V_{in} \approx V_{out} \quad Z_C = \infty$$

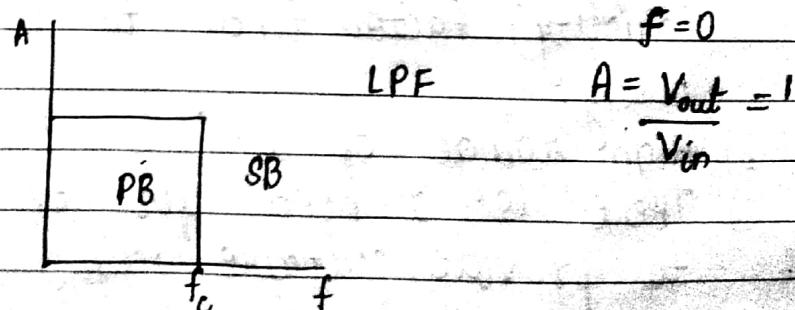
$$f = \infty \quad V_{out} = 0 \quad Z_C = 0$$



$$\text{Transfer function} = \frac{\frac{1}{Cs}}{R + \frac{1}{Cs}} = \frac{1}{RCS + 1}$$


At  $s=0$ :  $TF = 1$

At  $s=\infty$ :  $TF = 0$

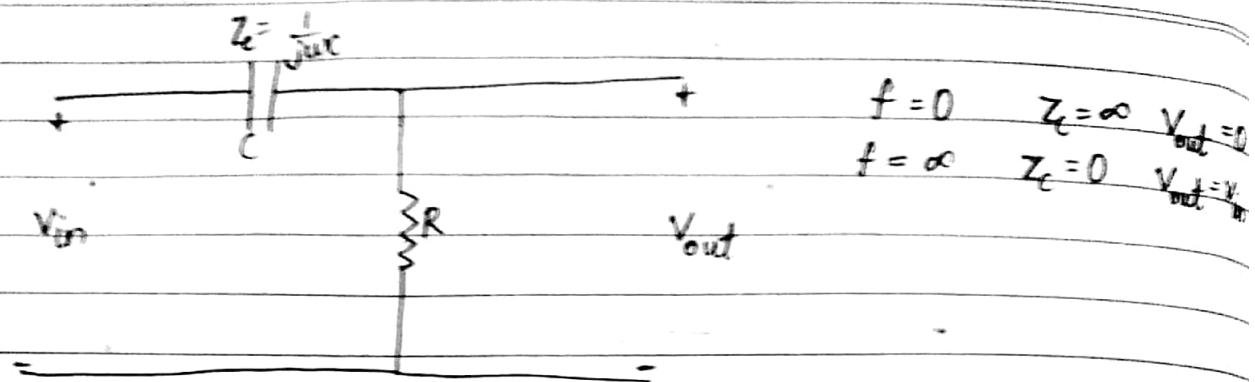

$$\begin{aligned} TF &= \frac{R}{R + \frac{1}{CS}} = \frac{CSR}{CSR + 1} \\ &= \frac{1}{1 + \frac{1}{CSR}} \end{aligned}$$
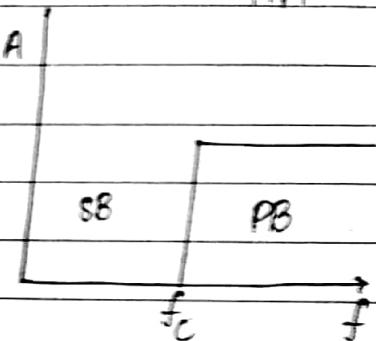
$$\begin{array}{ll} s=0 & TF = 0 \\ s=\infty & TF = 1 \end{array}$$



## \* Designing of filters

### i) Passive filter

limitation of passive filter:

- The use of inductor as a filter element is not desirable especially at low freq. as at these frequencies practical inductors of reasonable Q (Quality) factor tends to become large, bulky and costly.
- High range of Q-factor is not possible.
- There is a need for an external ~~amplifier~~ amplifier to provide suitable gain.


### ii) Active filter

Active filter are <sup>being</sup> widely used in place of passive filters. Inductors cannot be fabricated with high quality of IC technology. So the RC ckt with active device replace the conventional IC filter.

provide the sharp cutoff in attenuation band.
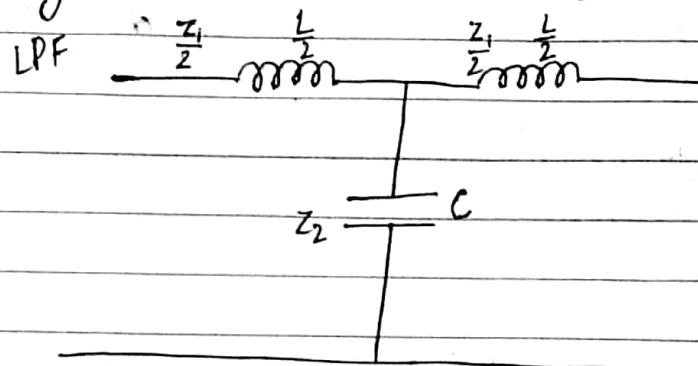
### Constant Gain Low Pass filter

A n/w either T or  $\Pi$  is said to be constant K type of  $z_1$  &  $z_2$  of a n/w if  $z_1$  &  $z_2$  satisfy the relation  $z_1 z_2 = K^2 = R_o^2$




$$z_1 = j\omega L$$

$$z_2 = \frac{1}{j\omega C}$$

$$z_1 z_2 = j\omega L \times \frac{1}{j\omega C} = \frac{L}{C} = \frac{R_o^2}{C}$$

$$R_o = \sqrt{\frac{L}{C}}$$

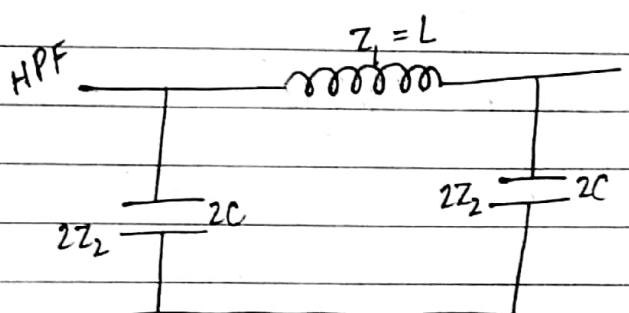

$$R_o = \sqrt{\frac{L}{C}} \quad f_c = \frac{1}{\pi\sqrt{LC}}$$

$$\alpha = 2\cos^{-1}\left(\frac{f}{f_c}\right)$$


attenuation factor (in nepers)

Q. Design a LPF having cut off freq. of 1 kHz to operate with terminate load Resistance of  $200\Omega$ . Find the freq. at which the filter offers the attenuation of 19.1 dB.

Sol<sup>n</sup>-  $f_c = 1\text{ kHz}$        $R = 200\Omega$   
 $R = \sqrt{\frac{L}{C}} \Rightarrow 200 = \sqrt{\frac{L}{C}}$

$$\sqrt{LC} = \frac{1}{\pi \times 1000} \Rightarrow C = \frac{1}{200 \times 1000 \times \pi} = 1.6 \times 10^{-6} \text{ F} = 1.6 \mu\text{F}$$

$$L = 0.06 H = 60 \text{ mH}$$

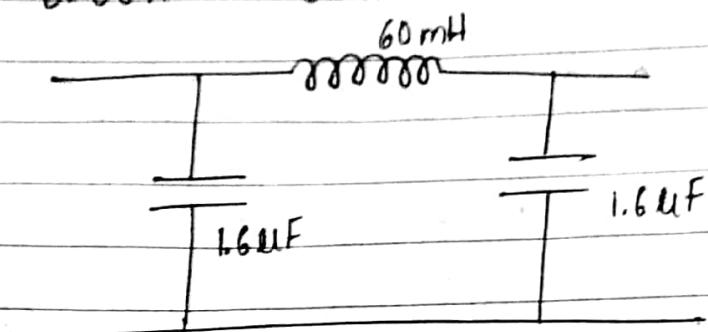

$$\frac{19.1}{2} = \cos^{-1} \left( \frac{f}{f_c} \right)$$

$$f = f_c \cos \left( \frac{19.1}{2} \right)$$

$$= 986.14 \text{ Hz}$$

$\alpha$  in dB =  $8.686 \times \alpha$  in nepers

$$\frac{19.1 \times 8.686}{2} = \cos^{-1} \left( \frac{f}{f_c} \right)$$

$$f = f_c \cos (19.1 \times 4.343)$$

$$= 122.71 \text{ Hz}$$